



Lecture 24

VE 311 Analog Circuits

Xuyang Lu
2023 Summer



上海交通大學
SHANGHAI JIAO TONG UNIVERSITY

Recap of Last Lecture



- General Time constant approach

Topics to Be Covered



- General Time constant approach
- Biasing Circuit: Review and Insight

Further discussion on P and Z



- $H(s) = \frac{H^0 + H^1 \tau s}{1 + \tau s} = H^0 \frac{1 + \frac{H^1}{H^0} \tau s}{1 + \tau s}$
- $P = -\frac{1}{\tau}$
- $Z = -\frac{1}{H^1} = \frac{H^0}{H^1} \tau \left(-\frac{1}{\tau}\right)$
- $Z = \frac{H^0}{H^1} P$
- This tells us that we can look at the sign of H^0 and H^1 to infer the location of zeros and poles
- The ratio also tells whether poles or zeros come earlier.

Further discussion on P and Z



	$ \frac{H_0}{H_1} < 1$	$ \frac{H_0}{H_1} > 1$
$\frac{H_0}{H_1} > 0$	P and Z in same half plane $ \frac{Z}{P} < 1$	P and Z in same half plane $ \frac{Z}{P} > 1$
$\frac{H_0}{H_1} < 0$	P and Z in opposite half planes $ \frac{Z}{P} < 1$	P and Z in opposite half planes $ \frac{Z}{P} > 1$




Further discussion on P and Z

$$H(s) = \frac{H^0 + H^1\tau S}{1 + \tau S} = H^0 \frac{1}{1 + \tau S} + H^1 \frac{\tau S}{1 + \tau S} \quad (1)$$

Low path filter

High path filter
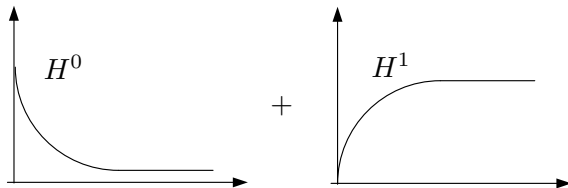
$$s(t) = H^0 (1 - e^{-t/\tau}) u(t) + H^1 e^{-t/\tau} u(t) \quad (2)$$




The final waveform also tells you the existence of poles and zeros.

Further discussion on P and Z



Transient Simulation

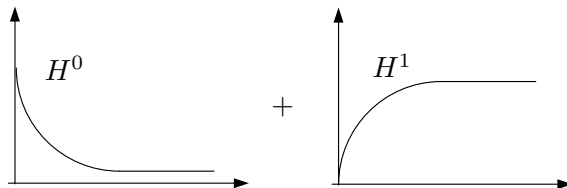


	$ \frac{H_0}{H_1} < 1$	$ \frac{H_0}{H_1} > 1$
$\frac{H_0}{H_1} < 0$	P and Z in opposite HP $ Z < P $	P and Z in opposite HP $ Z > P $

Further discussion on P and Z




	$ \frac{H_0}{H_1} < 1$	$ \frac{H_0}{H_1} > 1$
$\frac{H_0}{H_1} < 0$	P and Z in opposite HP $ Z < P $	P and Z in opposite HP $ Z > P $

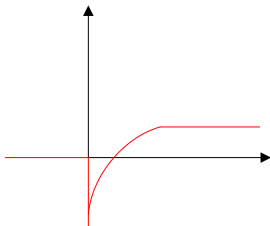


Opposite sign resulting in undershoot,
left half plane pole and **right half-plane zero**.

Further discussion on P and Z

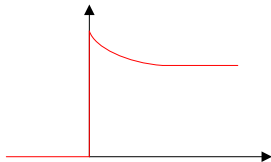

$$0 < \frac{H_0}{H_1} < 1$$

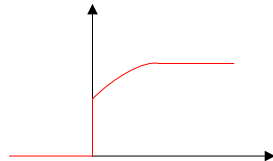
Left half plane low frequency zero that happens before the pole in a first order system.



$$1 < \frac{H_0}{H_1}$$

Zero happens after the pole freq.

Nth order system

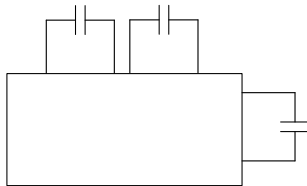

$$H(s) = \frac{a_0 + a_1 S + a_2 S^2 + \dots}{1 + b_1 S + b_2 S^2 + \dots} \quad (3)$$

- Only the caps and inductors produces S.
- To get a_1 we have to have a cap (or inductor)

N^{th} order system




- We can also infer that the s^2 term comes from two capacitors.
- $$H(s) = \frac{a_0 + \left(\sum_{i=1}^N \alpha_1^i C_i\right)s + \left(\sum_i^{1 \leq i < j \leq N} \alpha_j^{ij} C_i C_j\right)s^2 + \dots}{1 + \left(\sum_{i=1}^N \beta_1^i C_i\right)s + \left(\sum_i^{1 \leq i < j \leq N} \sum_j^{ij} \beta_2^{ij} C_i C_j\right)s^2 + \dots}$$
- If we set all c 's except c_i as zeros
- $$H_i(s) = \frac{a_0 + \alpha_1^i C_i s}{1 + \beta_1^i C_i s}$$
- $\tau_i^0 = R_i^0 C_i$
- $\beta_1^i = R_i^0$
- $b_1 = \sum_{i=1}^N \tau_i^0$

Nth order system



- $b_1 = \sum_{i=1}^N \tau_i^0$
- coefficient b_1 is the sum of all zero valued time constant.
- $a_1 = \sum_{i=1}^N \tau_i^0 H^i$
- This allows us to find out the dominant time constant.


N^{th} order system

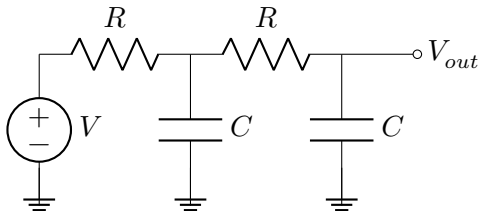

It is a two cap system, therefore the number of poles are two.

It is a system with an infinite response of zero if we short both capacitors, so there is no zeros.

N^{th} order system

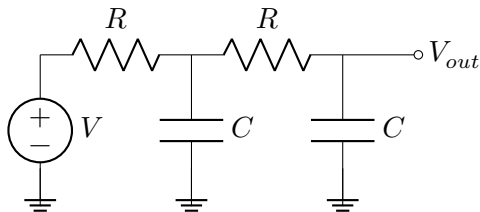

- $H(S) = \frac{1}{1+3RCS+(RC)^2S^2}$
- $b_1 = \sum_{i=1}^N \tau_i^0 = \tau_1^0 + \tau_2^0$
- $\tau_1^0 = RC$
- $\tau_2^0 = 2RC$
- $b_1 = 3R_c$

N^{th} order system



$$H(S) = \frac{1}{1 + 3RCS + (RC)^2 S^2} \quad (4)$$

- If the impedance seen by one cap does not change as we open or short the other cap, we say that the two-time constant are uncoupled to each other, and the expression can be written as

$$H(s) = \frac{H^0}{(1 + \tau_1 S)(1 + \tau_2 S)} \quad (5)$$

N^{th} order system



$$H(S) = \frac{1}{1 + 3RCS + (RC)^2 S^2} \quad (6)$$

- We now have the $3RC$ term. The question is whether it is true in this case to determine $(RC)^2 S^2$

$$H(s) = \frac{1}{(1 + \tau_1^0 s)(1 + \tau_2^0 s)} = \frac{1}{1 + (\tau_1^0 + \tau_2^0)s + \tau_1^0 \tau_2^0 s^2} \quad (7)$$

$$\tau_1^0 \tau_2^0 = 2(RC)^2 \quad (8)$$

N^{th} order system



We now know how to calculate a_1 , b_1 , and a_0 .

$$H(s) = \frac{a_0 + \left(\sum_{i=1}^N \alpha_1^i C_i\right) s + \left(\sum_i^{1 \leq i < j \leq N} \alpha_j^{ij} C_i C_j\right) s^2 + \dots}{1 + \left(\sum_{i=1}^N \beta_1^i C_i\right) s + \left(\sum_i^{1 \leq i < j \leq N} \sum_j \beta_2^{ij} C_i C_j\right) s^2 + \dots} \quad (9)$$

A_0 is the zero frequency response. B_1 is the summation of time constant A_1 can be obtained from infinite time response.

N^{th} order system



$$b_2 = \sum_i^{i < j < N} \sum_j^0 \tau_j^i \quad (10)$$

- That means you don't repeat τ_{12} and τ_{21}
- τ_j^i means the time constant of element j when element I is infinite frequency

$$a_2 = \sum_{i < j < N} \sum_j \tau_i^0 \tau_j^i H^{ij} \quad (11)$$

- We can expect b_n is a multiple summation of the product of many time constants

N^{th} order system



$$H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2} \quad (12)$$

$$H(s) = \frac{H^0 + (H^1 R_1^0 C_1 + H^2 R_2^0 C_2)s + (\alpha_2^{12} C_1 C_2)s^2}{1 + (R_1^0 C_1 + R_2^0 C_2)s + (\beta_2^{12} C_1 C_2)s^2} \quad (13)$$

- We notice that relabeling C_1 as C_2 and vice versa should not change the derived transfer function.
- So that $\alpha_2^{12} = \alpha_2^{21}$ and $\beta_2^{12} = \beta_2^{21}$
- R_2^1 is the resistance seen by C_2 (the subscript) when C_1 (the superscript) is infinite valued (shorted).

N^{th} order system



$$H(s) = \frac{H^0 + (H^1 R_1^0 C_1 + H^2 R_2^0 C_2)s + (\alpha_2^{12} C_1 C_2)s^2}{1 + (R_1^0 C_1 + R_2^0 C_2)s + (\beta_2^{12} C_1 C_2)s^2} \quad (14)$$

I want to determine the value of α_2^{12} and β_2^{12} .

It should be valid for $C_1 \rightarrow \infty$.

If I short C_1 , $C_1 \rightarrow \infty$.

$$H(s)|_{C_1 \rightarrow \infty} = \frac{C_1 s \cdot (H^1 R_1^0 + \alpha_2^{12} C_2 s)}{C_1 s \cdot (R_1^0 + \beta_2^{12} C_2 s)} = H^1 \cdot \frac{1 + \frac{\alpha_2^{12}}{H^1 R_1^0} C_2 s}{1 + \frac{\beta_2^{12}}{R_1^0} C_2 s} \quad (15)$$

It should be the same as a 1 cap system.

Therefore, $\beta_2^{12} = R_1^0 R_2^1$ and $b_2 = R_1^0 C_1 R_2^1 C_2 = \tau_1^0 \tau_2^1$.

N^{th} order system



$$H(s) = \frac{H^0 + (H^1 R_1^0 C_1 + H^2 R_2^0 C_2)s + (\alpha_2^{12} C_1 C_2)s^2}{1 + (R_1^0 C_1 + R_2^0 C_2)s + (\beta_2^{12} C_1 C_2)s^2} \quad (16)$$

We determine a_2 in by setting both C_1 and C_2 to infinity


- $C_1 \rightarrow \infty$ and $C_2 \rightarrow \infty$, $H^{12} = \frac{\alpha_2^{12}}{\beta_2^{12}}$
- $\beta_2^{12} = R_1^0 R_2^1$
- Therefore, $\alpha_2^{12} = R_1^0 R_2^1 H^{12}$.
- $a_2 = R_1^0 C_1 R_2^1 C_2 H^{12} = \tau_1^0 \tau_2^1 H^{12}$
- H_{12} is the low-frequency input-output transfer constant with the reactive elements 1 and 2 at their infinite value (C_1 and C_2 shorted).

N^{th} order system



- $b_2 = \tau_1^0 \tau_2^1 = \tau_2^0 \tau_1^2$
- $a_2 = \tau_1^0 \tau_2^1 H^{12} = \tau_2^0 \tau_1^2 H^{12}$
- $b_1 = \tau_1^0 + \tau_2^0$
- $a_1 = \tau_1^0 H^1 + \tau_2^0 H^2$


N^{th} order system

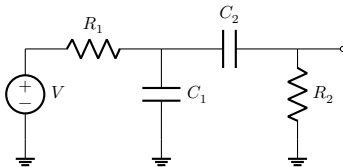

- Two pole and one zero
- How do we test this?
- $H^0 = 0$
- $\tau_1^0 = R_1 C_1$
- $\tau_2^0 = (R_1 + R_2) C_2$




N^{th} order system

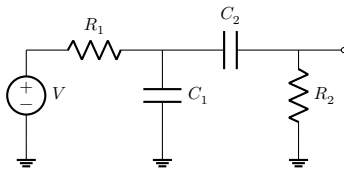

- $\tau_2^1 = R_2 C_2$
- $\tau_1^2 = (R_1 \parallel R_2) C_1$
- $\tau_1^0 \tau_2^1 = R_1 C_1 R_2 C_2 = \tau_2^0 \tau_1^2$
- $\tau_2^0 \tau_1^2 = (R_1 + R_2) C_2 \frac{R_1 R_2}{R_1 + R_2} C_1$
- $\tau_2^0 = (R_1 + R_2) C_2$
- $H^1 = 0$
- $H^2 = \frac{R_2}{R_2 + R_1}$
- $H^{12} = 0$

$$H(s) = \frac{R_2 C_2 S}{1 + (R_1 C_1 + R_1 C_2 + R_2 C_2) S + R_1 C_1 R_2 C_2 S^2} \quad (17)$$

N^{th} order system

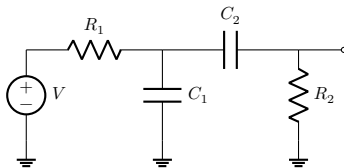


- $H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2}$
- $b_2 = \tau_1^0 \tau_2^1 = \tau_2^0 \tau_1^2$
- $a_2 = \tau_1^0 \tau_2^1 H^{12} = \tau_2^0 \tau_1^2 H^{12}$
- $b_1 = \tau_1^0 + \tau_2^0$
- $a_1 = \tau_1^0 H^1 + \tau_2^0 H^2$

N^{th} order system



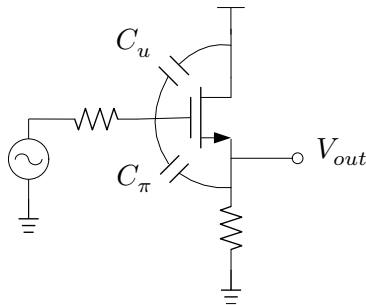- Two poles and one zero
- $H^0 = \frac{R_2}{R_2 + r_m}$
- $\tau_\pi^0 = C_\pi \frac{R_1 + R_2}{1 + g_m R_2}$
- $\tau_\mu^0 = C_\mu R_1$
- $\tau_\mu^\pi = C_\mu (R_1 \parallel R_2)$
- $H^\mu = 0$
- $H^\pi = \frac{R_2}{R_1 + R_2}$
- $H^{\mu\pi} = 0$



N^{th} order system




- Now we can write out the transfer function. If we assume that $R_2 \gg R_1$
- And $R_2 \gg R_m$

$$H^0 = \frac{R_2}{R_2 + r_m} \quad (18)$$

$$\tau_\pi^0 = C_\pi \frac{R_1 + R_2}{1 + g_m R_2} = r_m C_\pi \quad (19)$$

$$\tau_\mu^0 = C_\mu R_1 \quad (20)$$

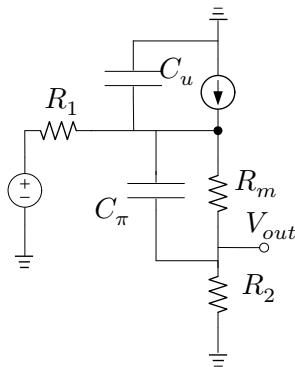


N^{th} order system



$$\tau_{\mu}^{\pi} = C_{\mu} (R_1 \parallel R_2) = C_{\mu} R_1 \quad (21)$$

$$H^{\mu} = 0 \quad (22)$$
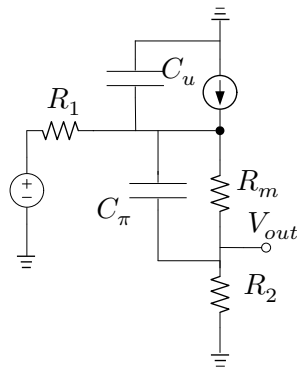
$$H^{\pi} = \frac{R_2}{R_1 + R_2} \quad (23)$$




N^{th} order system



$$\tau_{\pi}^0 \tau_{\mu}^{\pi} = r_m R_1 C_{\pi} C_{\mu} \quad (24)$$
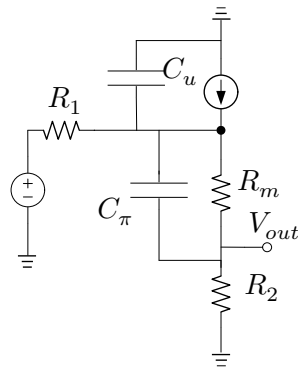
$$H^{\pi} \tau_{\pi}^0 = r_m C_{\pi} \frac{R_2}{r_m + R_2} = H^0 r_m C_{\pi} \quad (25)$$



$$H(S) = H^0 \frac{1 + r_m C_{\pi} S}{1 + (r_m C_{\pi} + R_1 C_{\mu}) S + r_m C_{\pi} R_1 C_{\mu} S^2} \quad (26)$$

N^{th} order system



$$H(S) = H^0 \frac{1 + r_m C_\pi S}{1 + (r_m C_\pi + R_1 C_\mu) S + r_m C_\pi R_1 C_\mu S^2} = \frac{H^0}{1 + R_1 C_\mu S} \quad (27)$$

- This essentially tells us the dominate pole is the C_μ , because C_π shares current between the capacitor and the resistor, so that it tells us to improve the bandwidth of operation, we need to use an inductor or some topology to cancel the effect of C_μ

Bandwidth Estimation



- The whole system can be expressed as the product of a high pass and a low pass transfer function.
- If I'm designing an analog circuit, I can use transfer function to estimate bandwidth, assuming I care about the lowpass one.
- For low frequency system, in many cases we can assume a zeroless system.
- For example, in common-source stage and the source-follower stage, the zero's frequencies are comparable to the cut-off frequency of the transistor itself

Bandwidth Estimation



- $H(s) \approx \frac{a_0}{1+b_1s+b_2s^2+\dots+b_ns^n}$
- At dc ($\omega = 0$), the only term in the denominator that matters is the leading 1.
- As the frequency goes up and starts approaching the ω_h , the first term that becomes non-negligible would be b_1 , so in the vicinity of the ω_h
- The system is pretty much
- $H(s) \approx \frac{a_0}{1+b_1s}$
- This tells us, in order to find out the cutoff frequency,
- We calculate b_1

Bandwidth Estimation



- $\omega_h \approx \frac{1}{b_1} = \frac{1}{\sum_{i=1}^N \tau_i^0}$
- $\frac{a_1}{1+b_1S+b_2S^2} \Rightarrow H(j\omega) = \frac{a_0}{(1-b_2\omega^2)+j\omega b_1}$
- It is a conservative estimation of bandwidth