

VE311 Electronic Circuits

Summer 2023 — Lab 3

Instructor: Dr. Xuyang Lu

Due: 11:59 pm, July 15, 2023 (Saturday)




Note:

1. Please use A4 size papers.
2. The lab report should be submitted online individually.
3. Use Proteus 8.10 for simulation before the lab session. In the Proteus library, you should be able to find all the components used in the schematics. The lab report must include both the simulation and measurement results.

Exercise 3.1

[Common-Source with Source Degeneration Amplifier]

1. [20%] ($R_L = \infty$) Design and build a common-source with source degeneration amplifier, which has a voltage gain $A_v > 5$, using NMOS (VN0104). Plot V_{OUT} vs V_{IN} . Is the voltage gain A_v close to R_D/R_S ? (Hint: First choose appropriate R_D and R_S . Second, perform *DC* sweep to find out a V_{IN} at which the magnitude of slope is more than 5. At the same time, make sure the NMOS is in the saturation region. If not, change for another R_D and R_S , and repeat the *DC* sweep again.)
2. [15%] ($R_L = \infty$) For $V_{in} = V_{IN} + 0.01 \sin(2\pi 10^2 \cdot \text{time})$, plot $V_{out} = V_{OUT} + v_{out}$ vs time. Confirm that the amplitude of v_{out} is equal to $0.01 \times A_v$.
3. [15%] ($R_L = 50k\Omega$) For $V_{in} = V_{IN} + 0.01 \sin(2\pi 10^2 \cdot \text{time})$, plot $V_{out} = V_{OUT} + v_{out}$ vs time. Does the amplitude of v_{out} become smaller than $0.01 \times A_v$? If so, explain the reasons. (Note: Make sure the NMOS remains in the saturation region.)

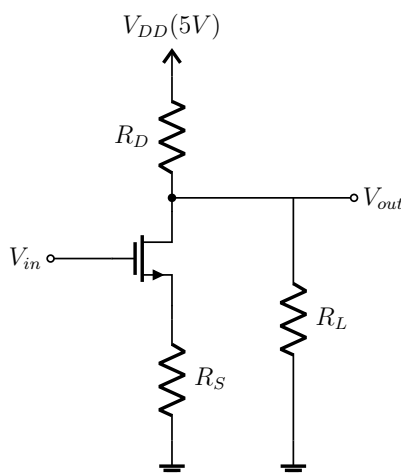

Exercise 3.2

[Source Follower]

1. [20%] ($R_L = \infty$) Design and build a source follower, which has a voltage gain $A_v > 0.5$, using NMOS (**VN0104**). Plot V_{OUT} vs V_{IN} . Is the voltage gain A_v close to unity? (Hint: First choose appropriate R_S . Second, perform *DC* sweep to find out a V_{IN} at which the magnitude of slope is more than 0.5. Here the NMOS is always in the saturation region.)
2. [15%] ($R_L = \infty$) For $V_{in} = V_{IN} + 0.05 \sin(2\pi 10^2 \cdot \text{time})$, plot $V_{out} = V_{OUT} + v_{out}$ vs time. Confirm that the amplitude of v_{out} is equal to $0.05 \times A_v$.
3. [15%] ($R_L = 50k\Omega$) For $V_{in} = V_{IN} + 0.05 \sin(2\pi 10^2 \cdot \text{time})$, plot $V_{out} = V_{OUT} + v_{out}$ vs time. Does the amplitude of v_{out} still maintain around $0.05 \times A_v$? If so, explain the reasons.

