

Lecture 18

VE 311 Analog Circuits

Xuyang Lu 2023 Summer



Recap of Last Lecture




- Common Gate
- Cascode (Telescopic, Folded)
- Differential Amplifier (Current Equation, Superposition)

3/33

Midterm Statistics



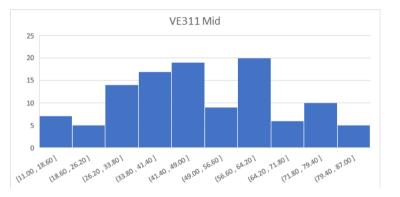

Q1=36, Q2=47, and Q3=61. Total mean=48.04, freshman and sophomore mean=59.56, junior mean=43.93, senior mean=42.61

Topics to be Covered





- Differential Amplifier (Half circuit method)
- More on differential amplifier topologies
- Current mirror

Folded Cascode ($\lambda \neq 0$, $\gamma \neq 0$)



We don't care about M_3 's non-ideality.

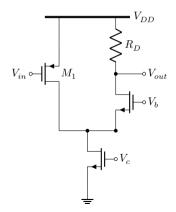

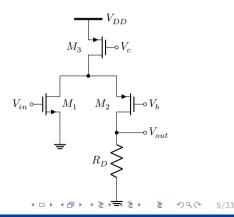

Folded Cascode ($\lambda \neq 0$, $\gamma \neq 0$)




$$G_m = -g_{m1} \frac{(r_{o1} \parallel r_{o3})}{(r_{o1} \parallel r_{o3}) + (r_{o2} \parallel \frac{1}{q_{m2} + q_{mb2}})}$$
(1)

$$R_{out} = \left[(r_{o1} \parallel r_{o3}) + r_{o2} + (g_{m2} + g_{mb2}) r_{o2} (r_{o1} \parallel r_{o3}) \right] \parallel R_D \tag{2}$$

$$A_v = G_m R_{out} \tag{3}$$

Differential-Mode (Superposition)



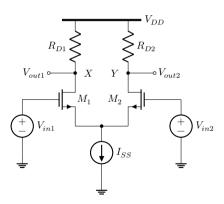


$$A_{DM} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} \tag{4}$$


$$=-g_m R_D \tag{5}$$

Small-Signal, Half-circuit ($\lambda \neq 0$, $\gamma \neq 0$)



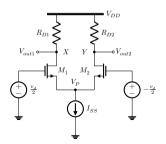
- Assume the circuit is fully symmetric.
- For $i_{d1}+i_{d2}=0$ and $g_{m1}\frac{v_d}{2}+g_{m2}(-\frac{v_d}{2})=0$, V_P must be a constant voltage in DC analysis and a virtual ground in small-signal analysis.




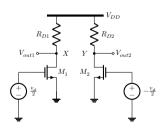

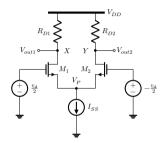Small-Signal, Half-circuit ($\lambda \neq 0$, $\gamma \neq 0$)





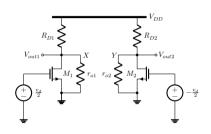

$$V_{out1} = -g_m(R_D \parallel r_o) \frac{v_d}{2} \tag{6}$$

$$V_{out2} = -g_m(R_D \parallel r_o)(-\frac{v_d}{2}) \tag{7}$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} = -g_m(R_D \parallel r_o) \tag{8}$$


Common-Mode Response ($\lambda \neq 0$, $\gamma \neq 0$)



If the circuit is fully symmetric,


$$A_{CM-DM} = \frac{V_{out1} - V_{out2}}{v_{in,CM}} = 0$$
 (9)

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \infty \qquad (10)$$

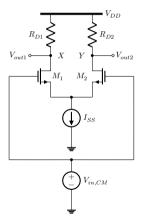


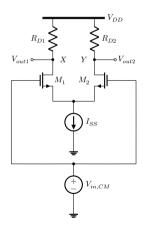Common-Mode Response ($\lambda \neq 0$, $\gamma \neq 0$)







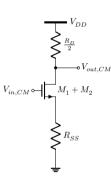

Perturbing biasing condition \rightarrow Altering transconductance (g_m)

◆□▶ ◆□▶ ◆臺▶ ◆臺▶ 臺 ∽9<</p>
○ 11/33

Common-Mode Response ($\lambda \neq 0$, $\gamma \neq 0$)




If the circuit is fully symmetric,

$$A_{CM} = \frac{V_{out,CM}}{V_{in,CM}} \tag{11}$$

$$= \frac{-2g_m \frac{r_o}{2}}{R_{SS} + \frac{r_o}{2} + (2g_m + 2g_{mb2})\frac{r_o}{2}R_{SS}} \cdot \frac{\left[R_{SS} + \frac{r_o}{2} + (2g_m + 2g_{mb})\frac{r_o}{2}R_{SS}\right]\frac{R_D}{2}}{\left[R_{SS} + \frac{r_o}{2} + (2g_m + 2g_{mb})\frac{r_o}{2}R_{SS}\right] + \frac{R_D}{2}}$$
(12)

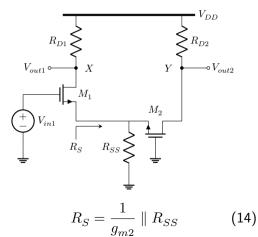
$$=0 \quad \text{if } R_{SS} = \infty \tag{13}$$






Nonzero R_{SS} ($\lambda=0$, $\gamma=0$)



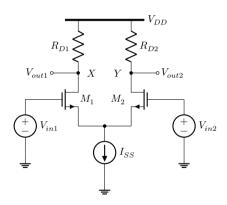

$$V_{out1} = -\frac{R_D}{\frac{1}{g_{m1}} + \left(\frac{1}{g_{m2}} \parallel R_{SS}\right)} V_{in1} \quad (15)$$


Nonzero R_{SS} ($\lambda=0$, $\gamma=0$)

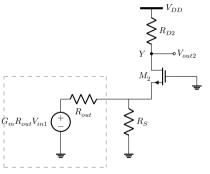

$$G_m = g_{m1} \tag{16}$$

$$R_{out} = \frac{1}{g_{m1}} \tag{17}$$




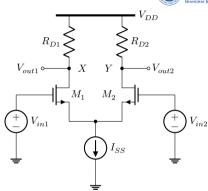

$$V_{out2} = -\frac{\frac{R_{SS}}{R_{SS} + \frac{1}{g_{m2}}} R_D}{\frac{1}{g_{m1}} + \left(\frac{1}{g_{\overline{m}2}} \parallel R_{SS}\right)} V_{in1}$$
(18)

Nonzero R_{ss}



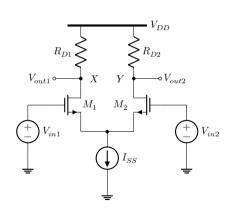

$$V_{out1} - V_{out2} = -\frac{(g_{m1} + 2R_{SS}g_{m1}g_{m2})R_D}{1 + (g_{m1} + g_{m2})R_{SS}}V_{in1}$$
 (19)


$$=-g_m R_D V_{in1} \tag{20}$$

$$V_{in2} = V_{out1} - V_{out2} = -\frac{(g_{m1} + 2R_{SS}g_{m1}g_{m2})R_D}{1 + (g_{m1} + g_{m2})R_{SS}}V_{in1}$$
(21)

$$=-g_{m}R_{D}V_{in2}\tag{22}$$

Nonzero R_{ss}



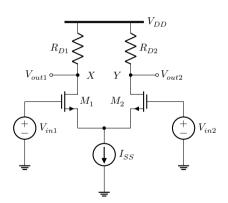

$$A_{DM} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_m R_D$$
 (23)


18/33

A_{DM} with MOS Loads ($\lambda \neq 0$, $\gamma \neq 0$)



Higher A_{DM}

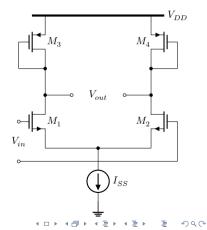- \rightarrow Smaller $(W/L)_P$
- \rightarrow Larger $(V_{SGP} V_{THP})$
- ullet \to Smaller $V_{in,CM}$ headroom






$$V_{out1} = -g_{mN}(r_{oN} \parallel r_{oP} \parallel \frac{1}{g_{mP}}) \frac{v_d}{2}$$
 (24)

$$V_{out2} = -g_{mN}(r_{oN} \parallel r_{oP} \parallel \frac{1}{g_{mP}})(-\frac{v_d}{2})$$
 (25)

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} = -g_{mN} \left(r_{oN} \parallel r_{oP} \parallel \frac{1}{g_{mP}} \right)$$
 (26)
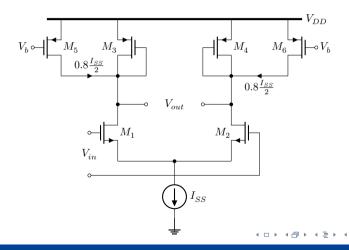
$$\approx -\frac{g_{mN}}{g_{mP}} \approx -\sqrt{\frac{\mu_n(W/L)_N}{\mu_p(W/L)_P}} \tag{27}$$





A_{DM} with MOS Loads



$$V_{out1} = -g_{m1,2} \left(r_{o1,2} \parallel r_{o3,4} \parallel \frac{1}{g_{m3,4}} \parallel r_{o5,6} \right) \frac{v_d}{2}$$
 (28)

$$V_{out2} = -g_{m1,2} \left(r_{o1,2} \parallel r_{o3,4} \parallel \frac{1}{g_{m3,4}} \parallel r_{o5,6} \right) \left(-\frac{v_d}{2} \right)$$
 (29)

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} \approx -\frac{g_{m1,2}}{g_{m3,4}} \approx -\sqrt{\frac{5\mu_n(W/L)_{1,2}}{\mu_p(W/L)_{3,4}}}$$
(30)




$$V_{out1} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \frac{v_d}{2}$$
 (31)

$$V_{out2} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4})(-\frac{v_d}{2}) \quad \text{(32)}$$

$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} \tag{33}$$
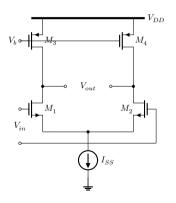
$$= -g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \tag{34}$$




上海交通大學 Shanghai Jiao Tong University

Higher R_{out}

- $\rightarrow {\sf High}\ A_{DM}$
- $\rightarrow \mathsf{Small}\ V_{in,CM}\ \mathsf{headroom}$

Telescopic cascode

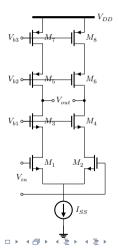




$$V_{out1} \cong -g_{m1,2} \left\{ [r_{o1,2} + r_{o3,4} + (g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2}] \parallel \\ [r_{o7,8} + r_{o5,6} + (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \right\} \frac{v_d}{2}$$
(35)

$$V_{out2} \cong -g_{m1,2} \left\{ [r_{o1,2} + r_{o3,4} + (g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2}] \parallel \\ [r_{o7,8} + r_{o5,6} + (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \right\} \left(-\frac{v_d}{2} \right)$$
(36)


$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} \cong -g_{m1,2}[(g_{m3,4} + gmb_{3,4})r_{o3,4}r_{o1,2} \parallel (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}]$$
(37)


A_{DM} with MOS Loads



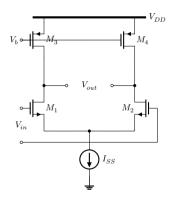
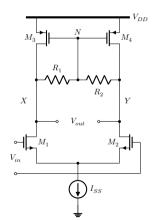
$$A_v = g_{mN} \parallel (r_{ON}r_{OP}) \quad \text{(38)}$$



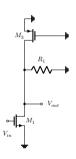


$$\mid A_v \mid = g_{m1}(r_{O1} = \parallel R_1 \parallel r_{O3}) \tag{39}$$

◆□▶◆□▶◆□▶◆□▶ □ つ٩○ 25

Current Defined by Resistors



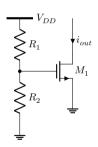

• I_{out} loosely defined.

If
$$\lambda = 0$$


$$I_{\rm out} = \frac{1}{2} \mu_{\rm n} C_{\rm ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} \ V_{\rm DD} - V_{\rm TH1} \right)^2 \label{eq:Iout}$$

(40)

Variations by temperature: μ_n, V_{TH1} Variations by process: $\frac{R_2}{R_1+R_2}, V_{TH1}$

Current Mirror



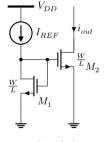

$$I_{\text{out}} = \frac{(W/L)_2}{(W/L)_1} I_{\text{REF}}$$

- $\mu_{\rm n}$ and $V_{\rm TH}$ still vary with temperature, but are canceled out in ratio
- ullet I_{out} precisely defined.

If
$$\lambda = 0$$

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_A - V_{TH1})^2$$


$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_A - V_{TH2})^2$$
(42)

TH1, TH2: Almost identical if two transistors are drawn close to each other in layout.

Current Mirror Examples



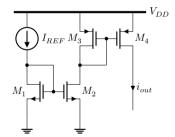Calculate I_{out} in terms of $I_{\rm REF}$




$$I_{\text{out}} = \frac{(W/L)_2}{(W/L)_1} \frac{(W/L)_4}{(W/L)_3} I_{\text{REF}}$$
 (43)

 DC or small-signal current amplification or reduction can be achieved if transistors are properly ratioed.

DC Amplification by Current Mirror




(44)

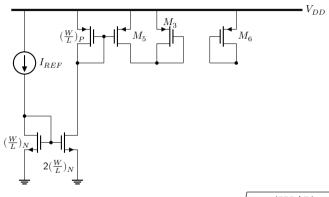

$$A_{\rm DM} \, = \frac{v_{\rm out \; 1} - v_{\rm out \; 2}}{v_{\rm d}} \approx -\frac{g m_{1,2}}{g m_{3,4}} \approx -\sqrt{\frac{5 \mu_n (W/L)_{1,2}}{\mu_p (W/L)_{3,4}}}$$

Amplification by Current Mirror



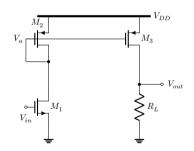

$$v_{a} = -v_{\text{in}} \; gm_{1}(r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_{2}}) \quad \text{(45)}$$


$$v_{\text{out}} = -v_a g m_3 (R_L \parallel r_{o3})$$
 (46)

$$\frac{v_{\mathrm{out}}}{v_{\mathrm{in}}} = gm_1(r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2})gm_3(R_L \parallel r_{o3}) \tag{47} \label{eq:vout}$$


If
$$\lambda = \gamma = 0$$

$$\frac{v_{\text{out}}}{v_{\text{in}}} = g m_1 \frac{g m_3}{g m_2} R_L = g m_1 \frac{(W/L)_3}{(W/L)_2} R_L \tag{48}$$

Differential Pair with Current Mirror

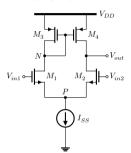

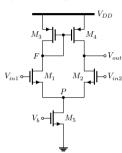
- V_{in} increases
- ullet I_{D1}, I_{D3}, I_{D4} increases
- ullet I_{D2} decreases
- \bullet V_{out} increases



- $V_{in1} > V_F + V_{TH1} \rightarrow M_1$ enters into triode
- \bullet For M_2 in saturation, $V_{\text{out}} \, \geq V_{\mathrm{in,CM}} V_{\mathrm{TH2}}$

Differential Pair with Active Load



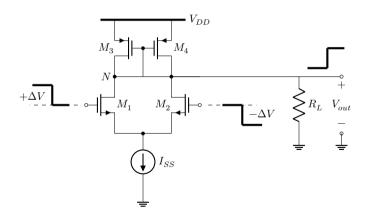

Asymmetric Differential Pair



Why N is not on the right branch? Caveat: Because of the vastly different resistance magnitude at the drains of M_1 and M_2 , the voltage swings at these two nodes are different and therefore node P cannot be viewed as a virtual ground when $V_{in2}=-V_{in1}$.

