

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier
oooooooo

VE311

Electronic Circuits

RC 3

Yucheng Huang

University of Michigan
Shanghai Jiao Tong University
Joint Institute

July 14, 2023

MOSFET Single Stage Amplifier

●oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier

oooooooo

1 MOSFET Single Stage Amplifier

Common Source Amplifier

Common Drain Amplifier (Source Follower)

Common Gate Amplifier

Cascode Amplifier

소

Razavi 3


3

4

2 MOSFET Differential Pair Amplifier

MOSFET Single Stage Amplifier
○●○○○○○○○○○○○○○○○○○○○○○○○○○○

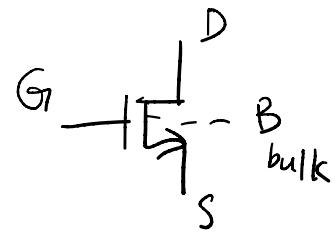MOSFET Differential Pair Amplifier
○○○○○○○○




- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier

- 2 MOSFET Differential Pair Amplifier

MOSFET Single Stage Amplifier
○○●○○○○○○○○○○○○○○○○○○○○○○



MOSFET Differential Pair Amplifier
○○○○○○○

CS with Resistive Load

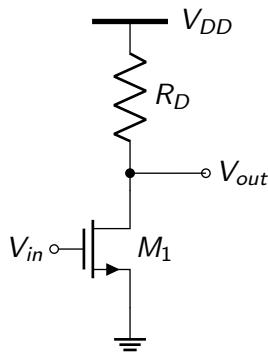

放大器 → 放大器, gain

Voltage gain: A_v
transfer curve i



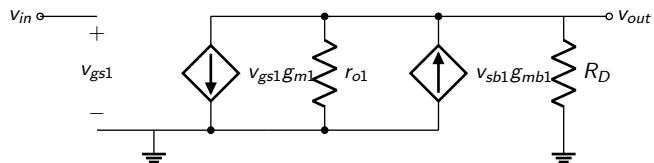
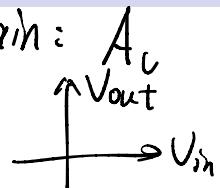


If no channel-length and body effect:

$$A_v = \frac{V_{out}}{V_{in}} = -g_{m1}R_D \quad (1)$$

No body effect:
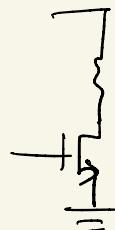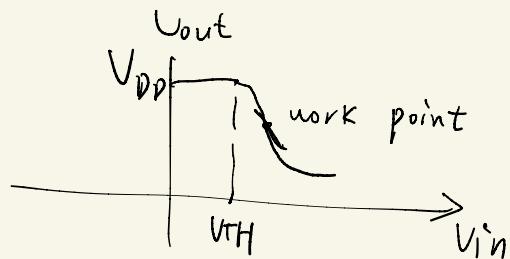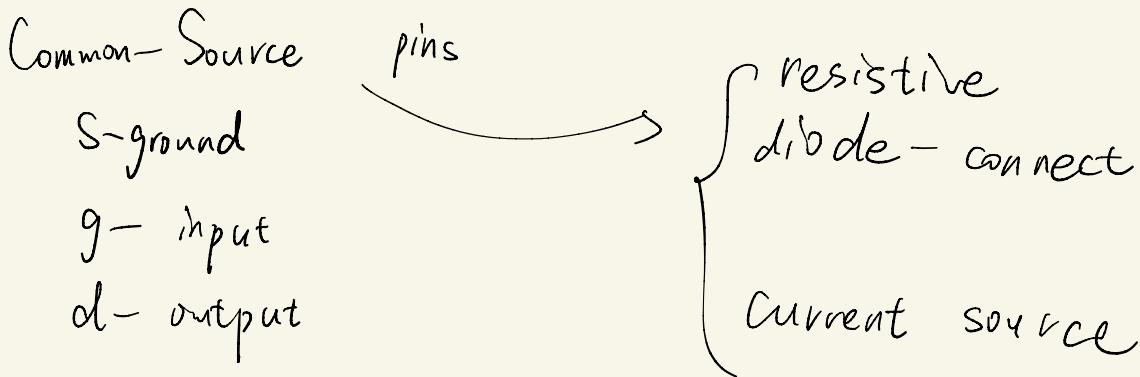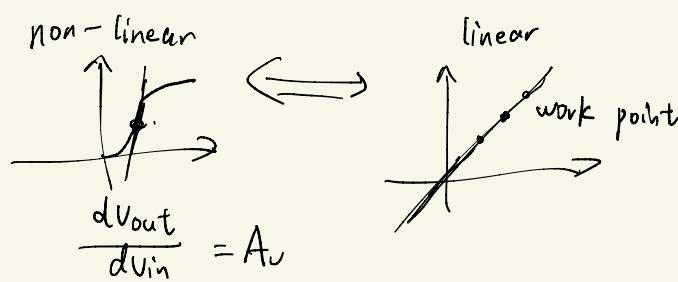
$$A_v = -g_{m1}(R_D \parallel r_{o1}) \quad (2)$$



Saturation: gain

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) R_D$$

$$= -g_m R_D$$

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})$$

$$A_V = \frac{\partial V_{out}}{\partial V_{in}} = -R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \frac{\partial V_{out}}{\partial V_{in}}$$


$$= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})(1 + \lambda V_{out})$$

$$\Rightarrow A_V = -R_D g_m - R_D I_o \lambda A_V$$


$$r_o = \frac{1}{\lambda I_o} \quad \Rightarrow \quad A_V = \frac{-g_m R_D}{1 + R_o \lambda I_o}$$

$$= -g_m \frac{R_o R_D}{R_o + r_o}$$

$$= -g_m (R_D // r_o)$$

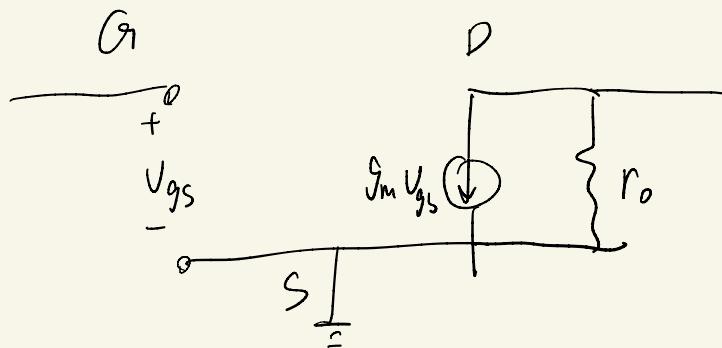

Resistive load:

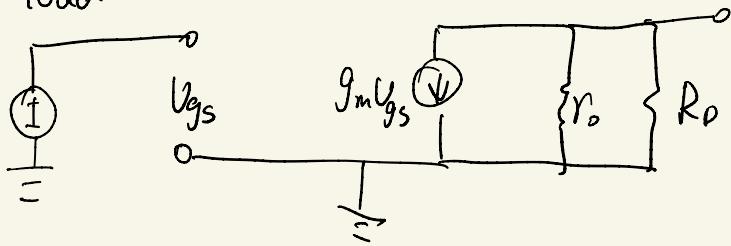

MOSFET Single Stage Amplifier
○○○●○○○○○○○○○○○○○○○○○○○○○○○○○○

MOSFET Differential Pair Amplifier
○○○○○○○○

Example 1

In the common source stage amplifier, $V_{DD} = 5V$, $R_D = 10k\Omega$, change the input voltage and let the current pass through M1 be 0.1mA. What is the gain of the amplifier? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,


$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

Example 1

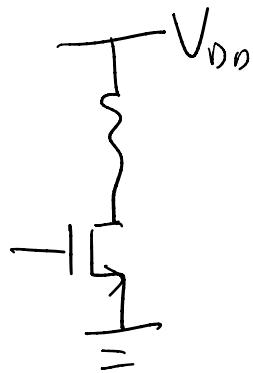

$V_{in} > V_{TH} \rightarrow \text{saturation}$

assume saturation, neglect channel-length effect

$$\begin{aligned} I &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= \frac{1}{2} \times 110 \times 10^{-4} \times 20 \times (V_{GS} - 0.7)^2 = 0.1 \text{ mA} \end{aligned}$$

$$\Rightarrow V_{GS} = 1.0015$$

$$\Rightarrow V_{DS} = V_{DD} - R_D I = 5 \times 10 \times 10^3 \times 0.1 \times 10^{-3} = 4$$

MOSFET Single Stage Amplifier
○○○○●○○○○○○○○○○○○○○○○○○○○

MOSFET Differential Pair Amplifier
○○○○○○○

Example 1

★ saturation

$$\Rightarrow g_m = \sqrt{2 K_n \frac{W}{L} I_D} = 663.3 \mu A/V$$



$$r_o = \frac{1}{g_m} = 250 k\Omega$$

$$A_v = -g_m (r_o / R_o) = \underbrace{-6.398}_{\text{inverse amplifier}} V/V$$

MOSFET Single Stage Amplifier
oooooooo●oooooooooooooooooooo

MOSFET Differential Pair Amplifier
oooooooooooo

CS with Diode-connected Load

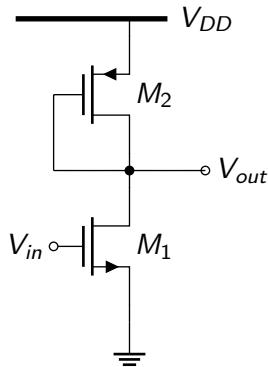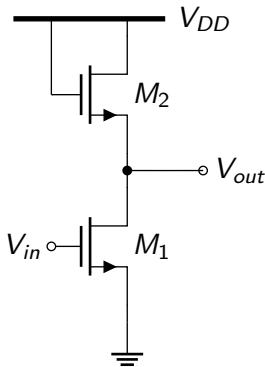

NMOS:


$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta} \quad \eta = g_{mb2}/g_{m2} \quad (3)$$

PMOS:

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}} \quad (4)$$

$G_1 - D$ connect : always saturation

small - signal

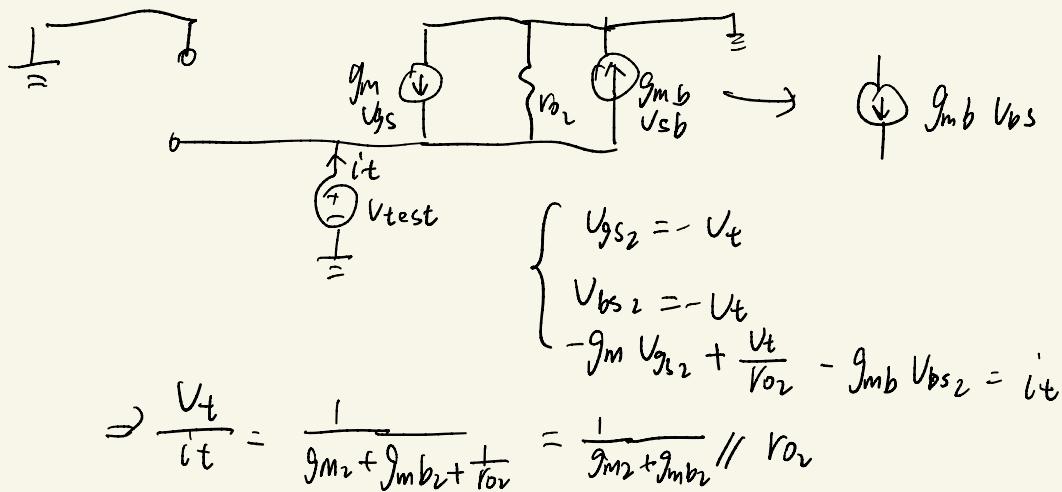

Connect M_1 :

$$\frac{V_t}{i_t} = \frac{1}{g_{m_2} + g_{m_b_2}} // r_{02} // r_0,$$


$$A_V = -g_{m_1} \cdot \frac{1}{g_{m_2} + g_{m_b_2}} // r_{02} // r_0,$$

$$\text{Since } \frac{1}{g_{m_2} + g_{m_b_2}} \ll r_0, r_{02}$$


$$A_V \approx -\frac{g_{m_1}}{g_{m_2} + g_{m_b_2}} = -\frac{g_{m_1}}{g_{m_2}} \cdot \frac{1}{1 + \eta} = -\sqrt{\frac{(w_L)_1}{(w_L)_2}} \cdot \frac{1}{1 + \eta}$$

$$\text{PMOS: } R_{\text{out}} = \frac{1}{g_{m_2}} // r_{02} // r_0 \quad (\text{no } g_{m_b_2}!)$$

N

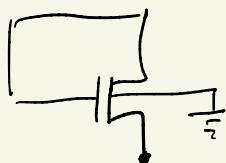

$$V_{SB} \neq 0$$

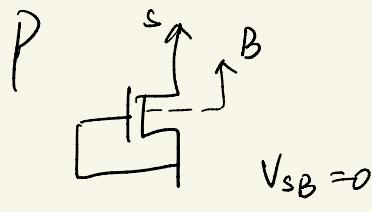

$$V_{SB} = 0$$



$$A_V = -g_m, \quad V_{out,p} = -\frac{g_{m_1}}{g_{m_2}} = -\sqrt{\frac{\mu_n C_{yL}}{\mu_p C_{yL}}}$$

MOSFET Single Stage Amplifier
oooooooo●oooooooooooooooooooo


MOSFET Differential Pair Amplifier
oooooooooooo

CS with Current Source Load

how to
realize

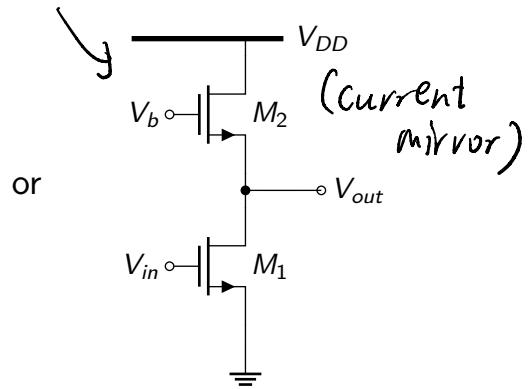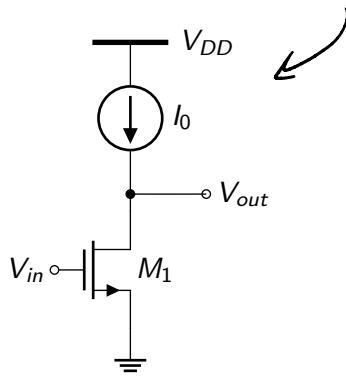
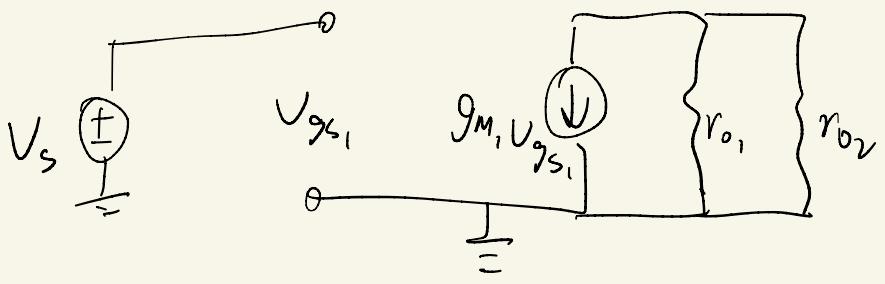
$$A_v = -g_{m1}(r_{o2} \parallel r_{o1}) \quad (5)$$



MOSFET Single Stage Amplifier
oooooooo●oooooooooooooooooooo

MOSFET Differential Pair Amplifier
oooooooo

Example 2

In the common source stage amplifier, the current source is ideal.

Find the intrinsic gain A_v for the amplifier when $I_0 = 0.01$ and $0.1mA$ respectively. (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,

$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,


$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

MOSFET Single Stage Amplifier
oooooooo●oooooooooooooo

MOSFET Differential Pair Amplifier
oooooooo

Example 2

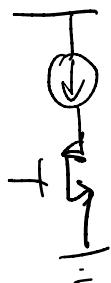

$$g_m = \frac{a}{2K_n W_L I_{D_s}} = 663.3 \text{ mA/V}$$
$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.04 \times 0.1 \times 10^{-3}} = 250 \text{ k}\Omega$$

$$A_v = -g_m r_o = -165.8 \text{ V/V}$$

0.01 mA

$$g_m = 209.76 \quad r_o = 2500 \text{ k}\Omega$$

$$A_v = -524.4 \text{ V/V}$$

- Swing :
- ① medium
 - ② short $V_{GS_1} - V_{TH} \leq V_{out} \leq V_{DD} - V_{GS_2}$
 - ③ high $V_{GS} - V_{TH} \leq V_{out} \leq V_B + |V_{TH}|$

MOSFET Single Stage Amplifier
oooooooooooo●oooooooooooo

MOSFET Differential Pair Amplifier
oooooooo

1 MOSFET Single Stage Amplifier

Common Source Amplifier

Common Drain Amplifier (Source Follower)

Common Gate Amplifier


Cascode Amplifier

2 MOSFET Differential Pair Amplifier



MOSFET Single Stage Amplifier
oooooooooooo●oooooooooooo

MOSFET Differential Pair Amplifier
oooooooooooo

Source Follower

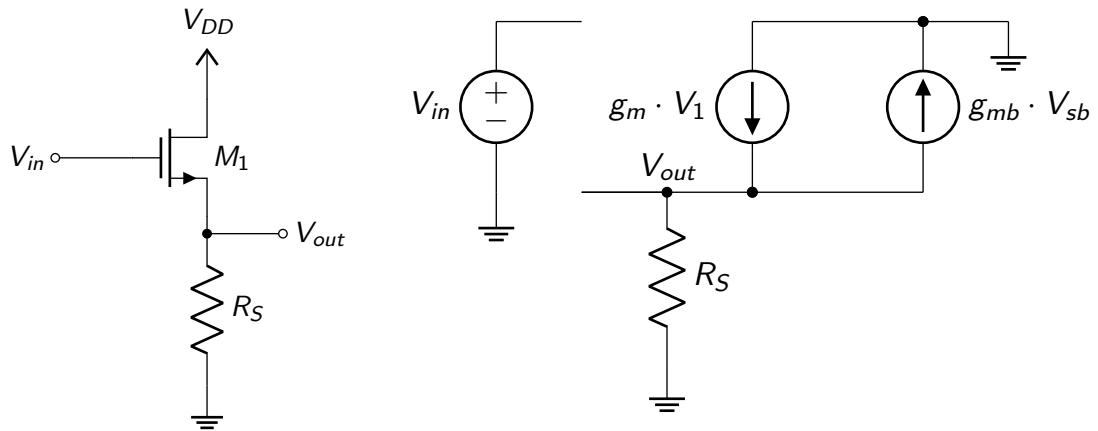
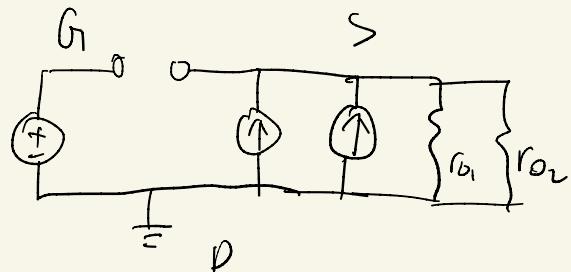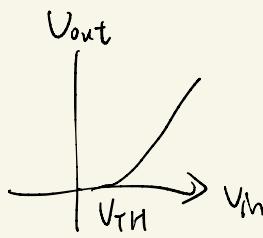
$$A_v = \frac{g_m R_S}{1 + g_m R_S (1 + \eta)} = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S} \approx \frac{1}{1 + \eta} \quad (6)$$



$$g_m V_{in} = g_{m1} V_{out} + g_{mb1} V_{out} + \frac{V_{out}}{R_{01} // R_{02}}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{m1} + g_{mb1} + \frac{1}{R_{01} // R_{02}}}$$

neglect channel-length

$$A_V = \frac{g_{m1}}{g_{m1} + g_{mb1}} = \frac{r}{1 + \eta}$$

MOSFET Single Stage Amplifier
oooooooooooo●oooooooooooo

MOSFET Differential Pair Amplifier
oooooooo

Example 3

In the source follower with current source load, the current source is ideal. Find the output impedance for the amplifier when

$I_0 = 0.01$ and 0.1mA respectively. (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,

$K_n = 110\mu\text{A}/\text{V}^2$, $\lambda = 0.04\text{V}^{-1}$

$(R_L = \infty)$

Parameter for PMOS: $V_{THP} = -0.7V$,


$K_p = 50\mu\text{A}/\text{V}^2$, $\lambda = 0.05\text{V}^{-1}$


All the size of transistor is $W = 20\mu\text{m}$, $L = 1\mu\text{m}$

MOSFET Single Stage Amplifier
oooooooooooo●oooooooooooo

MOSFET Differential Pair Amplifier
ooooooo

Example 3

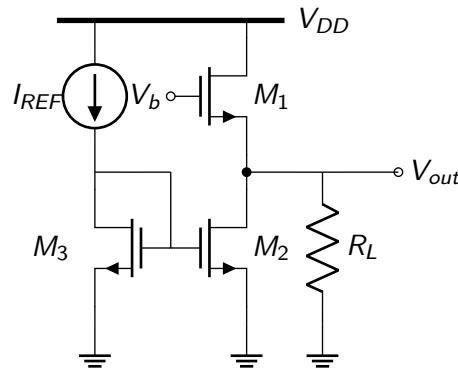

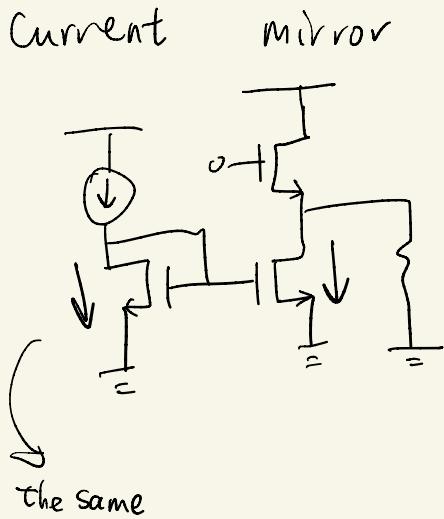

→ replicate the I_{REF}

$$g_{m1} = \sqrt{2Kn \frac{W}{L} I_D}$$

$$= \sqrt{2 \times 110 \times 10^{-6} \times 20 \times 0.1 \times 10^{-3}}$$

$$= 663.3 \mu A/V$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda I_D} = 250 k\Omega$$

$$\Rightarrow r_{out} = \frac{1}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} = 0$$

$$= 1489.6 \Omega$$

$$r_{out} \approx \frac{1}{g_{m1}} = 1507.6 \Omega$$

$$I = 0.01 mA$$

$$\Rightarrow r_{out} = 4749.2 \Omega$$

$$I \downarrow \quad r_{out} \uparrow$$

$$\frac{1}{g_m} = 4767 \Omega$$

MOSFET Single Stage Amplifier

○○○○○○○○○○●○○○○○○○○○○○○

MOSFET Differential Pair Amplifier

○○○○○○○

Example 3

MOSFET Single Stage Amplifier
oooooooooooo●oooooooooooo

MOSFET Differential Pair Amplifier
oooooooooooo

1 MOSFET Single Stage Amplifier

Common Source Amplifier

Common Drain Amplifier (Source Follower)

Common Gate Amplifier


Cascode Amplifier

2 MOSFET Differential Pair Amplifier

MOSFET Single Stage Amplifier
 ○○○○○○○○○○○○○○○○○○○○○



MOSFET Differential Pair Amplifier
 ○○○○○○○

Common Gate

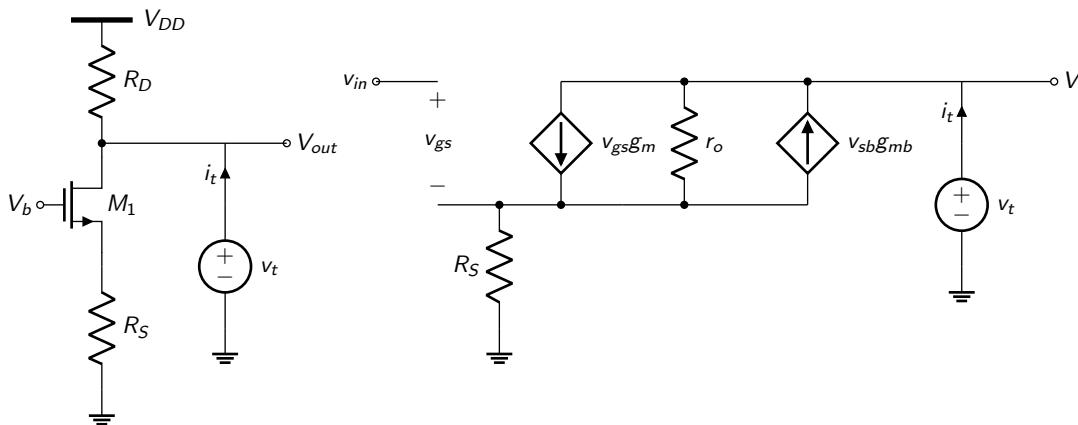

$$R_{in} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o} \begin{cases} \text{If } R_D = 0 & R_{in} = r_o \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \\ \text{If } R_D = \infty & R_{in} = \infty \end{cases} \quad (7)$$
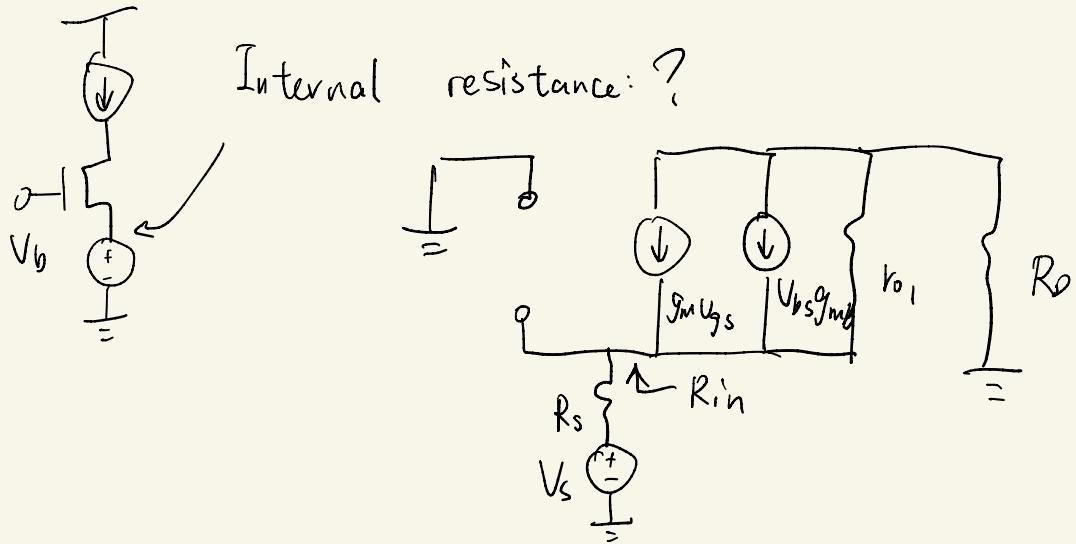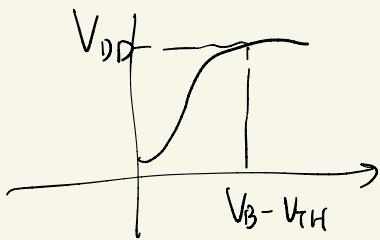
$$R_{out} = [R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S] \parallel R_D \quad (8)$$



MOSFET Single Stage Amplifier
oooooooooooo●oooooooooooo

MOSFET Differential Pair Amplifier
oooooooooooo

Example 4

In the common gate stage amplifier , what is the input resistance when $I_{REF} = 0.01mA$ and $0.1mA$ respectively? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,

$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,


$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

MOSFET Single Stage Amplifier
oooooooooooooooo●oooooooo

MOSFET Differential Pair Amplifier
oooooooo

Example 4

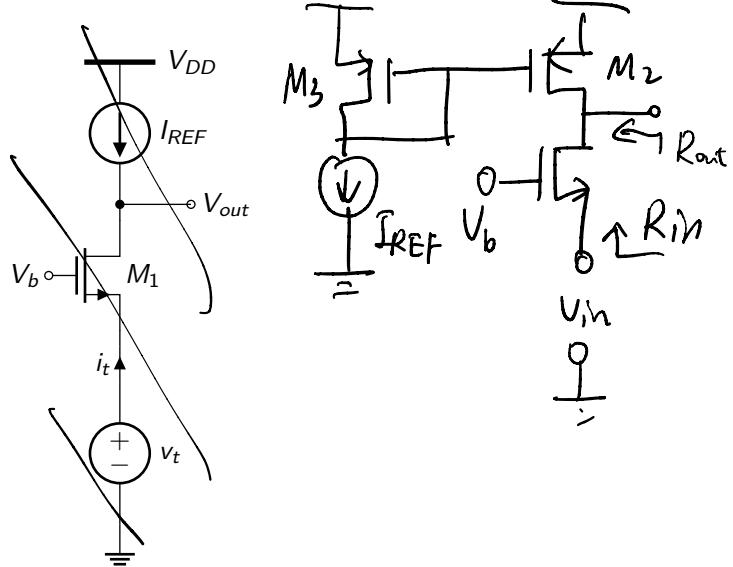

MOSFET Single Stage Amplifier

oooooooooooooooo●oooooooo

MOSFET Differential Pair Amplifier

oooooooo

Example 4

• Im A

$$g_m = \sqrt{2k_n w_L I_D} = 663.3 \mu A/V$$

$$r_{o_1} = r_{o_2} = 250 k\Omega$$

$$r_{o_2} = 200 k\Omega$$

$$= \frac{r}{0.5 \times 10^3 x_{o_1}}$$

$$r_{in} = \frac{R_D + r_o}{r_{o_1}(g_m + g_{m_{b1}}) (+ 1)}$$

$$r_{o_1}(g_m + g_{m_{b1}}) \gg 1 \quad \approx \quad \frac{200 \times 10^3 + 250 \times 10^3}{663.3 \times 10^{-6} \times 250 \times 10^3}$$

$$\frac{2}{g_{m_1}} = 3015.2 \Omega \quad \approx 2713.7 \Omega$$

MOSFET Single Stage Amplifier
oooooooooooooooo●oooooo

MOSFET Differential Pair Amplifier
oooooooo

1 MOSFET Single Stage Amplifier

Common Source Amplifier

Common Drain Amplifier (Source Follower)

Common Gate Amplifier


Cascode Amplifier

2 MOSFET Differential Pair Amplifier

MOSFET Single Stage Amplifier
oooooooooooooooooooo●oooooo

MOSFET Differential Pair Amplifier
ooooooooo


Cascode

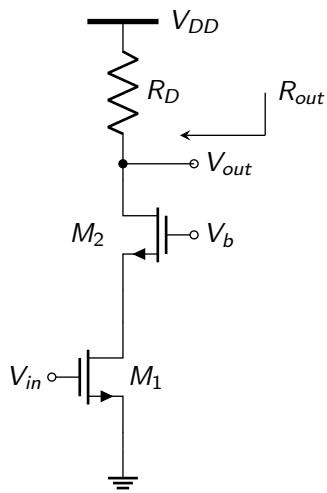

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (9)$$

$$R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \parallel R_D \quad (10)$$


Common Gate
+ Common Source → Cascode

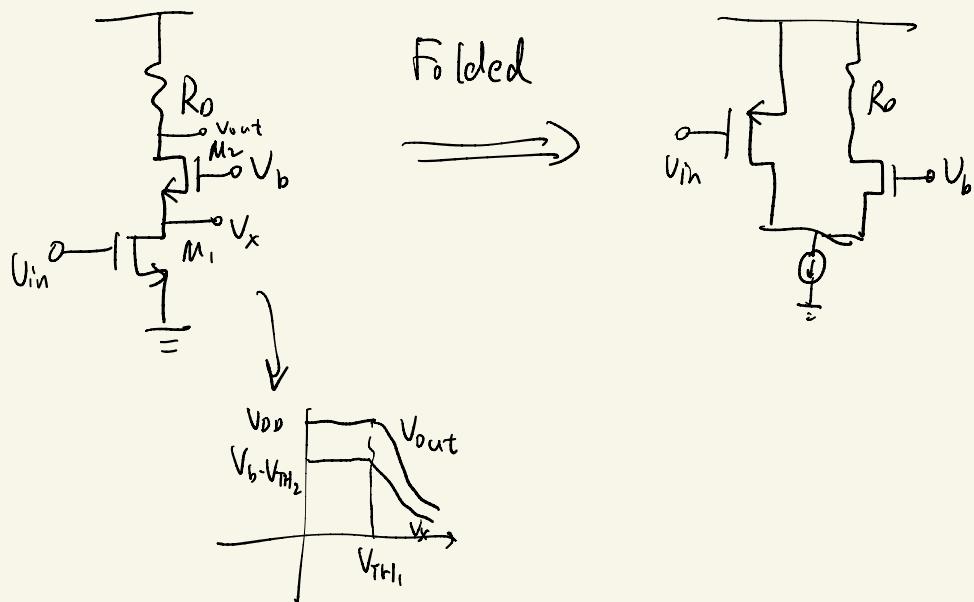

MOSFET Single Stage Amplifier
oooooooooooooooooooo●oooo

MOSFET Differential Pair Amplifier
oooooooo



Cascode

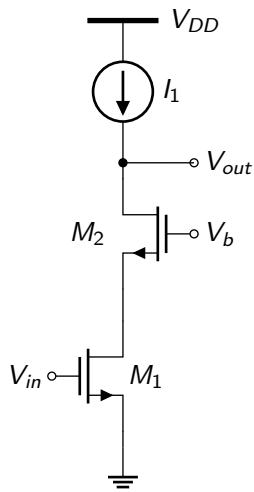

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (11)$$

$$R_{out} = r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1} \quad (12)$$

$$A_v = G_m R_{out} \quad (13)$$

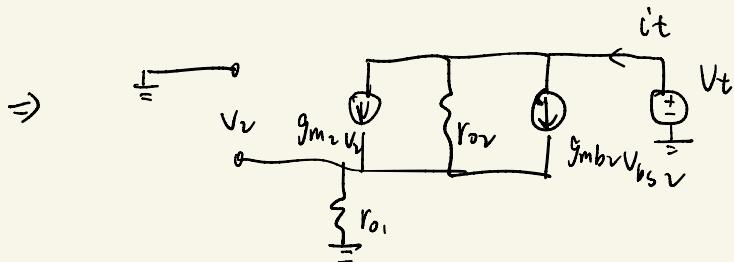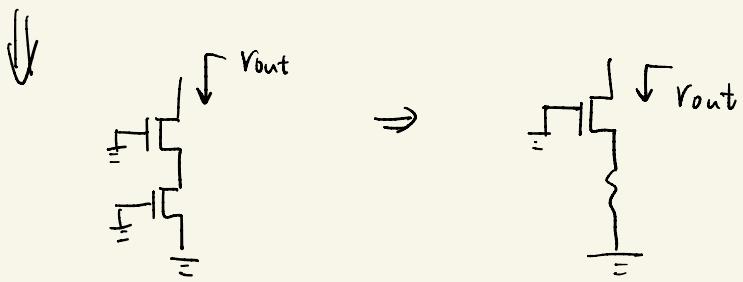

$$\Rightarrow r_{o2} [i_t - (g_{m2} + g_{mb2}) V_t] + i_1 r_{o1} = V_t$$

$$r_{out} = \frac{V_t}{i_t} = [1 + (g_{m2} + g_{mb2}) r_{o2}] r_{o1} + r_{o2}$$


$$r_{o2} (g_{m2} + g_{mb2}) \gg 1 \quad \Rightarrow \quad r_{out} \approx (g_{m2} + g_{mb2}) r_{o1} r_{o2} + r_{o2}$$

$$A_v \approx -g_{m1} [(g_{m2} + g_{mb2}) r_{o2} r_{o1}]$$

MOSFET Single Stage Amplifier
oooooooooooooooooooo●ooo

MOSFET Differential Pair Amplifier
oooooooo

Cascode

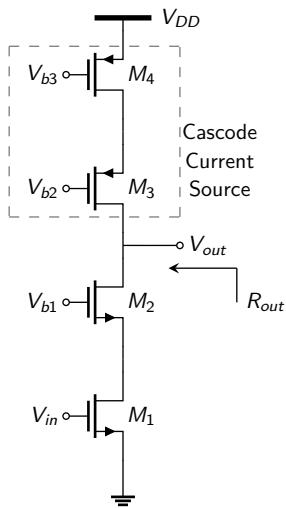

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + (r_{o2} \parallel \frac{1}{g_{m2}g_{mb2}})} \quad (14)$$

$$\begin{aligned} R_{out} &= [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \\ &\parallel [r_{o3} + r_{o4} + (g_{m3} + g_{mb3})r_{o3}r_{o4}] \end{aligned} \quad (15)$$

$$A_V = G_m R_{out} \quad (16)$$

$$R_{\text{out}} \approx (g_m r_o r_{o1}) // (g_m r_o r_{o4})$$

$$A_v \approx - g_m [(g_m r_o r_{o1}) // (r_o r_{o4} g_m)]$$

$$\Rightarrow g_m^2 r_o^2 \gg g_m r_o \quad (\text{Common Source})$$

MOSFET Single Stage Amplifier
○○○○○○○○○○○○○○○●○○

MOSFET Differential Pair Amplifier
○○○○○○○

Example 5

gain

In the cascode amplifier , what is the ~~input resistance~~ when $I_{REF} = 0.01mA$ and $0.1mA$ respectively? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,

$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,


$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo●○

MOSFET Differential Pair Amplifier
oooooooo○

Example 5

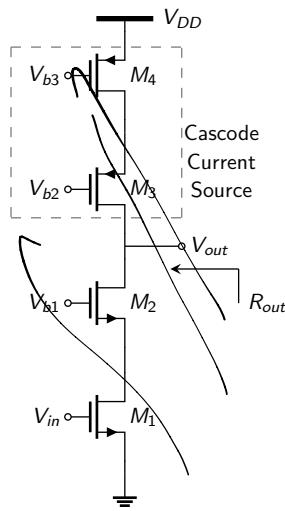

MOSFET Single Stage Amplifier

oooooooooooooooooooooooo●

MOSFET Differential Pair Amplifier

ooooooo

Example 5

$$g_{m_1} = g_{m_2} = \sqrt{2 K_n \gamma_L I_D}$$
$$= 68.3$$

$$r_{o_1} = r_{o_2} = \frac{1}{\lambda I_D}$$

$$A_v = -g_{m_1} \left[(g_{m_2} + g_{m_{b2}}) r_{o_2} r_{o_1} \right]$$
$$\approx 27498$$

	Gain	r_{out}	r_{in}	Swing
CS	$-g_m (R_D \parallel r_{o1})$	$R_D \parallel r_{o1}$	∞	medium
	$-\sqrt{\frac{m_n C_{L1}}{m_p C_{W/L} L}}$	$\approx \frac{1}{g_m} \parallel r_{o1}, r_{o2}$	∞	small
	$-g_m (r_{o1} \parallel r_{o2})$	$r_{o1} \parallel r_{o2}$	∞	high
CD	$\frac{g_m}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$	$\frac{1}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$	∞	/
CQ	$\frac{g_m + g_{mb1} + \frac{1}{r_{o1}}}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$	/	$\frac{r_{o1} + r_{o2}}{(g_{m1} + g_{mb1}) m_1 + 1}$	/
CAS + CAS	$-g_m [S_{m2} r_{o2} r_{o1} \parallel S_{m3} r_{o3} r_{o4}]$	[]	∞	/

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier
●oooooooo

1 MOSFET Single Stage Amplifier


- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier

2 MOSFET Differential Pair Amplifier

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier
○●○○○○○

Differential Pair

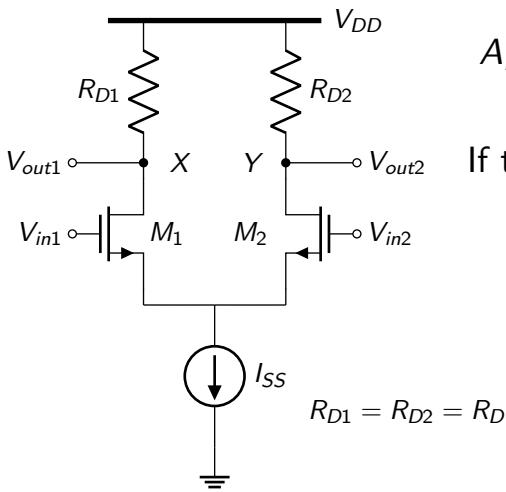

$$A_{DM} = \frac{V_{out1} - V_{out2}}{V_d} = -g_m(R_D \parallel r_o) \quad (17)$$

If the circuit is fully symmetric,

$$A_{CM-DM} = \frac{V_{out1} - V_{out2}}{V_{in,CM}} = 0 \quad (18)$$

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \infty \quad (19)$$


Differential Pair : Specific Structure

- ① Swing ↑
- ② Linearity ↑
- ③ Noise ↓

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier
oo●ooooo

Differential Pair with MOS Loads

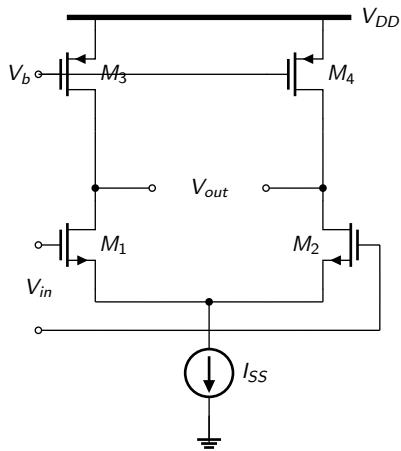


$$A_{DM} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \quad (20)$$

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier
oooo●oooo

Differential Pair with Cascode Loads

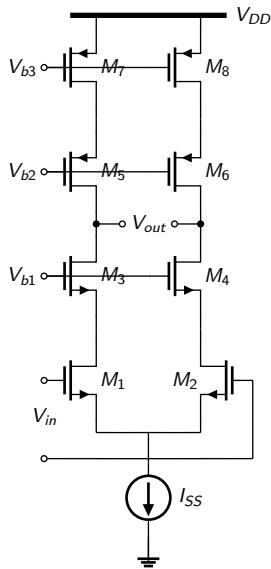

$$A_{DM} \cong -g_{m1,2}[(g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2} \parallel (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \quad (21)$$

MOSFET Single Stage Amplifier
oooooooooooooooooooo

MOSFET Differential Pair Amplifier
oooo●ooo

Example 6

gain

In the differential pair , what is the ~~input resistance when~~ $I_{SS} = 0.02mA$ and $0.2mA$ respectively? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,

$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,


$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier
ooooo●oo

Example 6

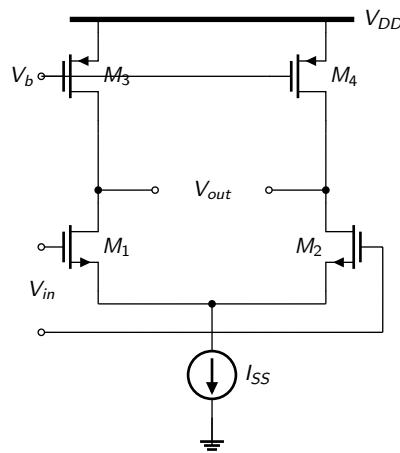

MOSFET Single Stage Amplifier
oooooooooooooooooooooooo

MOSFET Differential Pair Amplifier
ooooooo●○

Example 6

$$g_{m1,2} = \sqrt{2K_n w_L I_{D1,2}} = \sqrt{2 \times 10 \times 10^{-6} \times 20 \times 10^{-3}} = 663.3 \text{ mA/V}$$

$\hookrightarrow I_{D1,2} = \frac{1}{2} I_{ss} = 0.1 \text{ mA}$

$$r_{o1,2} = 250 \text{ k}\Omega \quad r_{o3,4} = 200 \text{ k}\Omega$$

$$A_{vd} = -663.3 \times 10^{-6} \times (250 \times 10^3 \parallel 200 \times 10^3) = \sim$$

MOSFET Single Stage Amplifier
oooooooooooooooooooo

MOSFET Differential Pair Amplifier
oooooo●

END

Thanks