



Lecture 13

VE 311 Analog Circuits

Xuyang Lu
2023 Summer



上海交通大學
SHANGHAI JIAO TONG UNIVERSITY

Recap of Last Lecture



- MOSFET Circuits: Diode Connected Load

Topics to Be Covered



- MOSFET Circuits




Schedule

	Apr	May					Jun				Jul				Aug				Sep	
Monday	24	1	8	15	22	29	5	12	19	26	3	10	17	24	31	7	14	21	28	4
Tuesday	25	2	9	16	23	30	6	13	20	27	4	11	18	25	1	8	15	22	29	5
Wednesday	26	3	10	17	24	31	7	14	21	28	5	12	19	26	2	9	16	23	30	6
Thursday	27	4	11	18	25*	1*	8*	15*	22	29*	6*	13*	20*	27*	3	10	17	24	31	7
Friday	28	5	12	19	26	2	9	16	23	30	7	14	21	28	4	11	18	25	1	8
Saturday	29	6	13	20	27	3	10	17	24	1	8	15	22	29	5	12	19	26	2	9
Sunday	30	7	14	21	28	4	11	18	25	2	9	16	23	30	6	13	20	27	3	10
JI Week			1	2	3	4	5	6	7	8	9	10	11	12	13					
JI Semester	Spr. Brk.	Summer Term													Summer Break					
SJTU Week	11	12	13	14	15	16	17	18	1	2	3	4								
SJTU Semester	Spring Term								Summer Term				Summer Break							

- Midterm on 30th. It will focus on the fundamentals, semiconductors, Diodes, Op-amps, BJT, MOSFET DC biasing.
- No MOSFET SS analysis, only BJT SS models.



Sign of η

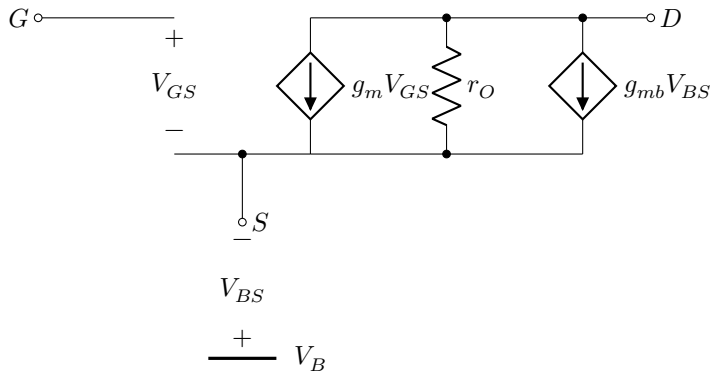

Sign of η



Razavi Textbook, equation 2.50

$$g_{mb} = \frac{\partial I_D}{\partial V_{SB}} = \frac{\partial I_D}{\partial V_{TH}} \cdot \frac{\partial V_{TH}}{\partial V_{SB}} = -\eta g_m \quad (1)$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{SB}} \quad (2)$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \left(-\frac{\partial V_{TH}}{\partial V_{BS}} \right) \quad (3)$$





$$\frac{\partial V_{TH}}{\partial V_{BS}} = -\frac{\partial V_{TH}}{\partial V_{SB}} \quad (4)$$

$$= -\frac{\gamma}{2} (2\Phi_F + V_{SB})^{-1/2} \quad (5)$$



$$g_{mb} = g_m \frac{V}{2\sqrt{2\Phi_F + V_{SB}}} \quad (6)$$

$$= \eta g_m \quad (7)$$


Different Load

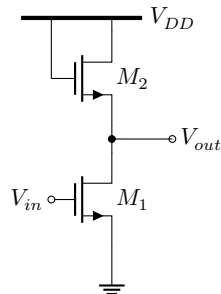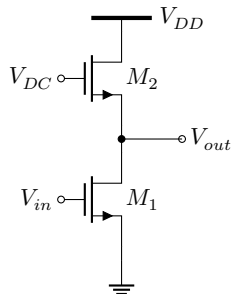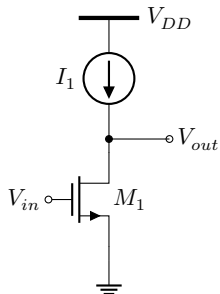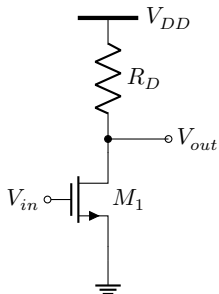

Different Load

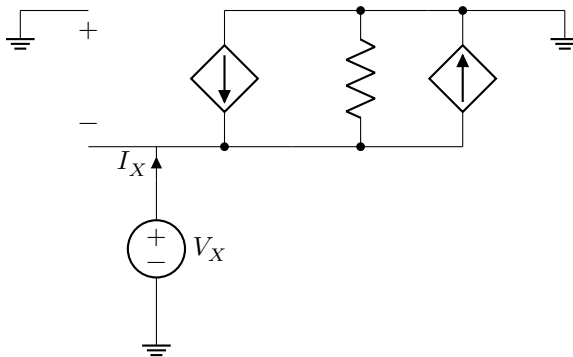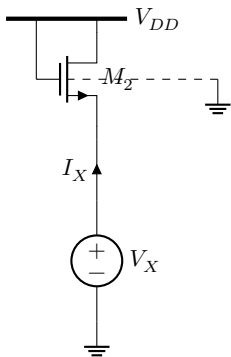

Example

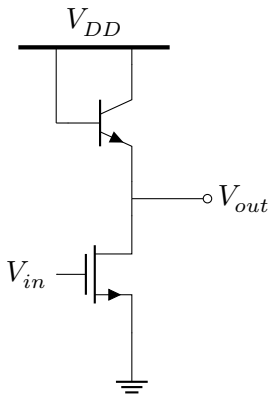




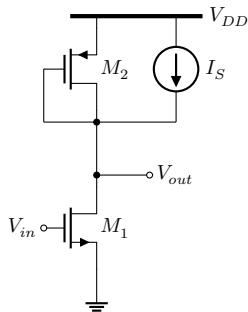Example

M_1 in saturation and $I_S = 0.75 \times I_1$. How do the disadvantages of CS stage with diode-connected load get improved?

Solution: Small-signal Analysis ($\lambda = 0$):




$$A_v = \frac{V_{out}}{V_{in}} = -\frac{g_{m1}}{g_{m2}} = -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}} \quad (8)$$

$$= -\frac{\sqrt{4\mu_n \left(\frac{W}{L}\right)_1}}{\sqrt{\mu_p \left(\frac{W}{L}\right)_2}} = \frac{4(V_{SG2} - V_{TH2})}{(V_{GS1} - V_{TH1})} \quad (9)$$




Example ($\lambda = \gamma = 0$)

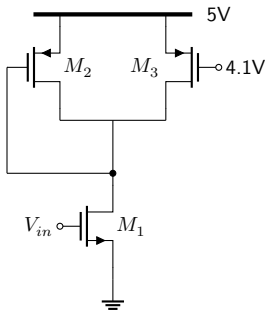



$$W_{drawn}/L_{drawn} = 10u/2u$$
$$V_{in} = 0.8V + 0.001 \sin(2\pi 100t)$$

Example ($\lambda = \gamma = 0$)

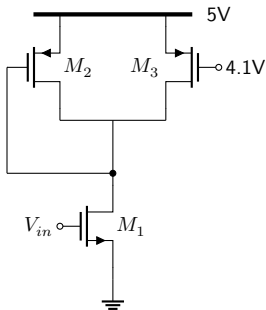

$$W_{drawn}/L_{drawn} = 10u/2u$$
$$V_{in} = 0.8V + 0.001 \sin(2\pi 100t)$$

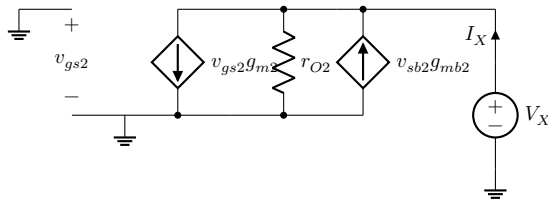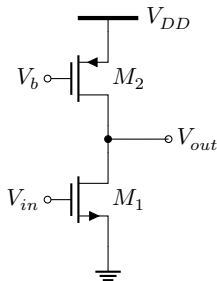CS with Current-Source Load ($\lambda \neq 0, \gamma \neq 0$)




$$v_{sb2} = v_{gs2} = 0 \quad (10)$$

$$R_{in2} = \frac{V_x}{i_x} = r_{o2} \quad (11)$$



CS with Current-Source Load

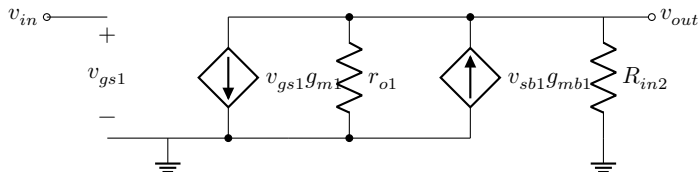


$$A_v = \frac{v_{out}}{v_{in}} \quad (12)$$

$$= -g_{m1}(r_{o2} \parallel r_{o1}) \quad (13)$$

- To achieve high A_v , the output swing is severely limited in the CS stages with resistive load and diode-connected load.
- Here $V_{out,max} = V_{DD} - (V_{SG2} - V_{TH2})$, which can be quite close to V_{DD}



CS with Current-Source Load

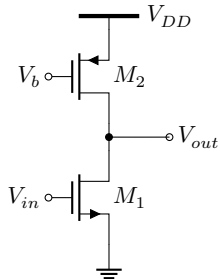

$$A_v = \frac{v_{out}}{v_{in}} \quad (14)$$

$$= -g_{m1}(r_{o2} \parallel r_{o1}) \quad (15)$$

$$r_o \approx \frac{1}{\lambda I_D} \quad (16)$$


$$V_{out,max} = V_{DD} - (V_{SG2} - V_{TH2}) \quad (17)$$

$$V_{out,min} = V_{GS1} - V_{TH1} \quad (18)$$

- For high g_{m1} and small $(V_{GS1} - V_{TH1})$, W of M_1 needs to be large.
- For high r_{o1} and r_{o2} , L of M_1 and M_2 need to be large and L of M_1 and M_2 needs to be increased proportionally. The cost is the **large parasitic drain junction capacitance** at the output.





Amplifier Equivalent Circuit

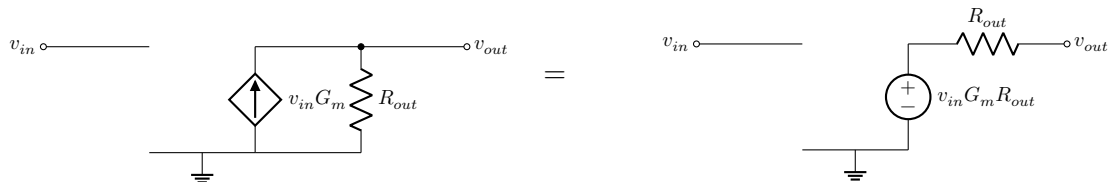

- How to calculate G_m ? v_{out} shorted to ground. $G_m = i_{out}/v_{in}$
- How to calculate R_{out} ? v_{in} shorted to ground and v_{out} connected to v_{test} .
 $R_{out} = v_{test}/i_{test}$

CS with Source Degradation

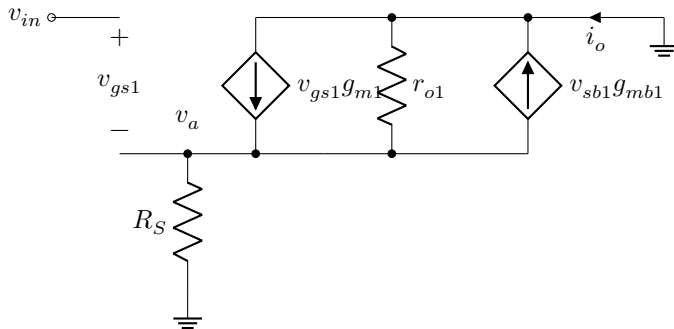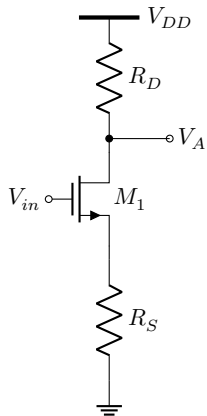

CS with Source Degradation



$$i_O = \frac{-v_a}{R_S} \quad (19)$$


$$(v_{in} - v_a)g_{m1} + i_O = \frac{v_a}{r_{o1}} + v_a g_{mb1} \quad (20)$$

$$G_m = \frac{i_O}{v_{in}} = \frac{-g_{m1}r_{o1}}{R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S} \approx -\frac{1}{R_S} \quad (21)$$

If $(g_{m1} + g_{mb1})r_{o1}R_S \gg r_{o1}$ and R_S



CS with Source Degradation


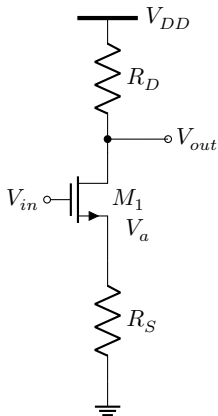


- At low V_{in} (g_m small), turn-on behavior of $R_S \neq 0$ is similar to that of $R_S = 0$.
- $V_{in} = 0V \rightarrow M_1$ off, no current flowing $\rightarrow V_a = 0V$ and $V_{out} = V_{DD}$.



CS with Source Degradation



$R_S = 0$

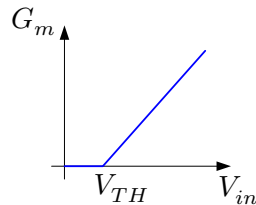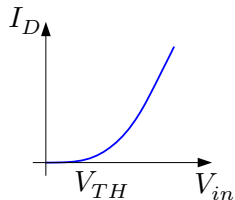


$R_S \neq 0$

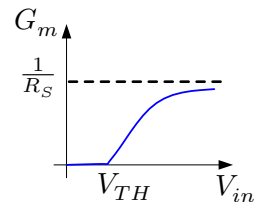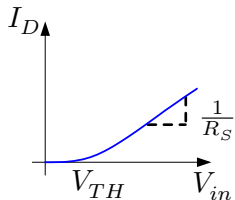



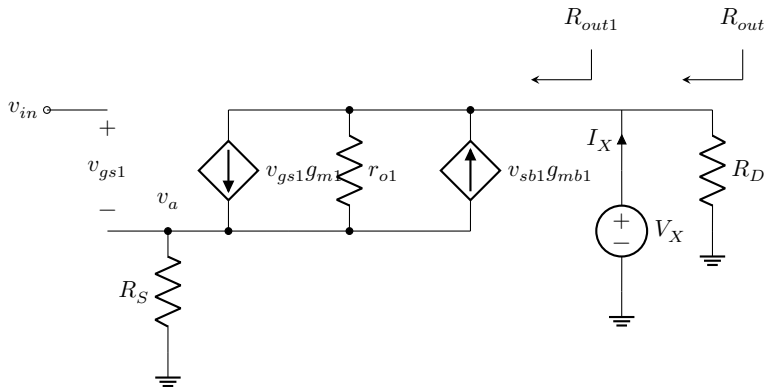CS with Source Degradation ($\lambda \neq 0, \gamma \neq 0$)



CS with Source Degradation




$$i_o = \frac{-v_a}{R_S} \quad (22)$$

$$v_a g_{m1} + v_a g_{mb1} + \frac{v_a - v_x}{r_o} + i_x = 0 \quad (23)$$

$$R_{out} = R_{out1} \parallel R_D = [R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S] \parallel R_D \approx R_D \quad (24)$$



CS with Source Degradation

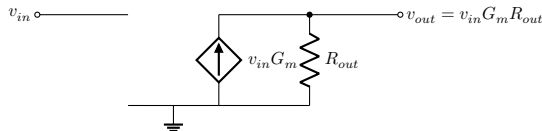

$$A_v = \frac{v_{out}}{v_{in}} = G_m R_{out} \quad (25)$$

$$= \frac{-g_{m1} r_{o1}}{R_S + r_{o1} + (g_{m1} + g_{mb1}) r_{o1} R_S} \cdot \frac{[R_S + r_{o1} + (g_{m1} + g_{mb1}) r_{o1} R_S] R_D}{[R_S + r_{o1} + (g_{m1} + g_{mb1}) r_{o1} R_S] + R_D} \quad (26)$$

$$\approx -\frac{R_D}{R_S} \quad (27)$$

If $(g_{m1} + g_{mb1}) r_{o1}$, the intrinsic gain is large.