



# Lecture 12

VE 311 Analog Circuits

Xuyang Lu  
2023 Summer



上海交通大學  
SHANGHAI JIAO TONG UNIVERSITY

# Recap of Last Lecture



- MOSFET Circuits

# Topic to be covered



- MOSFET Circuits

# Common-Source



$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} [(V_{GS} - V_{TH})V_{DS} - \frac{1}{2}V_{DS}^2] \quad (1)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad (2)$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH}) = \sqrt{2\mu_n C_{ox} \frac{W}{L'} I_D} = \frac{2I_D}{V_{GS} - V_{TH}} \quad (3)$$


$$r_o = \frac{\partial V_{DS}}{\partial I_D} = 1 / \frac{\partial I_D}{\partial V_{DS}} \approx \frac{1}{I_D \cdot \lambda} \quad (4)$$

$$V_{TH} = V_{TH0} + \gamma (|\sqrt{2\Phi_F + V_{SB}}| - \sqrt{|2\Phi_F|}) \quad (5)$$

# Common-Source



$$\lambda \neq 0, \gamma \neq 0$$

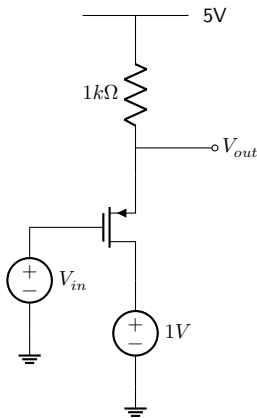

$$V_{in} = 1.8V + 0.001 \sin(2\pi \cdot 100t)$$

# Common-Source with Resistive Load




Reading: Razavi Chapter 3

## DC Analysis


$$\lambda = 0$$

$$\gamma = 0$$

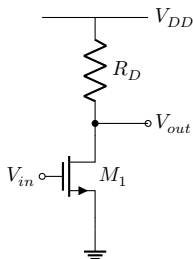

- $V_{in} < V_{TH} \rightarrow M_1$  off

$$V_{out} = V_{DD}$$

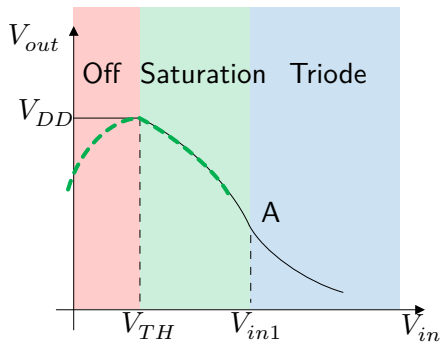


# Common-Source with Resistive Load



## DC Analysis


$$\lambda = 0$$

$$\gamma = 0$$

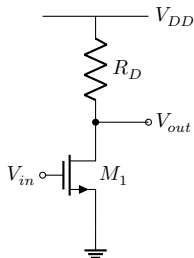

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$  in Saturation
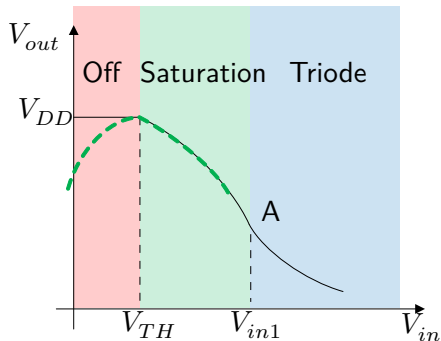
$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$




# Common-Source with Resistive Load



## DC Analysis


$$\lambda = 0$$

$$\gamma = 0$$

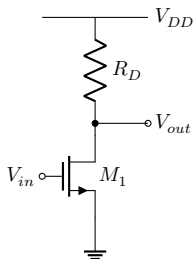

- $V_{in} > V_{in1} \rightarrow M_1$  in Triode
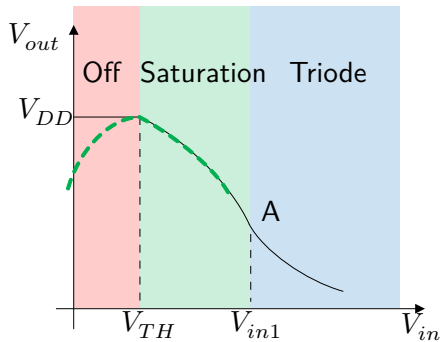
$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} ((V_{in} - V_{TH})V_{out} - \frac{1}{2}V_{out}^2)$$







# Common-Source with Resistive Load



## DC Analysis

$$\lambda = 0$$

$$\gamma = 0$$

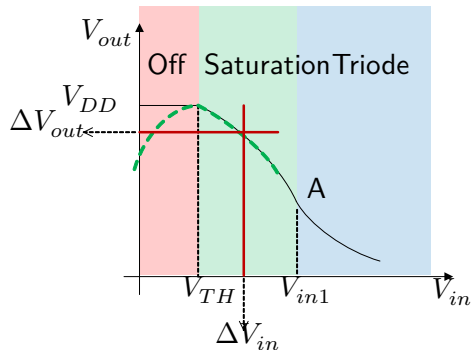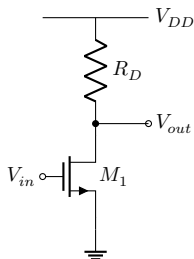

- $A_V = \frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) = -g_m \cdot R_D$


$V_{gs}$  increases by  $\partial V_{in} \rightarrow I_d$  increases by  $\partial V_{in} \cdot g_m \rightarrow V_{out}$  decreases by  $\partial V_{in} \cdot (g_m \cdot R_D)$

# Common-Source with Resistive Load




## Small-signal Analysis

$$\lambda = 0$$
$$\gamma = 0$$

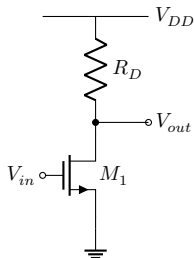
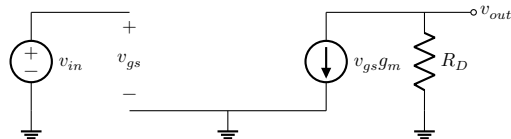
$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot R_D$$



(6)

- Small-signal analysis leads to the same result as DC analysis.



# Common-Source with Resistive Load



## DC Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

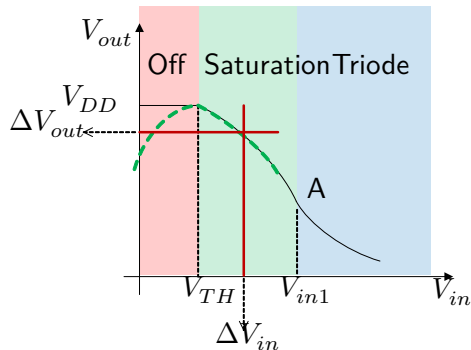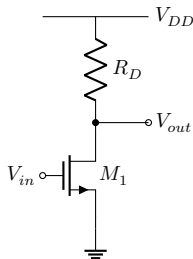

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = \frac{\partial \left[ V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out}) \right]}{\partial V_{in}} \quad (7)$$

## Common-Source with Resistive Load



$$\begin{aligned} A_v &= \frac{\partial V_{out}}{\partial V_{in}} = \frac{\partial [V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})]}{\partial V_{in}} \\ &= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) (1 + \lambda V_{out}) - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}} \end{aligned} \quad (8)$$



$$A_v = \frac{-g_m R_D}{1 + R_D I_D \lambda} = -g_m \frac{1}{\frac{1}{R_D} + \frac{1}{r_O}} = -g_m (R_D \parallel r_O) \quad (9)$$

# Common-Source with Resistive Load



## Small-signal Analysis

$\lambda \neq 0$   
 $\gamma \neq 0$

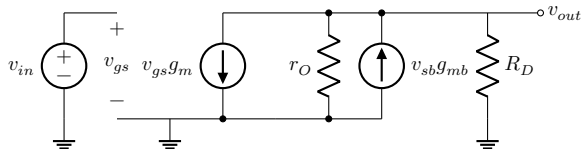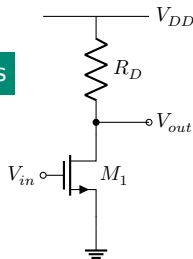




$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot (R_D \parallel r_O) \quad (10)$$

- Small-signal analysis leads to the same result as DC analysis.
- $g_m$  is a function of  $V_{GS}$  and  $V_{DS}$ , while  $r_O$  is a function of  $I_D$ .  $\rightarrow$  **Nonlinearity**
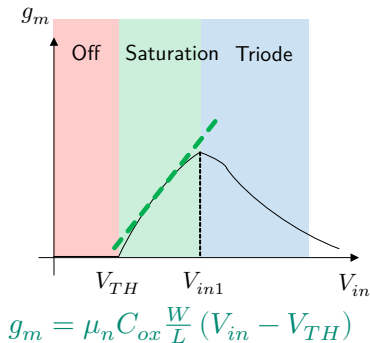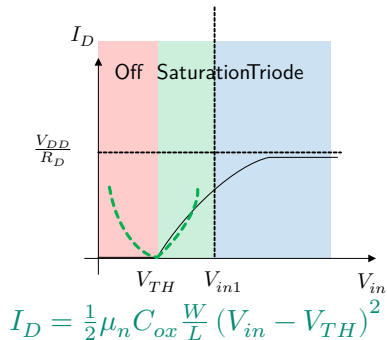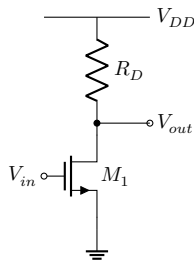
## Example




Sketch the drain current and transconductance of  $M_1$  as a function of input voltage. Assume  $\lambda = \gamma = 0$ .


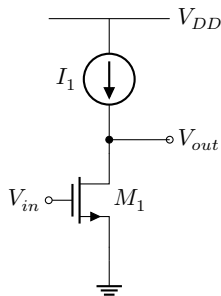
## Example



Assuming  $M_1$  in saturation, calculate its small-signal gain.




- Small-signal Analysis:

$$A_V = \frac{V_{out}}{V_{in}} = -gm_1 r_{o1} \quad (11)$$

- DC Analysis:

$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{DS}) \quad (12)$$

# Example

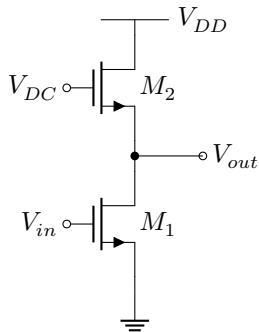

How to choose  $V_{in,DC}$ ?



# Example




# Diode-Connected Load




## DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

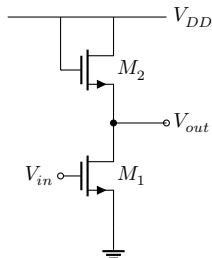

$$V_{out} = V_{in1} - V_{TH1}$$

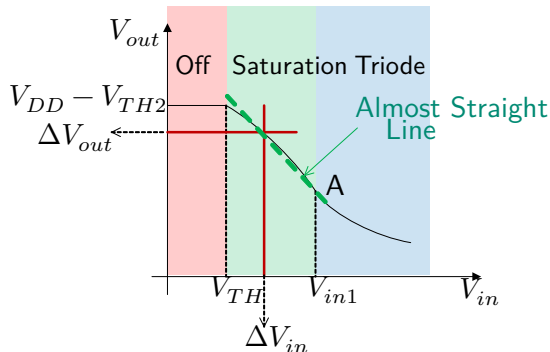

$$\frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_2 [V_{DD} - (V_{in1} - V_{TH1}) - V_{TH2}]^2 \quad (13)$$

## Diode-Connected Load



- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1$  in Saturation

$$\frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_2 [V_{DD} - V_{out} - V_{TH2}]^2 \quad (14)$$

$$\sqrt{\left(\frac{W}{L}\right)_1} (V_{in} - V_{TH1}) = \sqrt{\left(\frac{W}{L}\right)_2} (V_{DD} - V_{out} - V_{TH2}) \quad (15)$$

$$\sqrt{\left(\frac{W}{L}\right)_1} = \sqrt{\left(\frac{W}{L}\right)_2} \left( -\frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH2}}{\partial V_{in}} \right) \quad (16)$$

## Diode-Connected Load



DC Analysis  $\lambda = 0$ ,  $\gamma \neq 0$

$$\begin{aligned}\sqrt{\left(\frac{W}{L}\right)_1} &= \sqrt{\left(\frac{W}{L}\right)_2} \left( -\frac{\partial V_{out}}{\partial V_{in}} - \boxed{\frac{\partial V_{TH2}}{\partial V_{out}}} \frac{\partial V_{out}}{\partial V_{in}} \right) \\ &= \eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}\end{aligned}$$

$$A_V = \frac{\partial V_{out}}{\partial V_{in}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta} \quad (17)$$

- $\eta$  is a function of  $V_{SB}$
- $A_V$  is almost linear for  $M_1$  in saturation



# Diode-Connected Load



## Small-signal Analysis


$$\lambda = 0$$

$$\gamma \neq 0$$

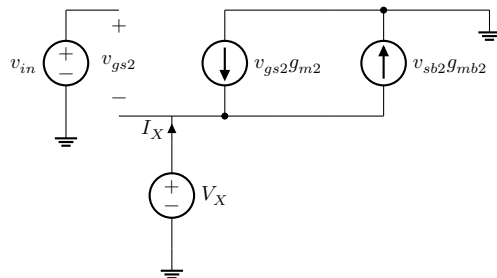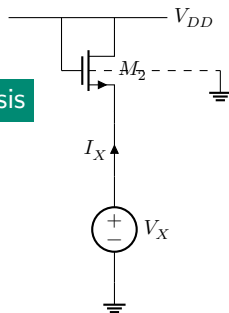

$$R_{in2} = \frac{V_x}{i_x} = \frac{1}{g_{m2} + g_{mb2}} \quad (18)$$

## Diode-Connected Load

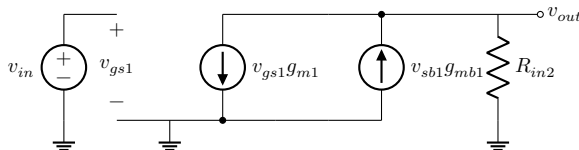

$$A_V = \frac{V_{out}}{V_{in}} = \frac{-g_{m1}}{g_{m2} + g_{mb2}} \quad (19)$$

$$= -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta} \quad (20)$$

- Small-signal analysis leads to the same result as DC analysis.



# Diode-Connected Load



## Small-signal Analysis


$$\lambda \neq 0$$

$$\gamma \neq 0$$

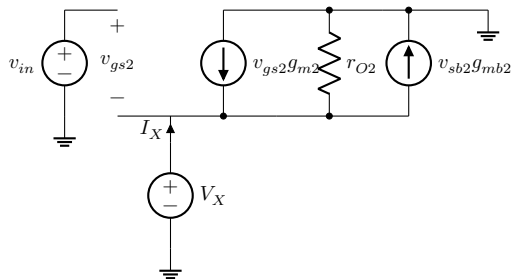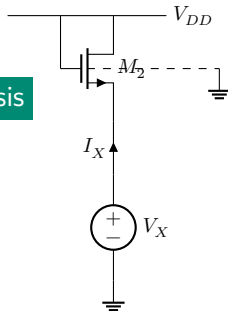

$$R_{in2} = \frac{V_x}{i_x} = \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2} \quad (21)$$

# Diode-Connected Load

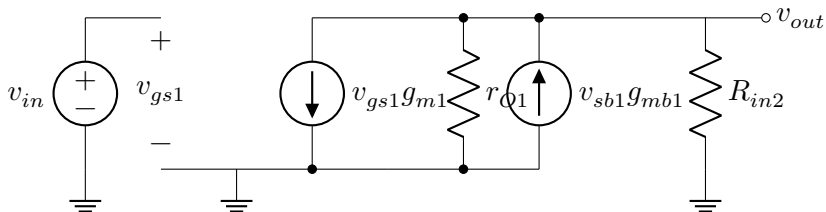

$$A_V = \frac{V_{out}}{V_{in}} = -g_{m1} \left( \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2} \parallel r_{o1} \right) \quad (22)$$






# Diode-Connected Load

$M_2$  has no body effect

Small-signal Analysis

$\lambda \neq 0$   
 $\gamma \neq 0$

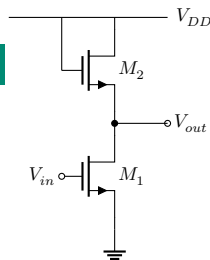

$$\begin{aligned}
 A_V &= \frac{V_{out}}{V_{in}} && r_o \gg 1/gm \\
 &= -g_{m1} \left( \frac{1}{g_{m2}} \parallel \boxed{r_{o2} \parallel r_{o1}} \right) \approx -\frac{g_{m1}}{g_{m2}} \\
 &= -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}} \\
 &= -\frac{V_{SG2} - V_{TH2}}{V_{GS1} - V_{TH1}}
 \end{aligned} \tag{23}$$

- For  $A_V = 10$ ,  $(\frac{W}{L})_1 \gg (\frac{W}{L})_2 \rightarrow$  **Disproportionally large transistor**
- For  $A_V = 10$ ,  $(V_{SG2} - V_{TH2}) = 10(V_{GS1} - V_{TH1}) \rightarrow$  **Limited output swing**