

VE311

Electronic Circuits

RC 3

Yucheng Huang

University of Michigan
Shanghai Jiao Tong University
Joint Institute

July 14, 2023

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier



2 MOSFET Differential Pair Amplifier

- Common Source Amplifier

- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier

2 MOSFET Differential Pair Amplifier

CS with Resistive Load

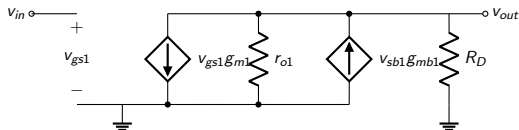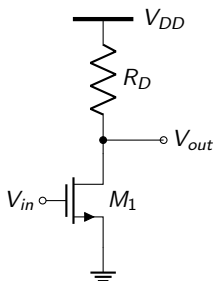

If no channel-length and body effect:

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1}R_D \quad (1)$$


No body effect:

$$A_v = -g_{m1}(R_D \parallel r_{o1}) \quad (2)$$

All the size of transistor is $W = 20\mu m, L = 1\mu m$

Example 1

CS with Diode-connected Load

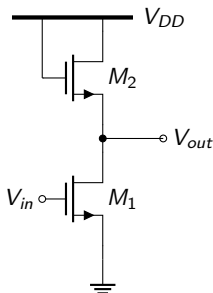


NMOS:

$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta} \quad \eta = g_{mb2}/g_{m2} \quad (3)$$


PMOS:

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}} \quad (4)$$

CS with Current Source Load

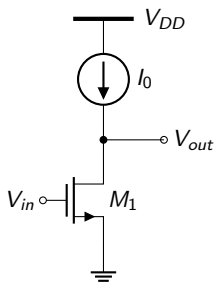

or

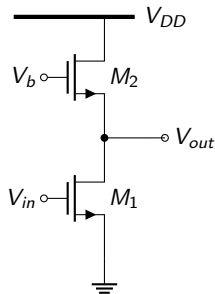

$$A_v = -g_{m1}(r_{o2} \parallel r_{o1}) \quad (5)$$

Example 2

In the common source stage amplifier, the current source is ideal.
Find the intrinsic gain A_v for the amplifier when $I_0 = 0.01$ and 0.1mA respectively. (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7\text{V}$,

$K_n = 110\mu\text{A}/\text{V}^2$, $\lambda = 0.04\text{V}^{-1}$

Parameter for PMOS: $V_{THP} = -0.7\text{V}$,



$K_p = 50\mu\text{A}/\text{V}^2$, $\lambda = 0.05\text{V}^{-1}$

All the size of transistor is $W = 20\mu\text{m}$, $L = 1\mu\text{m}$

Example 2

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier
- 2 MOSFET Differential Pair Amplifier

Source Follower

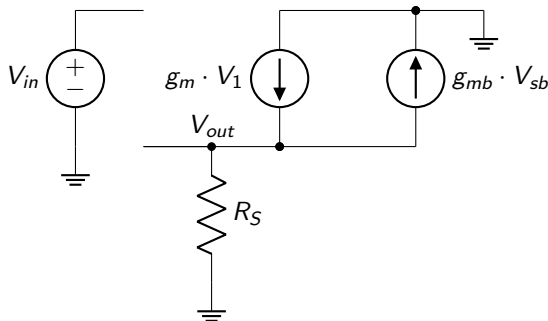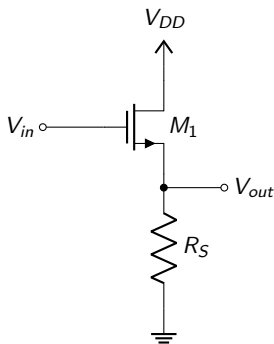

$$A_v = \frac{g_m R_S}{1 + g_m R_S (1 + \eta)} = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S} \approx \frac{1}{1 + \eta} \quad (6)$$

Example 3

In the source follower with current source load, the current source is ideal. Find the output impedance for the amplifier when $I_0 = 0.01$ and $0.1mA$ respectively. (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,


$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

Example 3

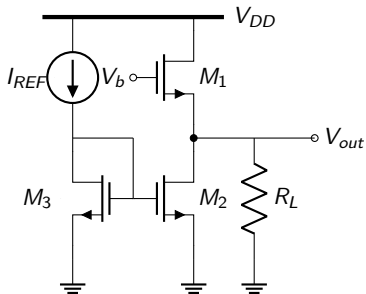


Example 3

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - **Common Gate Amplifier**
 - Cascode Amplifier

- 2 MOSFET Differential Pair Amplifier

Common Gate

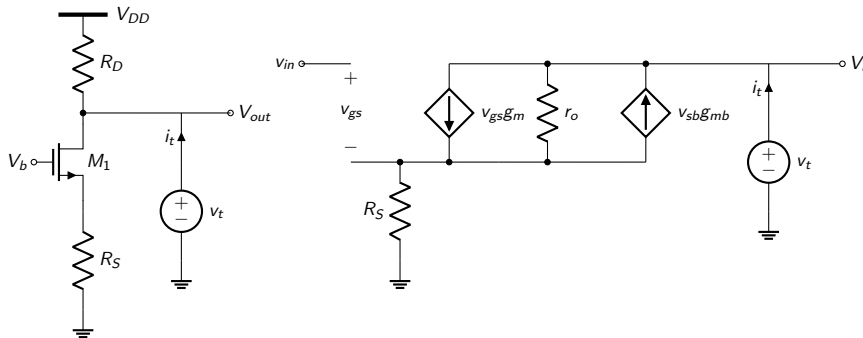

$$R_{in} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o} \begin{cases} \text{If } R_D = 0 & R_{in} = r_o \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \\ \text{If } R_D = \infty & R_{in} = \infty \end{cases} \quad (7)$$

$$R_{out} = [R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S] \parallel R_D \quad (8)$$

Example 4

In the common gate stage amplifier , what is the input resistance when $I_{REF} = 0.01mA$ and $0.1mA$ respectively? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,


$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

Example 4

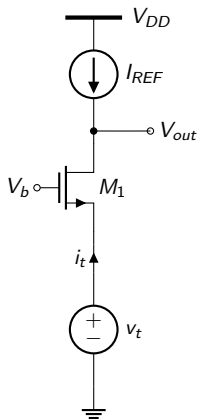


Example 4

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier

- 2 MOSFET Differential Pair Amplifier


Cascode

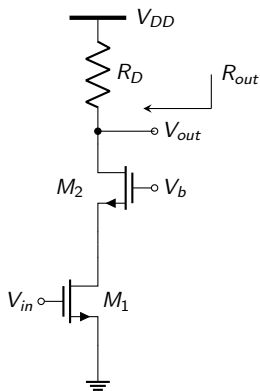

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (9)$$

$$R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \parallel R_D \quad (10)$$

Cascode

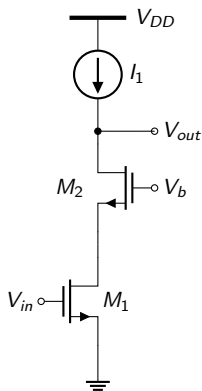


$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (11)$$

$$R_{out} = r_{o1} + r_{o2} + (g_{m2} + g_{mb2}) r_{o2} r_{o1} \quad (12)$$

$$A_v = G_m R_{out} \quad (13)$$

Cascode

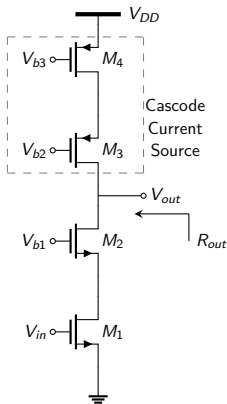

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + (r_{o2} \parallel \frac{1}{g_{m2}g_{mb2}})} \quad (14)$$

$$R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \parallel [r_{o3} + r_{o4} + (g_{m3} + g_{mb3})r_{o3}r_{o4}] \quad (15)$$

$$A_v = G_m R_{out} \quad (16)$$

Example 5

In the cascode amplifier , what is the input resistance when $I_{REF} = 0.01mA$ and $0.1mA$ respectively? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,


$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

Example 5

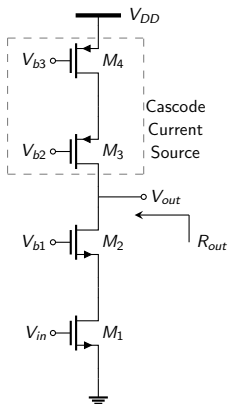


Example 5

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier

- 2 MOSFET Differential Pair Amplifier

Differential Pair

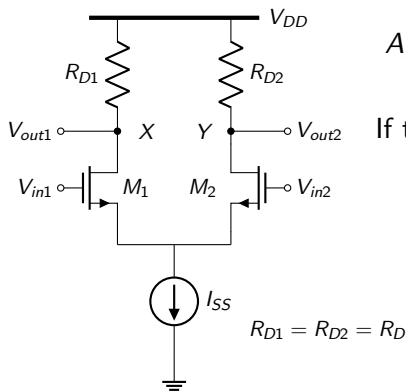


$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} = -g_m(R_D \parallel r_o) \quad (17)$$

If the circuit is fully symmetric,

$$A_{CM-DM} = \frac{V_{out1} - V_{out2}}{V_{in,CM}} = 0 \quad (18)$$


$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \infty \quad (19)$$

Differential Pair with MOS Loads

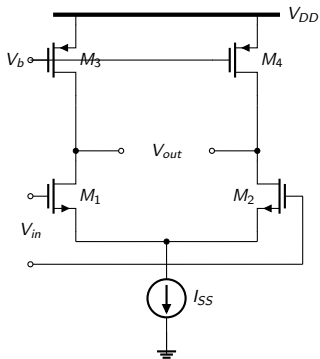


$$A_{DM} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \quad (20)$$

Differential Pair with Cascode Loads

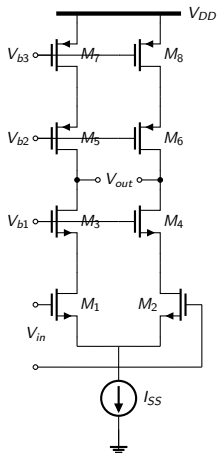

$$A_{DM} \cong -g_{m1,2}[(g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2} \parallel (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \quad (21)$$

Example 6

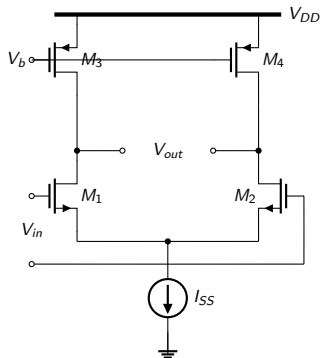

Example 6

END

Thanks