

## VE311 Electronic Circuit Homework 3

Due: May 25th

曾彦卓


Note:

520370910021

- 1) Please use A4 size paper or page.
- 2) Please clearly state out your final result for each question.
- 3) Please attach the screenshot of Pspice simulation result if necessary.

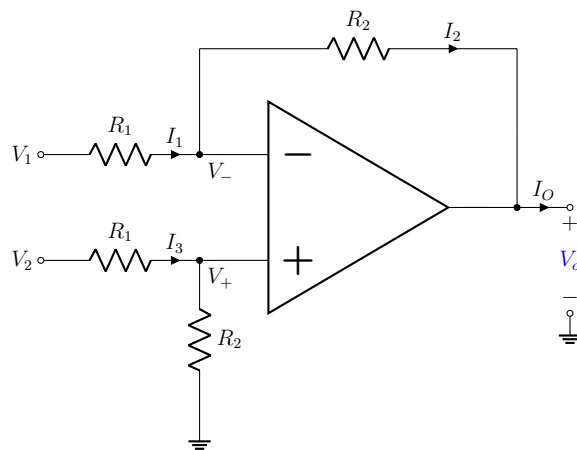
### Question 1. Difference Amplifier

Find the values of  $V_O$ ,  $V_+$ ,  $V_-$ ,  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_O$  for the difference amplifier shown below with  $V_1 = 5V$ ,  $V_2 = 3V$ ,  $R_1 = 10k\Omega$ , and  $R_2 = 100k\Omega$ .




### Question 2. Input and Output Resistance

Assuming the op amp to be ideal, derive an expression for the closed-loop gain  $v_O/v_I$  of the circuit shown below.

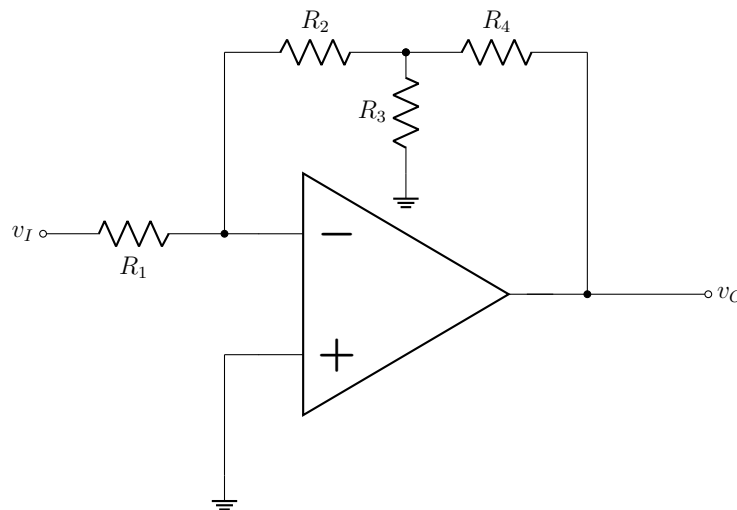

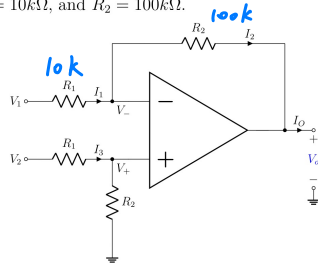**Question 1. Difference Amplifier**

Find the values of  $V_O$ ,  $V_+$ ,  $V_-$ ,  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_O$  for the difference amplifier shown below with  $V_1 = 5V$ ,  $V_2 = 3V$ ,  $R_1 = 10k\Omega$ , and  $R_2 = 100k\Omega$ .



$$I_3 = \frac{V_2}{R_1 + R_2} = \frac{3}{110 \times 10^3} = 2.73 \times 10^{-5} \text{ A}$$

$$V_+ = \frac{R_2}{R_1 + R_2} V_2 = \frac{10}{11} V_2 = 2.73 \text{ V}$$

$$\Rightarrow V_- = V_+ = \frac{10}{11} V_2 = 2.73 \text{ V}$$


$$\text{since } I_1 = \frac{V_1 - V_-}{10^4} = I_2 = \frac{V_- - V_O}{10^5} = 2.73 \times 10^{-6} \text{ A}$$

$$\Rightarrow 10(V_1 - V_-) = V_- - V_O$$

$$\Rightarrow V_O = 11V_- - 10V_1 = -20 \text{ V}$$
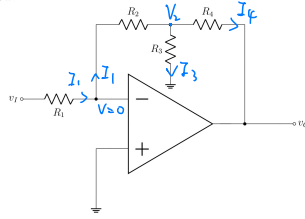
### Question 2. Input and Output Resistance

Assuming the op amp to be ideal, derive an expression for the closed-loop gain  $v_O/v_I$  of the circuit shown below.



$$I_1 = \frac{V_i}{R_1} \Rightarrow V_2 = -I_1 \cdot R_2 = \frac{-R_2}{R_1} V_i \quad (1)$$

$$I_3 = \frac{V_3}{R_3}, \quad I_4 = \frac{V_2 - V_O}{R_4} \Rightarrow \frac{V_3}{R_3} + \frac{V_2 - V_O}{R_4} = I_1 \quad (2)$$

Plug (1) into (2):


$$\frac{-R_2}{R_1 R_3} V_i + \frac{-R_2}{R_1 R_4} V_i - \frac{V_O}{R_4} = \frac{V_i}{R_1}$$

$$\Rightarrow -R_2^2 R_4 V_i - R_2^2 R_3 V_i - R_1 R_2 R_3 V_O = R_2 R_3 R_4 V_i$$

$$\Rightarrow G = \frac{V_O}{V_i} = - \frac{R_2 R_3 R_4 + R_2^2 R_3 + R_1^2 R_4}{R_1 R_2 R_3}$$

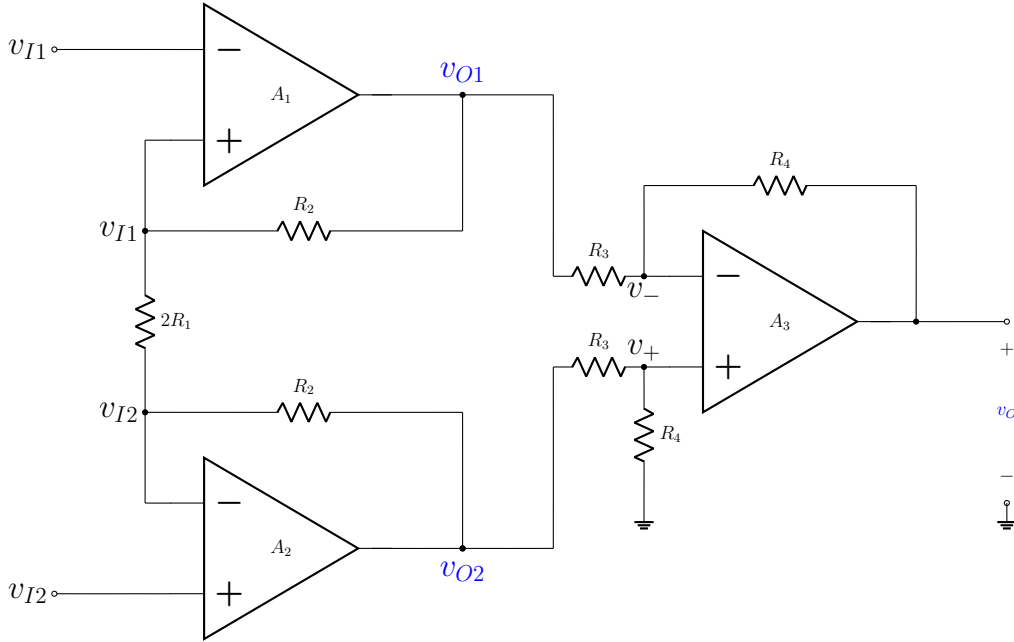
### Question 3. Instrumentation Amplifier

Consider the instrumentation amplifier shown below with a common-mode input voltage of  $+5V$  (dc) and a differential input signal of  $10 - mV$ -peak sine wave. Let  $(2R_1) = 1k\Omega$ ,  $R_2 = 0.5M\Omega$ , and  $R_3 = R_4 = 10k\Omega$ . Find the voltage at every node (total 9 nodes) in the circuit. Also find the differential voltage gain  $A_d$ .



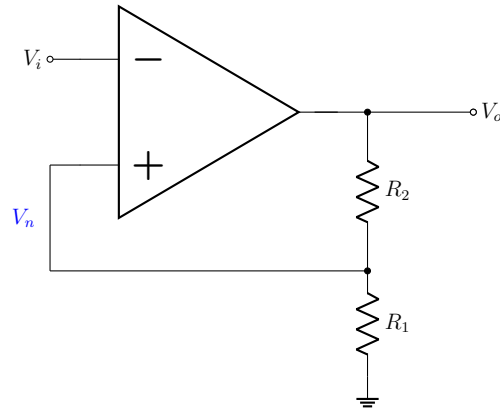
### Question 4. Nonideal Amplifier Analysis

A noninverting amplifier is constructed with  $R_1 = 1k\Omega$  and  $R_2 = 39k\Omega$  using an operational amplifier with an open-loop gain of  $80dB$  and an output resistance of  $50\Omega$ . Find the output resistance of the noninverting amplifier.


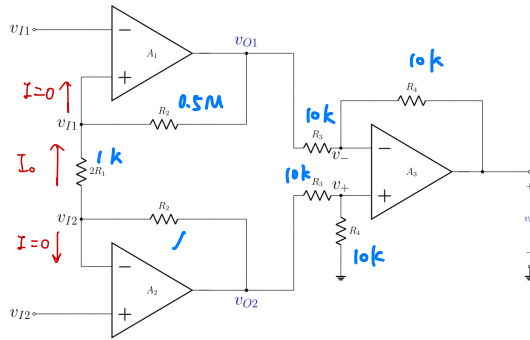
### Question 3. Instrumentation Amplifier

Consider the instrumentation amplifier shown below with a common-mode input voltage of  $+5V$  (dc) and a differential input signal of  $10 - mV$ -peak sine wave. Let  $(2R_1) = 1k\Omega$ ,  $R_2 = 0.5M\Omega$ , and  $R_3 = R_4 = 10k\Omega$ . Find the voltage at every node (total 9 nodes) in the circuit. Also find the differential voltage gain  $A_d$ .



Assume  $V_{Id} = 20 \times 10^{-3} k$   
where  $k = \sin(\omega t + \varphi)$

$$V_{I2} = 5 + 0.01 k$$

$$V_{I1} = 5 - 0.01 k$$

$$\Rightarrow V_{O2} = V_{I2} + \frac{V_{Id}}{2R_1} \cdot R_2 = 5 + 0.01 k + \frac{0.02 k}{10^3} \cdot 0.5 \times 10^6 = 5 + 10.01 k$$

$$V_{O1} = V_{I1} - \frac{V_{Id}}{2R_1} \cdot R_2 = 5 - 0.01 k - \frac{0.02 k}{10^3} \cdot 0.5 \times 10^6 = 5 - 10.01 k$$

$$\text{since } V_- = V_+ (= V)$$

$$\Rightarrow \frac{V_{O1} - V_-}{R_3} = \frac{V_- - V_O}{R_4} \Leftrightarrow \frac{(5 - 10.01 k) - V}{10 \times 10^3} = \frac{V - V_O}{10 \times 10^3}$$

$$\frac{0 - V_4}{R_4} = \frac{V_+ - V_{O2}}{R_3} \Leftrightarrow \frac{0 - V}{10 \times 10^3} = \frac{V - (5 + 10.01 k)}{10 \times 10^3}$$

$$\Rightarrow V_+ = V_- = V = 2.5 + 5.005 k,$$

$$V_O = 2V - (5 + 10.01 k) = 20.02 k$$


$$\Rightarrow A_d = \frac{V_O}{V_{Id}} = \frac{20.02 k}{20 \times 10^{-3} k} = 1.001 \times 10^3 \approx 1 \times 10^3$$

$$\text{According to the slide, } A_d = \frac{R_4}{R_3} \cdot \frac{R_2}{R_1} = 1 \cdot \frac{0.5 \times 10^6}{0.5 \times 10^3} = 1 \times 10^3$$

$\Rightarrow$  My answer is correct
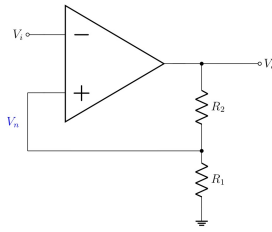
#### Question 4. Nonideal Amplifier Analysis


A noninverting amplifier is constructed with  $R_1 = 1k\Omega$  and  $R_2 = 39k\Omega$  using an operational amplifier with an open-loop gain of  $80dB$  and an output resistance of  $50\Omega$ . Find the output resistance of the noninverting amplifier.



$$\text{open-loop } G_1 = \frac{A}{1 + \beta A} \quad \text{and} \quad \beta = \frac{R_1}{R_1 + R_2} = \frac{1}{40}$$

$$\Rightarrow 80 = \frac{A}{1 + \frac{1}{40} A} \quad \Rightarrow \quad A = -80$$


To calculate  $R_{TH}$ :

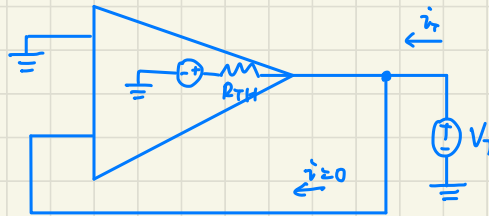

$$R_{TH} = \frac{R_{out}}{1 + A} = \frac{50}{-79} = -0.633$$
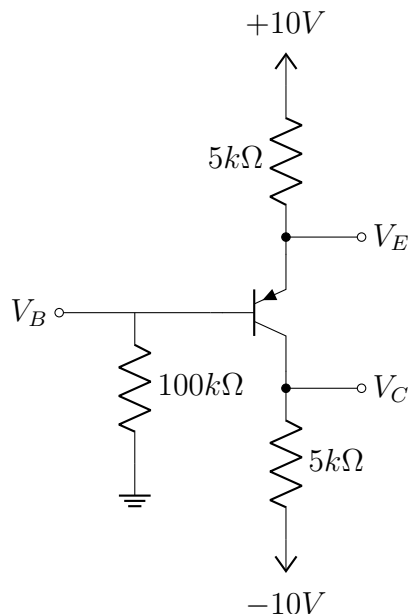
### Question 5. BJT

In the circuit shown below, measurement indicates  $V_B$  to be  $+1.0V$  and  $V_E$  to be  $+1.7V$ . What are  $\alpha$  and  $\beta$  for this transistor? What voltage  $V_C$  do you expect at the collector?




### Question 6. Saturation

For the circuit shown below, it is required to determine the value of the voltage  $V_{BB}$  that results in the transistor operating


- 1) in the active mode with  $V_{CE} = 5V$
- 2) at the edge of saturation
- 3) deep in saturation with  $\beta_{forced} = 10$

For simplicity, assume that  $V_{BE}$  remains constant at  $0.7V$ . The transistor  $\beta$  is specified to be 50.

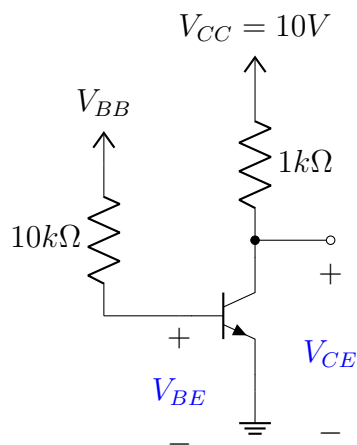

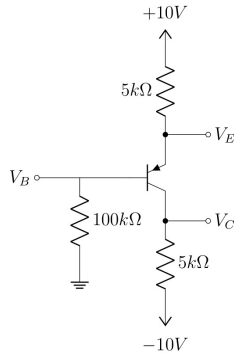**Question 5. BJT**

In the circuit shown below, measurement indicates  $V_B$  to be  $+1.0V$  and  $V_E$  to be  $+1.7V$ . What are  $\alpha$  and  $\beta$  for this transistor? What voltage  $V_C$  do you expect at the collector?



From  $V_B = 1V$ :

$$-1 + 100 \cdot 10^3 I_B = 0, \text{ so } I_B = 0.01 \text{ mA}$$

Also, From  $V_E = 1.7V$

$$-10 + 5 \cdot 10^3 I_E + 1.7 = 0$$

And as  $I_B + I_C = I_E$

$$\Rightarrow I_C = 1.65 \text{ mA}$$

$$\text{Therefore, } \alpha = I_C / I_E = 0.99$$

$$\beta = I_C / I_B = 165$$

$$V_C = I_C \cdot 5 \times 10^3 - 10 = -1.75 \text{ V}$$




**Question 6. Saturation**

For the circuit shown below, it is required to determine the value of the voltage  $V_{BB}$  that results in the transistor operating

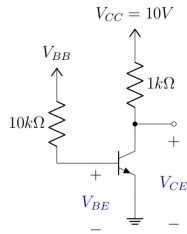- 1) in the active mode with  $V_{CE} = 5V$
- 2) at the edge of saturation
- 3) deep in saturation with  $\beta_{forced} = 10$

For simplicity, assume that  $V_{BE}$  remains constant at 0.7 V. The transistor  $\beta$  is specified to be 50.



(a)

$$\begin{cases} V_{BB} - I_B R_B - 0.7 = 0 \\ V_{CC} - I_C R_C - V_{CE} = 0 \\ \beta = \frac{I_C}{I_B} \text{ (in active region)} \end{cases} \Rightarrow \begin{cases} I_C = 5 \text{ mA} \\ I_B = 0.1 \text{ mA} \\ V_{BB} = 1.7 \text{ V} \end{cases}$$

(b)

We have known that:


$$\begin{cases} V_{CE} = 0.2 \\ V_{BE} = 0.7 \\ V_{BB} - I_B R_B - 0.7 = 0 \\ V_{CC} - I_C R_C - V_{CE} = 0 \\ I_B = \frac{I_C}{\beta} \approx \frac{I_C}{50} \end{cases} \Rightarrow \begin{cases} I_C = 9.8 \text{ mA} \\ I_B = 0.196 \text{ mA} \\ V_{BB} = 2.66 \text{ V} \end{cases}$$

(c)

$$\begin{cases} V_{BB} - I_B R_B - 0.7 = 0 \\ V_{CC} - I_C R_C - 0.2 = 0 \\ I_B = \frac{I_C}{\beta_f} \approx \frac{I_C}{10} \end{cases} \Rightarrow \begin{cases} I_C = 9.8 \text{ mA} \\ I_B = 0.98 \text{ mA} \\ V_{BB} = 10.5 \text{ V} \end{cases}$$
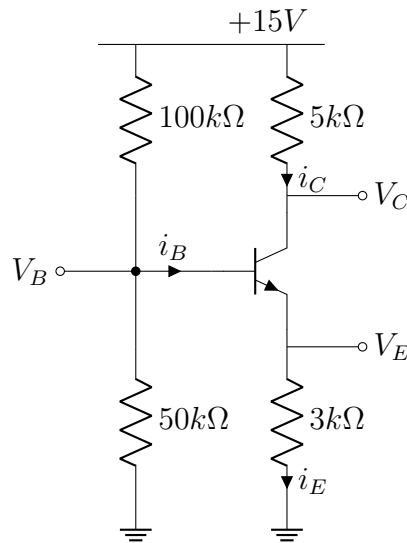
### Question 7. BJT at DC


We want to analyze the circuit shown below to determine the voltages at all nodes and the currents through all branches. Assume  $\beta = 100$ .



### Question 8. Small Signal Analysis


Consider the following BJT amplifier, determine its small-signal, open-circuit voltage gain  $A_v = \frac{v_o(t)}{v_i(t)}$ . Hint: Try to follow the steps to solve this question

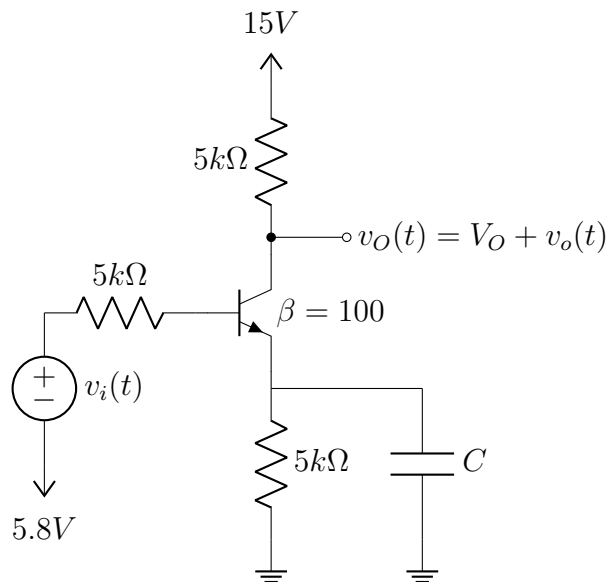- 1) Complete a D.C. Analysis.
- 2) Calculate the small-signal circuit parameters for each BJT.
- 3) Carefully replace all BJTs with their small-signal circuit model.
- 4) Set all D.C. sources to zero.
- 5) Analyze small-signal circuit.


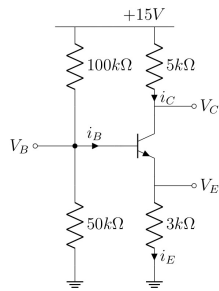
### Question 7. BJT at DC


We want to analyze the circuit shown below to determine the voltages at all nodes and the currents through all branches. Assume  $\beta = 100$ .



$$V_{TH} = 15 \cdot \frac{50}{150} = 5V$$

$$R_{TH} = \frac{100 \times 50}{100 + 50} = \frac{100}{3} k\Omega$$

$\Rightarrow$  The circuit is as below

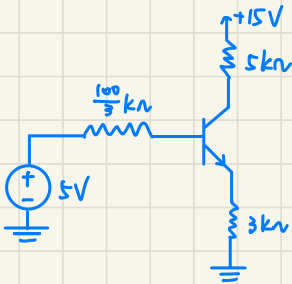

$$\Rightarrow -5 + 33.33k \cdot I_B + 0.7 + 3k I_E = 0$$

$$\text{and } I_E = (1 + \beta) \cdot I_B$$

$$\Rightarrow I_B = 0.0127 \text{ mA}, I_E = 1.291 \text{ mA}$$

$$\text{So } I_C = \beta I_B = 1.27 \text{ mA}$$

$$\Rightarrow V_E = 3k \cdot I_E = 3.873 \text{ V}$$

$$\text{So } V_B = V_E + 0.7 = 4.573 \text{ V}$$


$$\text{Since } 15 - 5k I_C - V_C = 0$$

$$\Rightarrow V_C = 8.65 \text{ V}$$

### Question 8. Small Signal Analysis

Consider the following BJT amplifier, determine its small-signal, open-circuit voltage gain  $A_v = \frac{v_o(t)}{v_i(t)}$ . Hint: Try to follow the steps to solve this question

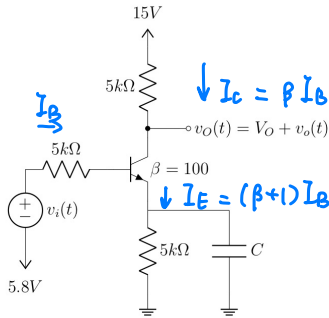- 1) Complete a D.C. Analysis.
- 2) Calculate the small-signal circuit parameters for each BJT.
- 3) Carefully replace all BJTs with their small-signal circuit model.
- 4) Set all D.C. sources to zero.
- 5) Analyze small-signal circuit.



DC Analysis :

By KVL :

$$5.8 = 5k I_B + V_{BE} + (\beta + 1) 5k I_B$$


$$\Rightarrow I_B = \frac{5.8 - 0.7}{5k + 101 \cdot 5k} = 10 \mu A$$

$$\Rightarrow I_C = \beta I_B = 1mA$$

$$g_m = \frac{I_C}{V_T} = \frac{1m}{25m} = 40mA/V$$

$$R_\pi = \frac{\beta}{g_m} = \frac{100}{40m} = 2.5k\Omega$$

Small Signal Analysis :

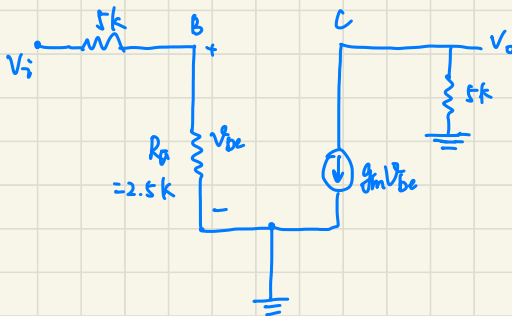

by voltage division rule:

$$v_{be} = \frac{2.5k}{2.5k + 5k} \cdot v_i$$
$$= \frac{1}{3} v_i$$

by ohm's law:

$$v_o = -g_m v_{be} \cdot 5k$$

$$\frac{v_o(t)}{v_i(t)} = \frac{-g_m 5k}{3} = \frac{-200}{3} = -66.67$$