

VE311 Final Review - Frequency Response (L19-L22)

Zeyu Zhang

University of Michigan-Shanghai Jiao Tong University Joint Institute

July 28, 2023




JOINT INSTITUTE

交大密西根学院

- ▶ Review of ve216
- ▶ Finite op amp bandwidth
- ▶ Miller effect

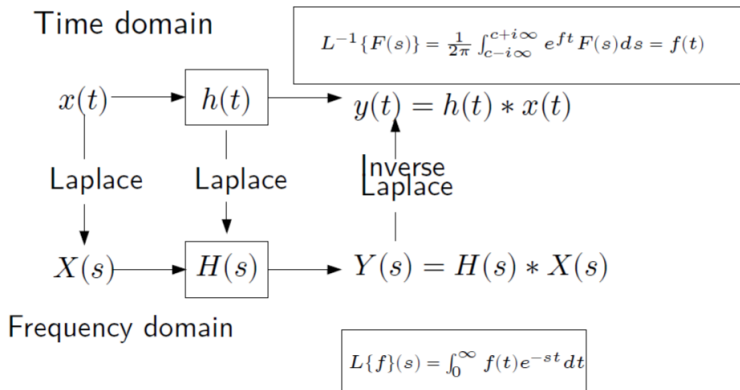- ▶ Input signal \Rightarrow *Circuit* \Rightarrow Output signal
- ▶ Time domain \iff Frequency domain (s-domain)



Transfer function:

$$H(s) = \frac{Y(s)}{X(s)} \quad (1)$$

Useful Laplace transform:

$$\frac{K}{(s + \alpha)(s + \beta)} \Leftrightarrow \frac{K}{(\beta - \alpha)} (e^{-\alpha t} - e^{-\beta t}) u(t) \quad (2)$$

$$H(s) = H_0 \frac{\prod_z (s - s_z)}{\prod_p (s - s_p)} = H'_0 \frac{\prod_z (\tau_z s - 1)}{\prod_p (\tau_p s - 1)} \quad (3)$$

- Zeros: s_z
- Poles: s_p
- Magnitude:


$$|H(s)| = K \frac{\prod_{i=1}^m |(s - z_i)|}{\prod_{i=1}^n |(s - p_i)|} \quad (4)$$

- Phase:

$$\angle H(s) = \sum_{i=1}^m \angle (s - z_i) - \sum_{i=1}^n \angle (s - p_i) \quad (5)$$

Pole-zero representation

► Complex plane

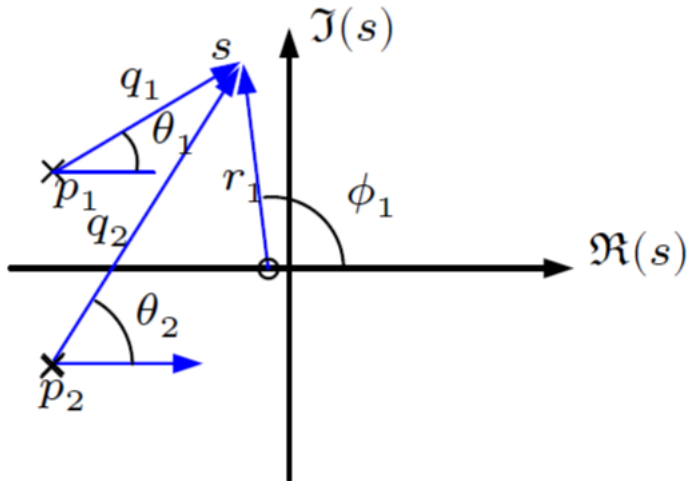

- ▶ Bode plot (magnitude)
 - ▶ Zero contributes 20dB/decade slope if $s > s_z$
 - ▶ Pole contributes -20dB/decade slope if $s > s_p$
 - ▶ Complex conjugate zeros contributes 40dB/decade slope if $s > |s_z|$
 - ▶ Complex conjugate poles contributes -40dB/decade slope if $s > |s_p|$
- ▶ Bode plot (phase)
 - ▶ 90° if $s_z = 0$
 - ▶ -90° if $s_p = 0$
 - ▶ Increase by 90° and passes through the midpoint of 45° at the break point $s = s_z \neq 0$
 - ▶ Decrease by 90° and passes through the midpoint of -45° at the break point $s = s_p \neq 0$

- ▶ Example: Find the Bode log magnitude and phase angle plot for the transfer function,


$$H(s) = \frac{200(s + 20)}{s(2s + 1)(s + 40)} \quad (6)$$

- ▶ Solution: Firstly, change the form to


$$H(s) = \frac{100(s/20 + 1)}{s(s/0.5 + 1)(s/40 + 1)} \quad (7)$$

Bode plot

► Magnitude

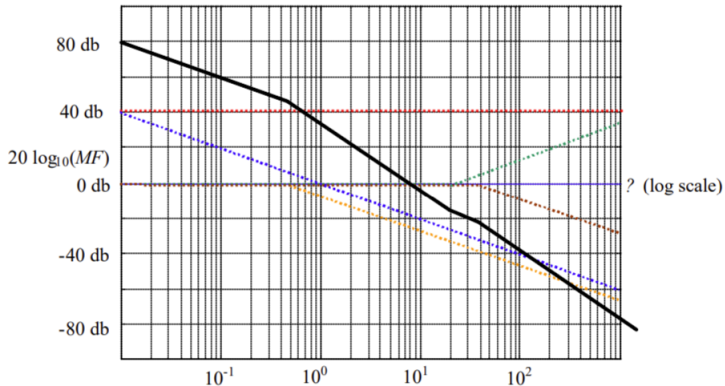


► Phase

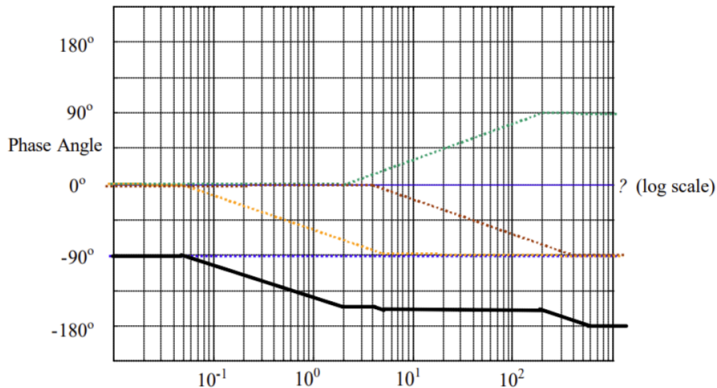

Finite op amp bandwidth
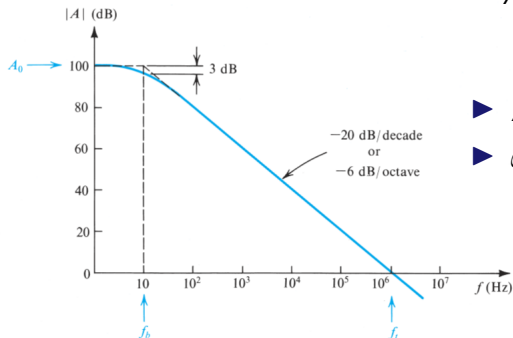
$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_b} \quad (8)$$



► A_0 : dc gain

► ω_b : 3-dB frequency

- Magnitude:

$$|A(j\omega)| = \frac{A_0\omega_b}{\omega} \quad (9)$$


- Unity gain:

$$A(j\omega_t) = 1 \quad (10)$$


- unity-gain bandwidth (gain–bandwidth product)

$$f_t = \frac{\omega_t}{2\pi} = \frac{A_0\omega_b}{2\pi} \quad (11)$$

Miller effect

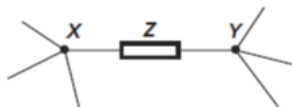

(a)

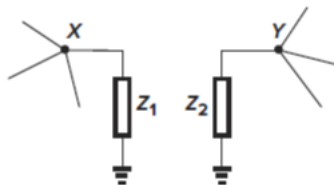


(b)

$$A_v = \frac{V_Y}{V_X} \quad (12)$$

$$Z_1 = \frac{Z}{1 - A_v} \quad (13)$$

$$Z_2 = \frac{Z}{1 - A_v^{-1}} \quad (14)$$

Miller effect

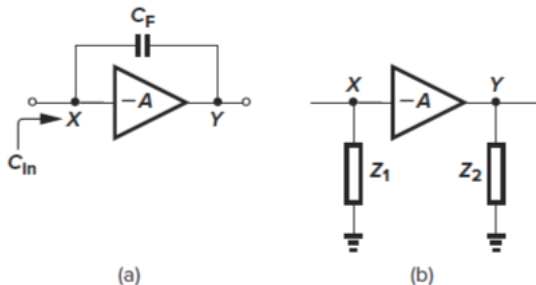

$$Z_1 = \frac{1}{1 + A} \frac{1}{sC_F} \quad (15)$$


Input Capacitance:

$$C_{in} = C_F(1 + A) \quad (16)$$


Reason:

$$\Delta Q = C_F(1 + A)\Delta V = C_{in}\Delta V \quad (17)$$

Invalid:

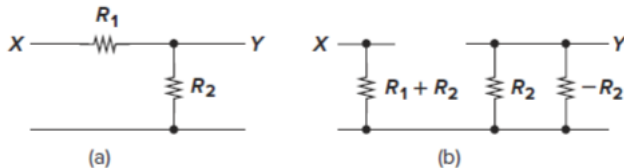


valid:

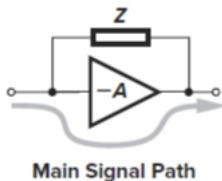

Miller effect

Example:

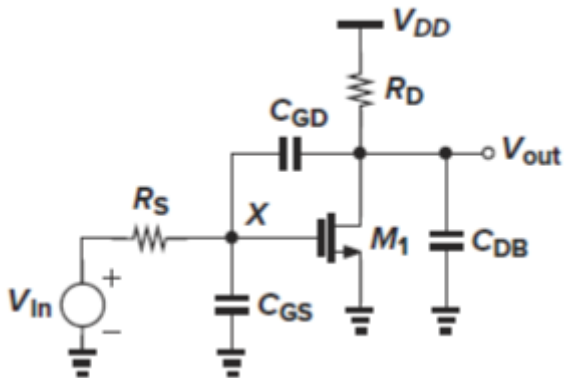


$$A_v = -g_m R_D \quad (18)$$

$$\omega_{in} = \frac{1}{R_S [C_{GS} + (1 + g_m R_D) C_{GD}]} \quad (19)$$

$$\omega_{out} = \frac{1}{R_D [C_{DB} + (1 + 1/(g_m R_D)) C_{GD}]} \quad (20)$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)} \quad (21)$$

Cascode

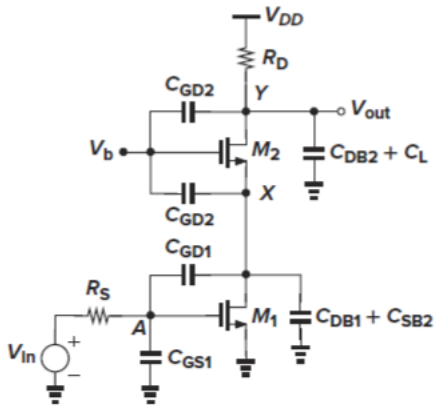

$$A_v = -\frac{g_{m1}}{g_{m2} + g_{mb2}}, \quad \text{negligible channel-length modulation} \quad (22)$$

$$\omega_{p,A} = \frac{1}{R_S \left[C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{GD1} \right]} \quad (23)$$

$$\omega_{p,X} = \frac{g_{m2} + g_{mb2}}{C_{DB1} + C_{SB2} + C_{GS2} + \left(1 + \frac{g_{m2} + g_{mb2}}{g_{m1}} \right) C_{GD1}} \quad (24)$$

$$\omega_{p,Y} = \frac{1}{R_D (C_{DB2} + C_L + C_{GD2})} \quad (25)$$

Good Luck