


Q1

1.



$$P(W) = [mW \cdot 10^{\frac{B}{10}}] = 0.1995 W$$

$$\Rightarrow V_{rms} = \sqrt{P \cdot R} = 1 V$$

2.

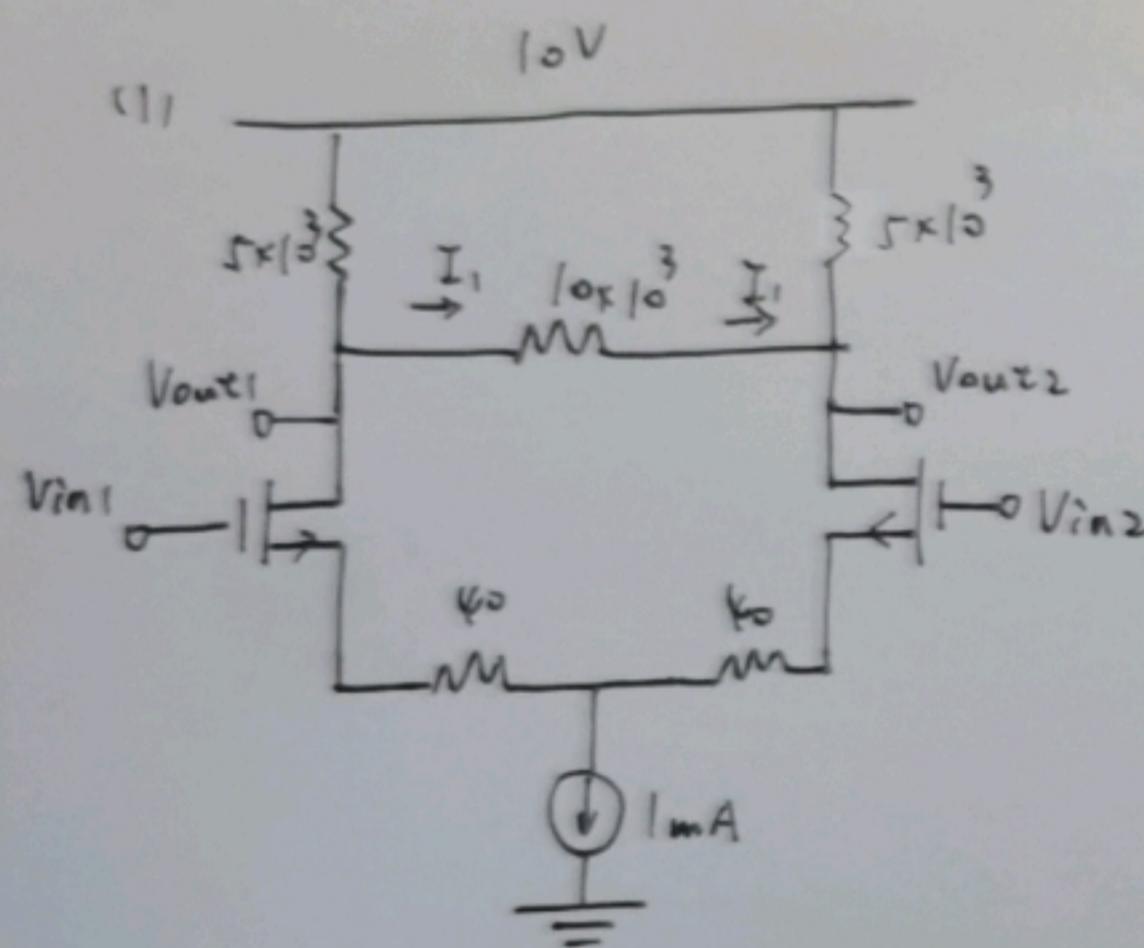

(2) $I_1 = 0$ when common mode

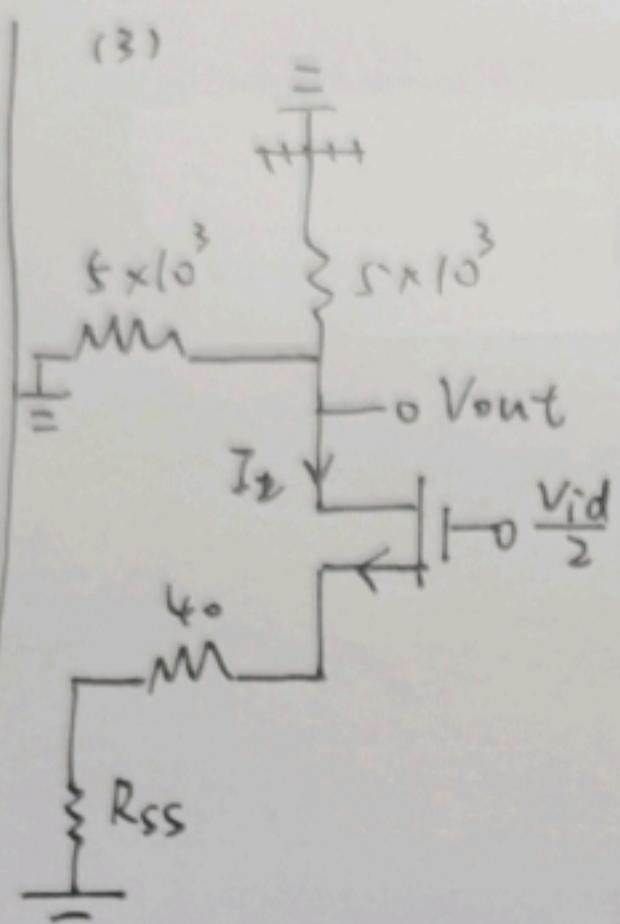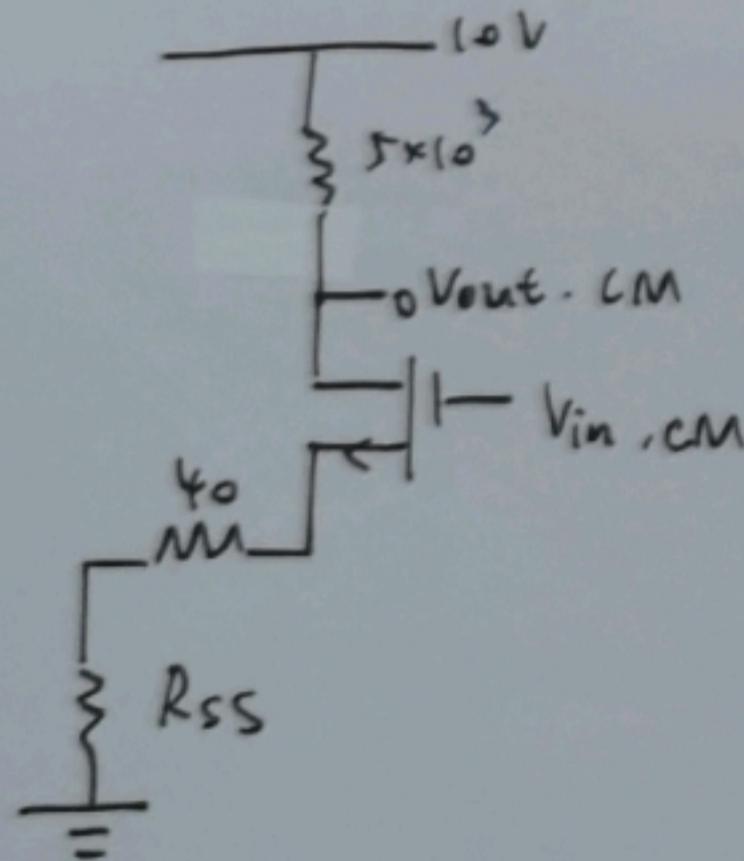


$$\frac{-V_{out}}{10^4} = \sqrt{10^{-2} I_2} \left(\frac{V_{id}}{2} - V_1 \right) = \frac{V_1}{40} = I_2$$

$$\Rightarrow \frac{\delta V_{out}}{\delta \frac{V_{id}}{2}} = A_{UDM}$$

(4)

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_2}$$

$$r_o = 0 \quad \cdot \quad g_{mb} = 0$$

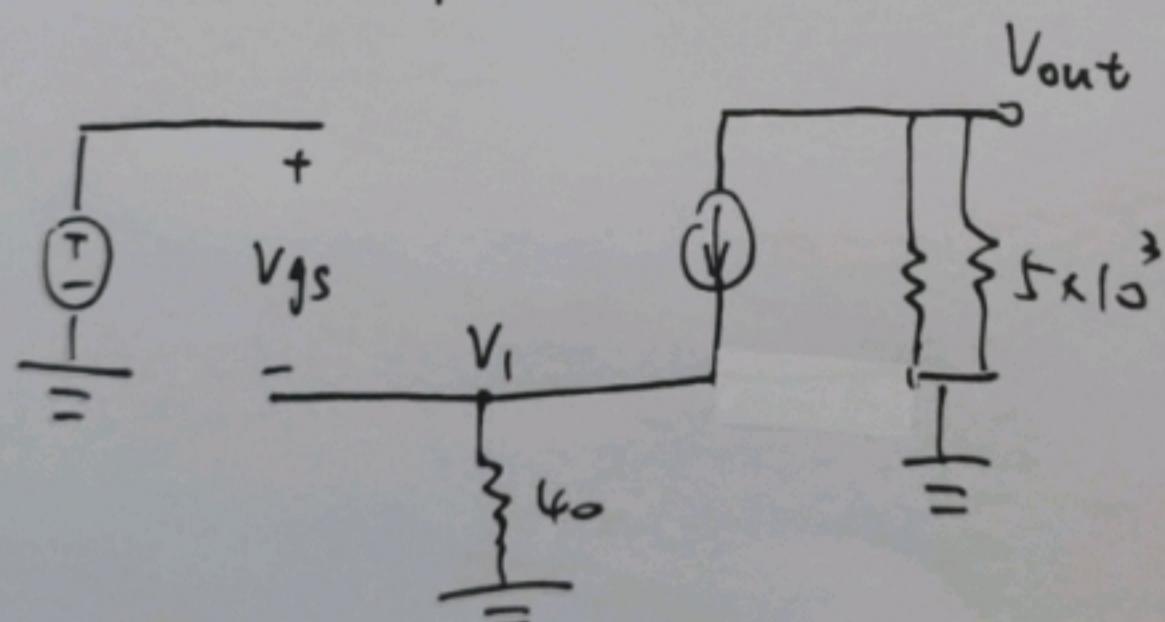

$$\frac{-V_{out}}{5 \times 10^3} \times 2 = g_m \left(\frac{V_{id}}{2} - V_1 \right)$$


$$= \frac{V_1}{40} = I_2$$

Q1

$$Z_1 = \frac{A}{1+Z} = \frac{2}{2+3} = \frac{2}{5}$$


$$Z_2 = \frac{1}{1+\frac{A}{Z}} = \frac{1}{1+\frac{4}{2}} = \frac{1}{3}$$
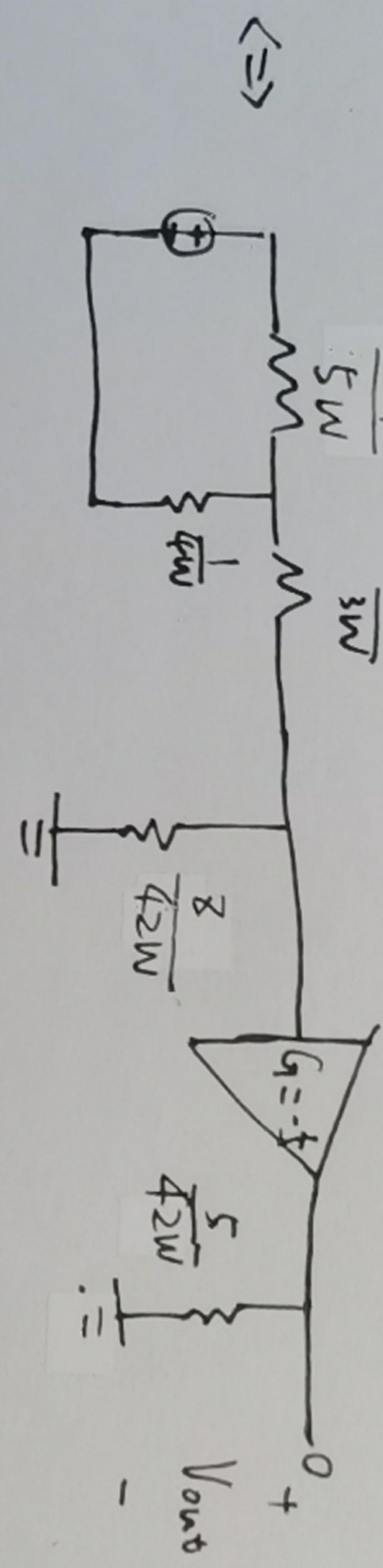
$$Z_C = \frac{1}{2\pi f C} = \frac{1}{WC}$$



$$\Rightarrow P_{out} = \frac{5}{42\pi} \times 10^{15} \text{ W}$$

(Q3)

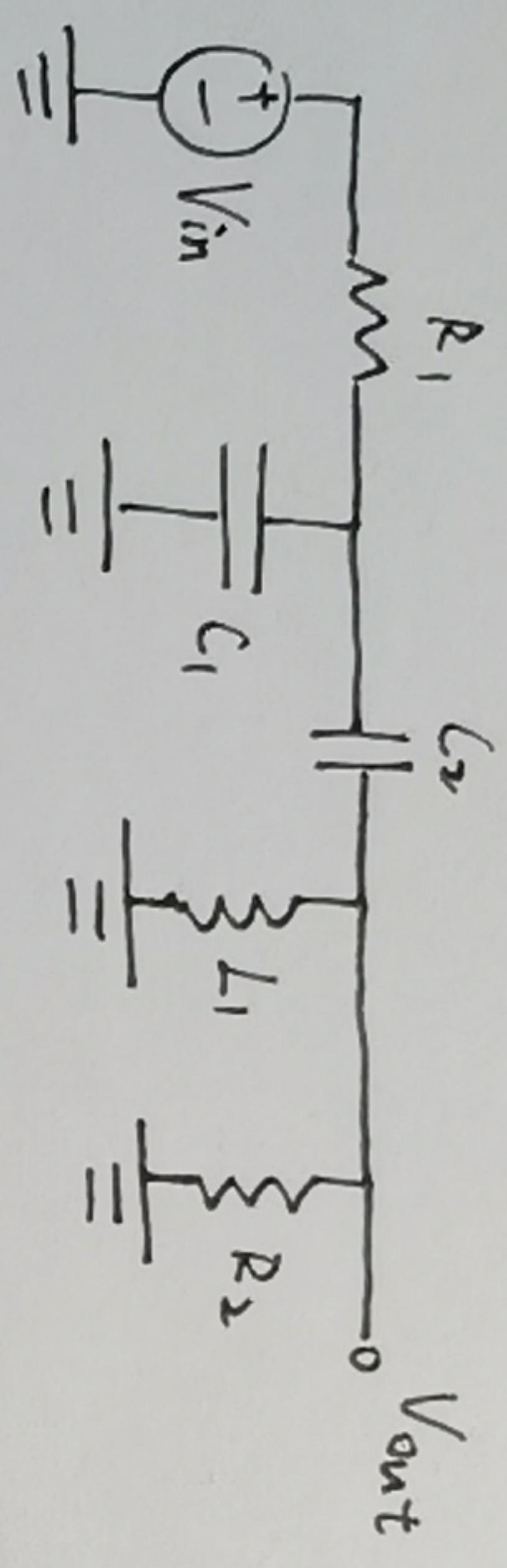

$$L_1 = 10 \times 10^{-9} \text{ H}, \quad C_1 = 120 \times 10^{-15} \text{ F},$$

$$C_2 = 150 \times 10^{-15} \text{ F}, \quad R_1 = 4\Omega \text{ and } R_2 = 8\Omega$$

Firstly, we need to calculate τ_i^0

$$\textcircled{1} \quad \tau_i^0 : \text{ cut off } \Rightarrow \tau_i^0 = R_1 C_1$$

$$\textcircled{2} \quad \tau_i^0 : \text{ cut off } \Rightarrow \tau_i^0 = \frac{R_1}{R_1 + R_2} C_1$$

$$\frac{V_t}{i_t} = R_1 \Rightarrow \tau_i^0 = R_1 C_2$$

$$\textcircled{3} \quad \tau_i^0 : C_2 \text{ cut off } \Rightarrow \tau_i^0 = \frac{L_1}{R_2}$$

Then we calculate τ_i^*

$$\textcircled{1} \quad \tau_i^* : \text{ cut off } \Rightarrow \tau_i^* = \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow \tau_i^* = R_2 C_2$$

Then we need to find H^{ii}

$$H^1 = 0$$

$$H^2 = \frac{R_2}{R_1 + R_2}$$


$$H^{12} = 0$$

4.

(a)

$$\Rightarrow \lambda = 0 \text{ and } \gamma = 0$$

$$V_{S_2} = I_{out} \cdot 100$$

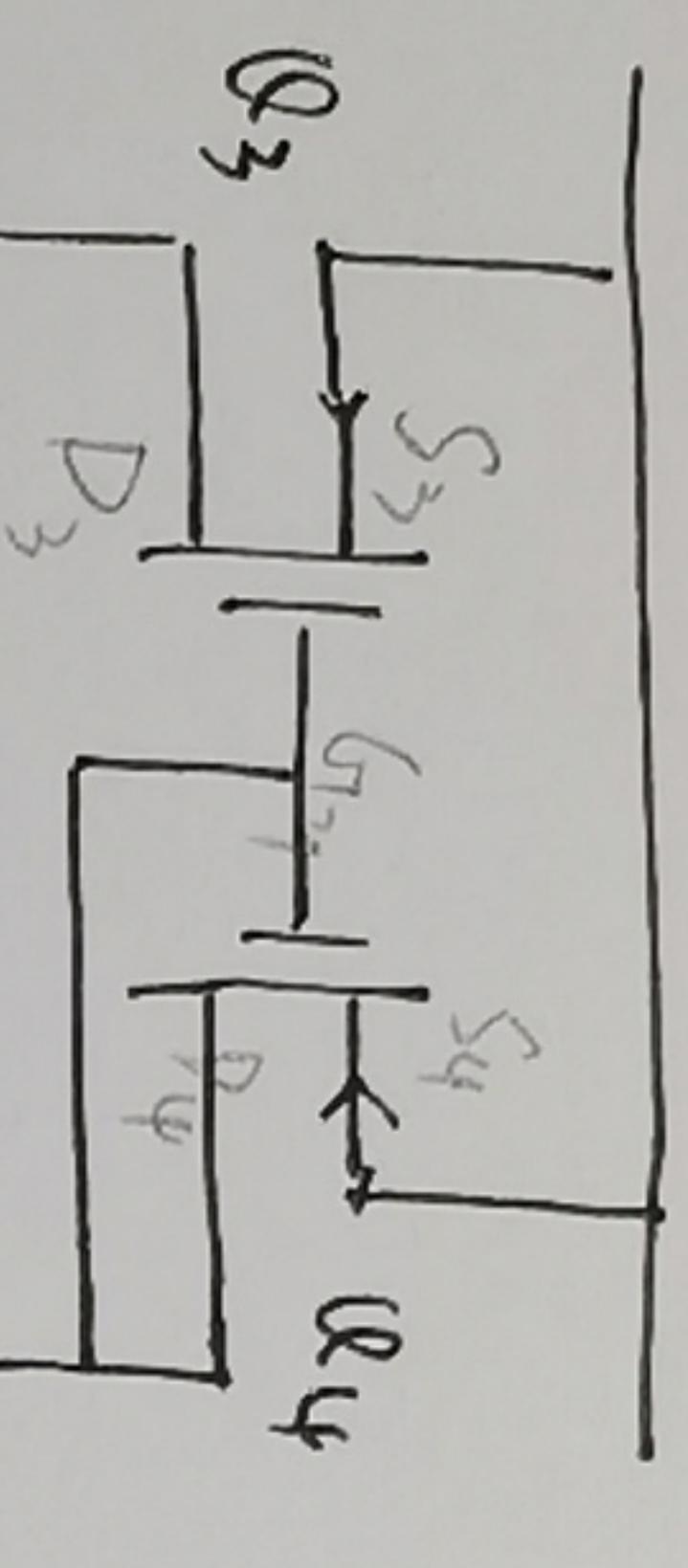

$$\text{Since } V_{D_1} = V_{A_1}$$

$$\Rightarrow V_{DS_1} > V_{AS_1} - V_{TH}$$


\Rightarrow saturation Q_1

$$\Rightarrow I_{S_1} = \frac{1}{2} \mu_N C_{ox} \left(\frac{W}{L} \right)_1 (V_{AS_1} - V_{TH})^2$$

Assume all saturation

$$I_{D_3} = \frac{1}{2} \mu_P C_{ox} (V_{AS_2} - V_{TH})^2 \cdot \left(\frac{W}{L} \right)_3$$
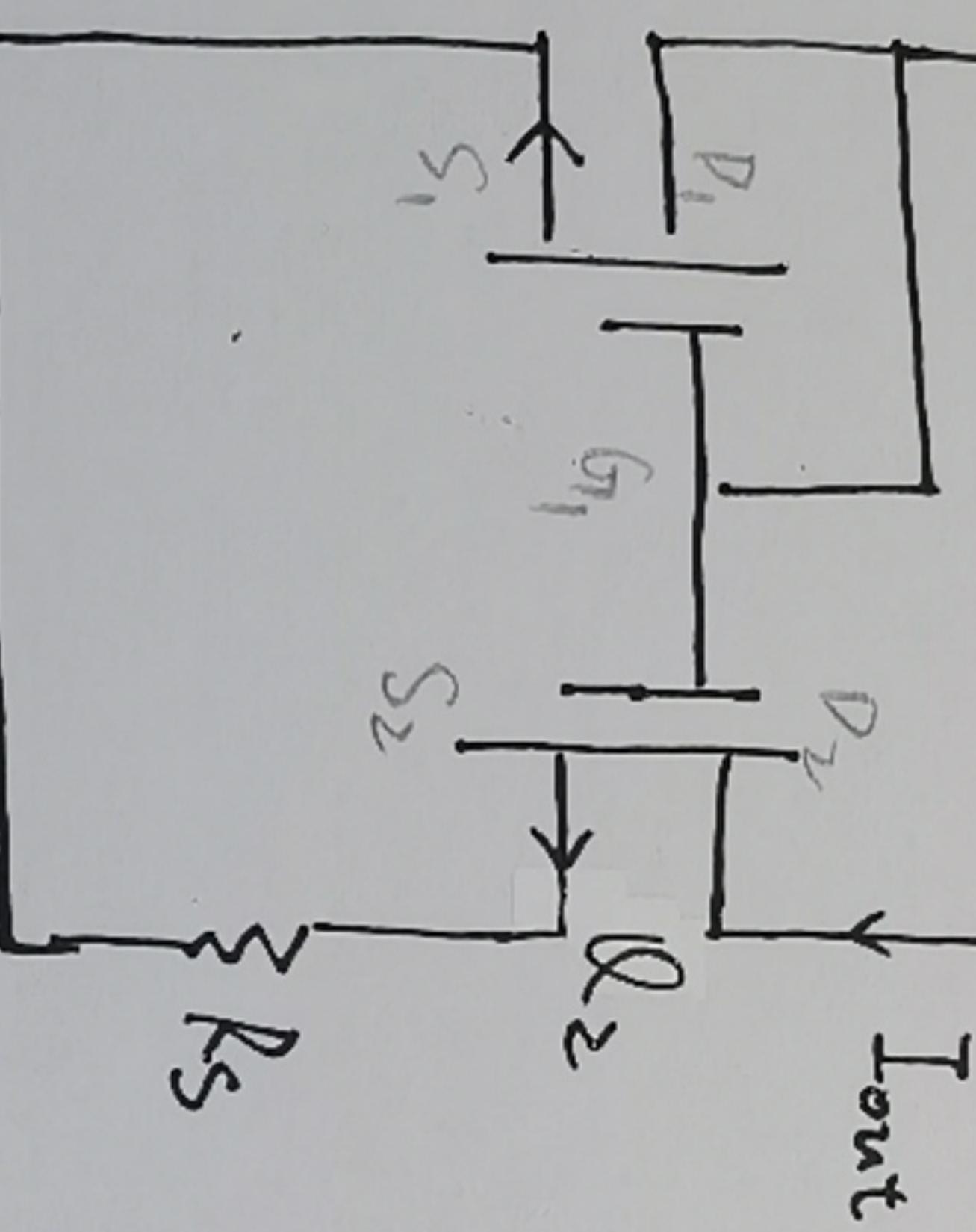
$$\Rightarrow I_{D_4} = \frac{1}{2} \mu_P C_{ox} (V_{AS_2} - V_{TH})^2 \cdot \left(\frac{W}{L} \right)_4$$



$$I_{D_2} = \frac{1}{2} \mu_N C_{ox} \left(\frac{W}{L} \right)_2 (V_{AS_2} - V_{TH})^2$$

$$\Rightarrow V_{AS_2} = V_{AS_1} - I_{out} \cdot 100$$

$$\Rightarrow \sqrt{\frac{2 I_{S_1}}{\mu_N C_{ox} \left(\frac{W}{L} \right)_1}} - I_{out} \cdot 100$$

$$\text{and } I_{S_1} = I_{S_2}$$

$$\Rightarrow \left(\frac{W}{L} \right)_1 (x - 0.7)^2 = \left(\frac{W}{L} \right)_2 (x - 100 I_{out})^2$$

$$\Rightarrow \sqrt{10} (x - 0.7) = \sqrt{\left(\frac{W}{L} \right)_2} (x - 100 I_{out})$$

$$= I_{out}$$

$$\Rightarrow I_{D_3} = I_{out} \cdot \frac{\left(\frac{W}{L} \right)_3}{\left(\frac{W}{L} \right)_4} = I_{out}$$

$$\downarrow$$

since same size

$$\Rightarrow \frac{10(x-0.7)^2}{(x-0.5)^2} = \left(\frac{W}{L} \right)_2$$


$$(b) \quad \sqrt{10} (x - 0.7) = \sqrt{\left(\frac{W}{L} \right)_2} (x - 0.5)$$

Q2.

(b)

$$I_B = I_S e^{\frac{V_{BE}}{V_T}} = 7.39 \text{ nA}$$
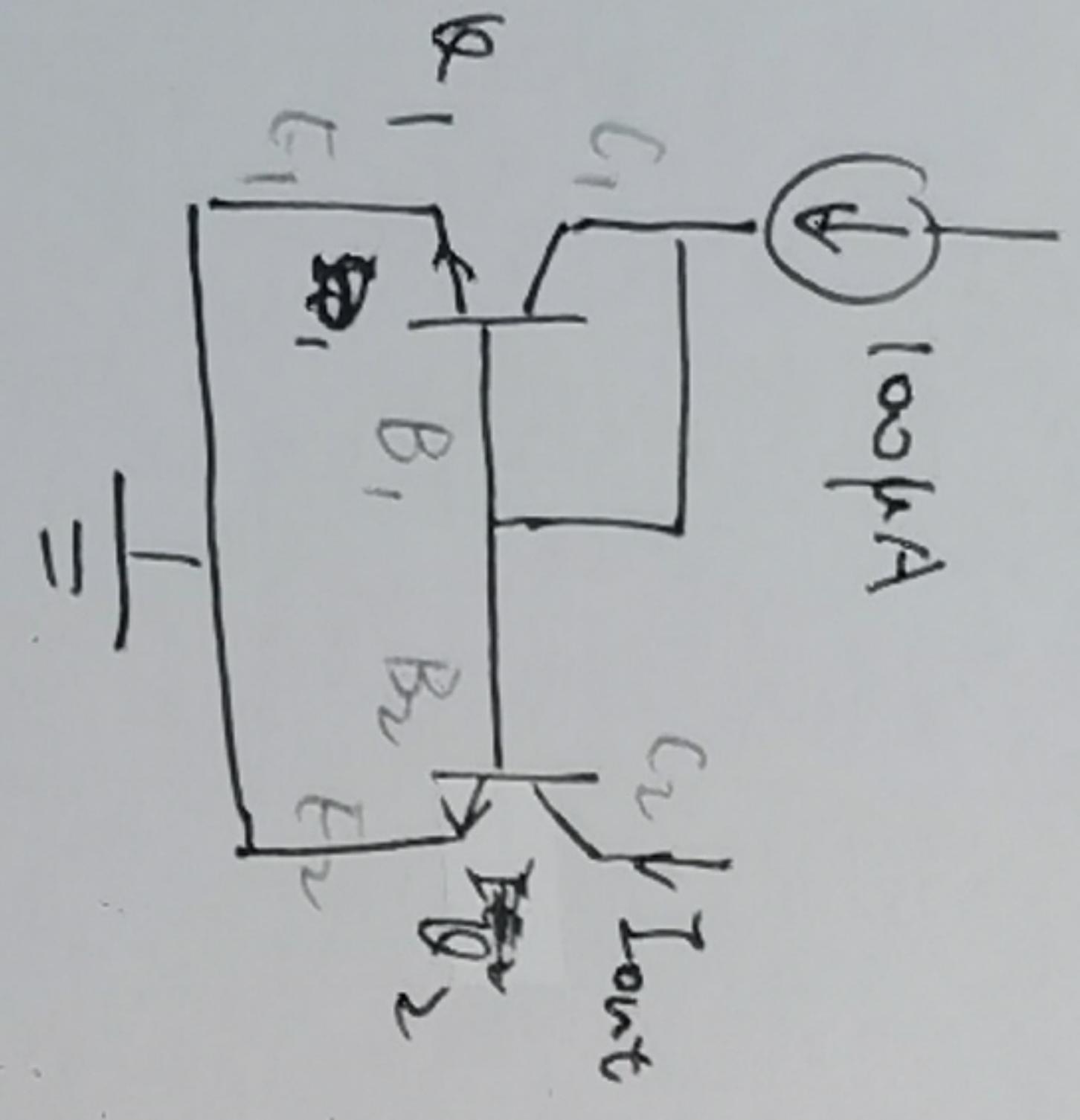
$$I_{out} = I_{REF} - 2I_B = 0.0147 \text{ A}$$



$$2. I_{out} = \frac{1}{4} I_{REF}$$

$$(a)$$

$$\cancel{I_{B1}} = I_B$$

$$I_{out} = I_u + I_{B1} + I_B$$

$$\cancel{I_{B1}} = I_B$$

~~ignore~~ $I_B \Rightarrow I_B = 100 \mu\text{A}$

$$(I_{out} + I_{B2}) R_E = I_{C2}$$

$$I_o R_E = V_T \ln \frac{I_{REF}}{I_o}$$

$$\Rightarrow R_E = \frac{V_T \ln 4}{I_o}$$

$$V_{BE} = V_T \ln \left(\frac{I_B}{I_S} \right) = 0.7 \text{ V}$$

$$V_{BE} = 2 V_{B1}$$

$$\frac{I_{REF}}{I_o} = e^{\frac{V_T}{V_T}}$$