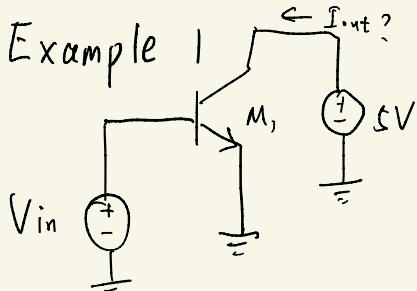


Example 1



$$V_{in} = 2 + 0.01 \sin(2\pi 100t)$$

$$NPN: I_s = 1e-15$$

$$\beta = 100$$


$$V_A = 50$$

$$\Rightarrow I_{out} = I_{outT} + i_{out}$$

$$V_{CE} = 5V > V_{BE} = 2V \quad I_{outT} = (10^{-15}) \left(e^{\frac{2}{0.026}} - 1 \right) \left(1 + \frac{5}{50} \right)$$

check M_1 : FAR

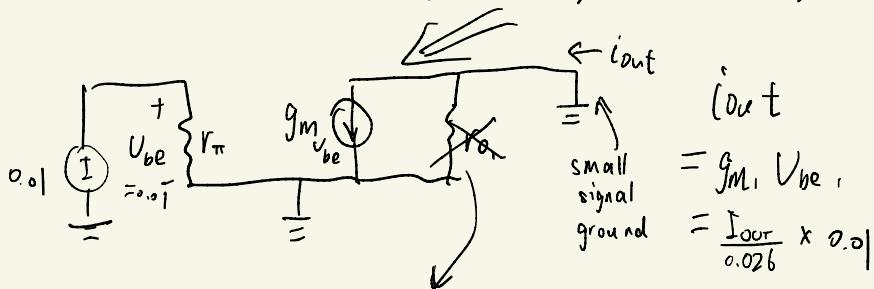
$$I_{out} = I_{outT} + \left(\frac{I_{outT}}{0.026} 0.01 \right) \sin(2\pi 100t)$$



two terminals

Connects to ground (Ignored!)

Example 2

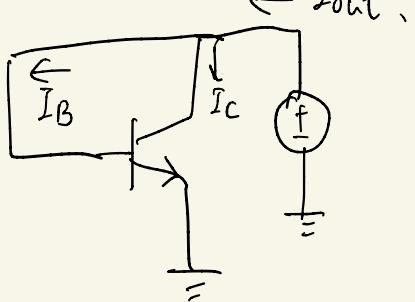

$$V_{in} = 2 + 0.01 \sin(2\pi f_0 t)$$


$$I_{out} = I_{outT} + i_{out}$$

$$I_{outT} = (10^{-15}) (e^{\frac{2}{0.026}} - 1) \left(1 + \frac{2}{50}\right)$$

$$I_S = 10^{-15}, \beta = 100, V_A = 50$$

$$V_{CE} = V_{BE}$$


\Rightarrow FAR

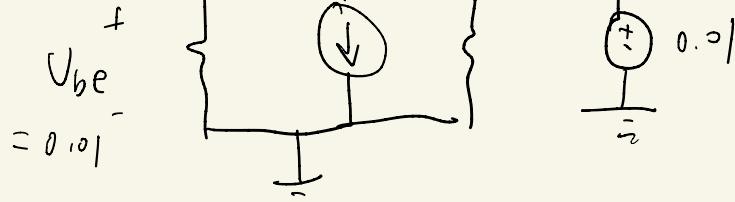

$$i_{out} = 0.01 \times \left(\frac{1}{R_{pi}} + g_m + \frac{1}{r_{oi}} \right)$$

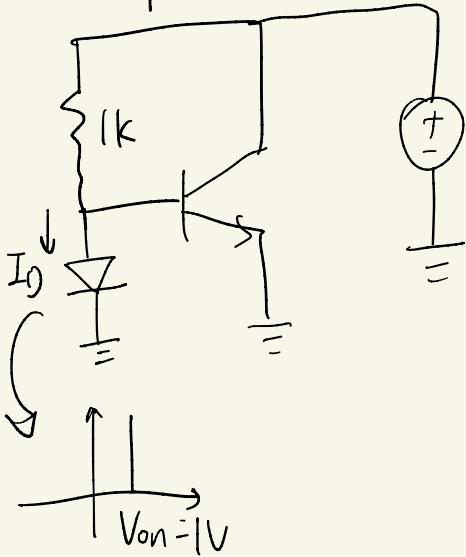Example 3

$$I_S = 10^{-15}, \beta = \infty, V_A = \infty$$




$$V_{in} = 2 + 0.01 \sin(2\pi 100t)$$

$$\begin{aligned} I_{out} &= I_{OUT} + i_{out} \\ &= (10^{-15}) (e^{\frac{v}{0.026}} - 1) (1 + \frac{2}{\infty}) \end{aligned}$$

$$I_D = \frac{V_{in} - 1}{1k}$$


\Downarrow Small-signal Analysis

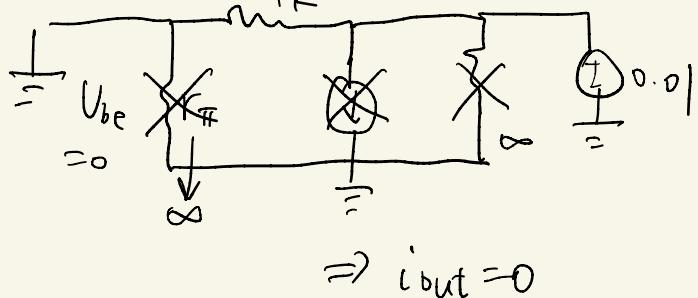

$$\Rightarrow i_{out} = 0$$

$$I_{out} = I_{OUT}$$

Example 4

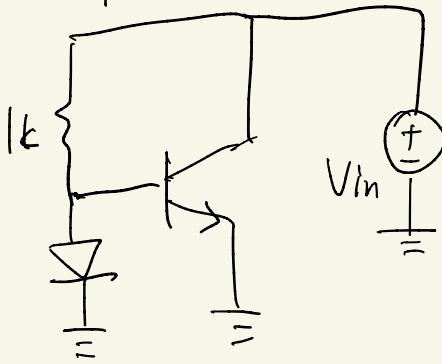

$$I_S = 10^{-15}, \beta = \infty, V_A = 100$$


$$V_{Dn} = 1V$$

$$V_{in} = 2 + 0.01 \sin(2\pi 100 t)$$

$$I_{out} = I_{outT} + i_{out}$$

$$I_{outT} = (10^{-15}) (e^{\frac{1}{0.026}} - 1) (1 + \frac{2}{100})$$


↓ Small-signal analysis

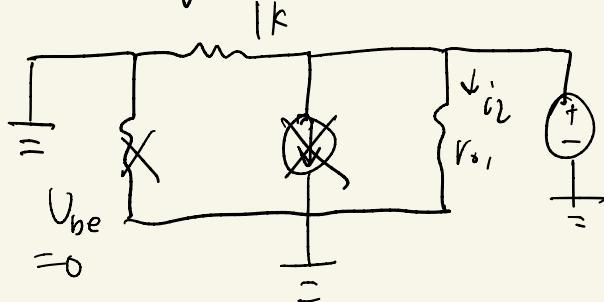

$$\Rightarrow i_{out} = i_2 = \frac{0.01}{R_{o1}}, \quad V_{o1} = \frac{V_A}{I_{out}}$$

Example 5

$$V_{in} = | + 0.00 | \sin(2\pi 100 t)$$

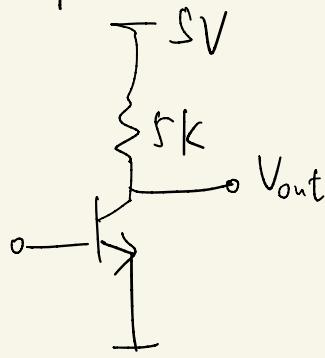

$$V_{out} = V_{outT} + U_{out} = ?$$

$$A_v = V_{out}/V_{in} = ?$$




$$I_S = 5 \times 10^{-16}, \beta = 200, V_A = \infty$$

$$V_{outT} = 5 - (5k) (5 \times 10^{-16}) (e^{\frac{1}{0.026}} - 1)$$

*check if ≥ 1 (in FAR)


Small signal

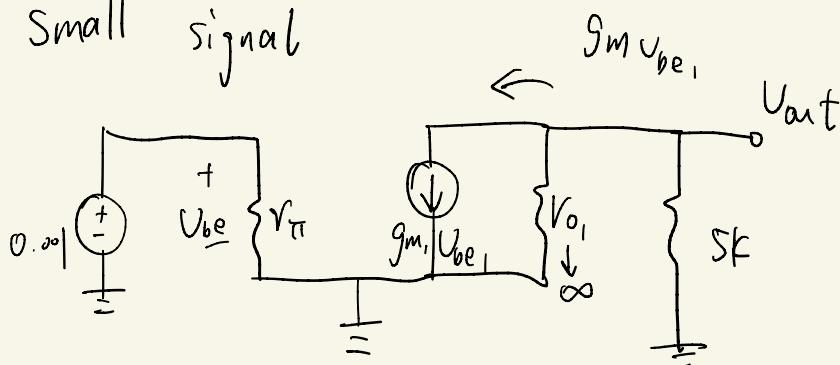

$$V_{out} = -g_m V_{be_1} (5k)$$

$$A_v = \frac{V_{out}}{V_{in}} = -g_m (5k)$$

Example b

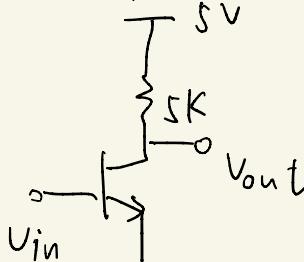

$$I_s = 5 \times 10^{-16}, \beta = 200$$

$$\underline{V_A = 100}$$

$$V_{in} = 0.7 + 0.001 \sin(2\pi 100t)$$

$$V_{out} = -g_m, V_m (r_o, 1/5k)$$

$$A_V = -g_m, (r_o, 1/5k)$$


$$V_{out} = ?$$




$$\frac{5 - V_{out}}{5k} = (5 \times 10^{-16}) \left(e^{\frac{0.7}{0.026}} - 1 \right) \left(1 + \frac{V_{out}}{100} \right)$$

check if $V_{out} \geq 0.7$

Small-signal

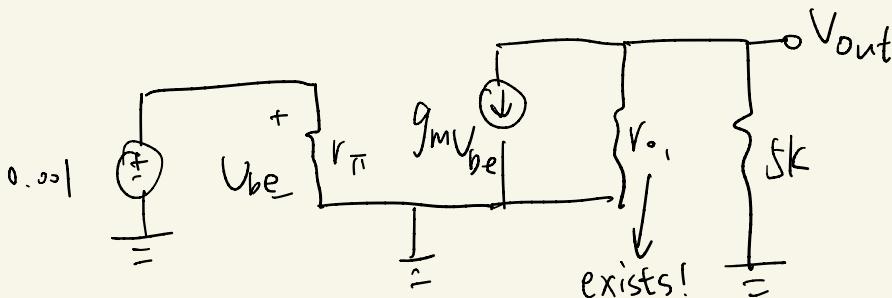

Example 7

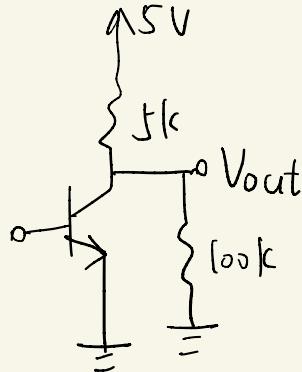

$$I_S = 5 \times 10^{-16}, \beta = 200,$$

$$V_A = 100$$

$$V_{in} = 0.7 + 0.001 \sin(2\pi f_0 t)$$

$$V_{out} = ?$$


$$\frac{5 - V_{out}}{5k} = (5 \times 10^{-16}) (e^{\frac{0.7}{0.026}} - 1) \left(1 + \frac{V_{out}}{100k} \right)$$


check V_{out}

↓ small signal

$$V_{out} = -g_m V_{in} (r_o \parallel 5k \parallel 100k)$$
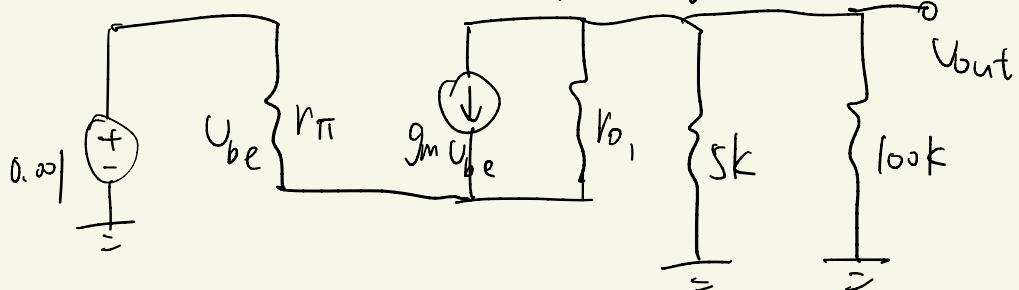
$$A_v = \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel 5k \parallel 100k)$$



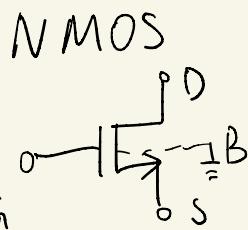

$$V_{TH} = V_{TH0} + \gamma (\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F})$$

$$L_{eff} = L_{drawn} - 2L_D$$

Triode: $V_{DS} < V_{GS} - V_{TH}$

$$I_D = \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$


Saturation: $V_{DS} \geq V_{GS} - V_{TH}$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

channel-length: $\lambda \neq 0$

body-effect: $\gamma \neq 0$

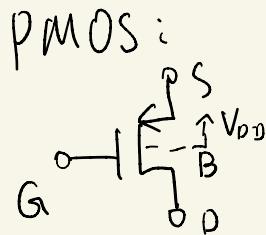★ Since the structure of MOSFET is symmetric, D & S terminals exchange automatically with the change of V_D & V_S



$$|V_{TH}| = |V_{TH0}| + \gamma \left(\sqrt{2\phi_F + |V_{BS}|} - \sqrt{2\phi_F} \right)$$


triode: $V_{SD} < V_{SG} - |V_{TH}|$

$$I_D = \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) \left[(V_{SG} - |V_{TH}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right]$$

saturation: $V_{SD} \geq V_{SG} - |V_{TH}|$

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{SG} - |V_{TH}|)^2 (1 + \lambda V_{SD})$$

Example 8

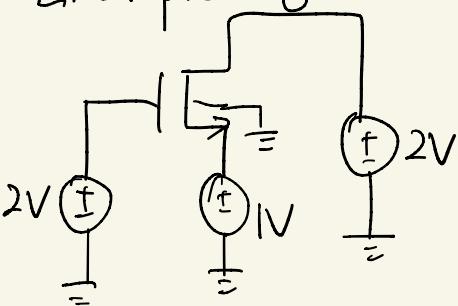

$$\lambda \neq 0 \quad \gamma \neq 0$$

$$\frac{W}{L} = \frac{10 \mu m}{2 \mu m} \quad V_{TH0} = 0.7 V$$

$$V_{GS} > V_{TH} \Rightarrow M_1 \text{ turns on}$$

$$\lambda = 0.1, \gamma = 0.45, L_0 = 0.08$$

$$V_{DS} > V_{GS} - V_{TH} \Rightarrow M_1 \text{ saturates}$$


$$I_D = ?$$

$$V_{TH} = 0.7 + 0.45 (\sqrt{0.9 + 1} - \sqrt{0.9})$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{10}{2 - 0.08 \times 2} \right) (1 - V_{TH})^2 (1 + 0.1 \times 1)$$

Example 9 $\lambda = 0$ $\gamma = 0$

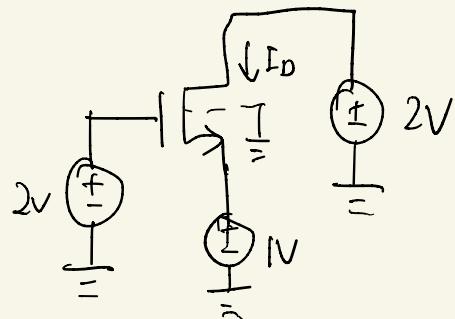

$$V_{GS} > V_{TH}$$


$$\& \quad V_{DS} > V_{GS} - V_{TH} \quad (\text{sat})$$

$$V_{TH} = 0.7 + 0 \left(\sqrt{0.9+1} - \sqrt{0.9} \right) = 0.7$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{1}{2-0.08x_2} \right) (1-0.7)^2$$

Example 10

$\lambda \neq 0$ $\gamma \neq 0$

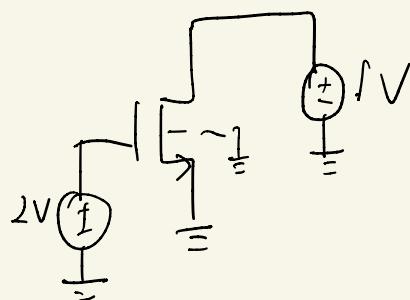

$V_{GS} > V_{TH} \Rightarrow$ on

$V_{DS} < V_{GS} - V_{TH} \Rightarrow$ triode

$$V_{TH} = 0.7 + 0.45 (\sqrt{0.9+0} - \sqrt{0.9}) \\ = 0.7$$


Although $\gamma \neq 0$, $V_{SB} = 0$, $V_{TH} = V_{TH0}$

$$I_D = \mu_n C_{ox} \left(\frac{w}{L_{eff}} \right) \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \\ = \mu_n C_{ox} \left(\frac{1}{2 - 0.08 \times 2} \right) \left[(1 - 0.7) \times 1 - \frac{1}{2} \times 1^2 \right]$$

Example 11

$$\lambda \neq 0$$

$$\gamma \neq 0$$

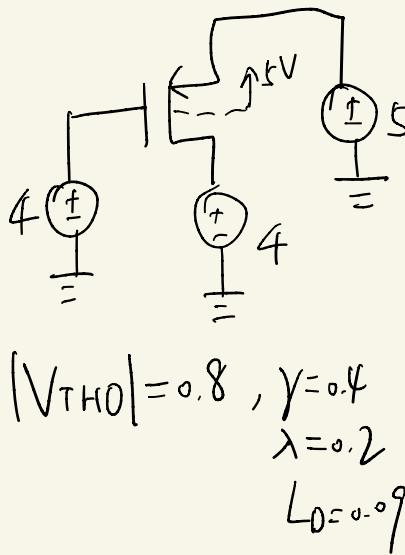

$V_{SG} > |V_{TH}| \Rightarrow$ turns on

$V_{SD} > V_{SG} - |V_{TH}| \Rightarrow$ saturates

$$|V_{TH}| = |-0.8| + 0.4 (\sqrt{0.8+0} - \sqrt{0.8})$$

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right) (V_{SG} - |V_{TH}|)^2 (1 + \lambda V_{SD})$$

$$= \frac{1}{2} \mu_p C_{ox} \left(\frac{10}{2 + 0.09 \times 2} \right) (1 - 0.8)^2 (1 + 0.2 \times 1)$$