

---

## VE311 Electronic Circuit Homework 3

Due: May 25th


---

*Note:*

- 1) Please use A4 size paper or page.
- 2) Please clearly state out your final result for each question.
- 3) Please attach the screenshot of Pspice simulation result if necessary.

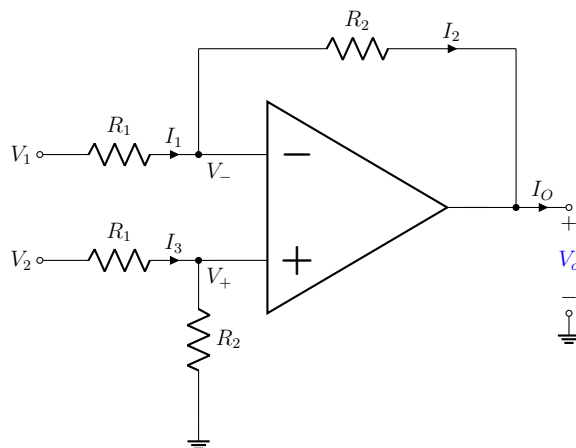
### Question 1. Difference Amplifier

Find the values of  $V_O$ ,  $V_+$ ,  $V_-$ ,  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_O$  for the difference amplifier shown below with  $V_1 = 5V$ ,  $V_2 = 3V$ ,  $R_1 = 10k\Omega$ , and  $R_2 = 100k\Omega$ .



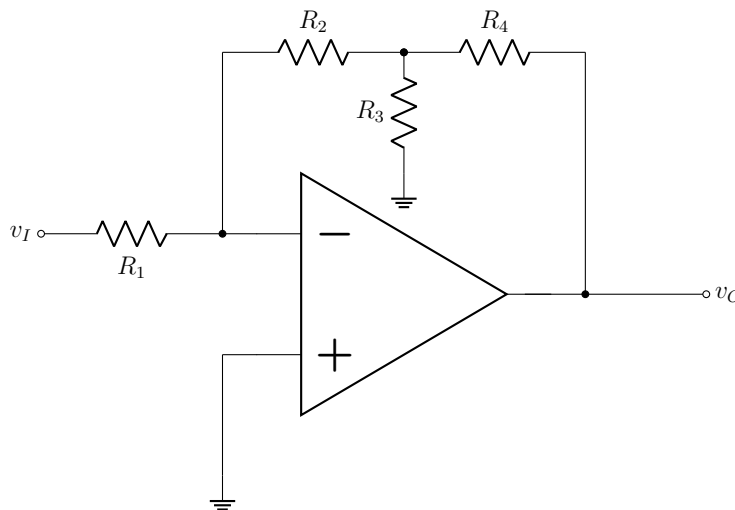
### Question 2. Input and Output Resistance

Assuming the op amp to be ideal, derive an expression for the closed-loop gain  $v_O/v_I$  of the circuit shown below.



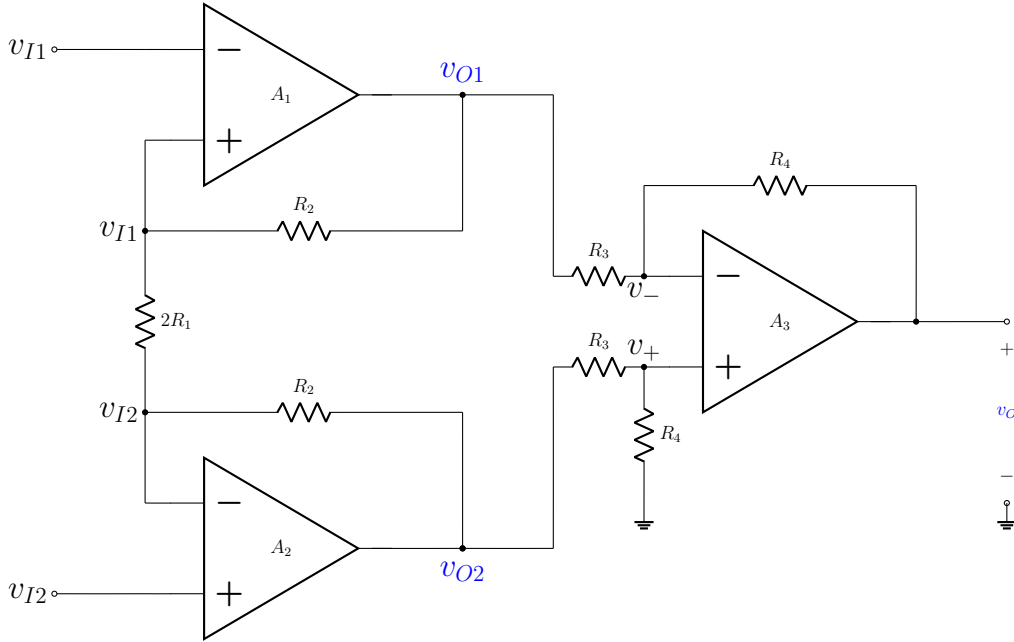
### Question 3. Instrumentation Amplifier

Consider the instrumentation amplifier shown below with a common-mode input voltage of  $+5V$  (dc) and a differential input signal of  $10 - mV$ -peak sine wave. Let  $(2R_1) = 1k\Omega$ ,  $R_2 = 0.5M\Omega$ , and  $R_3 = R_4 = 10k\Omega$ . Find the voltage at every node (total 9 nodes) in the circuit. Also find the differential voltage gain  $A_d$ .



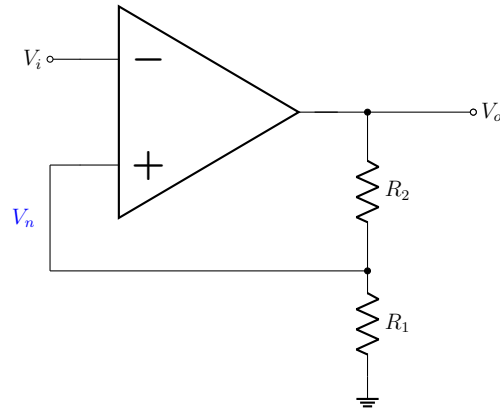
### Question 4. Nonideal Amplifier Analysis

A noninverting amplifier is constructed with  $R_1 = 1k\Omega$  and  $R_2 = 39k\Omega$  using an operational amplifier with an open-loop gain of  $80dB$  and an output resistance of  $50\Omega$ . Find the output resistance of the noninverting amplifier.


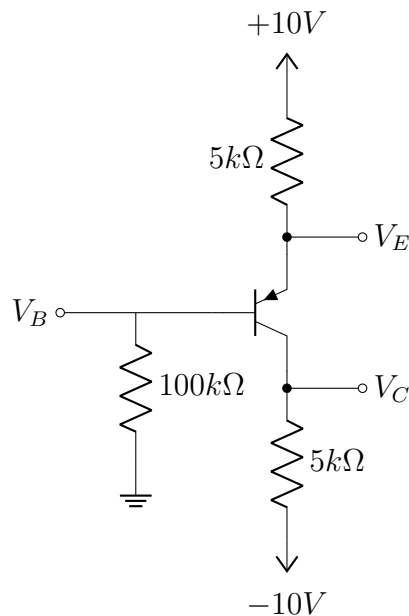
### Question 5. BJT

In the circuit shown below, measurement indicates  $V_B$  to be  $+1.0V$  and  $V_E$  to be  $+1.7V$ . What are  $\alpha$  and  $\beta$  for this transistor? What voltage  $V_C$  do you expect at the collector?




### Question 6. Saturation

For the circuit shown below, it is required to determine the value of the voltage  $V_{BB}$  that results in the transistor operating

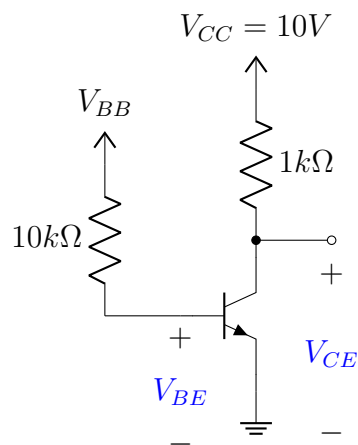
- 1) in the active mode with  $V_{CE} = 5V$
- 2) at the edge of saturation
- 3) deep in saturation with  $\beta_{forced} = 10$

For simplicity, assume that  $V_{BE}$  remains constant at  $0.7V$ . The transistor  $\beta$  is specified to be 50.


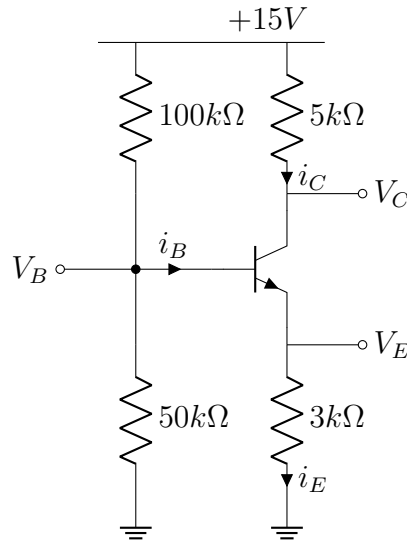
### Question 7. BJT at DC

We want to analyze the circuit shown below to determine the voltages at all nodes and the currents through all branches. Assume  $\beta = 100$ .



### Question 8. Small Signal Analysis

Consider the following BJT amplifier, determine its small-signal, open-circuit voltage gain  $A_v = \frac{v_o(t)}{v_i(t)}$ . Hint: Try to follow the steps to solve this question

- 1) Complete a D.C. Analysis.
- 2) Calculate the small-signal circuit parameters for each BJT.
- 3) Carefully replace all BJTs with their small-signal circuit model.
- 4) Set all D.C. sources to zero.
- 5) Analyze small-signal circuit.

