
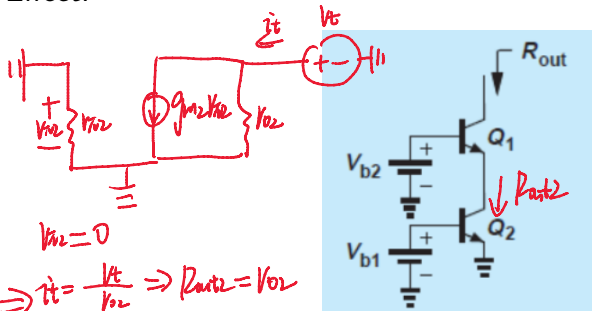


Extra Exercise 1

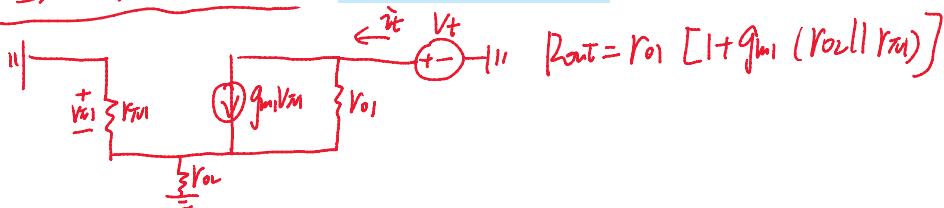Determine the output resistance of the circuit below. With Early Effect.




$$\Rightarrow i_t = \frac{V_t}{r_{o2}} \Rightarrow R_{out2} = r_{o2}$$



$$R_{out} = r_{o1} [1 + g_{m1} (r_{o2} || r_{e2})]$$

Extra Exercise 2

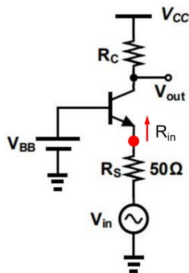(23FA Mid/9) The figure below shows a BJT amplifier. Assume $V_{BE} = 0.7$ V, $V_T = 25$ mV, β is very large (to be infinity). No Early effect. [15 points]






(a) Draw the small signal model and derive the gain for the amplifier. [5 points]

Extra Exercise 2

(b) Find values of V_{BB} and R_C to have a gain of 20 and a matched resistance of $100\ \Omega$ at the input, i.e. $R_{in} = 100\ \Omega$ from the point above R_S . [5 points]

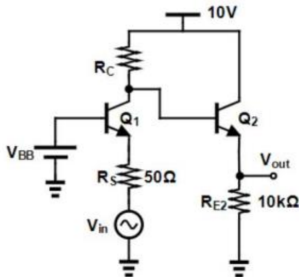(c) By cascading another BJT circuit to the circuit in part b as shown below, find the total parametric gain of the amplifier. [5 points]



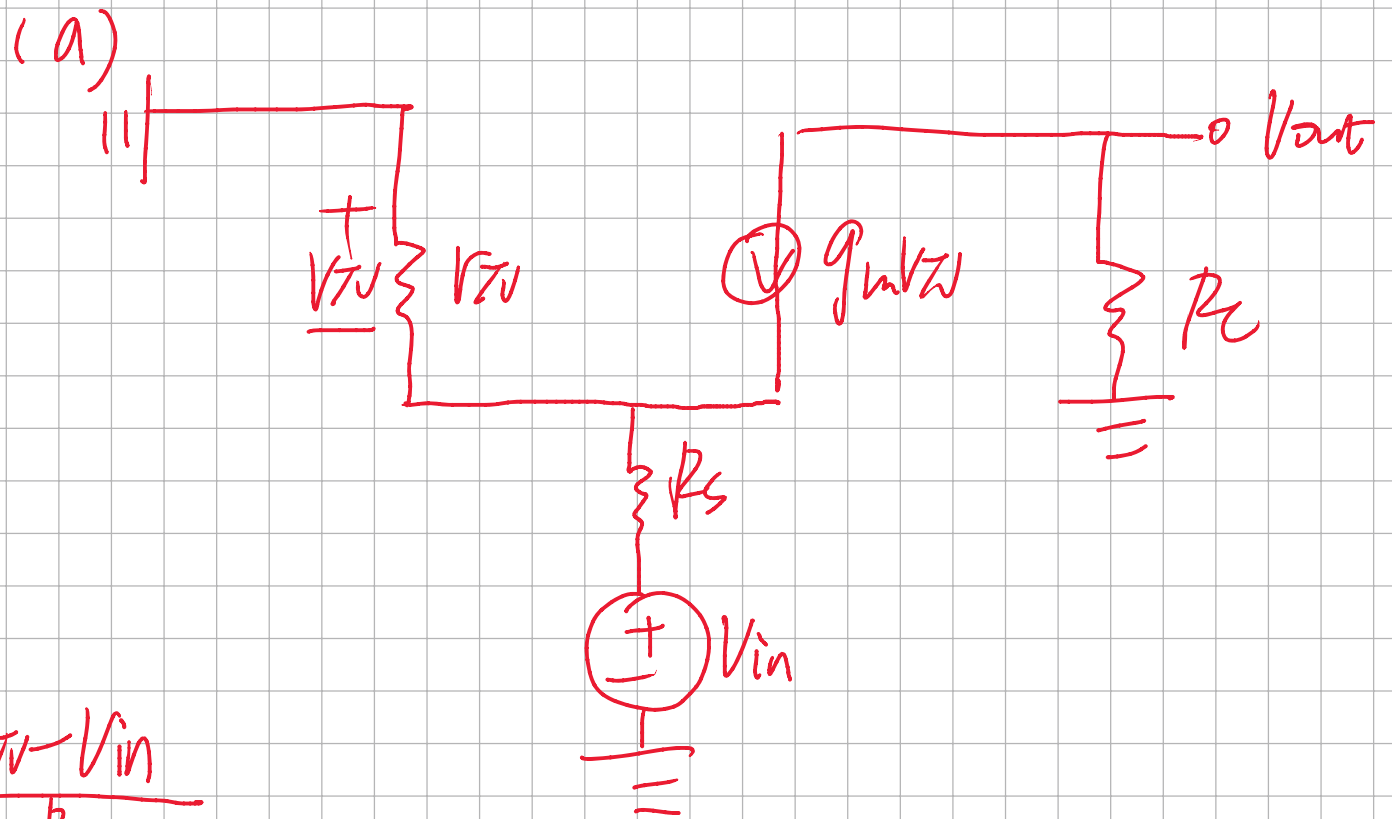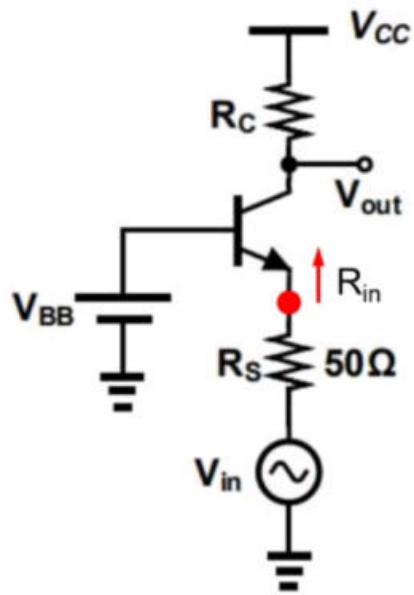

$$\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} = \frac{-v_{\pi} - V_{in}}{R_S}$$

$$v_{\pi} \left(\frac{1}{r_{\pi}} + g_m + \frac{1}{R_S} \right) = -\frac{1}{R_S} V_{in}$$

$$\Rightarrow v_{\pi} = -\frac{1}{R_S \left(\frac{1}{r_{\pi}} + g_m + \frac{1}{R_S} \right)} V_{in}$$

$$g_m v_{\pi} + \frac{V_{out}}{R_C} = 0$$


$$\Rightarrow V_{out} = -g_m R_C v_{\pi} = \frac{g_m R_C}{\frac{R_S}{r_{\pi}} + R_S g_m + 1} V_{in}$$

$$\because \beta \rightarrow \infty$$

$$\therefore r_{\pi} = \frac{\beta}{g_m} \rightarrow \infty$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_m R_C}{g_m R_S + 1}$$

b) ① R_{in}

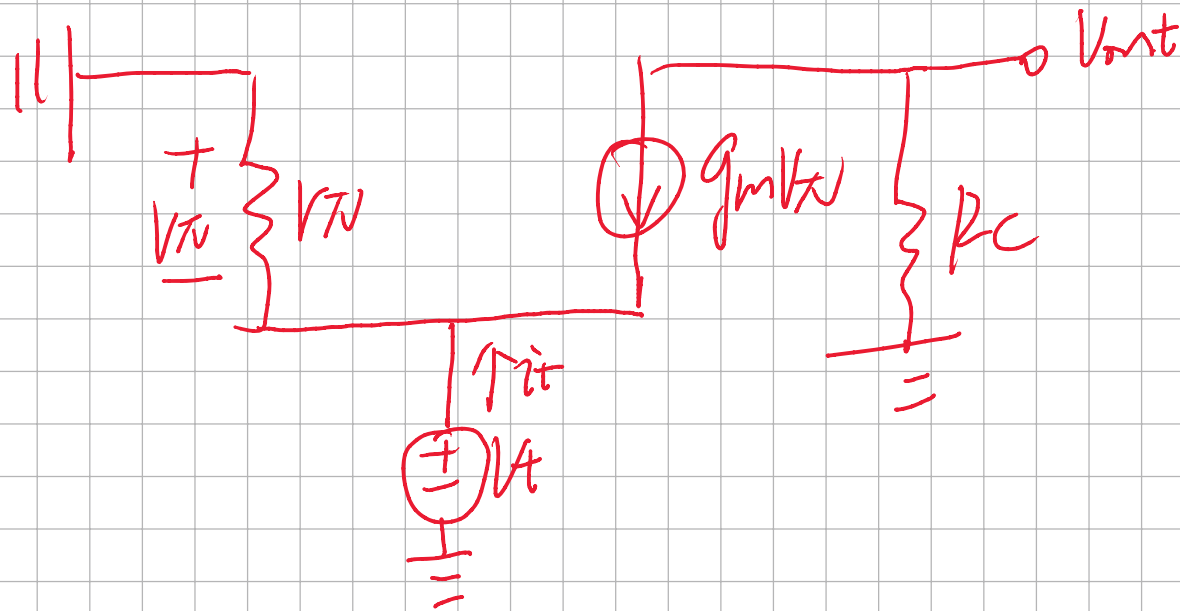

$$V_{tu} = -V_t$$

$$i_t = -\frac{V_{tu}}{R_{tu}} - g_m V_{tu}$$

$$= V_t \left(\frac{1}{R_{tu}} + g_m \right)$$

$$\Rightarrow R_{in} = \frac{V_t}{i_t} = \frac{1}{\frac{1}{R_{tu}} + g_m} = \frac{1}{g_m} = 100 \Omega$$

$$\Rightarrow g_m = 0.01 \Omega^{-1}$$

② A_v

$$A_v = \frac{g_m R_c}{g_m R_s + 1} = 20$$

$$\Rightarrow \frac{0.01 R_c}{0.01 \times 50 + 1} = 20$$

$$\Rightarrow R_c = 3 \times 10^3 \Omega$$

③ V_{BB}

$$g_m = \frac{I_c}{V_T}$$

$$V_{BB} = V_{BE} + V_E \Rightarrow I_c = 2.5 \times 10^{-4} A$$


$$\beta \rightarrow \infty \Rightarrow I_B = 0$$

$$g_m \rightarrow I_c \Rightarrow I_E = I_c = 2.5 \times 10^{-4} A$$

$$V_E = R_s I_E = 1.25 \times 10^{-2} V$$

$$V_{BB} = V_{BE} + V_E = 0.7125 V$$

(c)

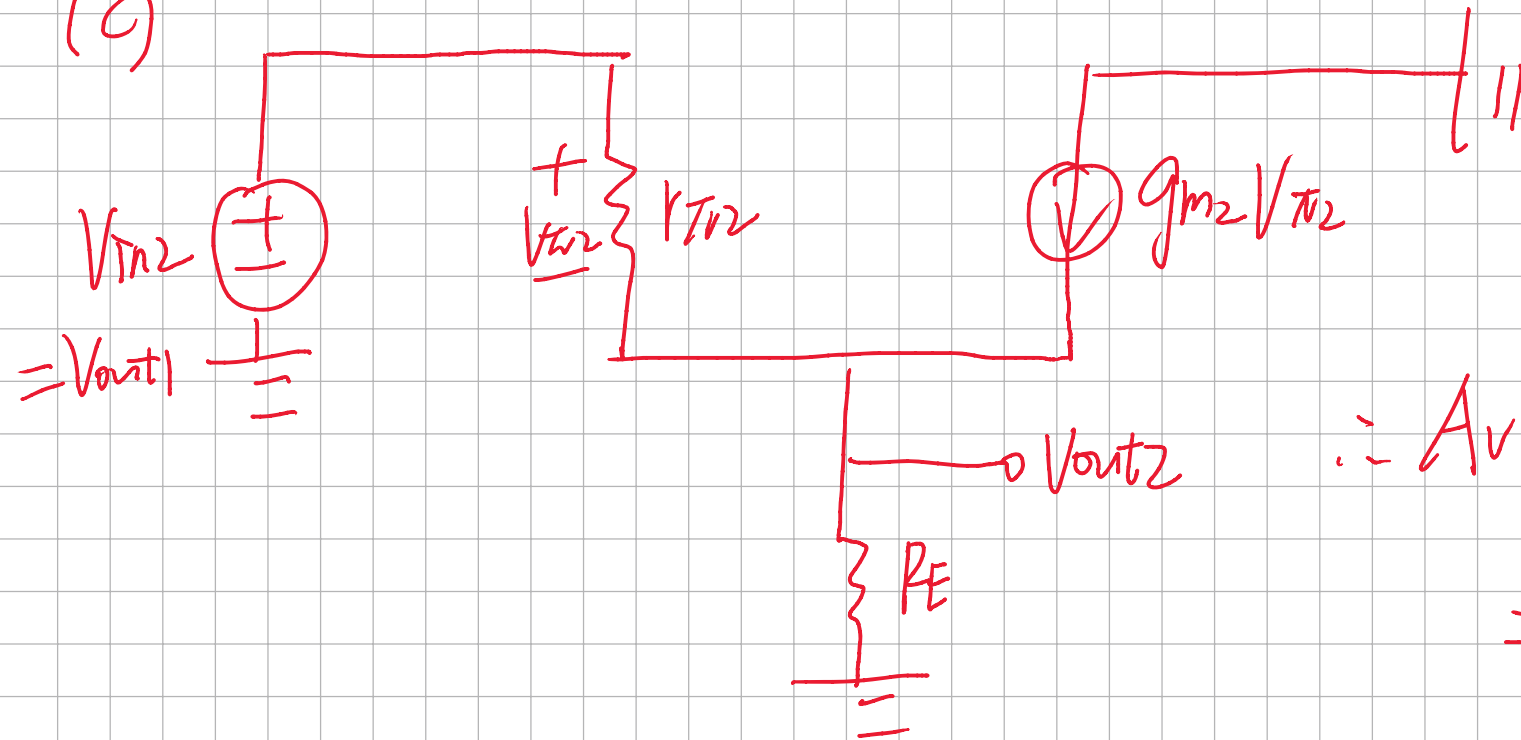

$$\therefore A_v = \frac{g_{m2} R_{E2}}{1 + g_{m2} R_{E2}} \cdot \frac{g_{m1} R_C}{g_{m1} R_S + 1}$$

$$= \frac{R_C}{R_S + \frac{1}{g_{m1}}} \cdot \frac{R_{E2}}{R_{E2} + \frac{1}{g_{m2}}}$$

$$\beta \rightarrow \infty, r_{\pi 2} \rightarrow \infty, \frac{V_{\pi 2}}{r_{\pi 2}} \rightarrow 0$$

$$V_{out2} = R_E g_{m2} V_{\pi 2} = R_E g_{m2} (V_{in2} - V_{out2})$$

$$\Rightarrow \frac{V_{out2}}{V_{in2}} = \frac{g_{m2} R_{E2}}{1 + g_{m2} R_{E2}}$$