



# Lecture 11: MOSFET Circuits

VE311 Electronic Circuits

Xuyang Lu  
2023 Summer



上海交通大学  
SHANGHAI JIAO TONG UNIVERSITY

上海交通大学  
SHANGHAI JIAO TONG UNIVERSITY

- MOSFET

上海交通大学  
SHANGHAI JIAO TONG UNIVERSITY

- MOSFET Circuits

## Spice Models

NMOS Model			
LEVEL=1	VTO=0.7	GAMMA=0.45	PHI=0.9
NSUB=9e+14	LD=0.08e-6	UO=350	LAMBDA=0.1
TOX=9e-9	PB=0.9	CJ=0.56e-3	CJSW=0.35e-11
MJ=0.45	MJSW=0.2	CGDO=0.4e-9	JS=1.0e-8
PMOS Model			
LEVEL=1	VTO=-0.8	GAMMA=0.4	PHI=0.8
NSUB=5e+14	LD=0.09e-6	UO=100	LAMBDA=0.2
TOX=9e-9	PB=0.9	CJ=0.94e-3	CJSW=0.32e-11
MJ=0.5	MJSW=0.3	CGDO=0.3e-9	JS=0.5e-8

# Spice Models

- Simulators such as SPICE and Cadence need accurate models for each device.
- Above is the simplest MOS SPICE model, known as “Level 1,” and provide typical values for each parameter corresponding to 0.5- $\mu\text{m}$  technology.

# Spice Models

VTO : threshold voltage with zero  $V_{SB}$  ( unit : V )

GAMMA : body effect coefficient ( unit :  $V^{1/2}$  )

$$\text{PHI} : 2\Phi_F \text{ ( unit : V )}$$

TOX : gate oxide thickness ( unit : m )

NSUB : substrate doping ( unit :  $cm^{-3}$  )

LD : source/drain side diffusion ( unit : m )

UO : channel mobility ( unit :  $cm^2/V/s$  )

LAMBDA : channel-length modulation coefficient ( unit :  $V^{-1}$  )

# Spice Models

CJ : source/drain bottom-plate junction capacitance per unit area ( unit :  $F/m^2$  )

CJSW : source/drain sidewall junction capacitance per unit length ( unit :  $F/m$  )

PB : source / drain junction built-in potential ( unit : V )

MJ : exponent in CJ equation ( unitless )


MJSW : exponent in CJSW equation ( unitless )

CGDO: gate-drain overlap capacitance per unit width ( unit :  $F/m$  )

CGSO : gate-source overlap capacitance per unit width ( unit :  $F/m$  )

JS : source/drain leakage current per unit area ( unit :  $A/m^2$  )

# Body Effect Example

 

$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10\mu m}{2\mu m} \quad (1)$$


$$V_{th} = 0.7 + 0.45(\sqrt{0.9 + 1} - \sqrt{0.9}) \quad (2)$$

$$I_D = \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L_{eff}}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad (3)$$


 
# Body Effect Example

$$\lambda \neq 0 \quad \gamma \neq 0 \quad (4)$$





$$V_{th} = 0.7 + 0.45(\sqrt{0.9 + 1} - \sqrt{0.9}) \quad (6)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L_{eff}} \right) [(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2] \quad (7)$$

$$\left( \frac{W_{drawn}}{L_{drawn}} \right) = \frac{10 \mu m}{2 \mu m} \quad (5)$$

 
 
# Body Effect Example

Sketch  $I_D$  as a function of  $V_X$  increasing from  $-\infty$  to 0. Assume  $V_{TH} = 0.6V$ ,  $\gamma = 0.4V^{1/2}$  and  $2\Phi_F = 0.7V$ .





Solution:  $1.2 = 0.6 + 0.4 (\sqrt{0.7 - V_X} - \sqrt{0.7}), V_X = -4.76 V$

# Drain-induced Barrier Lowering

  




In short-channel devices, the drain is close enough to gate the channel, and so a high drain voltage can open the bottleneck and turn on the transistor prematurely.

# Drain-induced Barrier Lowering

  


In short-channel devices, the drain is close enough to gate the channel, and so a high drain voltage can open the bottleneck and turn on the transistor prematurely.

# NMOS vs PMOS

   


# PMOS Example

 
 
# Small-Signal Example


$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10\mu m}{2\mu m} \quad (8)$$



- No bulk connect means ground for NMOS
 
# Transconductance

- For the NMOS operating in the saturation region ( $V_{DS} \geq V_{GS} - V_{TH}$ ):



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2 \quad (9)$$

- $\Delta V_{GS}$  results in  $\Delta I_D = g_m \times \Delta V_{GS}$ .



# Transconductance



$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH}) = \sqrt{2\mu_n C_{ox} \frac{W}{L'} I_D} = \frac{2I_D}{V_{GS} - V_{TH}} \quad (10)$$

With channel-length modulation




$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) \quad (11)$$

$$= \sqrt{2\mu_n C_{ox} (W/L) I_D} (1 + \lambda V_{DS}) \quad (12)$$

# Transconductance

  

# Transconductance

   


- For a given NMOS,  $g_m$  changes according to the DC biasing condition.
- If a small signal is applied to a NMOS with defined biasing values, we assume the signal amplitude is small enough that the variation in  $g_m$  is negligible.

# Small-Signal Model for NMOS


$$r_o = \frac{\partial V_{DS}}{\partial I_D} \quad (13)$$

$$= \frac{1}{\partial I_D / \partial V_{DS}} \quad (14)$$
 
$$= \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \cdot \lambda} \quad (15)$$



# Small-Signal Model for NMOS

 

# Small-Signal Model for NMOS

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} \quad (16)$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \left( -\frac{\partial V_{TH}}{\partial V_{BS}} \right) \quad (17)$$


$$\frac{\partial V_{TH}}{\partial V_{BS}} = -\frac{\partial V_{TH}}{\partial V_{SB}} \quad (18)$$

$$= -\frac{\gamma}{2} (2\Phi_F + V_{SB})^{-1/2} \quad (19)$$


$$g_{mb} = g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} \quad (20)$$

$$= \eta g_m \quad (21)$$

# Small-Signal Model for NMOS

 

 
$$\downarrow i_d = g_m \cdot v_{gs} \quad \uparrow i_d = g_{mb} \cdot v_{sb} \quad (22)$$



# Small-Signal Example

$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10 \mu m}{2 \mu m} \quad (23)$$


$$1V + 0.001 \sin(2\pi 100t)$$

 



 
# Small-Signal Example


$$\left(\frac{W_{drawn}}{L_{drawn}}\right) = \frac{10\mu m}{2\mu m} \quad (24)$$



# Small-Signal Model for PMOS

 

 
$$\uparrow i_d = g_m \cdot v_{gs} \quad \downarrow i_d = g_{mb} \cdot v_{sb} \quad (25)$$




# Layout

NMOS

 

PMOS

 


# Layout

- $W/L$  is chosen to determine  $g_m$ .
- Minimum  $L$  is dictated by the process.
- Design rules:
  - Poly-Si extends beyond the channel area by some amount.
  - Enough  $n^+$ ,  $p^+$  or poly-Si area surrounding each via.
  - Enough distance between two vias.
  - Many others.

# NMOS vs PMOS in Performance


- PMOS devices are quite inferior to NMOS in most CMOS technology.
- Lower mobility of holes ( $\mu_p C_{ox} \approx 0.5\mu_n C_{ox}$ ) yield lower current drive and conductance.
- NMOS exhibit higher output resistance, providing more ideal current sources and higher voltage gain.
- It is preferable to use NMOS rather than PMOS wherever possible.

# Common-Source

 

$$V_{in} = 0.8 + 0.001 \sin(2\pi 100t) \quad (26)$$

# Common-Source

 

$$V_{in} = 4.1 + 0.001 \sin(2\pi 100t) \quad (27)$$