

Question 1

(a)

Case (i):

For the positive half cycle:

The diode D_1 is in forward bias condition and the diode acts as a short circuited.

The diode D_2 is in reverse bias condition and the diode acts as an open circuited.

Therefore the overall circuit is conducting. Ideally the diode voltage is treated 0 V.

For positive half cycle, the output voltage is equal to input voltage.

Case (ii):

For the negative half cycle:

The diode D_1 is in reverse bias condition and the diode acts as an open circuited.

The diode D_2 is in forward bias condition and the diode acts as a short circuited.

Therefore the overall circuit is conducting. Ideally the diode voltage is treated 0 V.

For negative half cycle, the output voltage is equal to input voltage.

The output waveform is shown in Figure 5.

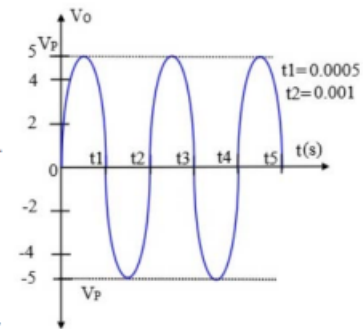


Figure 5

Therefore, the positive peak value is $+5 V$.

Therefore, the negative peak value is $-5 V$.

(b)

Case (i):

For the positive half cycle $v_i > 0$, the diode D_1 is in reverse bias condition and the diode acts as an open circuit.

The total input voltage is flows as output voltage.

Therefore, the output voltage is equal to input voltage.

Case (ii):

For the negative half cycle $v_i < 0$, the diode D_1 is in forward bias condition and the diode acts as a short circuit.

The circuit acts a voltage divider circuit.

Find the total output voltage.

$$\begin{aligned}v_o &= \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 1 \text{ k}\Omega} v_i \\&= \frac{1 \text{ k}\Omega}{2 \text{ k}\Omega} (5 \text{ V}) \\&= 0.5(5) \\v_o &= 2.5 \text{ V}\end{aligned}$$

Therefore, the output voltage is -2.5 V.

The output waveform is shown in Figure 9.

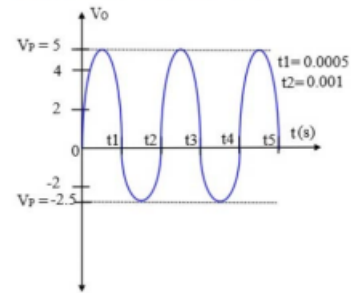


Figure 9

Therefore, the positive peak value is $+5 \text{ V}$.

Therefore, the negative peak value is -2.5 V .

(c)

Case (i):

For the positive half cycle $v_i > 0$:

The diode D_1 is in reverse bias condition and the diode D_2 is in forward bias condition.

Hence, the diode D_1 acts as a open circuited to ground and D_2 acts as short circuit.

Find the voltage across the $1\text{ k}\Omega$ resistor.

Current flowing $1\text{ k}\Omega$ resistor is 1 mA .

Voltage across $1\text{ k}\Omega$ resistor is $V_o = (1\text{ k}\Omega)(1\text{ mA}) = 1\text{ V}$.

Case (ii):

For the negative half cycle $v_i < 0$:

The diode D_1 is in forward bias condition and the diode D_2 is in reverse bias condition.

Hence, the diode D_1 acts as a short circuited to ground and D_2 acts as open circuit.

Find the voltage across the $1\text{ k}\Omega$ resistor.

Current flowing $1\text{ k}\Omega$ resistor is 1 mA .


Voltage across $1\text{ k}\Omega$ resistor is $V_o = V_i + 1\text{ V}$.

$V_o = -5 + 1\text{ V}$

$V_o = -4\text{ V}$

Voltage across $1\text{ k}\Omega$ resistor is $V_o = -4\text{ V}$.

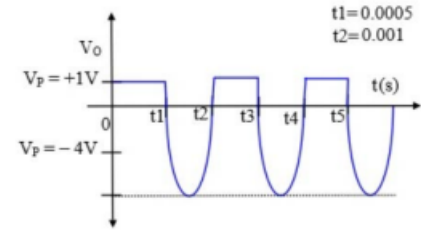The output waveform is shown in Figure 11.




Figure

Therefore, the positive peak value is $+1\text{ V}$.

Therefore, the negative peak value is -4 V .

Question 2

① D1 on, D2 off

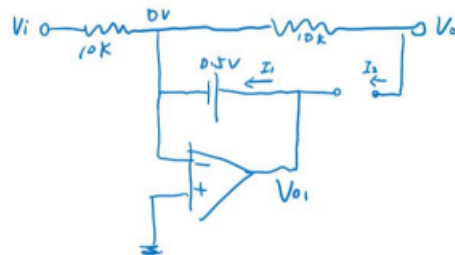

swing ok
 $V_{01} = 0.5 > 0 \Rightarrow V_i < 0$
 $I_1 > 0, I_2 = 0$

$$\frac{V_i - 0}{10k} + \frac{V_0 - 0}{10k} + I_1 = 0$$


$$\frac{0 - V_0}{10k} - I_2 = 0 \Rightarrow V_0 = 0$$

$$\left. \begin{array}{l} V_0 = 0 \\ V_{01} = 0.5 \end{array} \right\} \Rightarrow D2 \text{ off } \checkmark$$

Therefore, when $V_i < 0 \Rightarrow V_0 = 0$

② D1 on, D2 on

$$I_1 > 0, I_2 > 0$$

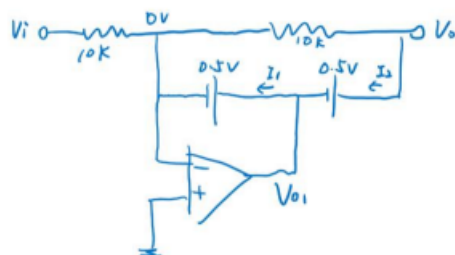


swing ok
 $V_{01} = 0.5 > 0 \Rightarrow V_i < 0$
 $V_0 = V_{01} + 0.5 = 1$

$$\frac{V_i - 0}{10k} + \frac{V_0 - 0}{10k} + I_1 = 0$$

$$\frac{V_0 - 0}{10k} + I_2 = 0$$

impossible, since $\begin{cases} V_0 = 1 > 0 \\ I_2 > 0 \end{cases}$

③ D_1 off, D_2 off

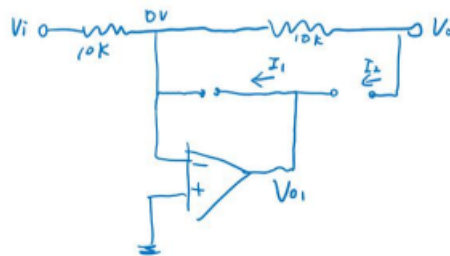

$$I_1 = I_2 = 0$$

$$V_{o1} < 0.5$$

$$\frac{V_i - 0}{10k} + \frac{V_o - 0}{10k} = 0$$

$$\Rightarrow V_o = -V_i$$


$$\frac{0 - V_o}{10k} - I_2 = 0$$

$$\Rightarrow V_o = 0$$

$$\therefore V_i = 0 \Rightarrow V_{o1} = 0 \text{ swing ok}$$

Therefore, when $V_i = 0 \Rightarrow V_o = 0$

④ D_1 off, D_2 on

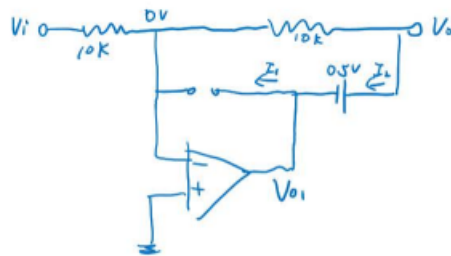

$$I_1 = 0, I_2 > 0$$

$$V_{o1} < 0.5V, V_o = V_{o1} + 0.5$$

$$\frac{V_i - 0}{10k} + \frac{V_o - 0}{10k} = 0$$

$$\Rightarrow V_o = -V_i$$

$$\frac{0 - V_o}{10k} - I_2 = 0$$

$$\Rightarrow V_o = -10k \cdot I_2 < 0$$

$$\Rightarrow V_i > 0 \Rightarrow V_{o1} < 0$$

$\therefore \pm 3V$ swing

$$\therefore -3 \leq V_{o1} < 0$$

$$V_{o1} = V_o - 0.5 = -V_i - 0.5$$

$$\therefore -3 \leq -V_i - 0.5 < 0$$

$$-0.5 < V_i \leq 2.5$$

$$\Rightarrow 0 < V_i \leq 2.5$$


Therefore, when $0 < V_i \leq 2.5$

$$\Rightarrow V_o = -V_i$$

When $2.5 < V_i \leq 5$, the opamp

output saturates $\Rightarrow V_{o1} = -3V$

$$\Rightarrow V_o = -2.5V$$

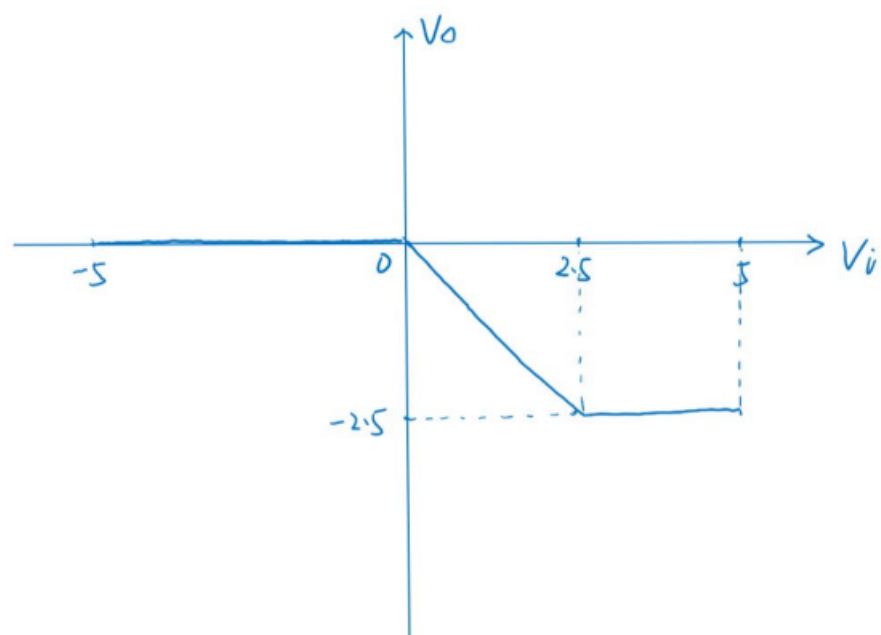

Question 3

(a) Assume that $\omega T \ll \pi$

$$V_r \approx (V_s - V_{on}) \left(\frac{T}{R_s} \right) = (5 - 0.8) \left(\frac{20}{10000} \right) < 0.1$$

$$\frac{4.2}{10000} < 0.1$$

$$C > 4.2 \times 10^{-8} \text{ F}$$

$$V_{dc} = V_s - V_{on} = 5\text{V} - 0.8\text{V} = 4.2\text{V}$$

$$I_{dc} = \frac{V_{dc}}{R_s} = \frac{4.2\text{V}}{10000} = 4.2 \times 10^{-4} \text{ A}$$

$$\theta_c = \sqrt{\frac{2\pi f}{V_s}} < \sqrt{\frac{2\pi \times 10^4}{5}} = 0.2\text{rad}$$


$$\Delta T = \frac{\theta_c}{\omega} < \frac{0.2}{2\pi \times 10^4} = 3.18 \times 10^{-6} \text{ s} \ll T, \text{ assumption is right}$$

$$I_{\text{peak}} = \frac{2V_{dc}}{\Delta T} > \frac{2 \times 4.2 \times 10^{-2} \times 100}{3.18 \times 10^{-6}} = 2.64 \text{ A}$$

$$I_{\text{surge}} = \omega C V_s > 2\pi \times 10^4 \times 4.2 \times 10^{-8} \times 5 = 13.19 \text{ A}$$

$$\text{PIV} = 2V_s - V_{on} = (10\text{V} - 0.8\text{V}) = 9.2\text{V}$$

(b)

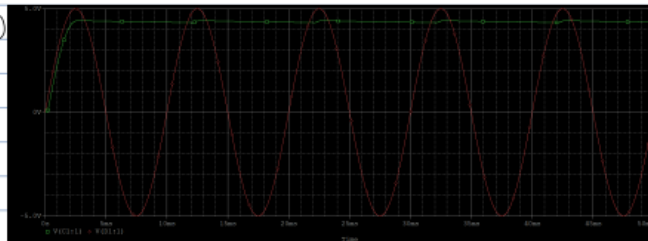

From the graph, we can know that

$$V_{dc} \approx 4.4\text{V}$$


$$I_{dc} = \frac{V_{dc}}{R_s} = 4.4 \times 10^{-4} \text{ A}$$

$$V_{on} \approx 0.1\text{V}$$

$$\text{PIV} \approx 9.4\text{V}$$

Compared with calculated ones, they are very close

(c)

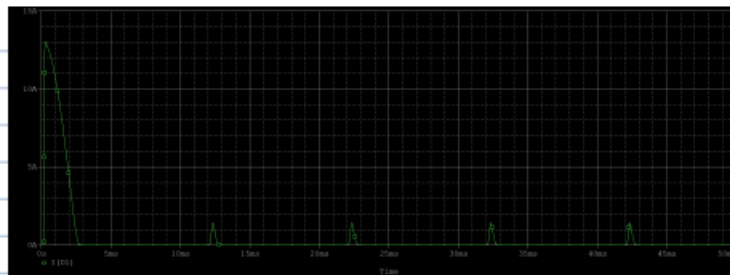

From the graph, we can know that

$I_{\text{peak}} \approx 1.44 \text{ A}$

$I_{\text{surge}} \approx 3.01 \text{ A}$

Compared with calculated ones, I_{peak} is very different
but I_{surge} is very close