

---

## VE311 Electronic Circuit Homework 4

Due: July 4th

---

*Note:*

- 1) *Please use A4 size paper or page.*
- 2) *Please clearly state out your final result for each question.*
- 3) *Please attach the screenshot of Pspice simulation result if necessary.*

### Question 1. MOSFET DC Biasing





Use the drain current equations below. Don't consider channel-length modulation and body effect. Assuming  $\mu_n = 350 \times 10^{-4} \text{m}^2/\text{V}/\text{s}$ ,  $\mu_p = 350 \times 10^{-4} \text{m}^2/\text{V}/\text{s}$ ,  $V_{TH} = 0.7\text{V}$  (NMOS),  $V_{TH} = -0.8\text{V}$  (PMOS),  $W_{drawn}/L_{drawn} = 20\mu\text{m}/2\mu\text{m}$ ,  $t_{ox} = 9 \times 10^{-9}\text{m}$ ,  $L_D = 0.08\mu\text{m}$ , sketch  $I_X$  of  $M_1$  as a function of  $V_X$  increasing from 0V to  $V_{DD} = 5\text{V}$ .

$$(1) \quad I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \text{ (NMOS in triode region)}$$

$$(2) \quad I_D = \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 \text{ (NMOS in saturation region)}$$


$$(3) \quad I_D = \mu_p C_{ox} \frac{W}{L_{eff}} \left[ (V_{SG} - |V_{TH}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right] \text{ (PMOS in triode region)}$$

$$(4) \quad I_D = \mu_p C_{ox} \frac{W}{L_{eff}} (V_{SG} - |V_{TH}|)^2 \text{ (PMOS in saturation region)}$$

    


**Question 2. Combination of MOSFET**

For the circuit below, find the labeled node voltages. The NMOS transistor has  $V_{TH} = 0.9V$ ,  $k_n = \mu_n C_{ox}(W/L) = 1.5mA/V^2$ .

 


**Question 3. Small Signal of of MOSFET**

The circuit shown below is a MOSFET cascode amplifier. Draw the small signal model and derive  $R_{out}$  for the amplifier. Assume transistors  $M_1$  and  $M_2$  are in saturation and include  $r_O$  in your calculation.

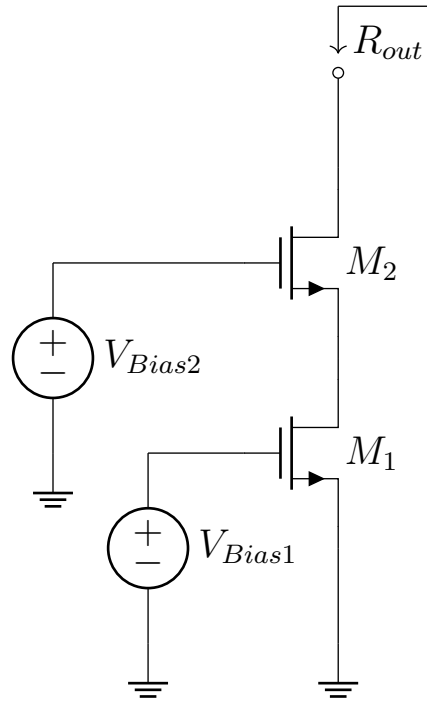

**Question 4. Common-Source with Resistive Load**

Assume  $\lambda = 0$  and  $\gamma = 0$ . For  $V_{DD} = 5V$ ,  $V_{in} = 0.9V + \text{small signal}$ ,  $R_D = 15k\Omega$  and  $L_{drawn} = 2\mu m$ , find out the value  $W_{drawn}$  to obtain a voltage gain  $|A_v| > 10$  and  $V_{OUT}$  (the DC biasing voltage at the output) close to 2.5 V as much as possible.

 

NMOS Model			
LEVEL=1	VTO=0.7	GAMMA=0.45	PHI=0.9
NSUB=9e+14	LD=0.08e-6	UO=350	LAMBDA=0.1
TOX=9e-9	PB=0.9	CJ=0.56e-3	CJSW=0.35e-11
MJ=0.45	MJSW=0.2	CGDO=0.4e-9	JS=1.0e-8
PMOS Model			
LEVEL=1	VTO=-0.8	GAMMA=0.4	PHI=0.8
NSUB=5e+14	LD=0.09e-6	UO=100	LAMBDA=0.2
TOX=9e-9	PB=0.9	CJ=0.94e-3	CJSW=0.32e-11
MJ=0.5	MJSW=0.3	CGDO=0.3e-9	JS=0.5e-8

VTO : threshold voltage with zero  $V_{SB}$  ( unit : V )

GAMMA : body effect coefficient ( unit :  $V^{1/2}$  )

PHI :  $2\Phi_F$  ( unit : V )

TOX : gate oxide thickness ( unit : m )

NSUB : substrate doping ( unit :  $cm^{-3}$  )

LD : source/drain side diffusion ( unit : m )

UO : channel mobility ( unit :  $cm^2/V/s$  )

LAMBDA : channel-length modulation coefficient ( unit :  $V^{-1}$  )

CJ : source/drain bottom-plate junction capacitance per unit area ( unit :  $F/m^2$  )

CJSW : source/drain sidewall junction capacitance per unit length ( unit :  $F/m$  )

PB : source / drain junction built-in potential ( unit : V )

MJ : exponent in CJ equation ( unitless )

MJSW : exponent in CJSW equation ( unitless )

CGDO: gate-drain overlap capacitance per unit width ( unit :  $F/m$  )

CGSO : gate-source overlap capacitance per unit width ( unit :  $F/m$  )

JS : source/drain leakage current per unit area ( unit :  $A/m^2$  )

Vacuum permittivity ( $\epsilon_o$ ) =  $8.85 \times 10^{-12}$ (F/m)

Silicon oxide dielectric constant ( $\epsilon_r$ ) = 3.9