



## Lecture 14

VE 311 Analog Circuits

Xuyang Lu  
2023 Summer



上海交通大學  
SHANGHAI JIAO TONG UNIVERSITY

# Recap of Last Lecture



- MOSFET Circuits:
  - Diode Connected Load and its variations
  - Source degeneration

# Topic to be covered



- Review for the midterm

# Format of the Midterm



- 100 minutes, 4 sections in total.
- 1<sup>st</sup> section consists of several quick-response questions, each shall take several minutes.
- The following four questions are
  - Diode Circuit
  - MOSFET
  - BJT

# Suggestions on the Midterm



Suggestions on the exam:


- During preparation, you shall get very familiar with the basic concepts. Remember most of the stuff or know precisely where to find it in your cheating sheet.
- The suggested amount of time (which also implies the credit) is shown. If you find a question difficult, you can come back and solve it.
- If you find a question not reasonable, state your reason for receiving credit.
- To receive partial credit, you must write something.
- The exam will be curved, show your best effort.
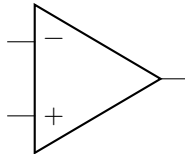
# Review of the first-half of our course




How to make an amplifier.


- ① What is amplification?  
concepts: DC+AC / Diff+Comm Gain
- ② The big picture of amplifiers  
input/output impedance, non-ideal op-amp
- ③ Component required:  
Linear and non-linear components  
Diode, BJT, MOSFET  
Till this stage, we' ve only investigated Common Emitter/source.
- ④ To be discussed: Inside an op-amp.  
(Bias, circuit components, Gain boosting, bandwidth and frequency.)




# DC + AC Analysis

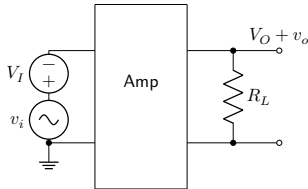

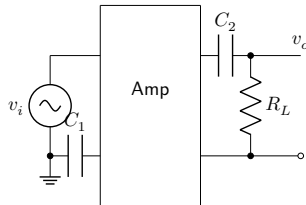- DC sets the biasing condition.
- AC sets the gain at a specific frequency.





# Small-Signal/Large-Signal

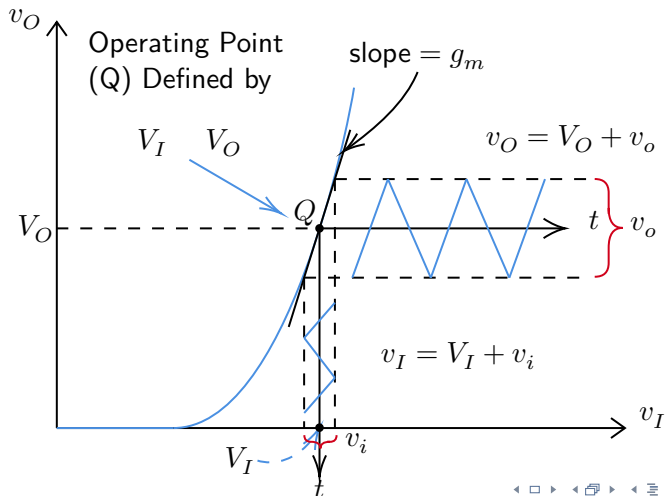




# What is Amplification

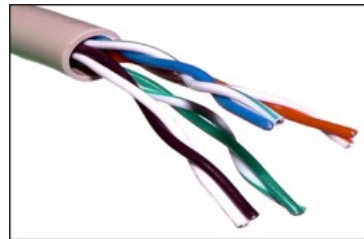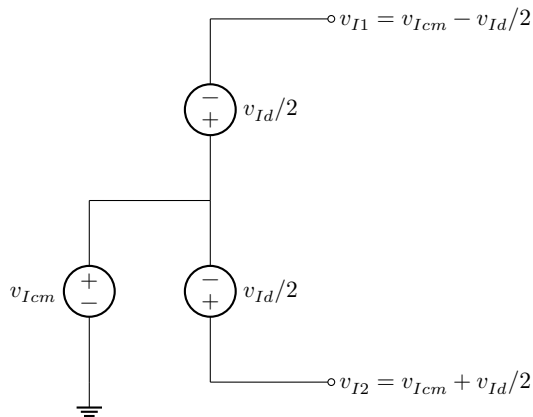


# What is Amplification

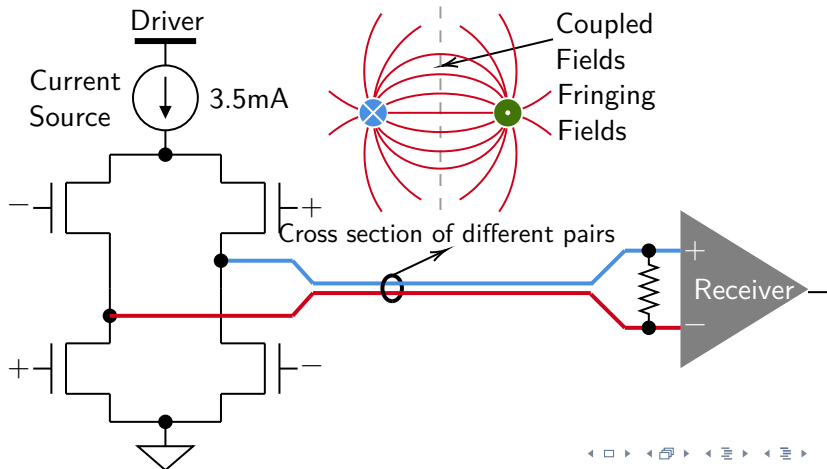


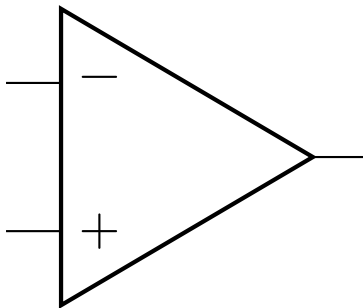
# Non-Ideal Opamps



- Gain
- $R_{out}$
- $R_{in}$
- CMRR
- Offset voltage
- Clipping
- Bandwidth
- Slew rate



# Non-Ideal Opamps

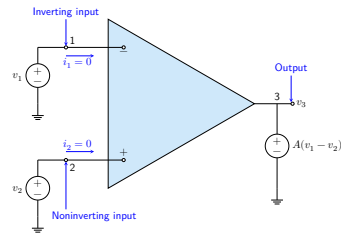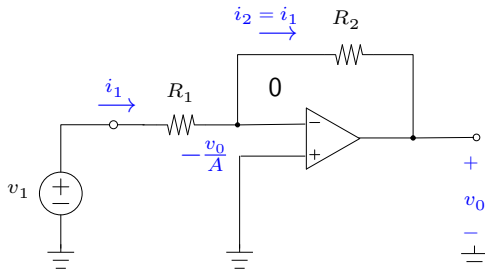


$$v_- - v_+ = -\frac{v_o}{A}$$
$$i_1 = \frac{v_i - (-v_o/A)}{R_1} = \frac{v_i + v_o/A}{R_1}$$
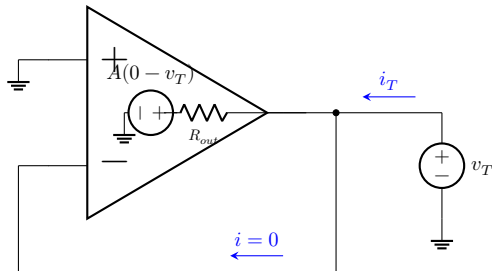
# Output Impedance



Make sure you know how to find out output impedance.




- How to find out the output impedance?
- Apply a test voltage and see what is  $V_T/i_T$

In general, We want large input impedance and small output impedance.

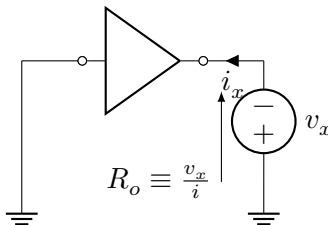
## Determining $R_o$

To find the output resistance, we follow the same procedure as we did for finding the Thevenin equivalent resistance.






- Short the input terminal, since the input is an independent voltage source
- Apply a test source  $v_x$
- Find  $i_x$
- Find the ratio of  $R_o = v_x / i_x$

# Difference Amplifier

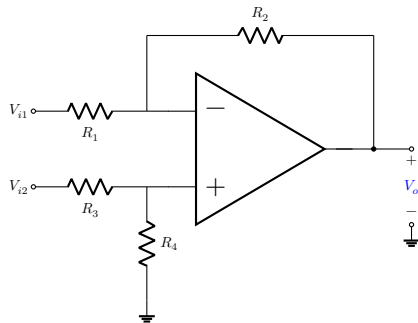

Cons: Input impedance is finite.  
Gain is not high.



# Difference Amplifier

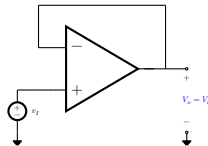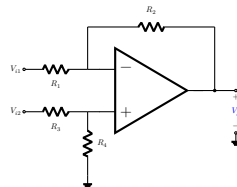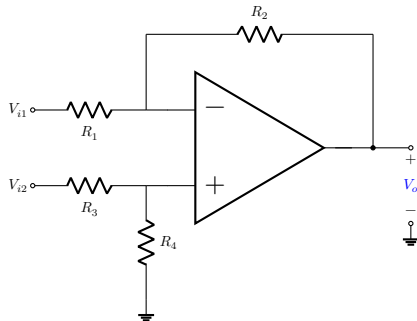


Use a unit gain buffer?  
Impedance is fine. Gain is not.



# Difference Amplifier

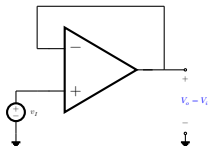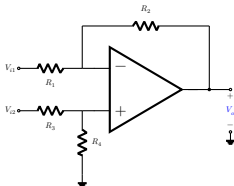

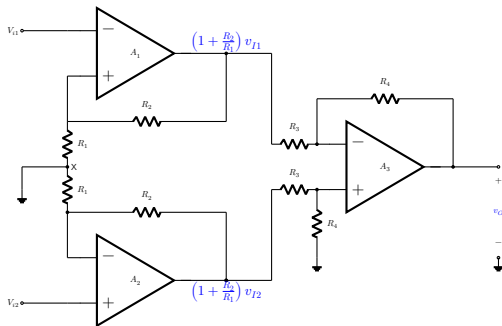
Cons: Possible op-amps saturation  
Mismatch between branches


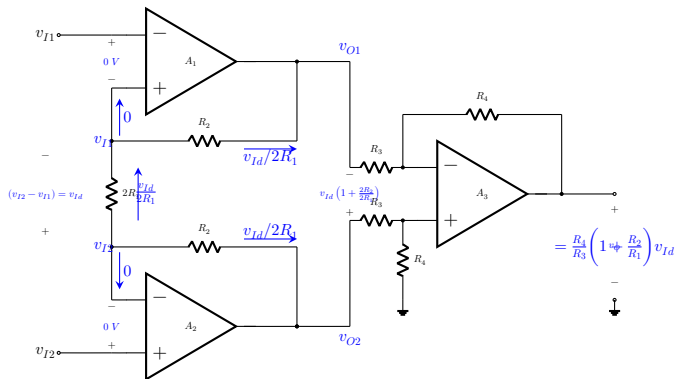
# Instrumentation Amplifier



What defines a good amplifier? Common/ differential (CMRR ratio)



# Instrumentation Amplifier



$$A_d \equiv \frac{v_O}{v_{Id}} = \frac{R_4}{R_3} \left( 1 + \frac{R_2}{R_1} \right)$$

Common mode first stage gain = 1

# Thevenin and Norton Model of Amps







Voltage Amp.

Transimpedance


Transconductance

Current Amp.

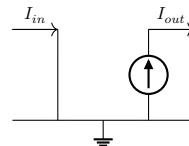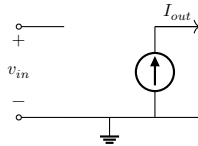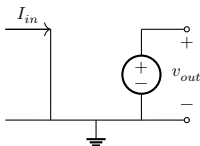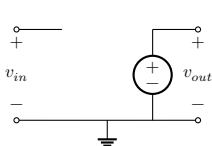


Do we want large or small input/output impedance?

# Thevenin and Norton Model of Amps

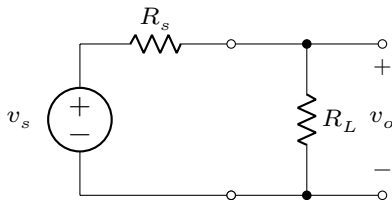

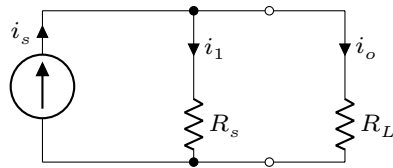Do we want larger or smaller  $R_s$  to get the largest output voltage?




From a current perspective, do we want large or small  $R_s$ ?
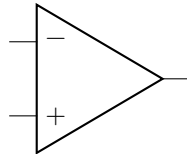
# Review of the first-half of our course




How to make an amplifier.

- ① What is amplification?  
concepts: DC+AC / Diff+Comm Gain
- ② The big picture of amplifiers  
input/output impedance, non-ideal op-amp
- ③ Component required:  
Linear and non-linear components  
Diode, BJT, MOSFET  
Till this stage, we' ve only investigated Common Emitter/source.
- ④ To be discussed: Inside an op-amp.  
(Bias, circuit components, Gain boosting, bandwidth and frequency.)




# Electrons and Holes

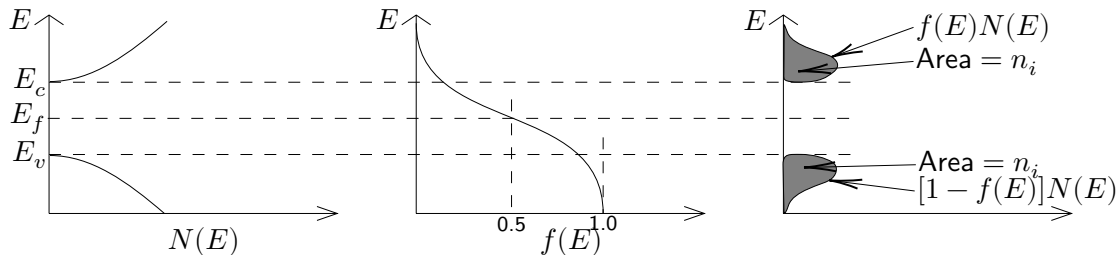

I will not ask you for any calculations on devices this time.

# P-Type

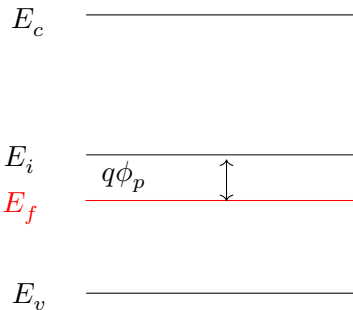

$$np = n_i^2 \quad (1)$$


$$p = N_a = n_i e^{\frac{E_i - E_f}{kT}} = n_i e^{\frac{q\phi_p}{kT}} \quad (2)$$

$$n = \frac{n_i^2}{N_a} = n_i e^{\frac{E_f - E_i}{kT}} = n_i e^{\frac{-q\phi_p}{kT}} \quad (3)$$

- Hu, Chenming. Modern semiconductor devices for integrated circuits.



# N-Type


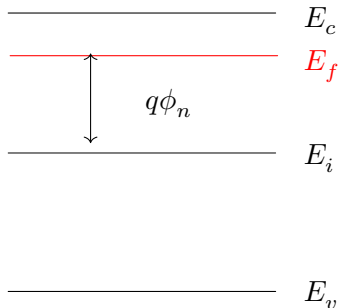


$$np = n_i^2 \quad (4)$$

$$n = N_d = n_i e^{\frac{E_f - E_i}{kT}} = n_i e^{\frac{q\phi_n}{kT}} \quad (5)$$

$$p = \frac{n_i^2}{N_d} = n_i e^{\frac{E_i - E_f}{kT}} = n_i e^{\frac{-q\phi_n}{kT}} \quad (6)$$


# Diffusion

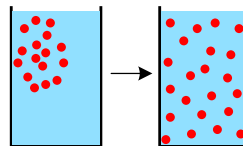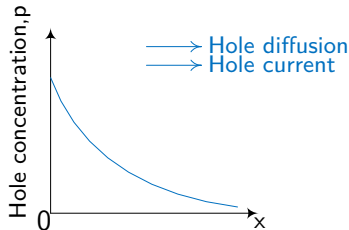

- Magnitude of the current at any point is proportional to the slope of the concentration profile, or the **concentration gradient** , at that point

$$J_{D,n} = qD_n \frac{dn(x)}{dx} \quad (7)$$

# Drift Current

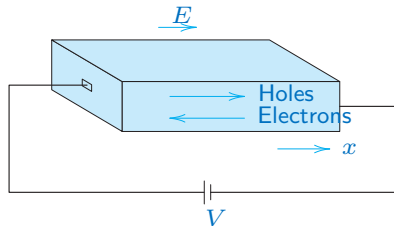


Drift current is independent of the value of the depletion-layer voltage  $V_0$ .

- The Junction Built-in Voltage

$$V_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right) \quad (8)$$


## Forward Bias (When $V_a > 0$ )

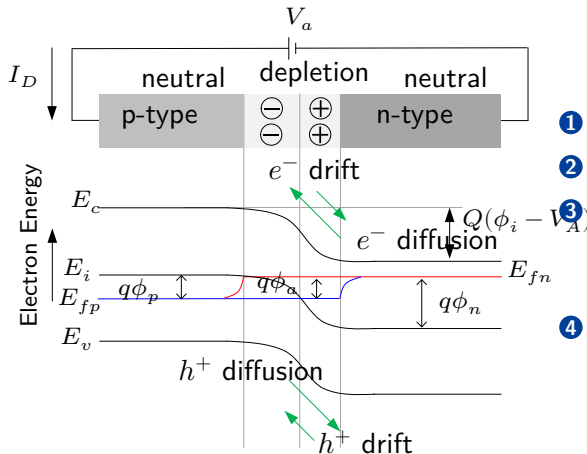

$$I_D = I_S \left( e^{\frac{qV_a}{kT}} - 1 \right) > 0 \quad (9)$$


- ①  $e \frac{qV_a}{kT}$  is the diffusion current.
- ②  $-1$  stands for the drift current.
- ③ The energy barrier formed by the built-in electric field becomes smaller,  $q(\phi_i - V_a)$ .
- ④ Neamen, Donald A. Semiconductor Physics and Devices Basic Principles, chapter 8

## Forward Bias (When $V_a > 0$ )

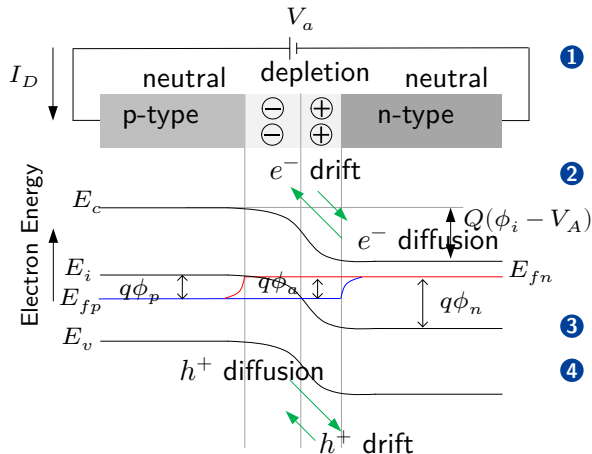

- ① More electrons/holes diffuse to the opposite sides. → Diffusion current increases.
- ② The drift current is limited by the number of minority carriers on either side of the p-n junction and is unchanged by the increased E-field.
- ③ There is (+) net current flowing.
- ④ The depletion width becomes narrower.

# Reverse Bias ( $V_a < 0$ )

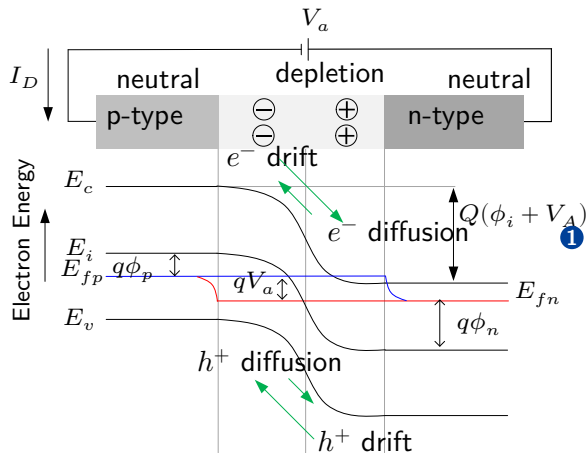


$$I_D = I_S \left( e^{\frac{qV_a}{kT}} - 1 \right) < 0 \quad (10)$$

① The energy barrier formed by the built-in electric field becomes larger,  $q(\phi_i + V_a)$ .




## Reverse Bias ( $V_a < 0$ )

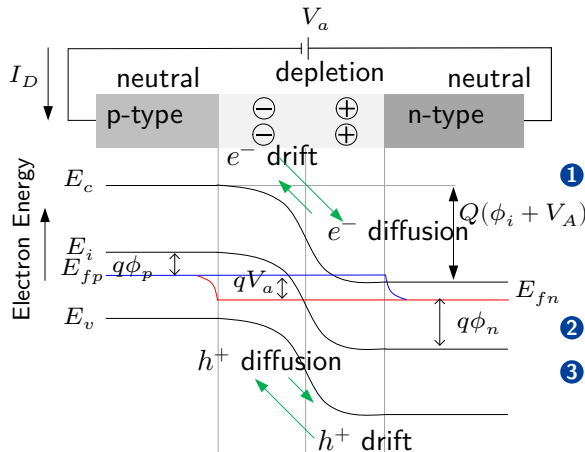

$$I_D = I_S \left( e^{\frac{qV_a}{kT}} - 1 \right) < 0 \quad (11)$$

- ① Less electrons/holes diffuse to the opposite sides. → Diffusion current decreases, while drift current remains the same.
- ② There is (-) net current flowing.
- ③ The depletion width becomes wider.

# Diode model

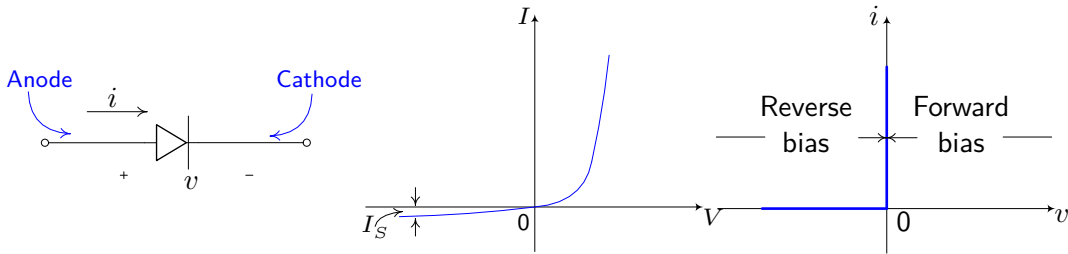

Remember the following equation

- $I = I_S (e^{V/V_T} - 1)$

Ideal model

Constant voltage model

I will ask you to solve a diode related circuit!




# Application of Diodes





- Regulators
- Photodetectors
- Rectifiers

# Regulator


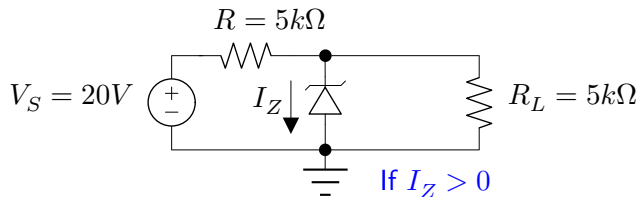


# Rectifier

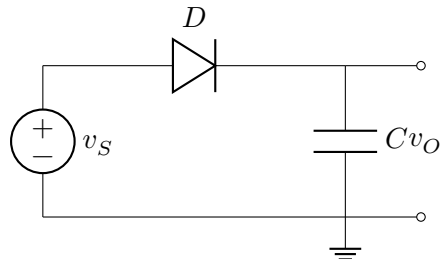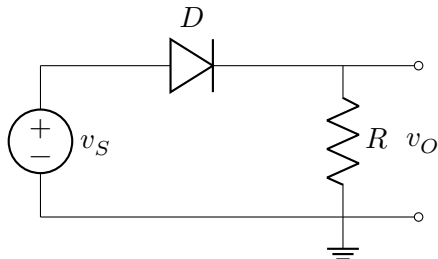

There is not going to be a difficult calculation on a full-wave rectifier. All caps are treated as ideal since we did not cover the frequency domain yet.

# Full Wave Rectifier

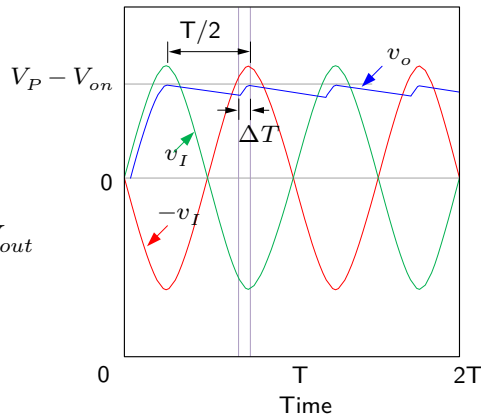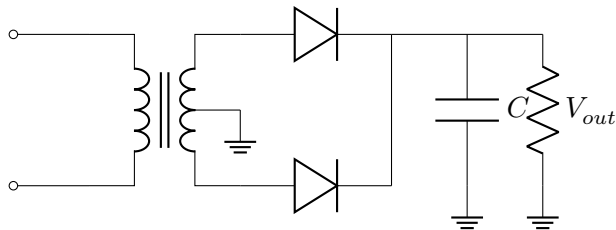

# Full Wave Rectifier



$$V_{dc} = V_s - V_{on} \quad (12)$$



$$I_{dc} = \frac{V_{dc}}{R} \quad (13)$$

$$V_r = (V_s - V_{on}) \left(1 - e^{-\frac{T/2 - \Delta T}{RC}}\right) \quad (14)$$


$$\cong (V_s - V_{on}) \left(\frac{T/2 - \Delta T}{RC}\right) \text{ if } \left(\frac{T}{2} - \Delta T\right) \ll RC \quad (15)$$

$$\cong (V_s - V_{on}) \left(\frac{T}{2RC}\right) \text{ if } \Delta T \ll \frac{T}{2} \quad (16)$$
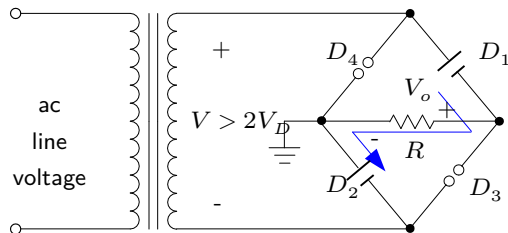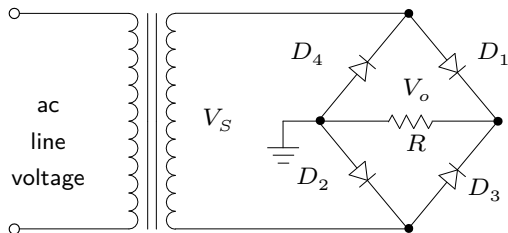
# Diode-Based Full Wave Rectifier ( $V > 2V_D$ )



## Ripple Voltage Derivation

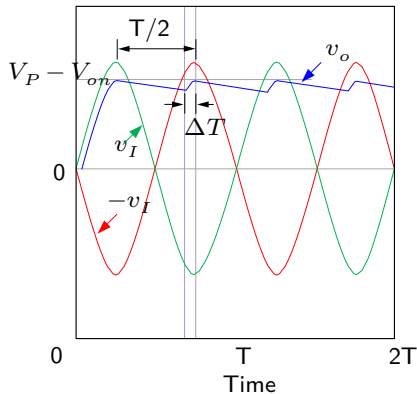


$$V_{dc} = V_s - V_{on} \quad (17)$$

$$I_{dc} = \frac{V_{dc}}{R} \quad (18)$$

$$V_r = (V_s - V_{on}) (1 - e^{-\frac{T/2 - \Delta T}{RC}}) \quad (19)$$

# Ripple Voltage Derivation

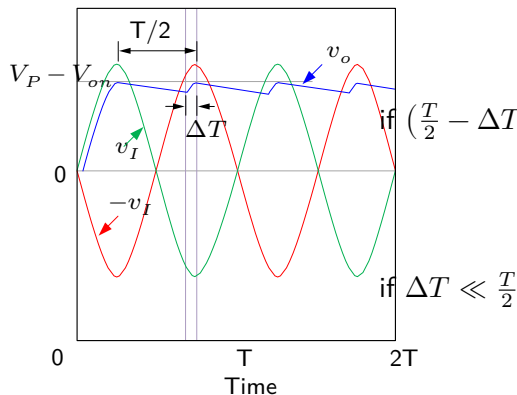

$$V_r = (V_s - V_{on}) (1 - e^{-\frac{T/2 - \Delta T}{RC}}) \quad (20)$$

$$\text{if } (\frac{T}{2} - \Delta T) \ll RC$$


$$\cong (V_s - V_{on}) \left( \frac{T/2 - \Delta T}{RC} \right) \quad (21)$$

$$\text{if } \Delta T \ll \frac{T}{2}$$

$$\cong (V_s - V_{on}) \left( \frac{T}{2RC} \right) \quad (22)$$



# I-V Curve of Solar Cells

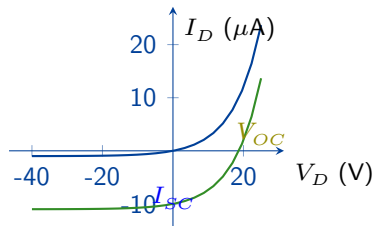

Blue:

$$I = I_S \left( e^{\frac{qV}{kT}} - 1 \right)$$


Green:

$$I = I_S \left( e^{\frac{qV}{kT}} - 1 \right) - I_{SC}$$


IV of Diodes vs. that of solar Cells

What are fill factor and power conversion efficiency?

# nnp BJT Transistors

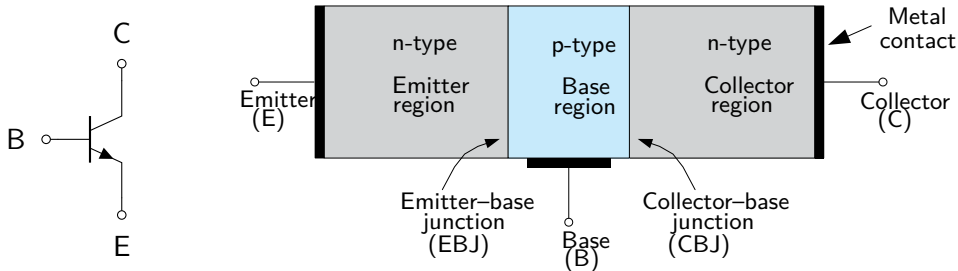

# pnp BJT Transistors

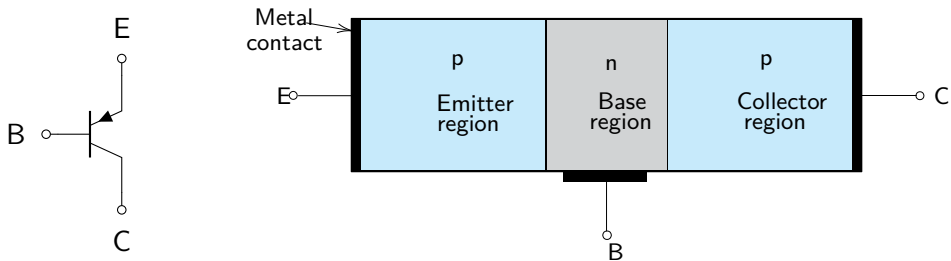



$V_{BE} > 0$  and  $V_{CB} = 0$  ( $N_{d1} \gg N_a$ ,  $W_B$  very short)


$$I_B \cong 0 \quad (23)$$

$$I_C \cong I_E \quad (24)$$

$$I_E = I_C + I_B \quad (25)$$

$$\frac{I_C}{I_E} = \alpha \quad (26)$$

$$\frac{I_C}{I_B} = \beta \quad (27)$$

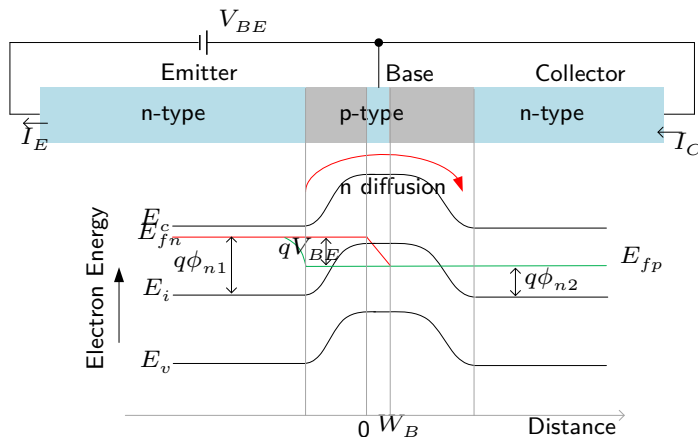


$V_{BE} > 0$  and  $V_{CB} = 0$  ( $N_{d1} \gg N_a$ ,  $W_B$  very short)



- The n (electron) diffusion is much larger than the p (hole) diffusion at the Base-Emitter junction.
- Nearly all the n (electron) diffusion from the Base-Emitter junction pass through the Base, enter into the depletion region of the Base-Collector junction, and are swept to the Collector side by the built-in electric field.

# NPN & PNP BJT Transistors

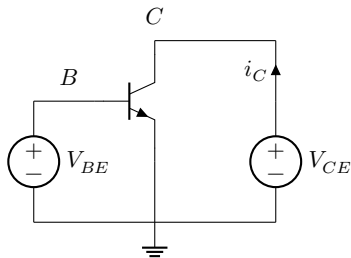

$$V_{CE} \geq V_{BE} \quad (28)$$


$$I_C = I_S \left( e^{\frac{qV}{kT}} - 1 \right) \quad (29)$$

$$\alpha = \frac{I_C}{I_E} \cong 1 \quad (30)$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha} \quad (31)$$

$I_S$  is a constant in the spice model

# Hybrid- $\pi$ Model

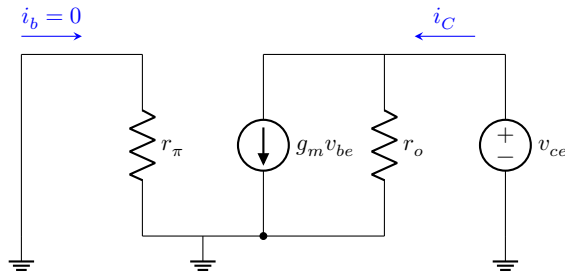

$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right) \quad (32)$$


$$r_\pi = \frac{dV_{BE}}{dI_B} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} \quad (33)$$

$$= \frac{1}{\frac{g_m}{\beta}} = \frac{\beta}{g_m} \quad (34)$$

$$g_m = \frac{dI_C}{dV_{BE}} \cong \frac{I_C}{kT/q} \quad (35)$$


$$r_o = \frac{1}{\frac{dI_C}{dV_{CE}}} \cong \frac{V_A}{I_C} \quad (36)$$

# Impedance Looking into Emitter

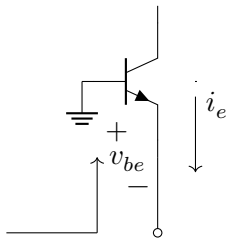


$$r_e = \frac{r_\pi}{(\beta + 1)} \quad (37)$$
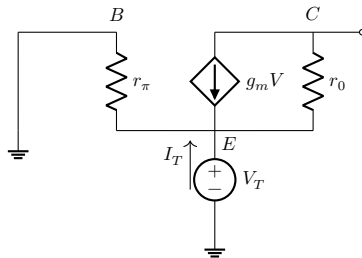
$$= \frac{1}{(\beta + 1)} \frac{\beta}{g_m} = \frac{\alpha}{g_m} \cong \frac{1}{g_m} \quad (38)$$





# Common Emitter With Degeneration

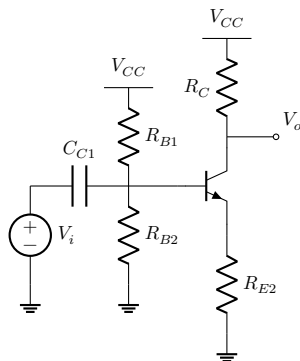

$$\frac{v_o}{v_i} \approx \frac{-g_m R_C}{1 + g_m R_E} \quad (39)$$

the gain has reduced by  $1 + g_m R_E$

- If  $g_m R_E \gg 1$  then the gain is:

$$\frac{v_o}{v_i} \approx \frac{-R_C}{R_E} \quad (40)$$

- This means the gain is independent of the BJT transistor