

# VE311

## Electronic Circuits

### RC Final

Yucheng Huang

University of Michigan  
Shanghai Jiao Tong University  
Joint Institute

July 28, 2023

3 questions

① Short response

① Concept

L13 L16 - 24

2) Half-circuit

3) Miller

② Current Mirror (Hard)

③ L19 - 24

~~Single-Stage~~

## 1 MOSFET Single Stage Amplifier

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier

Ravazi

C3

## 2 MOSFET Differential Pair Amplifier

C4

## 3 Current Mirror

- Current Mirror

C5

Frequency Response

C6


## 1 MOSFET Single Stage Amplifier

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier

## 2 MOSFET Differential Pair Amplifier

## 3 Current Mirror

- Current Mirror

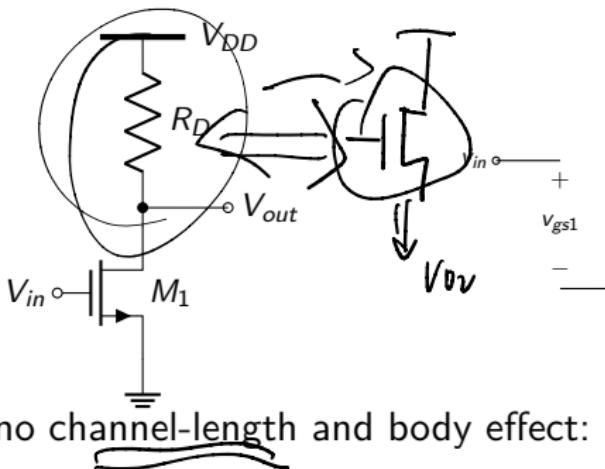CS with Resistive Load


$$\underline{\underline{A_v = \frac{V_{out}}{V_{in}} = -g_{m1}R_D}}$$
(1)

No body effect:

$$A_v = -g_{m1}(R_D \parallel r_{o1})$$
(2)

$$A_v = -g_{m1}(r_{o1} \parallel r_{o2})$$

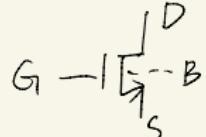{ Common Source  
 Drain (Source Follower)  
 Gate  
 Cascade




Resistive Load

\* Diode-connected Load




\* Current Source Load

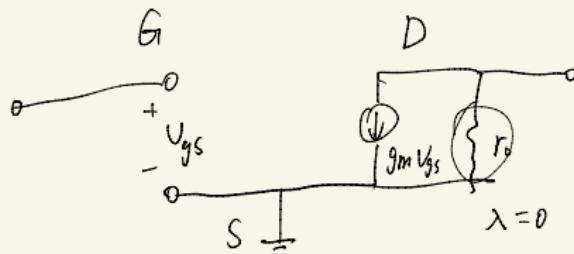

Neglect channel length ---

## CS with Diode-connected Load

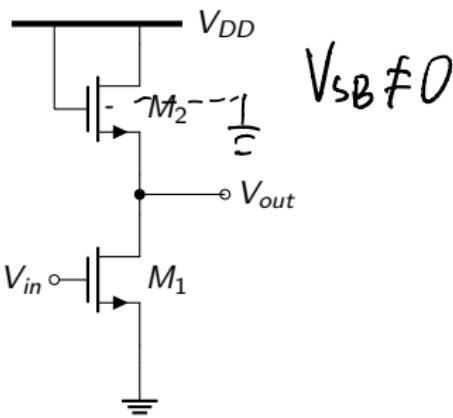



NMOS:

$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta} \quad \eta = \frac{g_{mb2}}{g_{m2}} \quad (3)$$

PMOS:

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}} \quad (4)$$

## CS with Current Source Load

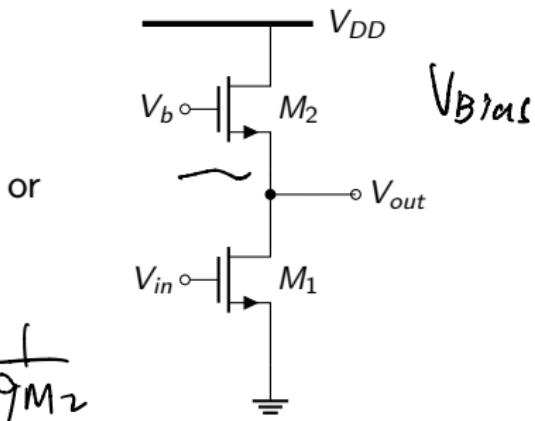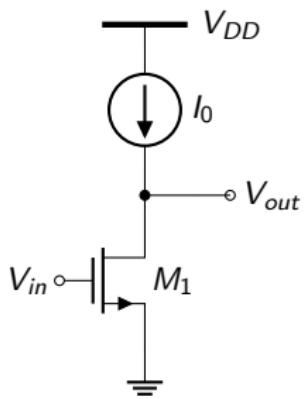

$$A_v = -g_{m1}(\textcircled{1} \parallel r_{o1}) \quad (5)$$

## 1 MOSFET Single Stage Amplifier



- Common Source Amplifier
- **Common Drain Amplifier (Source Follower)**
- Common Gate Amplifier
- Cascode Amplifier

## 2 MOSFET Differential Pair Amplifier

## 3 Current Mirror

- Current Mirror

## Source Follower

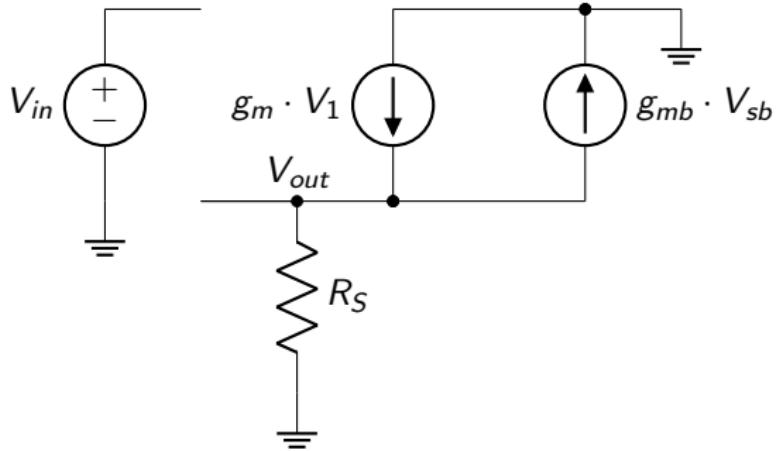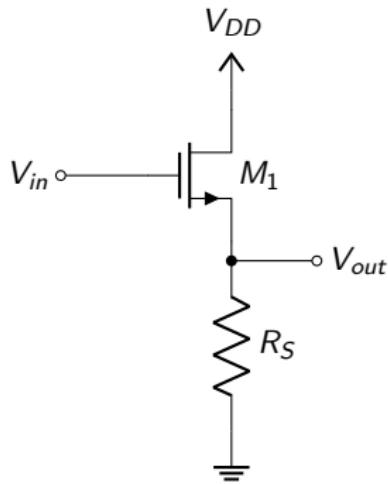

$$A_v = \frac{g_m R_S}{1 + g_m R_S(1 + \eta)} = \frac{g_m R_S}{1 + (g_m + g_{mb})R_S} \approx \frac{1}{1 + \eta} \quad (6)$$

## Example 1 |

In the source follower with current source load, the current source is ideal. Find the output impedance for the amplifier when  $I_0 = 0.01$  and  $0.1mA$  respectively. (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,


$K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,

$K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$

## Example 1

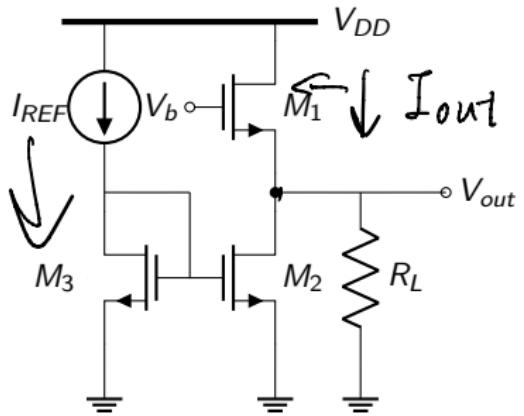

## Example 1

$$g_{M1} = \sqrt{2K_a W_L I_D} = 663.3 \mu A/V$$

$$R_{O1} = R_{O2} = \frac{1}{2I_D} = 250 k\Omega$$

$$V_{out} = \frac{1}{g_{M1} + \underbrace{g_{M1} b_1}_{\downarrow 0} + \frac{1}{R_{O1}} + \frac{1}{R_{O2}}}$$

$$V_{out} \approx \frac{1}{g_{M1}}$$

## 1 MOSFET Single Stage Amplifier


- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- **Common Gate Amplifier**
- Cascode Amplifier

## 2 MOSFET Differential Pair Amplifier

## 3 Current Mirror

- Current Mirror

## Common Gate

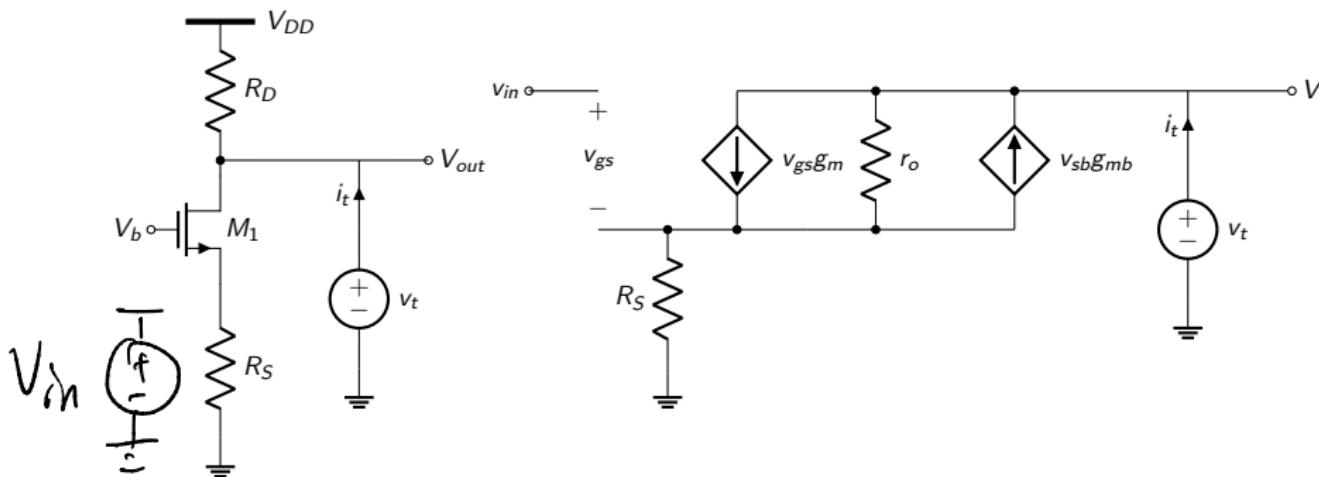

$$\boxed{R_{in}} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o} \begin{cases} \text{If } R_D = 0 & R_{in} = r_o \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \\ \text{If } R_D = \infty & R_{in} = \infty \end{cases} \quad (7)$$

$$\underline{\underline{R_{out}}} = [R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S] \parallel R_D \quad (8)$$

## 1 MOSFET Single Stage Amplifier

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier


## 2 MOSFET Differential Pair Amplifier

## 3 Current Mirror

- Current Mirror

# Cascode Common Gate + Common Source

~~EE221~~

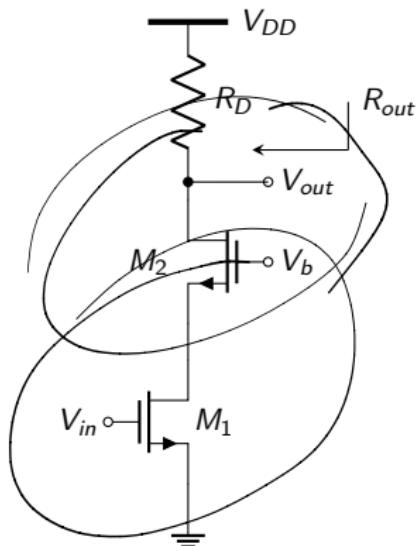


$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left( r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (9)$$

$$R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \parallel R_D \quad (10)$$

## Cascode

$$A_v = \underline{G_m} R_{out}$$

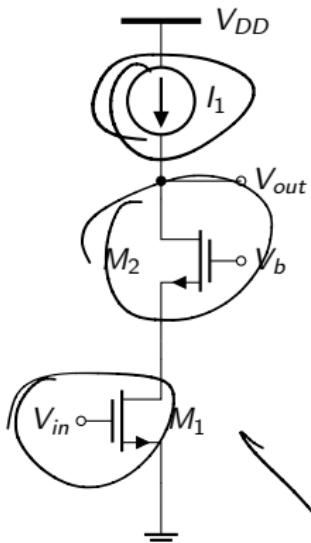



$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left( r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (11)$$

$$R_{out} = r_{o1} + r_{o2} + (g_{m2} + g_{mb2}) r_{o2} r_{o1} \quad (12)$$

$$A_v = G_m R_{out} \quad (13)$$

$G_m$        $g_m$


## Cascode

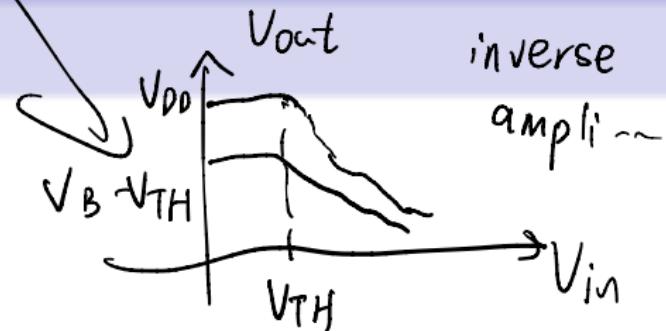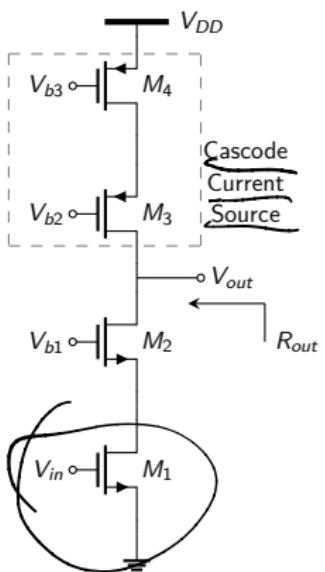

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + (r_{o2} \parallel \frac{1}{g_{m2}g_{mb2}})} \quad (14)$$

$$R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \parallel [r_{o3} + r_{o4} + (g_{m3} + g_{mb3})r_{o3}r_{o4}] \quad (15)$$

$$A_v = G_m R_{out} \quad (16)$$

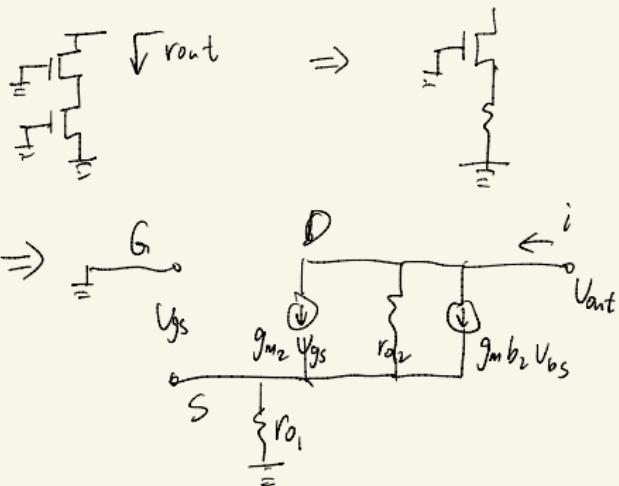

$$\Rightarrow R_{o2} [i - (g_{M2} + g_{mb2}) V_2] + i R_o = V_{out}$$

$$R_{out} = \frac{V_{out}}{i} = [(i + (g_{M2} + g_{mb2}) V_2) R_{o1} + R_{o2}]$$

## Example 5

hw 5

In the cascode amplifier , what is the gain when  $I_{REF} = 0.01mA$  and  $0.1mA$  respectively? (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,

$K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,

$K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$

$$g_{m_1} = g_{m_2}$$

$$r_{01} = r_{02}$$

$$A_v = -g_{m_1} [ (g_{m_2} + g_m b_2) r_{02} v_{01} ]$$

$$= 27498 \text{ } \text{--}$$

		Gain	$R_{out}$	$R_{in}$	Swing
CS	R	$\sim$	$r_o \parallel r_{o1}$	$\infty$	Medium
PMOS		$\sim$	$\approx \frac{1}{g_{me}} \parallel r_{o2} \parallel r_{o1}$	$\infty$	Small
I		$\sim$	$r_{o2} \parallel r_{o1}$	$\infty$	high
CD				$\infty$	
CG				$\frac{r_{o1} + r_{oL}}{(g_{m1} + g_{mb1}) r_{o1} + 1}}$	
CAS		$-g_{m1} [g_{m2} \\ r_{o2} r_{o1} \parallel g_{m1} r_{o3} r_{o4}]$	$[g_{m2}, r_{o2}, r_{o1} \parallel \\ g_{m1}, r_{o3}, r_{o4}]$	$\infty$	

## 1 MOSFET Single Stage Amplifier

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier


## 2 MOSFET Differential Pair Amplifier

half-circuit

## 3 Current Mirror

- Current Mirror

## Differential Pair

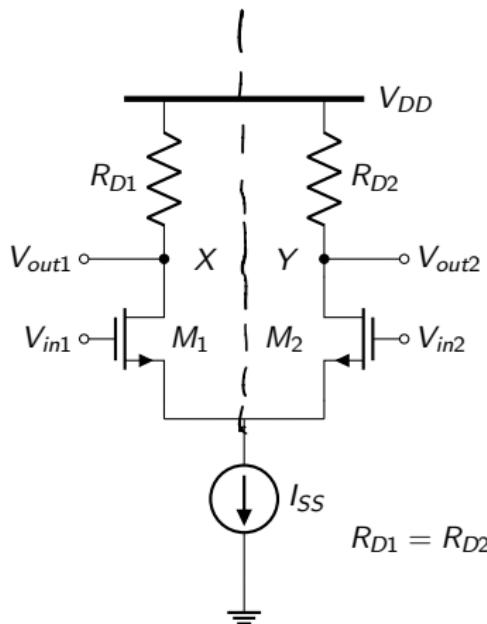

$A_{CM}$


$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} = -g_m(R_D \parallel r_o) \quad (17)$$

If the circuit is fully symmetric,

$$A_{CM-DM} = \frac{V_{out1} - V_{out2}}{v_{in,CM}} = 0 \quad (18)$$

$$CMRR = \left| \frac{\frac{A_{DM}}{A_{CM-DM}}}{A_{CM}} \right| = \infty \quad (19)$$

# Differential Pair with MOS Loads

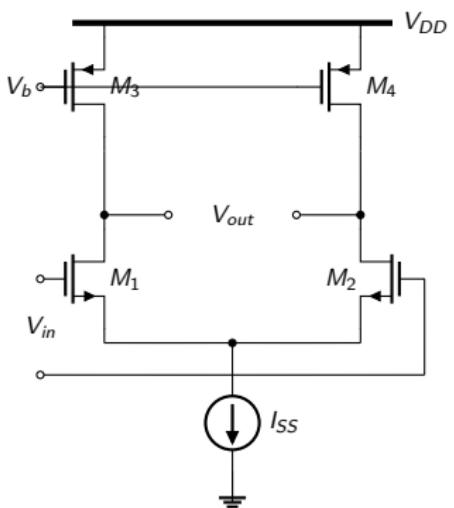


$A_{DM}$ : Differential Response Gain

$A_{CM}$ : Common Response

$$A_{DM} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \quad (20)$$

## Differential Pair with Cascode Loads

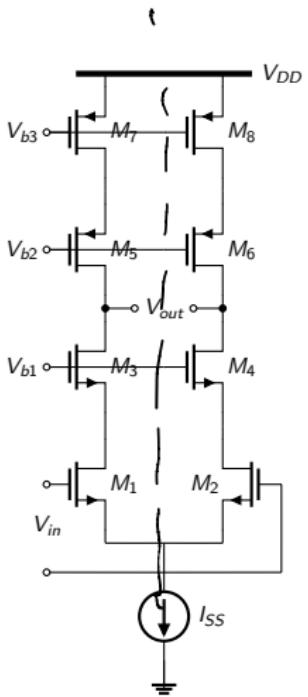

$$A_{DM} \cong -g_{m1,2} [(g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2} \parallel (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \quad (21)$$

## Example 2

In the differential pair , what is the gain when  $I_{SS} = 0.02mA$  and  $0.2mA$  respectively? (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,


$K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,

$K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$

## Example 2

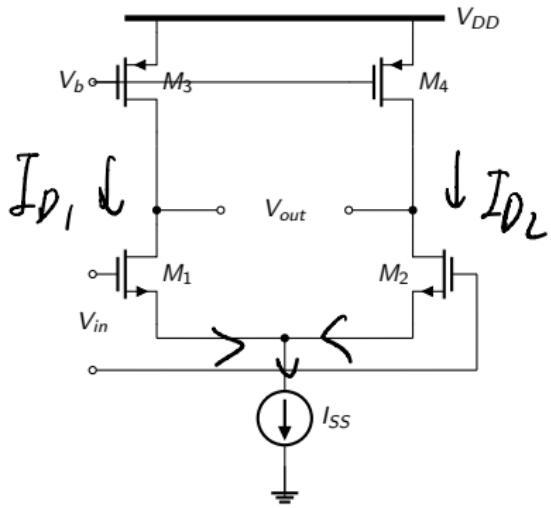




## Example 2

$$g_{M1,2} = \sqrt{2K_n W_L I_{D1,2}} \quad R_{O1,2} = 250k\Omega$$

$$I_{D1,2} = \frac{1}{2} I_{SS} = 0.1 \text{ mA} \quad R_{O3,4} = 200k\Omega$$

$$A_{vd} = \dots$$


## Common Mode Response

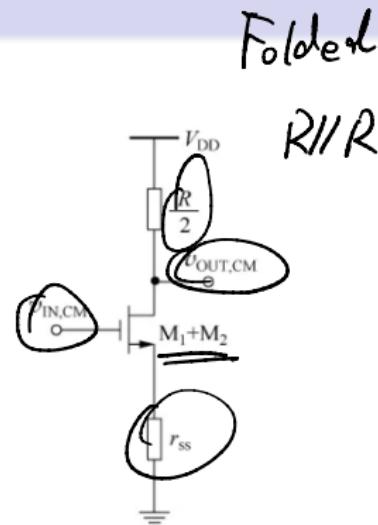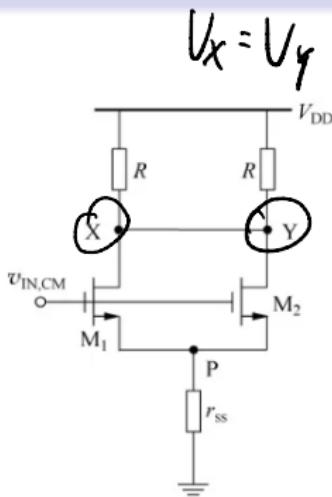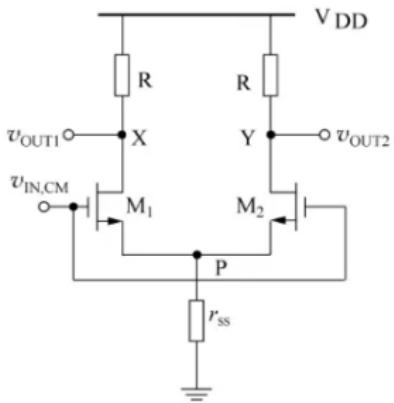

$$\begin{aligned} \underline{\underline{v_{in,cm}}} &= v_{gs} + 2g_m v_{gs} \cdot r_{ss} \\ \underline{\underline{2g_m v_{gs} + \frac{v_{out,cm}}{R/2}}} &= 0 \end{aligned} \quad \left. \right\} KCL$$

$$\frac{A_{vd}}{A_{vc}}$$

$$CMRR = \frac{|A_{vd}|}{|A_{vc}|} = \underline{\underline{1 + 2g_m r_{ss}}}$$

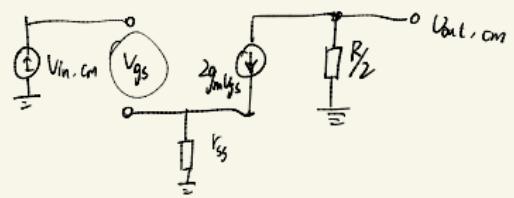

## Example 3

In the differential pair , what is the common gain and differential gain and CMRR when  $I_{SS} = 0.2mA$  ? (Neglect body effect,  
 $R = 10k\Omega$ ,  $V_{DD} = 5V$ )

Parameter for NMOS:  $V_{THN} = 0.7V$ ,


$K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,

$K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$

## Example 3

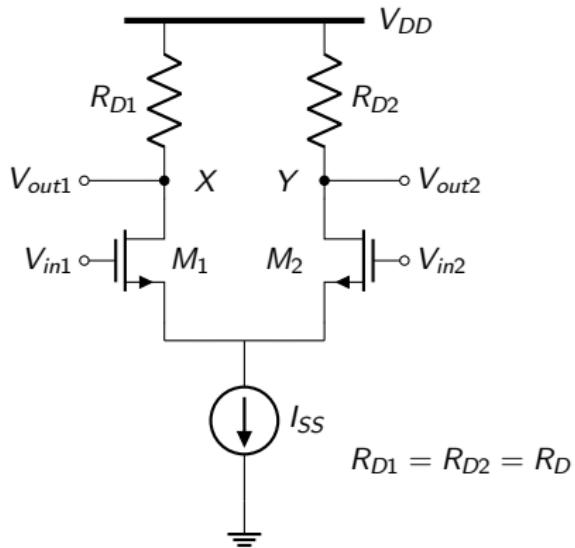

$$R_{D1} = R_{D2} = R_D$$

## Example 3

$$|A_{vd}| = g_m R$$

$$|A_{vc1}| = \frac{g_m R}{1 + 2g_m r_{ss}}$$

$$CMRR = \frac{|A_{vd}|}{|A_{vc1}|}$$



$$g_m = \sqrt{2K_n V_L I_D}$$

$$I_D = \frac{1}{2} I_{ss} = 0.1 \text{ mA}$$

$$r_{ss} = \frac{1}{\lambda I_{ss}}$$

$$\begin{aligned} &= \frac{1}{0.04 \times 0.2 \times 10^{-3}} \\ &= 125 \text{ k}\Omega \end{aligned}$$

## Mismatch 失配

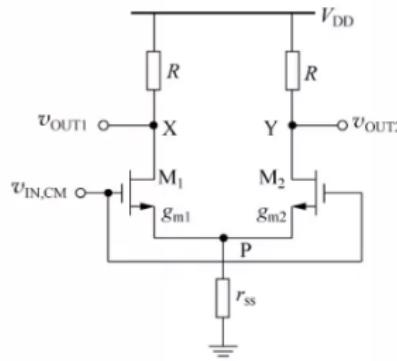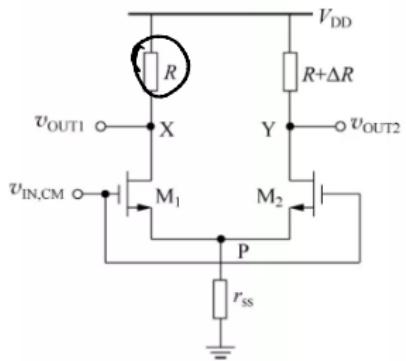

$$\underline{A_{cm-dm}} = - \left( \frac{g_m \Delta R + \Delta g_m R}{2g_m r_{ss} + 1} \right)$$

## 1 MOSFET Single Stage Amplifier

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier

## 2 MOSFET Differential Pair Amplifier

## 3 Current Mirror

- Current Mirror

## 1 MOSFET Single Stage Amplifier

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier


## 2 MOSFET Differential Pair Amplifier

## 3 Current Mirror


- Current Mirror

# Current Mirror

Replicate

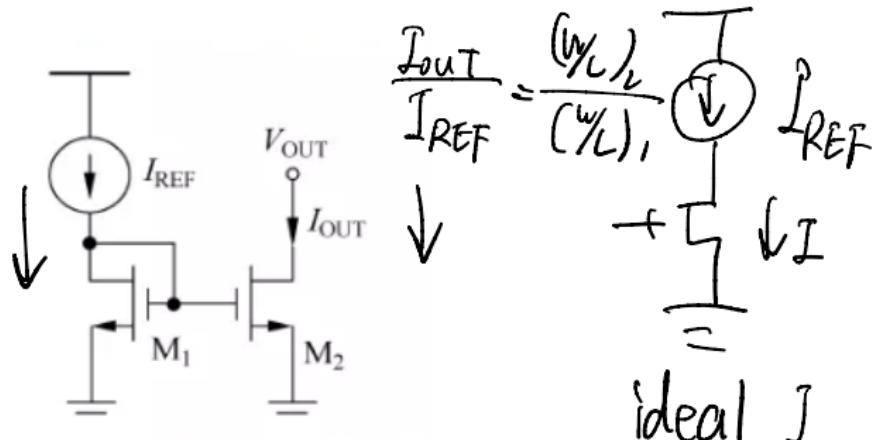
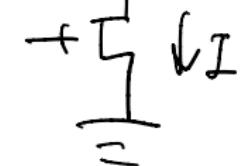
$$\frac{I_{OUT}}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$




ideal  $I$

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{THN1})^2$$

$$I_{OUT} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{THN2})^2$$

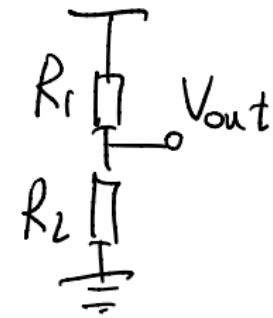
$$I_{OUT} = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$



Resistor

Temperature /  
P S

## Current Mirror

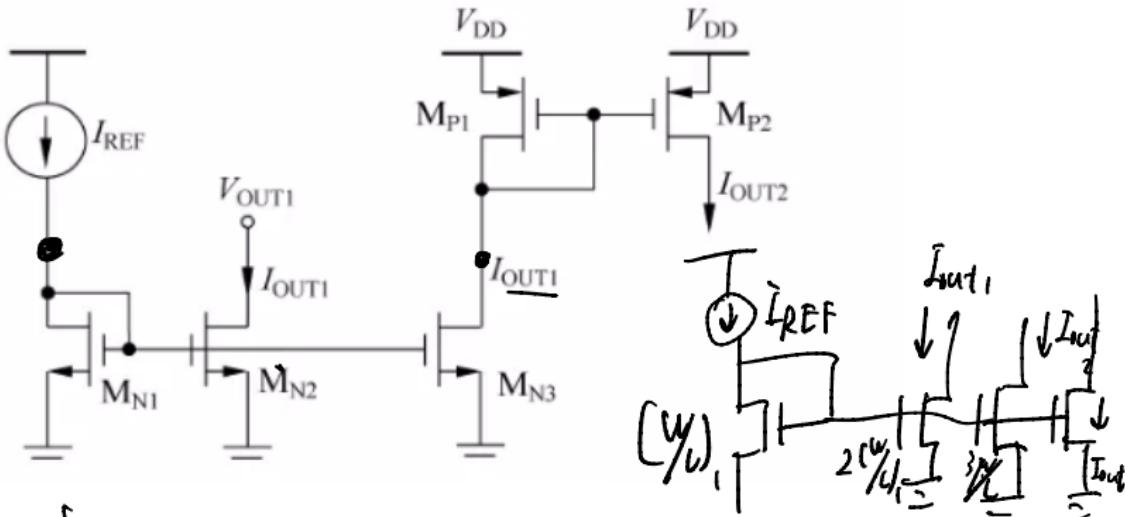at most 4 MOSFET


$$\underline{I_{OUT1}} = \frac{(W/L)_{N2}}{(W/L)_{N1}} \underline{I_{REF}}$$

$$I_{OUT2} = \frac{(W/L)_{N3}}{(W/L)_{N1}} \frac{(W/L)_{P2}}{(W/L)_{P1}} I_{REF}$$

$$I_{out1} = 2 I_{REF}$$

$$I_{out2} = 3 I_{REF}$$

## Cascode Current Mirror

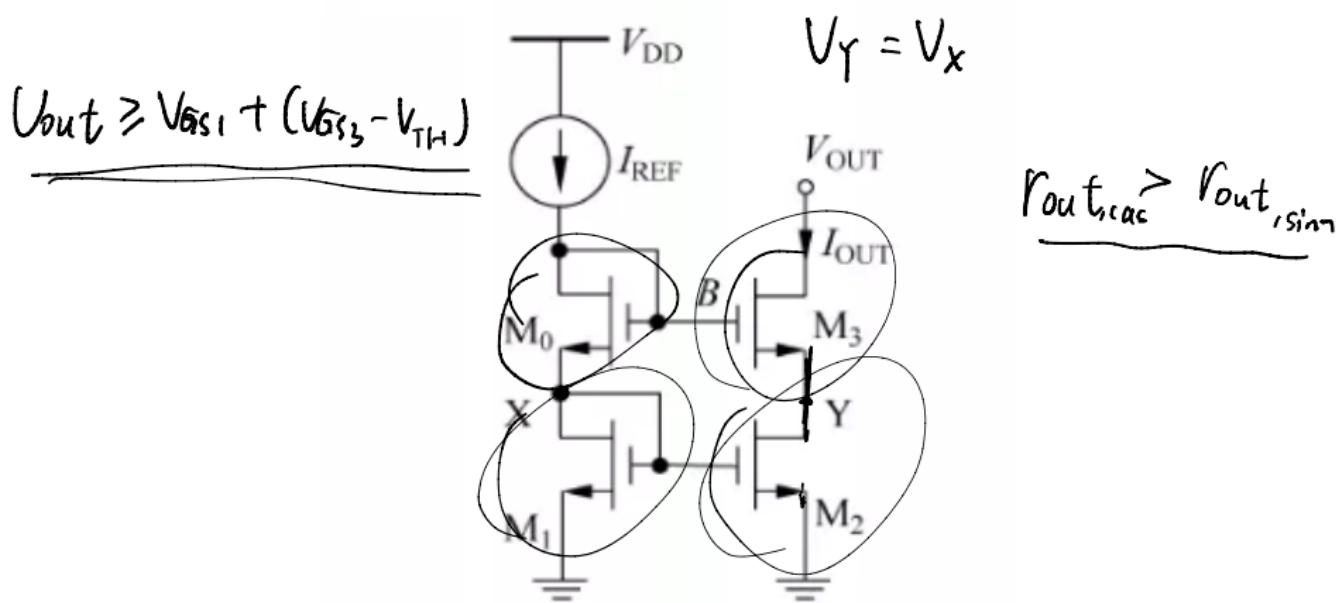

## Example 4

In the cascode current mirror , what is the range of output voltage when  $I_{REF} = 0.1mA$  ? (Neglect body effect, channel-length effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,

$K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,

$K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$

MOSFET Single Stage Amplifier  
oooooooooooooooo

MOSFET Differential Pair Amplifier  
oooooooooooo

Current Mirror  
oooooooo●oooo




## Example 4

## Differential Pair with Current Mirror Load

provide

$$V_X = V_Y$$
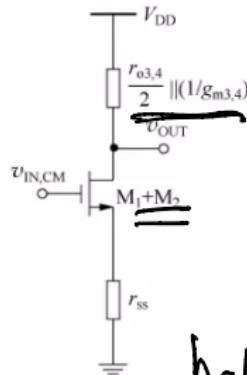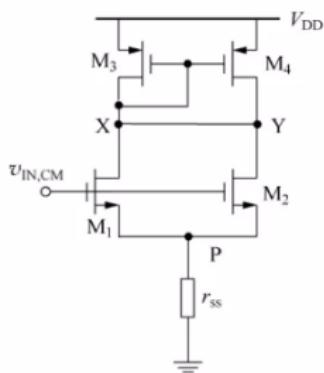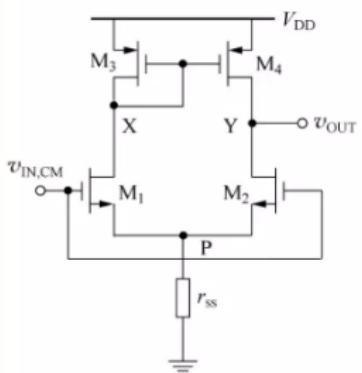
$$\frac{1}{g_{M_{3,4}}} \parallel \frac{r_o}{2}$$



half-circuit

# Differential Pair with Current Mirror Load

$$A_{vd} = \frac{v_{out}}{v_d} = g_m r_{out} = g_m (r_{o2} \| r_{o4})$$

$$A_{vc} \approx -\frac{\frac{1}{2g_{m3,4}} \parallel \frac{r_{o3,4}}{2}}{\frac{1}{2g_{m1,2}} + r_{ss}} \approx -\frac{1}{1 + 2g_{m1,2}r_{ss}} \frac{g_{m1,2}}{g_{m3,4}}$$

$$\text{CMRR} = \frac{|A_{vd}|}{|A_{vc}|} = (1 + 2g_{m1,2}r_{ss}) g_{m3,4} (r_{o2} \| r_{o4})$$

MOSFET Single Stage Amplifier  
oooooooooooooooo

MOSFET Differential Pair Amplifier  
oooooooooooo

Current Mirror  
oooooooo●

=

MOSFET Single Stage Amplifier  
oooooooooooooooo

MOSFET Differential Pair Amplifier  
oooooooooooo

Current Mirror  
oooooooo●

END

Thanks