

Final RC - part3

Jiaying Li


University of Michigan-Shanghai Jiao Tong University Joint Institute

July 28, 2023



JOINT INSTITUTE
交大密西根学院

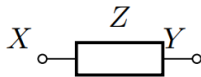
- 1 Miller Effect
- 2 First Order Systems
- 3 Nth Order Systems





$$A_v = \frac{Y}{X} \quad (1)$$

$$Z_1 = \frac{Z}{1 - A_v} \quad (2)$$


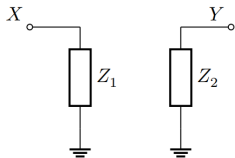
$$Z_2 = \frac{Z}{1 - \frac{1}{A_v}} \quad (3)$$



If the impedance Z forms the **ONLY** signal path between X and Y , then Miller conversion is often invalid.

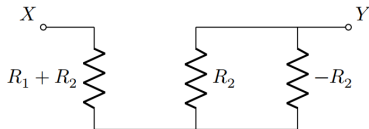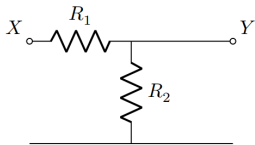

Example 1

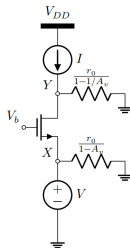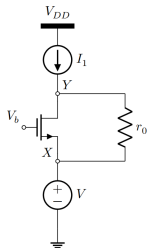

$$A_v = \frac{Y}{X} = 1 + (g_{m1} + g_{mb1}) r_{o1} \quad (4)$$

$$Z_1 = \frac{r_{o1}}{1 - [1 + (g_{m1} + g_{mb1}) r_{o1}]} = \frac{-1}{g_{m1} + g_{mb1}} \quad (5)$$

$$R_{in} = \frac{-1}{g_{m1} + g_{mb1}} \parallel \frac{1}{g_{m1} + g_{mb1}} = \infty \quad (6)$$

Example 1

R_{in} from source in NMOS:


$\lambda = 0$:

$$R_{in} = \frac{1}{g_{m1} + g_{mb1}} \quad (7)$$

$\lambda \neq 0$:

Apply Miller Effect


Association of Poles with Nodes

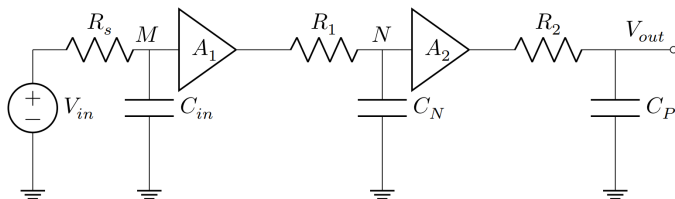

$$\frac{V_{out}}{V_{in}}(\omega) = A_1 A_2 \frac{1}{\left(1 + \frac{s}{\omega_M}\right) \left(1 + \frac{s}{\omega_N}\right) \left(1 + \frac{s}{\omega_P}\right)} \quad (8)$$

$$\omega_M = \frac{1}{R_S C_{in}} \quad (9) \quad \omega_N = \frac{1}{R_1 C_N} \quad (10) \quad \omega_P = \frac{1}{R_2 C_P} \quad (rad/s) \quad (11)$$

Example 2

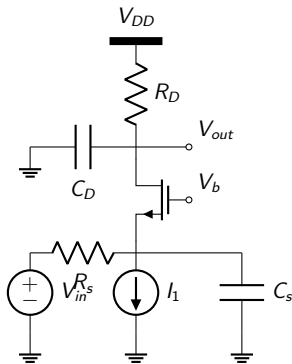


$$\frac{v_{out}}{v_{in}} = \frac{(g_{m1} + g_{mb1}) R_D}{1 + (g_{m1} + g_{mb1}) R_s} \frac{1}{\left(1 + \frac{s}{\omega_X}\right) \left(1 + \frac{s}{\omega_Y}\right)} \quad (12)$$

$$\omega_X = \frac{1}{\left(\frac{1}{g_{m1} + g_{mb1}} \parallel R_s\right) C_s} \text{ (rad/s)} \quad (13)$$

$$\omega_Y = \frac{1}{R_D C_D} \text{ (rad/s)} \quad (14)$$

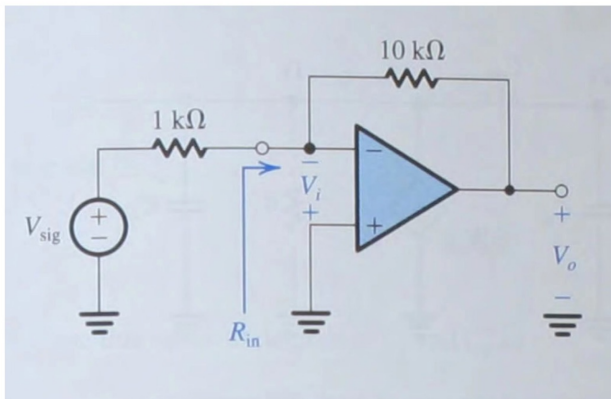Exercise 1

Assume the op amp to be ideal except for having a finite differential gain A and $V_{sig} = 1V$. Use Miller's theorem to find R_{in} , V_i , V_o for each of the following values of A : 10, 100, 1000 (without using knowledge of op-amp circuit analysis)




- 1 Miller Effect
- 2 First Order Systems
- 3 Nth Order Systems

$$H(s) = \frac{H^0 + H^1 \tau S}{1 + \tau S} \quad (15)$$

- ▶ Time constant: (1) For capacitor: $\tau = RC$; (2) For inductor: $\tau = \frac{L}{R}$
- ▶ To find the time constant, remove the cap/ind nulling all the sources and find the resistance.
- ▶ To find H^0 , use low frequency gain(cap cut off and ind shorted).
- ▶ To find H^1 , use high frequency gain(cap shorted and ind cut off).

Example 1

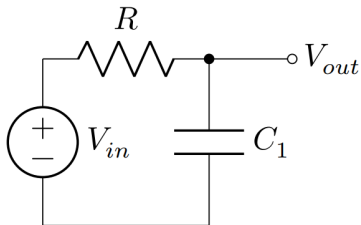



$$H^0 = 1 \quad (16)$$

$$\tau = RC_1 \quad (17)$$

$$H^1 = 0 \quad (18)$$

$$H(s) = \frac{1}{1 + RCS} \quad (19)$$

Example 2

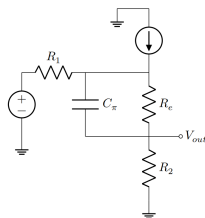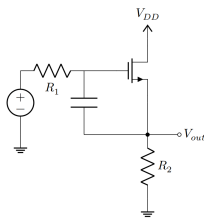

$$H^0 = \frac{R_2}{R_2 + R_e} \quad (20)$$

$$H^1 = \frac{R_2}{R_2 + R_1} \quad (21)$$

$$R = \frac{R_1 + R_2}{1 + g_m R_2} \quad (22)$$

Example 2


$$H(s) = \frac{R_2}{R_2 + R_e} \cdot \frac{1 + \frac{R_e + R_2}{R_1 + R_2} \cdot \frac{R_1 + R_2}{1 + g_m R_2} C_\pi S}{1 + R_\pi^0 C_\pi S} \quad (23)$$

$$= \frac{R_2}{R_2 + R_e} \cdot \frac{1 + R_e C_\pi S}{1 + R_\pi^0 C_\pi S} \quad (24)$$

Exercise 2

For the circuit shown below

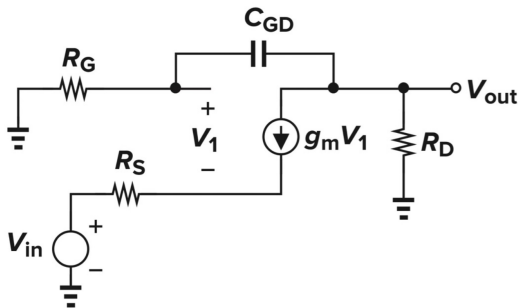- (a) Calculate H^0, H^1, τ
- (b) Write down the transfer function



- 1 Miller Effect
- 2 First Order Systems
- 3 Nth Order Systems

$$H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2} \quad (25)$$

$$b_1 = \sum_{i=1}^N \tau_i^0 \quad (26)$$


$$b_2 = \sum_i^{i < j < N} \sum_j^0 \tau_j^i \quad (28)$$

$$a_1 = \sum_{i=1}^N \tau_i^0 H^i \quad (27)$$

$$a_2 = \sum_{i < j < N} \sum_j \tau_i^0 \tau_j^i H^{ij} \quad (29)$$

- ▶ τ_j^i : the time constant of capacitor j when capacitor i is shorted
- ▶ τ_i^0 : cut off all other caps

Example

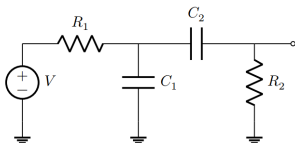

- ▶ $\tau_2^1 = R_2 C_2$
- ▶ $\tau_1^2 = (R_1 \parallel R_2) C_1$
- ▶ $\tau_1^0 \tau_2^1 = R_1 C_1 R_2 C_2 = \tau_2^0 \tau_1^2$
- ▶ $\tau_2^0 \tau_1^2 = (R_1 + R_2) C_2 \frac{R_1 R_2}{R_1 + R_2} C_1$
- ▶ $\tau_2^0 = (R_1 + R_2) C_2$
- ▶ $H^1 = 0$
- ▶ $H^2 = \frac{R_2}{R_2 + R_1}$
- ▶ $H^{12} = 0$

Example

- ▶ $H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2}$
- ▶ $b_2 = \tau_1^0 \tau_2^1 = \tau_2^0 \tau_1^2$
- ▶ $a_2 = \tau_1^0 \tau_2^1 H^{12} = \tau_2^0 \tau_1^2 H^{12}$
- ▶ $b_1 = \tau_1^0 + \tau_2^0$
- ▶ $a_1 = \tau_1^0 H^1 + \tau_2^0 H^2$

$$H(s) = \frac{R_2 C_2 S}{1 + (R_1 C_1 + R_1 C_2 + R_2 C_2) S + R_1 C_1 R_2 C_2 S^2} \quad (30)$$

If you couldn't understand first order systems and n-th order systems clearly, just treat capacitor as $\frac{1}{sC}$ and inductor as sL , then use KCL and KVL!

Good luck in final exam!