
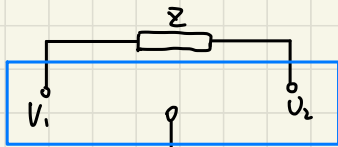


Miller Effect:

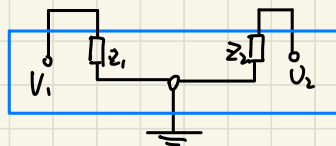


论已经 $A = \frac{V_2}{V_1}$

\Leftrightarrow




$Z_1 = \frac{Z}{1-A}, Z_2 = \frac{Z}{1+A}$

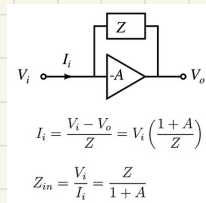

Example 1




Association of Poles with Nodes

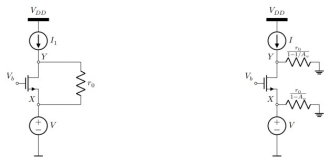

$A_v = \frac{Y}{X} = 1 + (g_{m1} + g_{mb1}) r_{o1}$ (4)

$Z_1 = \frac{r_{o1}}{1 - [1 + (g_{m1} + g_{mb1}) r_{o1}]} = \frac{-1}{g_{m1} + g_{mb1}}$ (5)

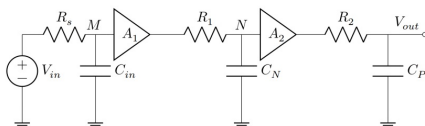$R_{in} = \frac{-1}{g_{m1} + g_{mb1}} \parallel \frac{1}{g_{m1} + g_{mb1}} = \infty$ (6)



$\frac{v_{out}}{V_{in}}(\omega) = A_1 A_2 \frac{1}{\left(1 + \frac{s}{\omega_M}\right) \left(1 + \frac{s}{\omega_N}\right) \left(1 + \frac{s}{\omega_P}\right)}$ (8)


$\omega_M = \frac{1}{R_S C_{in}}$ (9) $\omega_N = \frac{1}{R_1 C_N}$ (10) $\omega_P = \frac{1}{R_2 C_P}$ (rad/s) (11)



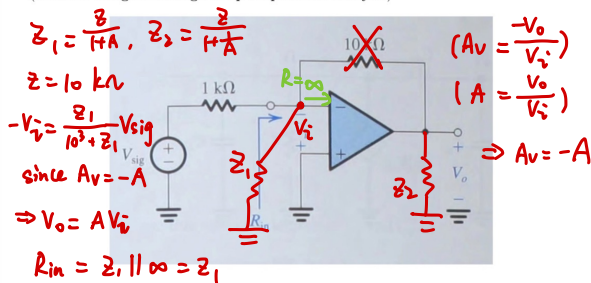Exercise 1






Assume the op amp to be ideal except for having a finite differential gain A and $V_{sat} = 1V$. Use Miller's theorem to find R_{in}, V_i, V_o for each of the following values of A : 10, 100, 1000 (without using knowledge of op-amp circuit analysis)





$$H(s) = \frac{H^0 + H^1 s}{1 + \tau s} \quad (15)$$

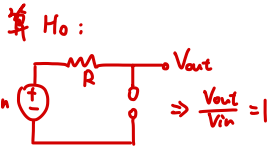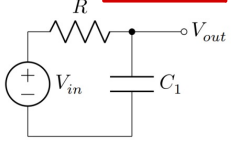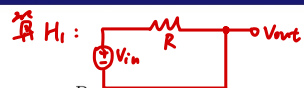- Time constant: (1) For capacitor: $\tau = RC$; (2) For inductor: $\tau = \frac{L}{R}$
- To find the time constant, remove the cap/ind nulling all the sources and find the resistance.
- To find H^0 , use low frequency gain(cap cut off and ind shorted).
- To find H^1 , use high frequency gain(cap shorted and ind cut off).




$$V_{out} = 0 \Rightarrow \frac{V_{out}}{V_{in}} = 0$$

$$H^0 = 1 \quad (16)$$

$$\tau = RC_1 \quad (17)$$

$$H^1 = 0 \quad (18)$$

$$H(s) = \frac{1}{1 + RCS} \quad (19)$$

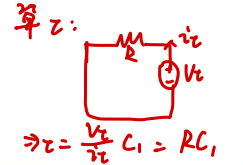

Exercise 2



Nth Order Systems



For the circuit shown below

- (a) Calculate H^0, H^1, τ
- (b) Write down the transfer function

① H^0 (Cap 断)


$$V_{in} + R_S g_m V_1 = V_{out}$$
$$V_{out} = -R_D g_m V_1$$

$$\Rightarrow H^0 = \frac{g_m R_D}{R_S g_m + 1}$$

② H^1 (Cap 短)

$$V_{in} + R_S g_m V_1 = V_{out} - V_1$$
$$\frac{V_{out}}{R_D} + \frac{V_{out}}{R_D + g_m V_1} = 0$$

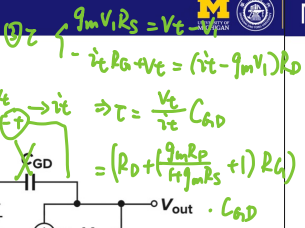
$$\Rightarrow H^1 = \frac{1}{1 + (R_S + \frac{1}{g_m})(R_D + R_S)}$$



Example



Example

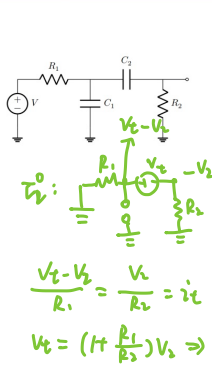

- $\tau_1^2 = R_2 C_2$
- $\tau_1^2 = (R_1 \parallel R_2) C_1$
- $\tau_1^0 \tau_1^2 = R_1 C_1 R_2 C_2 = \tau_2^0 \tau_1^2$
- $\tau_2^0 \tau_1^2 = (R_1 + R_2) C_2 \frac{R_1 R_2}{R_1 + R_2} C_1$
- $\tau_2^0 = (R_1 + R_2) C_2$
- $H^1 = 0$
- $H^2 = \frac{R_2}{R_2 + R_1}$
- $H^{12} = 0$

H^1 : 断 C_2 , 短 C_1
 H^2 : 断 C_1 , 短 C_2
 H^{12} : 都断

- $H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2}$
- $b_2 = \tau_1^0 \tau_2^0 = \tau_2^0 \tau_1^2$
- $a_2 = \tau_1^0 \tau_2^1 H^{12} = \tau_2^0 \tau_1^2 H^{12}$
- $b_1 = \tau_1^0 + \tau_2^0$
- $a_1 = \tau_1^0 H^1 + \tau_2^0 H^2$

> 二阶的公式

$$H(s) = \frac{R_2 C_2 S}{1 + (R_1 C_1 + R_1 C_2 + R_2 C_2) S + R_1 C_1 R_2 C_2 S^2} \quad (30)$$