



Lecture 19

EECS 311 Analog Circuits


Xuyang Lu
2023 Fall



上海交通大學
SHANGHAI JIAO TONG UNIVERSITY



Representation of Poles and Zeros

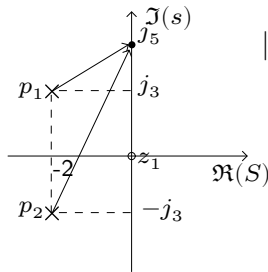

$$\begin{aligned} |H(s)| &= K \frac{\sqrt{(0-5)^2}}{\sqrt{(0-(-2))^2 + (5-3)^2} \sqrt{(0+2)^2 + (5+3)^2}} \\ &= K \frac{5}{4\sqrt{34}} \end{aligned} \quad (1)$$

$$\begin{aligned}\angle H(s) &= \tan^{-1}(5/0) - \tan^{-1}(2/2) - \tan^{-1}(8/2) \\ &= -31^\circ\end{aligned}\tag{2}$$

Frequency Response



y substituting $j\omega$ for s



$$H(j\omega) = K \frac{(j\omega - z_1)(j\omega - z_2) \dots (j\omega - z_{m-1})(j\omega - z_m)}{(j\omega - p_1)(j\omega - p_2) \dots (j\omega - p_{n-1})(j\omega - p_n)} \quad (3)$$

$$|j\omega - p_i| = \sqrt{\sigma_i^2 + (\omega - \omega_i)^2} \quad (4)$$



$$\angle(s - p_i) = \tan^{-1} \left(\frac{\omega - \omega_i}{-\sigma_i} \right) \quad (5)$$





Frequency Response Example

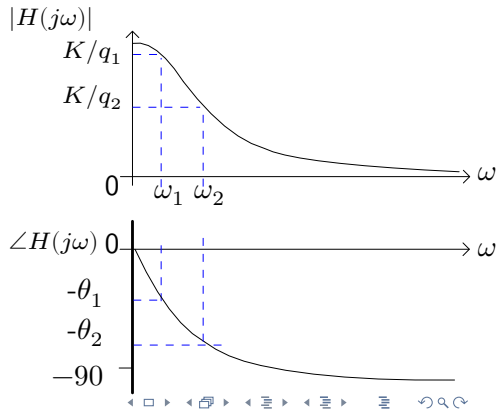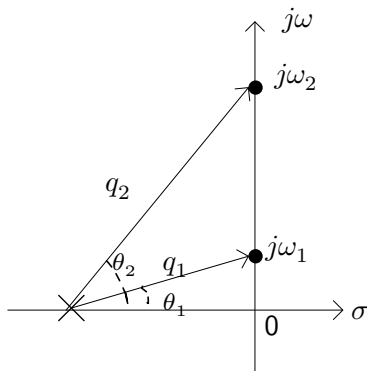

Frequency Response Example

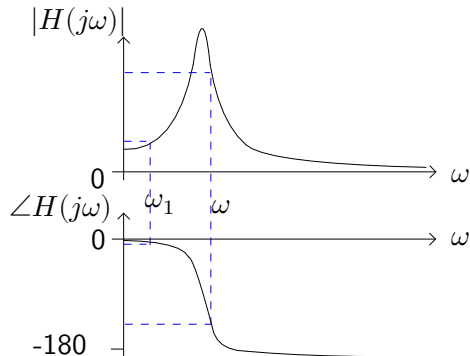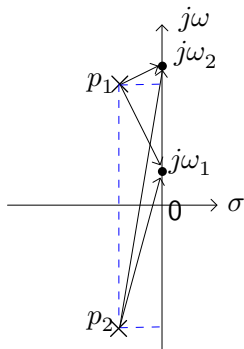

Frequency Response Example

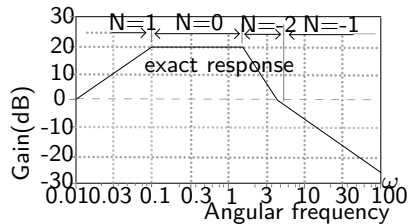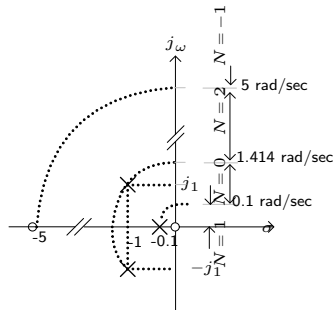

- Each pole or zero contributes a change in the slope of the asymptotic plot of ± 20 dB/decade above its break frequency. A complex conjugate pole or zero pair gives a total change in the slope of ± 40 dB/decade.

Constructing Magnitude Bode Plot




- For lefthand plane
 - Slope changes by -20 dB/decade
 - Phase decreases by 90°
- Zero
 - Slope changes by 20 dB/decade
 - Phase increase by 90°

Constructing Magnitude Bode Plot



- $H(s) = \frac{1}{s+1} \Rightarrow H(j\omega) = \frac{1}{j\omega+1}$
- $\angle H(j\omega) = -\tan^{-1}(\omega)$
- $\angle H(j\omega) = \begin{cases} 0^\circ & \omega \ll 1 \\ -90^\circ & \omega \gg 1 \end{cases}$

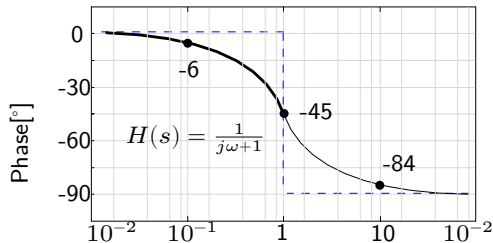The behavior for a zero is similar. The phase increases by 90° and passes through the midpoint of 45° at the break point



Zero @ Origin



- $H(s) = s$
- $|H(j\omega)| = \omega \Rightarrow \omega = 1 \Rightarrow \log |H(j\omega)| = 0dB$
- Slope 20 dB/decade

Code Plot Example




- $H(s) = \frac{s}{(1 + \frac{s}{10})(1 + \frac{s}{10^4})}$

Zero @ 0

Pole @ -10

Pole @ -10^4


Finite Op-amp Bandwidth

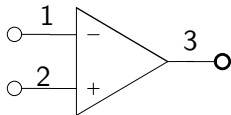

- Remember for a RC circuit
- $V_{\text{out}} = \frac{1}{1+j\omega CR} V_{\text{in}}$
- $\omega_p = -\frac{1}{RC} \Rightarrow$
- $Av(\omega) = \frac{1}{1+j\omega/\omega_p}$

- Ideal : Gain is Infinite
- Gain is finite, bandwidth infinite
- Gain is finite, bandwidth finite
- Assume single pole amplifier
- A_0 is the *DC* gain,
- $A(j\omega) = \frac{A_0}{1+j\omega/\omega_p}$


Finite Op-amp Bandwidth

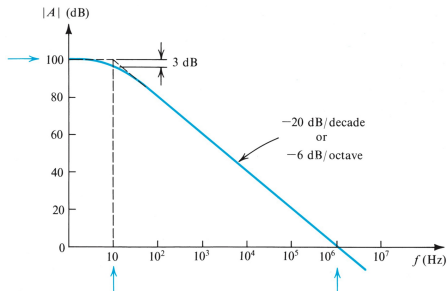

Typical op-amps have every low 3dB bandwidth

$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_p} \quad (11)$$

Finite Op-amp Bandwidth

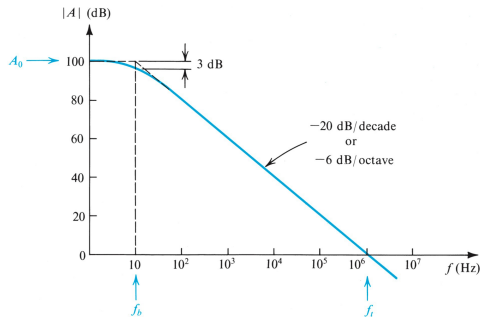


- ω_t is ω Where $|A(j\omega)| = 1$
- $A(j\omega) = \frac{A_0}{1+j\omega/\omega_b}$
- $1 = \frac{A_0}{\omega_T/\omega_b} \Rightarrow \omega_T = A_0\omega_b$
- $\omega_T = A_0\omega_b$
- Gain bandwidth product (GBW) important parameter

Finite Op-amp Bandwidth



- ω_t is ω Where $|A(j\omega)| = 1$
- $A(j\omega) = \frac{A_0}{1+j\omega/\omega_b}$
- $1 = \frac{A_0}{\omega_T/\omega_b} \Rightarrow \omega_T = A_0\omega_b$
- $\omega_T = A_0\omega_b$
- Gain bandwidth product (GBW) important parameter

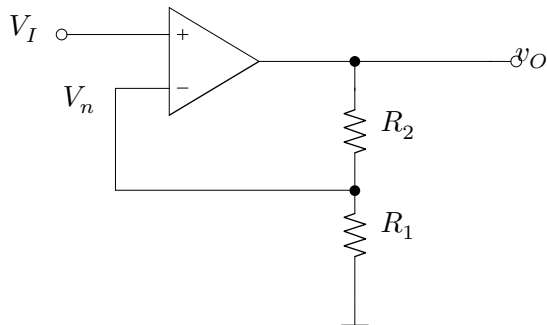




Non-Inverting Amplifier

$$v_O = \frac{A_0}{1 - \frac{s}{\omega_p}} (v_I - \beta v_O) \quad (12)$$

$$v_O \left(1 - \frac{s}{\omega_p}\right) + A_0 \beta v_O = A_0 v_I \quad (13)$$

$$\frac{v_O}{v_I} = \frac{A_0}{1 + \beta A_0 - s/\omega_p} = \frac{A_0}{1 + \beta A_0} \frac{1}{1 - \frac{s}{\omega_p(1+\beta A_0)}} \quad (14)$$


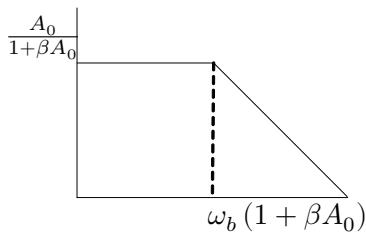
- This tells me the bandwidth of a noninverting amplifier is $\omega_p (1 + \beta A_0)$



Parasitic Capacitance





NMOS

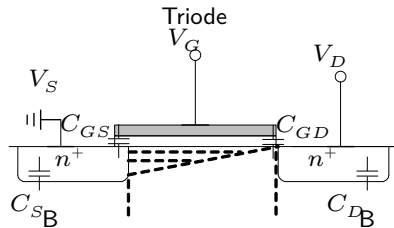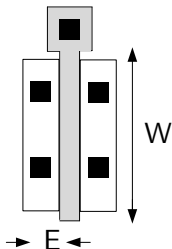

Parasitic Capacitance





NMOS

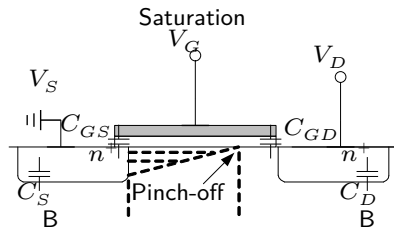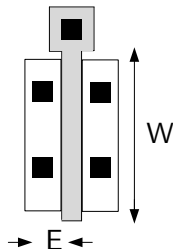



Parasitic Capacitance

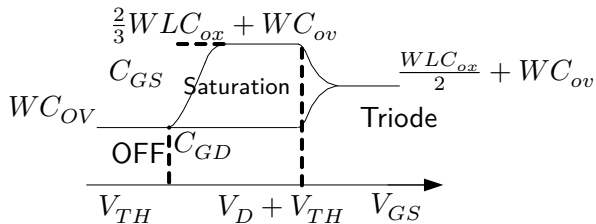
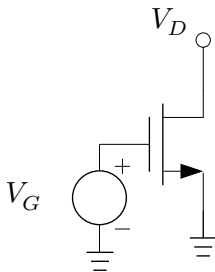


Parasitic Capacitance



Calculate C_{SB} and C_{DB} of the two structures below.

NMOS

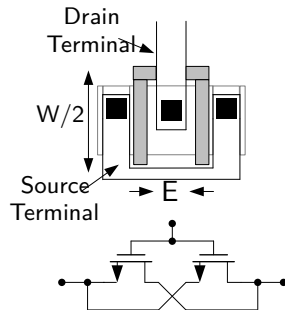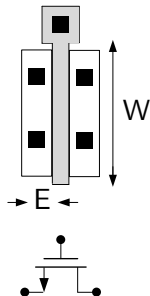

Parasitic Capacitance



Solution:

$$\text{Left: } C_{DB} = \frac{W}{2}EC_j + 2\left(\frac{W}{2} + E\right)C_{jsw} \quad (23)$$


$$\text{Right: } C_{DB} = C_{SB} = WEC_j + 2(W + E)C_{jsw} \quad (24)$$

$$\begin{aligned}
C_{SB} &= 2 \left[\frac{W}{2} EC_j + 2 \left(\frac{W}{2} + E \right) C_{jsw} \right] \\
&= WEC_j + 2(W + 2E)C_{jsw}
\end{aligned} \tag{25}$$

- Drain junction capacitance is greatly reduced



Complete Small-Signal Model

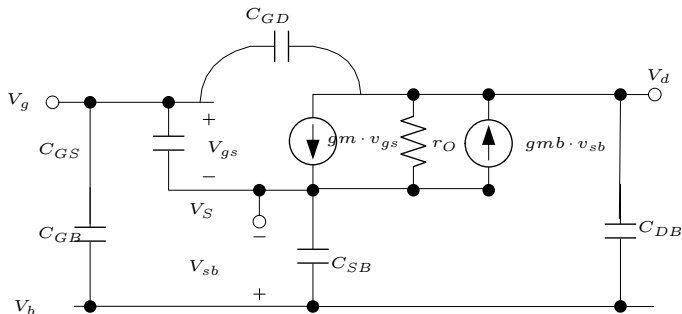

Only when MOSFET is off should we need to consider C_{GB} , which includes the gate oxide capacitance and the depletion region capacitance in series.

Spice Model



NMOS Model

LEVEL = 1

$$\text{NSUB} = 9e + 14$$
$$\text{TOX} = 9e - 9$$
$$\text{MJ} = 0.45$$

PMOS Model

LEVEL = 1

$$\text{NSUB} = 5e + 14$$
$$\text{TOX} = 9e - 9$$
$$\text{MJ} = 0.5$$
 $V_{T0} = 0.7$
$$\text{LD} = 0.08\text{e} - 6$$

PB = 0.9

$$\text{MJSW} = 0.2$$
$$V_{T0} = -0.8$$
$$\text{LD} = 0.09\text{e} - 6$$

PB = 0.9

$$\text{MJSW} = 0.3$$

GAMMA = 0.45

$$UO = 350$$
$$\text{CJ} = 0.56e - 3$$
$$\text{CGDO} = 0.4e-9$$

$\text{GAMMA} = 0.4$

$$UO = 100$$
$$\text{CJ} = 0.94e - 3$$
$$\text{CGDO} = 0.3e - 9$$
$$\text{PHI} = 0.9$$

LAMBDA = 0.1

$$\text{CJSW} = 0.35\text{e} - 11$$
$$JS = 1.0e - 8$$
$$\text{PHI} = 0.8$$

LAMBDA = 0.2

$$\text{CJSW} = 0.32\text{e} - 11$$
$$\text{JS} = 0.5e - 8$$




First Order Systems

- $H_i(s) = \frac{a_0 + \alpha_1^i C_i s}{1 + \beta_1^i C_i s}$ goes to $\inf H(s) = \frac{\alpha_1}{\beta_1}$

$$H(s) = \frac{H^0 + H^1 \tau s}{1 + \tau s} \quad (26)$$

- If it is an inductor, $\tau = \frac{L_1}{R_0}$
- To find the time constant, remove the cap/ind nulling all the sources, find the resistance.
- To find transfer constant H_0 , it is just the low frequency gain.
- To find the transfer constant H_1 , we look into high frequency response, so the cap shall be shorted. For inductor it is the opposite.

First Order Systems

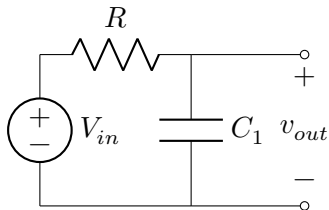

$$H^0 = 1 \quad (27)$$


$$\tau = RC_1 \quad (28)$$

$$H^1 = 0 \quad (29)$$


$$H(s) = \frac{1}{1 + RCS} \quad (30)$$



First Order Systems

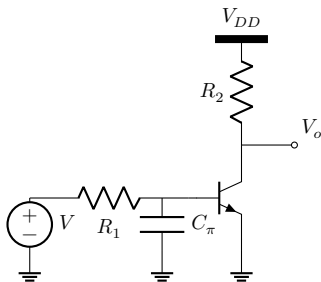

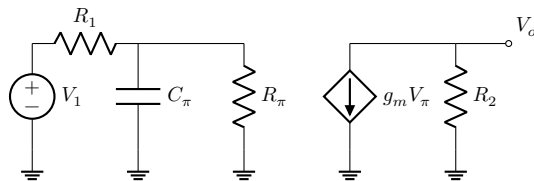
$$H^0 = -\frac{r_\pi}{R_1 + r_\pi} g_m R_2 \quad (31)$$



$$H^\pi = 0 \quad (32)$$




First Order Systems

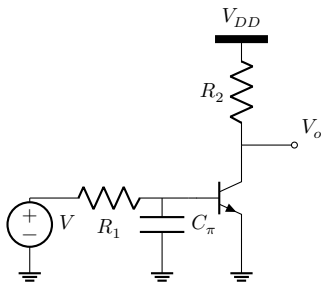



$$\tau = (R_1 \parallel r_\pi) C_\pi \quad (33)$$

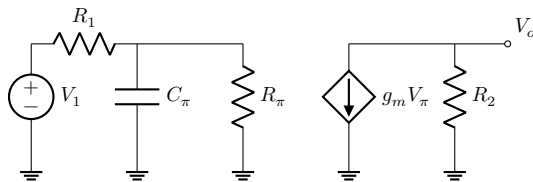If there is a zero in the system, then we can test it with a shorted cap/ open ind and see if the output still have some value.



$$H(S) = \frac{H^0}{1 + \tau S} \quad (34)$$


First Order Systems

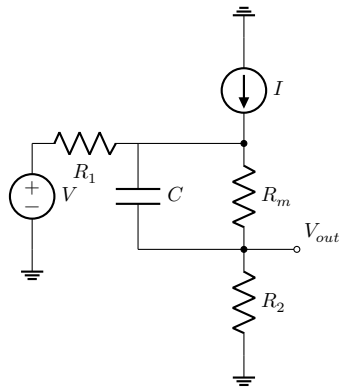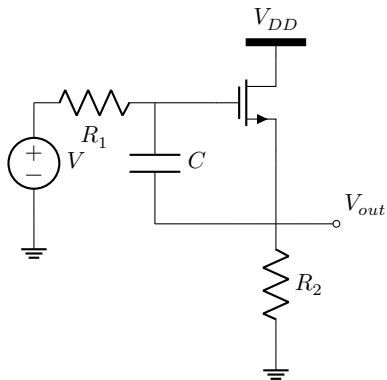

First Order Systems



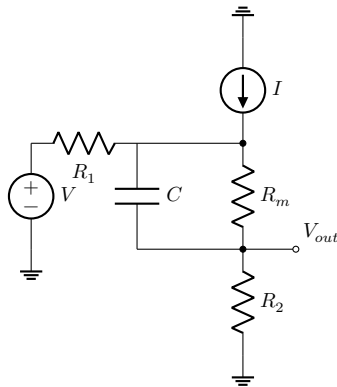- Low frequency, $V_x = V_{in}$
- V_{out} is voltage divider,
- $H^0 = \frac{R_2}{R_2 + r_m}$ (assume it's a bjt)
- $H^1 = \frac{R_2}{R_2 + r_1}$
- $R_2 (g_m v_x - i_x) + v_x = R_1 i_x$
- $R = \frac{R_1 + R_2}{1 + g_m R_2}$
- You can imagine the existence of a zero and a pole.



First Order Systems





transistor model statement for the 2N696

```
.model Q2N696 NPN (Is=14.34f Xti=3 Eg=1.11 Vaf=74.03 Bf=65.62 Ne=1.208
Ise=19.48f Ikf=.2385 Xtb=1.5 Br=9.715 Nc=2 Isc=0 Ikr=0 Rc=1 Cjc=9.393p
Mjc=.3416 Vjc=.75 Fc=.5 Cje=22.01p Mje=.377 Vje=.75 Tr=58.98n Tf=408.8p
Itf=.6 Vtf=1.7 Xtf=3 Rb=10)
```




First Order Systems
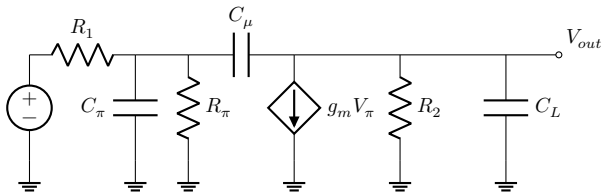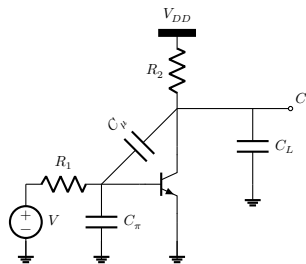
```
.model NPN (Cje = 20 fF, Cjc = 20 fF, β0 = 100, Cjs = 50 fF, τF = 2 ps,
CL = 150 fF) cje Zero bias B-E depletion capacitance
```





First Order Systems

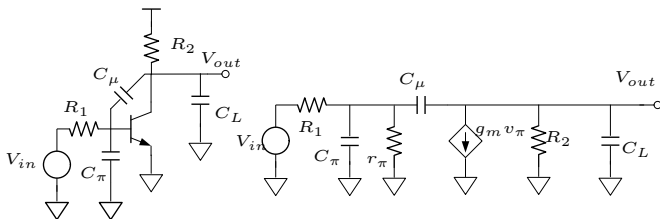


We can use those parameters to determine small signal parameters. a collector current of 1mA which give you a $G_m = 40mS$ $\beta_0 = 100$

- $C_\pi = C_{je} + C_b = 100\text{fF}$
- $C_L = C_{\text{out}} + C_{js} = 200\text{fF}$
- $C_b = g_m \tau_F = 80\text{fF}$
- $R_1 = 1\text{K}\Omega$
- $R_2 = 2\text{K}\Omega$




First Order Systems

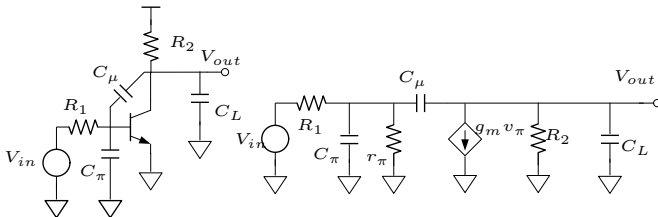

- $b_1 = \sum_i \tau_i^0 = \tau_\pi^0 + \tau_\mu^0 + \tau_L^0$
- $H^0 = -57$
- $\tau_\pi^0 \approx 70\text{ps}$ $\tau_\mu^0 \approx 1200\text{ps}$ $\tau_L^0 = 400\text{ps}$
- $\omega_h \approx 1/b_1 \approx 2\pi \cdot 95\text{MHz}$
- This allows you to determine the lowest operating frequency, and also the contribution of each nodes in the circuit.

First Order Systems

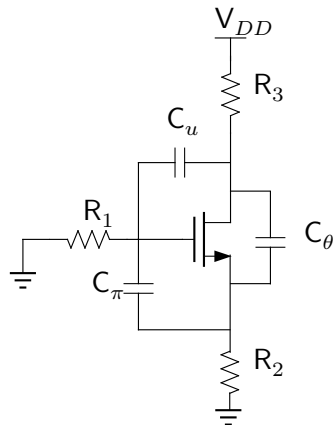- $R_{\pi}^0 = r_{\pi} \parallel \frac{R_1 + R_2}{1 + g_m R_2}$
- $R_{\mu}^0 = R_{\text{left}} + R_{\text{right}} + G_m R_{\text{left}} R_{\text{right}}$
- $R_{\text{left}} \equiv R_B \parallel [r_{\pi} + (1 + \beta) R_E]$
- $R_{\text{right}} \equiv R_C$
- $G_m = \frac{g_m}{1 + g_m R_2}$
- $R_{\theta}^0 \approx \frac{R_2 + R_3}{1 + g_m R_2}$
- $b_1 = \sum_{i=1}^N \tau_i^0$



Further discussion on P and Z



- $H(s) = \frac{H^0 + H^1 \tau s}{1 + \tau s} = H^0 \frac{1 + \frac{H^1}{H^0} \tau s}{1 + \tau s}$
- $P = -\frac{1}{\tau}$
- $Z = -\frac{1}{H^1} = \frac{H^0}{H^1} \tau \left(-\frac{1}{\tau}\right)$
- $Z = \frac{H^0}{H^1} P$


Further discussion on P and Z

$$H(s) = \frac{H^0 + H^1 \tau S}{1 + \tau S} = H^0 \frac{1}{1 + \tau S} + H^1 \frac{\tau S}{1 + \tau S} \quad (35)$$

Low path filter


High path filter
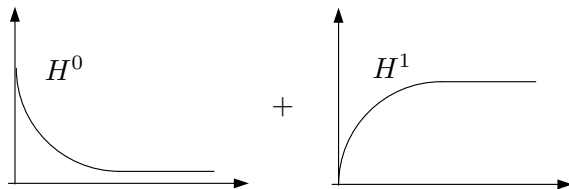
$$s(t) = H^0 (1 - e^{-t/\tau}) u(t) + H^1 e^{-t/\tau} u(t) \quad (36)$$



The final waveform also tells you the existence of poles and zeros.

Nth order system

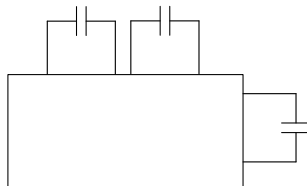

$$H(s) = \frac{a_0 + a_1 S + a_2 S^2 + \dots}{1 + b_1 S + b_2 S^2 + \dots} \quad (37)$$

- Only the caps and inductors produces S.
- To get a_1 we have to have a cap (or inductor)



Nth order system

- We can also infer that the s^2 term comes from two capacitors.

- $$H(s) = \frac{a_0 + \left(\sum_{i=1}^N \alpha_1^i C_i\right)s + \left(\sum_{1 \leq i < j \leq N} \alpha_j^{ij} C_i C_j\right)s^2 + \dots}{1 + \left(\sum_{i=1}^N \beta_1^i C_i\right)s + \left(\sum_{1 \leq i < j \leq N} \beta_2^{ij} C_i C_j\right)s^2 + \dots}$$

- If we set all c's except c_i as zeros

- $$H_i(s) = \frac{a_0 + \alpha_1^i C_i s}{1 + \beta_1^i C_i s}$$

- $$\tau_i^0 = R_i^0 C_i$$

- $$\beta_1^i = R_i^0$$


- $$b_1 = \sum_{i=1}^N \tau_i^0$$



Nth order system

- $b_1 = \sum_{i=1}^N \tau_i^0$
- coefficient b_1 is the sum of all zero valued time constant.
- $a_1 = \sum_{i=1}^N \tau_i^0 H^i$
- This allows us to find out the dominant time constant.


N^{th} order system

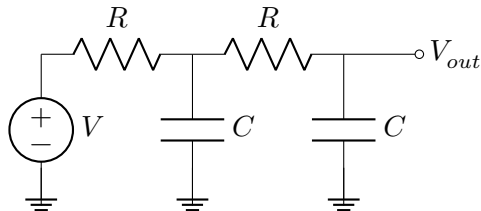

It is a two cap system, therefore the number of poles are two.

It is a system with an infinite response of zero if we short both capacitors, so there is no zeros.

Nth order system

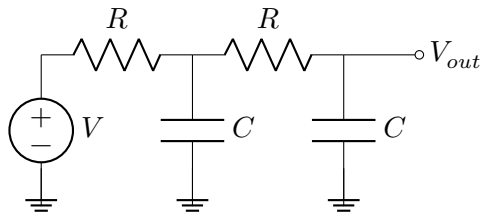

- $H(S) = \frac{1}{1+3RCS+(RC)^2S^2}$
- $b_1 = \sum_{i=1}^N \tau_i^0 = \tau_1^0 + \tau_2^0$
- $\tau_1^0 = RC$
- $\tau_2^0 = 2RC$
- $b_1 = 3R_c$



Nth order system

$$H(S) = \frac{1}{1 + 3RCS + (RC)^2 S^2} \quad (38)$$

- If the impedance seen by one cap does not change as we open or short the other cap, we say that the two-time constant are uncoupled to each other, and the expression can be written as

$$H(s) = \frac{H^0}{(1 + \tau_1 S)(1 + \tau_2 S)} \quad (39)$$

- We now have the $3RC$ term. The question is whether it is true in this case to determine $(RC)^2 S^2$

$$H(s) = \frac{1}{1 + 3RCS + (RC)^2 S^2} \quad (40)$$

Nth order system



We now know how to calculate a_1 , b_1 , and a_0 .

$$H(s) = \frac{a_0 + \left(\sum_{i=1}^N \alpha_1^i C_i\right) s + \left(\sum_i^{1 \leq i < j \leq N} \alpha_j^{ij} C_i C_j\right) s^2 + \dots}{1 + \left(\sum_{i=1}^N \beta_1^i C_i\right) s + \left(\sum_i^{1 \leq i < j \leq N} \sum_j \beta_2^{ij} C_i C_j\right) s^2 + \dots} \quad (42)$$

A_O is the zero frequency response. B_1 is the summation of time constant A_1 can be obtained from infinite time response.

Nth order system



$$b_2 = \sum_i^{i < j < N} \sum_j^0 \tau_j^i \quad (43)$$

- That means you don't repeat τ_{12} and τ_{21}
- τ_j^i means the time constant of element j when element I is infinite frequency

$$a_2 = \sum_{i < j < N} \sum_j \tau_i^0 \tau_j^i H^{ij} \quad (44)$$

- We can expect b_n is a multiple summation of the product of many time constants

Nth order system



$$b_n = \sum_i^{1 \leq i < j < k} \sum_j \sum_{k \dots}^{\dots} \dots \tau_i^0 \tau_j^i \tau_k^{ij} \dots \quad (45)$$

$$a_n = \sum_i^{1 \leq i < j < k \dots N} \sum_j \dots \tau_i^0 \tau_j^i \tau_k^{ij} \dots H^{ijk \dots} \quad (46)$$


I will skip the derivations and show you how to use it.

Nth order system



- $H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2}$
- $b_2 = \tau_1^0 \tau_2^1 = \tau_2^0 \tau_1^2$
- $a_2 = \tau_1^0 \tau_2^1 H^{12} = \tau_2^0 \tau_1^2 H^{12}$
- $b_1 = \tau_1^0 + \tau_2^0$
- $a_1 = \tau_1^0 H^1 + \tau_2^0 H^2$

Nth order system

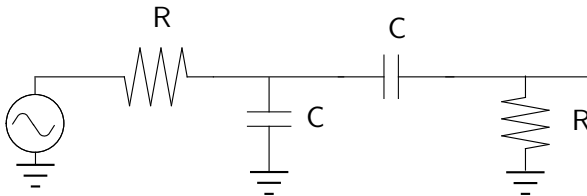


- Two pole and one zero
- How do we test this?
- $H^0 = 0$

$$\tau_1^0 = R_1 C_1 \quad (47)$$

$$\tau_2^0 = (R_1 + R_2) C_2 \quad (48)$$

Nth order system

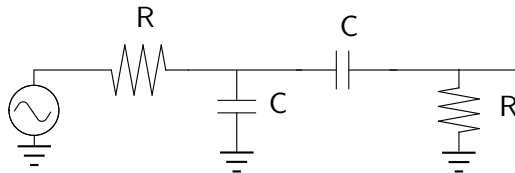

$$\tau_2^1 = R_2 C_L \quad (49)$$

$$\tau_1^2 = (R_1 \parallel R_2) C_1 \quad (50)$$


$$H^1 = 0 \quad (53)$$

$$\tau_1^0 \tau_2^1 = R_1 C_1 R_2 C_2 = \tau_2^0 \tau_1^2 \quad (51)$$

$$H^2 = \frac{R_2}{R_2 + R_1} \quad (54)$$

Nth order system

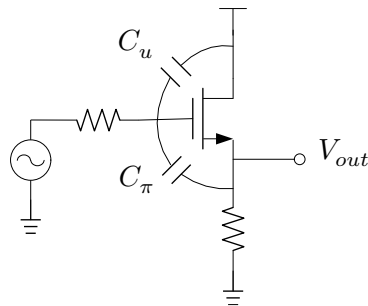- Two poles and one zero
- $H^0 = \frac{R_2}{R_2 + r_m}$
- $\tau_\pi^0 = C_\pi \frac{R_1 + R_2}{1 + g_m R_2}$
- $\tau_\mu^0 = C_\mu R_1$
- $\tau_\mu^\pi = C_\mu (R_1 \parallel R_2)$
- $H^\mu = 0$
- $H^\pi = \frac{R_2}{R_1 + R_2}$
- $H^{\mu\pi} = 0$




Nth order system

- Now we can write out the transfer function. If we assume that $R_2 \gg R_1$
- And $R_2 \gg R_m$

$$H^0 = \frac{R_2}{R_2 + r_m} \quad (57)$$

$$\tau_\pi^0 = C_\pi \frac{R_1 + R_2}{1 + g_m R_2} = r_m C_\pi \quad (58)$$

$$\tau_\mu^0 = C_\mu R_1 \quad (59)$$

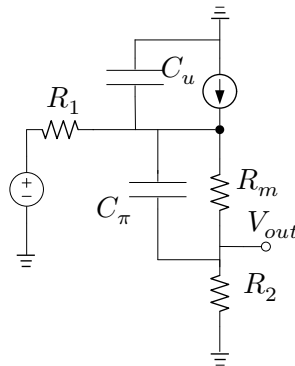

Nth order system




$$\tau_{\mu}^{\pi} = C_{\mu}(R_1 \parallel R_2) = C_{\mu}R_1 \quad (60)$$

$$H^\mu = 0 \quad (61)$$

$$H^\pi = \frac{R_2}{R_1 + R_2} \quad (62)$$

$$\tau_\pi^0 \tau_\mu^\pi = r_m R_1 C_\pi C_\mu \quad (63)$$
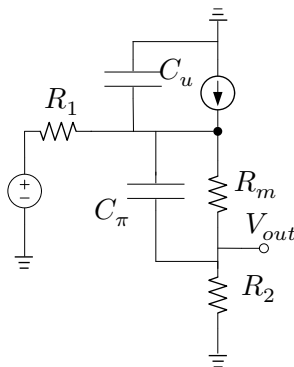
$$H^\pi \tau_\pi^0 = r_m C_\pi \frac{R_2}{r_m + R_2} = H^0 r_m C_\pi \quad (64)$$



Nth order system



- $H(S) = H^0 \frac{1+r_m C_\pi S}{1+(r_m C_\pi + R_1 C_\mu)S + r_m C_\pi R_1 C_\mu S^2} = \frac{H^0}{1+R_1 C_\mu S}$
- This essentially tells us the dominate pole is the C_μ , because C_π shares current between the capacitor and the resistor, so that it tells us to improve the bandwidth of operation, we need to use an inductor or some topology to cancel the effect of C_μ



- The whole system can be expressed as the product of a high pass and a low pass transfer function.
- If I'm designing an analog circuit, I can use transfer function to estimate bandwidth, assuming I care about the lowpass one.
- For low frequency system, in many cases we can assume a zeroless system.
- For example, in common-source stage and the source-follower stage, the zero's frequencies are comparable to the cut-off frequency of the transistor itself

