

VE311

Electronic Circuits

RC Final

Yucheng Huang

University of Michigan
Shanghai Jiao Tong University
Joint Institute

July 28, 2023

1 MOSFET Single Stage Amplifier

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier



2 MOSFET Differential Pair Amplifier

3 Current Mirror

- Current Mirror

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier
- 2 MOSFET Differential Pair Amplifier
- 3 Current Mirror
 - Current Mirror

CS with Resistive Load

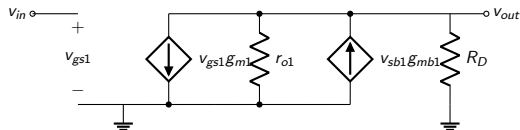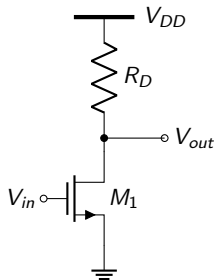


If no channel-length and body effect:

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1} R_D \quad (1)$$

No body effect:

$$A_v = -g_{m1} (R_D \parallel r_{o1}) \quad (2)$$

CS with Diode-connected Load

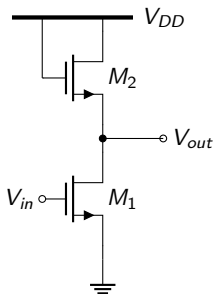


NMOS:

$$A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta} \quad \eta = g_{mb2}/g_{m2} \quad (3)$$


PMOS:

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}} \quad (4)$$

CS with Current Source Load

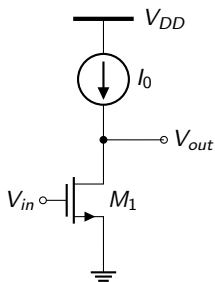



or

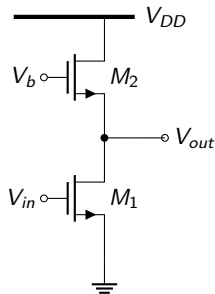

$$A_v = -g_{m1}(r_{o2} \parallel r_{o1}) \quad (5)$$

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier
- 2 MOSFET Differential Pair Amplifier
- 3 Current Mirror
 - Current Mirror

Source Follower

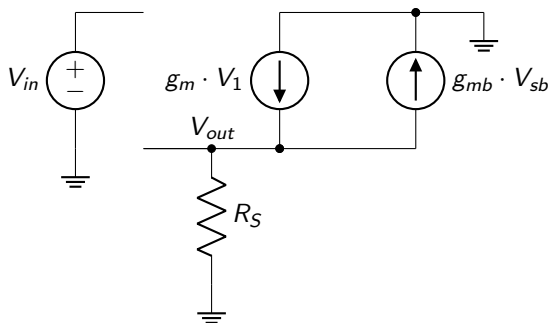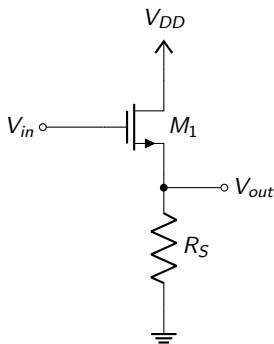

$$A_v = \frac{g_m R_S}{1 + g_m R_S (1 + \eta)} = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S} \approx \frac{1}{1 + \eta} \quad (6)$$

Example 3

In the source follower with current source load, the current source is ideal. Find the output impedance for the amplifier when $I_0 = 0.01$ and $0.1mA$ respectively. (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,


$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$


Example 1

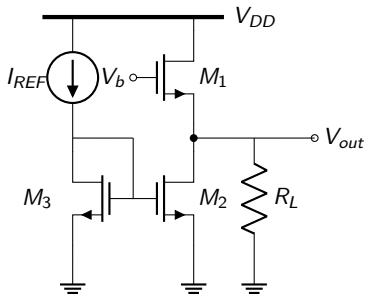

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier**
- Cascode Amplifier

- Current Mirror

Common Gate

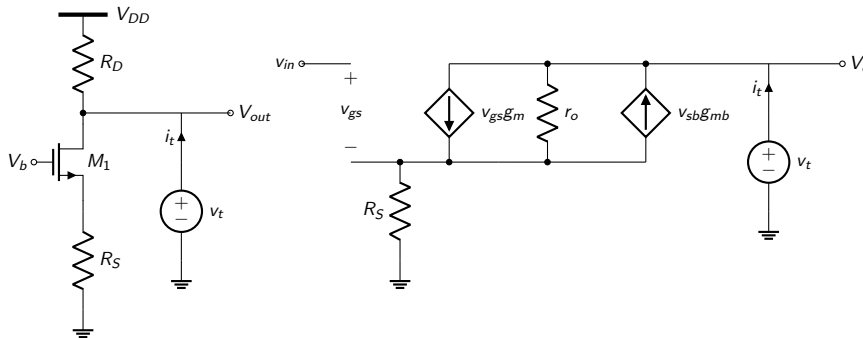


$$R_{in} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o} \begin{cases} \text{If } R_D = 0 & R_{in} = r_o \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \\ \text{If } R_D = \infty & R_{in} = \infty \end{cases} \quad (7)$$

$$R_{out} = [R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S] \parallel R_D \quad (8)$$

- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier**

- Current Mirror


Cascode

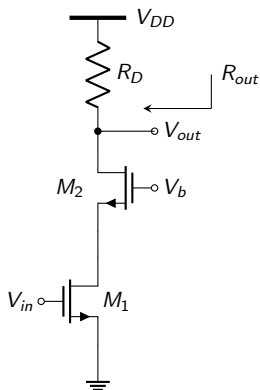

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (9)$$

$$R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \parallel R_D \quad (10)$$

Cascode

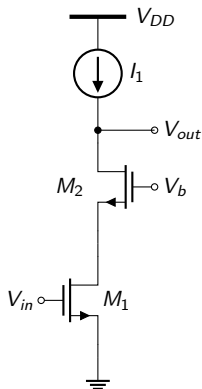


$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \quad (11)$$

$$R_{out} = r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1} \quad (12)$$

$$A_v = G_m R_{out} \quad (13)$$

Cascode

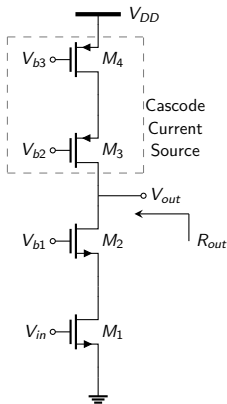

$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + (r_{o2} \parallel \frac{1}{g_{m2}g_{mb2}})} \quad (14)$$

$$R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}] \parallel [r_{o3} + r_{o4} + (g_{m3} + g_{mb3})r_{o3}r_{o4}] \quad (15)$$

$$A_v = G_m R_{out} \quad (16)$$

Example 5

In the cascode amplifier , what is the gain when $I_{REF} = 0.01mA$ and $0.1mA$ respectively? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,

$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

1 MOSFET Single Stage Amplifier


- Common Source Amplifier
- Common Drain Amplifier (Source Follower)
- Common Gate Amplifier
- Cascode Amplifier

2 MOSFET Differential Pair Amplifier

3 Current Mirror

- Current Mirror

Differential Pair

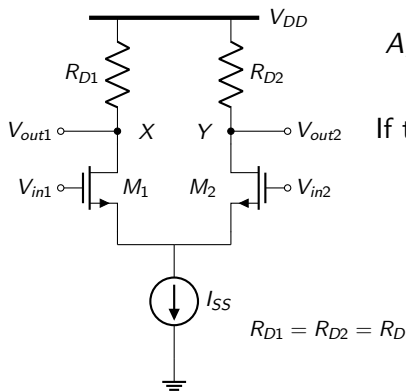


$$A_{DM} = \frac{V_{out1} - V_{out2}}{v_d} = -g_m(R_D \parallel r_o) \quad (17)$$

If the circuit is fully symmetric,

$$A_{CM-DM} = \frac{V_{out1} - V_{out2}}{v_{in,CM}} = 0 \quad (18)$$


$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \infty \quad (19)$$

Differential Pair with MOS Loads

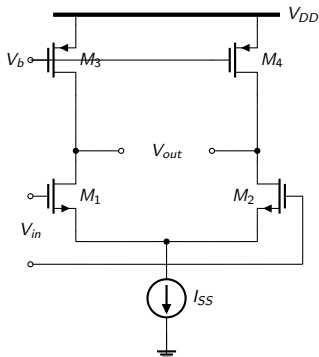

$$A_{DM} = -g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \quad (20)$$

Differential Pair with Cascode Loads

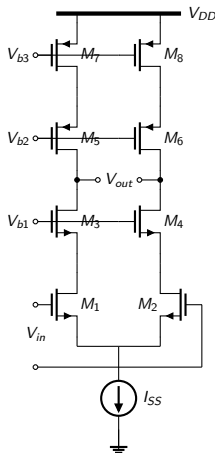

$$A_{DM} \cong -g_{m1,2}[(g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2} \parallel (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}] \quad (21)$$

Example 2

In the differential pair , what is the gain when $I_{SS} = 0.02mA$ and $0.2mA$ respectively? (Neglect body effect)

Parameter for NMOS: $V_{THN} = 0.7V$,


$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$




All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

Example 2

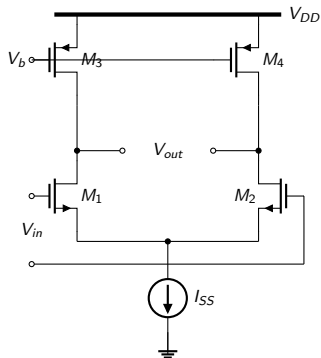

Example 2

Common Mode Response

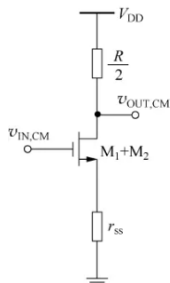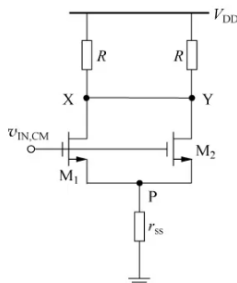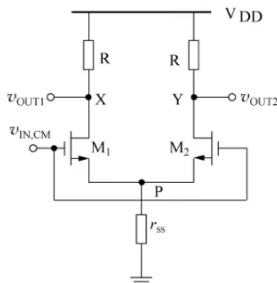

$$v_{in,cm} = v_{gs} + 2g_m v_{gs} \cdot r_{ss}$$

$$2g_m v_{gs} + \frac{v_{out,cm}}{R/2} = 0$$

$$CMRR = \frac{|A_{vd}|}{|A_{vc}|} = 1 + 2g_m r_{ss}$$

Example 3

In the differential pair , what is the common gain and differential gain and CMRR when $I_{SS} = 0.2mA$? (Neglect body effect,

$R = 10k\Omega$, $V_{DD} = 5V$)

Parameter for NMOS: $V_{THN} = 0.7V$,


$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$

Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$



All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

Example 3

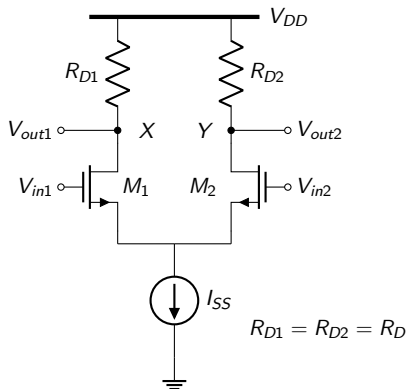

Example 3

Mismatch

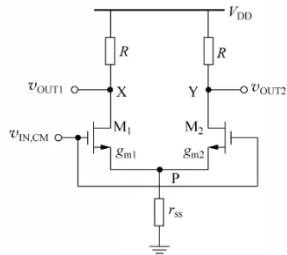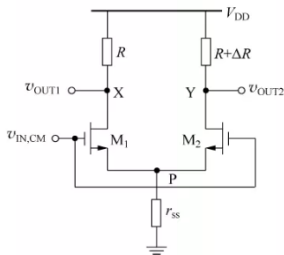


$$A_{cm-dm} = - \left(\frac{g_m \Delta R + \Delta g_m R}{2g_m r_{ss} + 1} \right)$$

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier
- 2 MOSFET Differential Pair Amplifier
- 3 Current Mirror
 - Current Mirror

- 1 MOSFET Single Stage Amplifier
 - Common Source Amplifier
 - Common Drain Amplifier (Source Follower)
 - Common Gate Amplifier
 - Cascode Amplifier
- 2 MOSFET Differential Pair Amplifier
- 3 Current Mirror
 - Current Mirror

Current Mirror

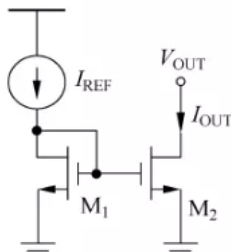


$$I_{\text{REF}} = \frac{1}{2} \mu_n C_{\text{ox}} \left(\frac{W}{L} \right)_1 (V_{\text{GS}} - V_{\text{THN1}})^2$$

$$I_{\text{OUT}} = \frac{1}{2} \mu_n C_{\text{ox}} \left(\frac{W}{L} \right)_2 (V_{\text{GS}} - V_{\text{THN2}})^2$$

$$I_{\text{OUT}} = \frac{(W/L)_2}{(W/L)_1} I_{\text{REF}}$$


Current Mirror

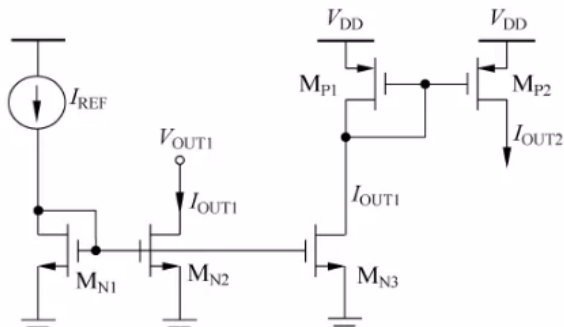

$$I_{OUT1} = \frac{(W/L)_{N2}}{(W/L)_{N1}} I_{REF}$$

$$I_{OUT2} = \frac{(W/L)_{N3}}{(W/L)_{N1}} \frac{(W/L)_{P2}}{(W/L)_{P1}} I_{REF}$$

Cascode Current Mirror

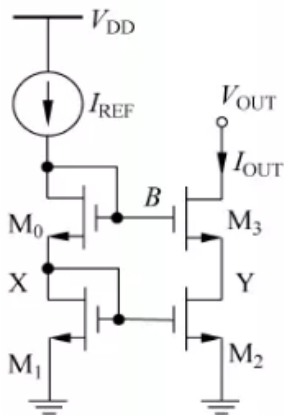

Example 4

In the cascode current mirror , what is the range of output voltage when $I_{REF} = 0.1mA$? (Neglect body effect, channel-length effect)

Parameter for NMOS: $V_{THN} = 0.7V$,

$K_n = 110\mu A/V^2$, $\lambda = 0.04V^{-1}$




Parameter for PMOS: $V_{THP} = -0.7V$,

$K_p = 50\mu A/V^2$, $\lambda = 0.05V^{-1}$

All the size of transistor is $W = 20\mu m$, $L = 1\mu m$

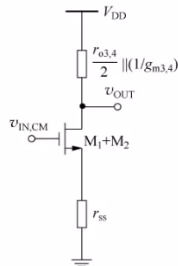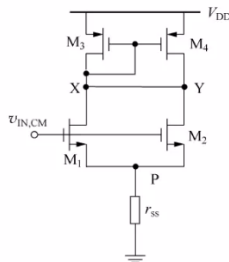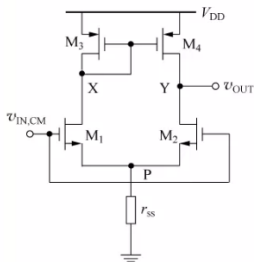Example 4

Differential Pair with Current Mirror Load



Differential Pair with Current Mirror Load

$$A_{vd} = \frac{v_{out}}{v_d} = g_m r_{out} = g_m (r_{o2} \parallel r_{of})$$

$$A_{vc} \approx -\frac{\frac{1}{2g_{m3,4}} \parallel \frac{r_{o3,4}}{2}}{\frac{1}{2g_{m1,2}} + r_{ss}} \approx -\frac{1}{1 + 2g_{m1,2}r_{ss}} \frac{g_{m1,2}}{g_{m3,4}}$$

$$CMRR = \frac{|A_{vd}|}{|A_{vc}|} = (1 + 2g_{m1,2}r_{ss}) g_{m3,4} (r_{o2} \parallel r_{o4})$$

END

Thanks