
UM-SJTU JOINT INSTITUTE
ELECTRONIC CIRCUITS SUMMER
(ECE3110J)

LAB4 REPORT

COMMON-SOURCE WITH NMOS AND PMOS DIODE-CONNECTED
LOAD

INSTRUCTED BY

DR. XUYANG LU

July 25, 2023

Name	ID
CAO YANZHUO	520370910021

1 Exercise 4.1.1

Since Proteus does not allow connecting the source directly to ground, I add a resistor of 1ω to the drain as shown in Figure 1. The obtained values thus may vary slightly from real theoretical values.

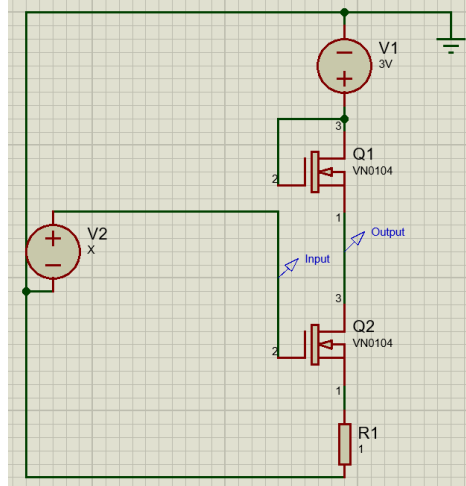


Figure 1: Circuit of 4.1.1

The resulting graph of V_{OUT} vs. V_{IN} is shown in Figure 2. From the curve, when $V_{IN} = 0.99V$, $V_{OUT} = 2.01V$ and when $V_{IN} = 1.01V$, $V_{OUT} = 1.98V$. Thus, at $V_{IN} = 1V$, the slope is,

$$\left| \frac{2.01 - 1.98}{0.99 - 1.01} \right| = -1.5 \quad (1)$$

So when $V_{IN} = 1V$, $A_V = -1.5$. At this time, $V_{OUT} \approx V_{IN} - V_{TH}$ and $3 - V_{OUT} \approx V_{TH}$ so the NMOSes are both on and in saturation region.

 


Figure 2: DC sweep of 4.1.1

2 Exercise 4.1.2

According to Figure 3, when $V_{IN} = 0.99V$, $V_{OUT} = 1.97V$ and when $V_{IN} = 1.01V$, $V_{OUT} = 1.94V$. Thus, at $V_{IN} = 1V$, the slope is,

$$\left| \frac{1.97 - 1.94}{0.99 - 1.01} \right| = -1.5 \quad (2)$$

So when $V_{IN} = 1V$, $A_V = -1.5$. At this time, three NMOSes are in saturation region. Comparing the value of A_V with that in 4.1.1, we can conclude it does not double.

This is because in (a),

$$A_V = -gm_1 \left(\frac{1}{gm_2} \parallel r_{01} \parallel r_{02} \parallel \frac{1}{gm_{b2}} \right), \quad (3)$$

while in (b),

$$A_V = -(gm_1 + gm_3) \left(\frac{1}{gm_2} \parallel r_{01} \parallel r_{02} \parallel r_{03} \parallel \frac{1}{gm_{b2}} \right), \quad (4)$$

Hence, the relation between two A_V s is not double or half.

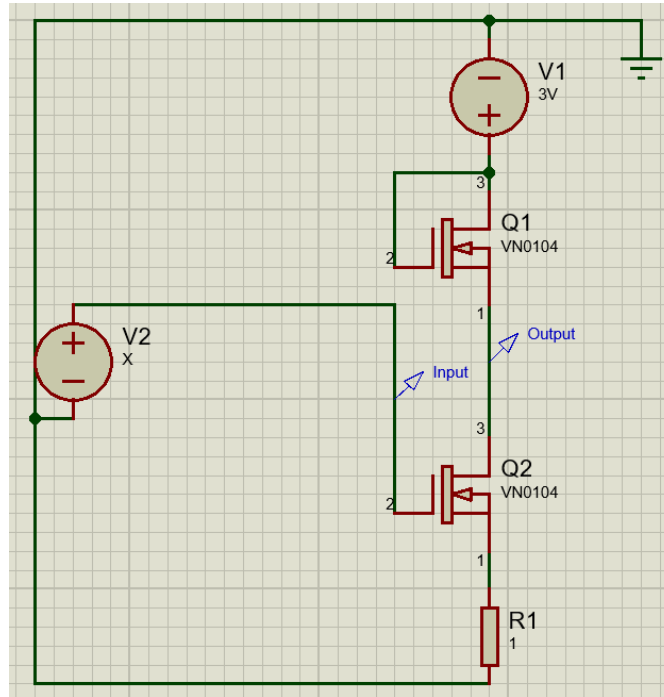


Figure 3: Circuit of 4.1.2

 


Figure 4: DC sweep of 4.1.2

3 Exercise 4.1.3

According to Figure 5, the amplitude of V_{OUT} is

$$\left| \frac{14m + 14m}{2} \right| = 0.014 \quad (5)$$

This value is quite close to $0.01|A_V| = 0.015$.

 


Figure 5: Simulation of 4.1.3

 


Figure 6: Circuit of 4.1.3

The experimental result is shown below:

 


Figure 7: Lab result of 4.1.3

4 Exercise 4.2.1

In this part, I add a resistor of 10ω to the source of NMOS as shown in Figure 8.

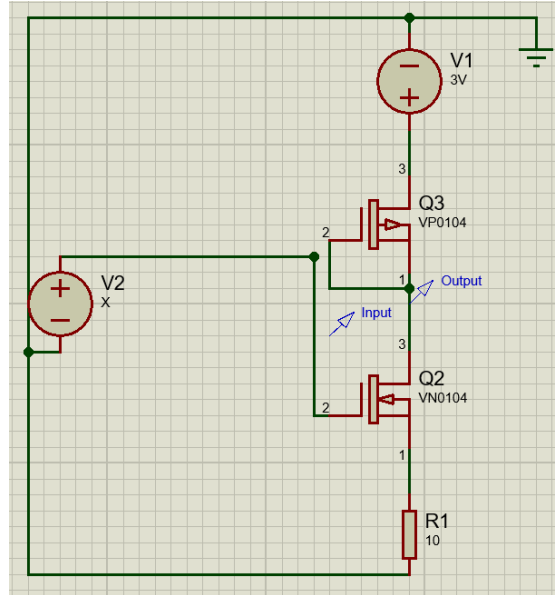


Figure 8: Circuit of 4.2.1

The resulting graph of V_{OUT} vs. V_{IN} is shown in Figure 9. From the curve, when $V_{IN} = 0.79V$, $V_{OUT} = 2.51V$ and when $V_{IN} = 0.81V$, $V_{OUT} = 2.49V$. Thus, at $V_{IN} = 0.8V$, the slope is,

$$\frac{2.51 - 2.49}{0.79 - 0.81} = -1 \quad (6)$$

So when $V_{IN} = 0.8V$, $A_V = -1$. At this time, The NMOS and PMOS are both in saturation region.

5 Exercise 4.2.2

According to Figure 9, when $V_{IN} = 0.79V$, $V_{OUT} = 2.53V$ and when $V_{IN} = 0.81V$, $V_{OUT} = 2.51V$. Thus, at $V_{IN} = 0.8V$, the slope,

 


Figure 9: Simulation of 4.2.2

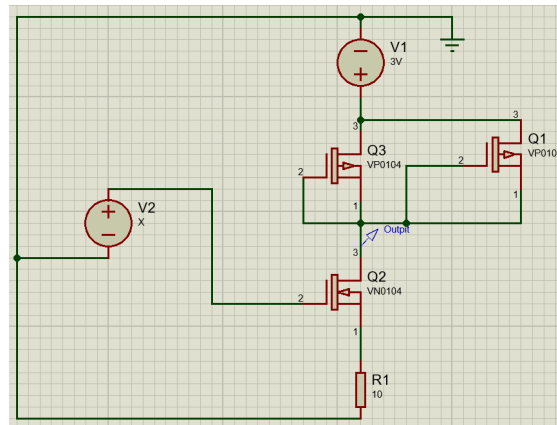


Figure 10: Circuit of 4.2.2

6 Exercise 4.2.3

According to Figure 11, the amplitude of V_{out} is

$$\frac{6.25m + 6.25m}{2} = 0.000625 \quad (7)$$

 


Figure 11: Simulation of 4.2.3

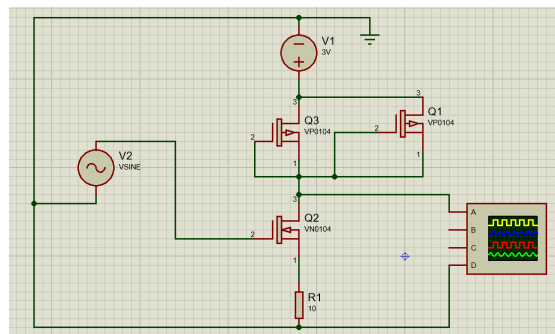


Figure 12: Circuit of 4.2.3

This value is somehow close to $0.01A_V = 0.001$. The reason why it's not quite close may be the source degeneration caused by the resistor.

The experimental result is shown below:

 


Figure 13: Lab result of 4.2.3