

## VE311 Electronic Circuit Homework 5

Due: June 19th

Note:

- 1) Please use A4 size paper or page.
- 2) Please clearly state out your final result for each question.
- 3) Please attach the screenshot of Pspice simulation result if necessary.

### Question 1. Common Gate (Easy)

In the common gate stage amplifier, the internal resistance of I is  $1k\Omega$ , what is the output resistance when  $I_{REF} = 0.01mA$  and  $0.1mA$  respectively? (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,  $K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$



Parameter for PMOS:  $V_{THP} = -0.7V$ ,  $K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$


$$\text{Transconductance } g_m = \sqrt{2K_n' \frac{W}{L} I_D}$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$

Then we do the small signal analysis:

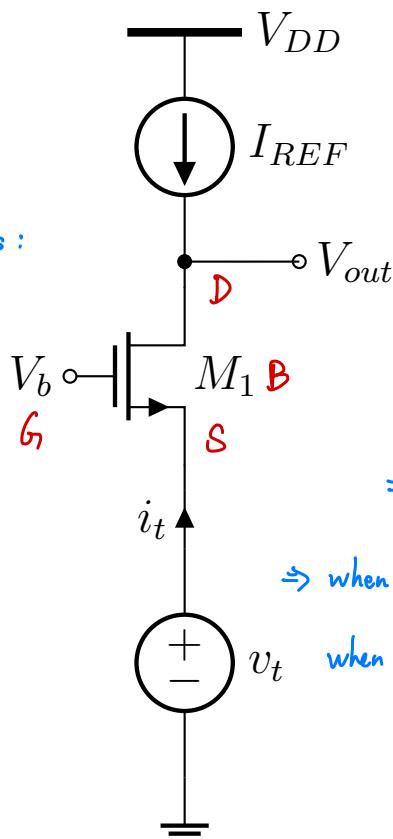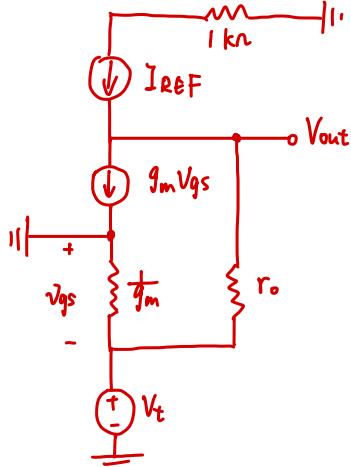

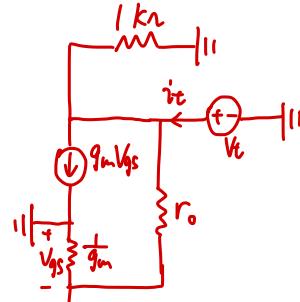To find the output resistance, we just need to analyze the following circuit:



$$\Rightarrow R_{out} = 1k\Omega \parallel r_o$$

$$\Rightarrow \text{when } I_D = 0.1mA, R_{out} = \frac{1}{\lambda \cdot 0.1 \times 10^3} \parallel (1k) = 996.02\Omega$$

$$\text{when } I_D = 0.01mA, R_{out} = \frac{1}{\lambda \cdot 0.01 \times 10^3} \parallel (1k) = 999.60\Omega$$

### Question 2. Common Gate Common Source (Medium)

Find the intrinsic gain  $A_v$  and output impedance  $R_{out}$  for the amplifier when  $I_1 = 0.01$  and  $0.1mA$  respectively. (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,  $K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$


Parameter for PMOS:  $V_{THP} = -0.7V$ ,  $K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$


$$\text{Transconductance } g_m = \sqrt{2k' \frac{W}{L}} I_D$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$


Small signal analysis:

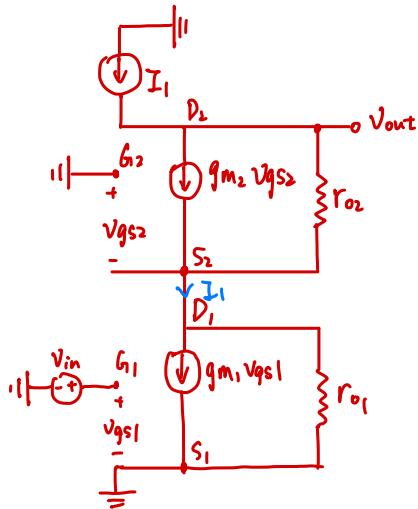

To find the output resistance:

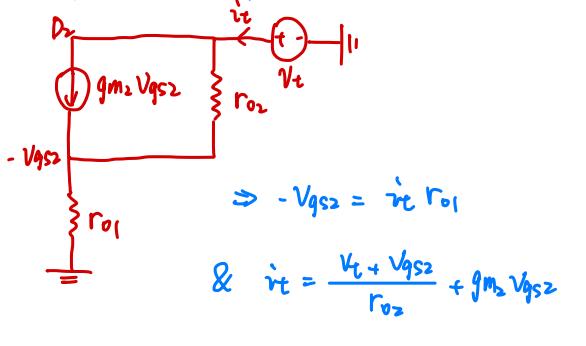
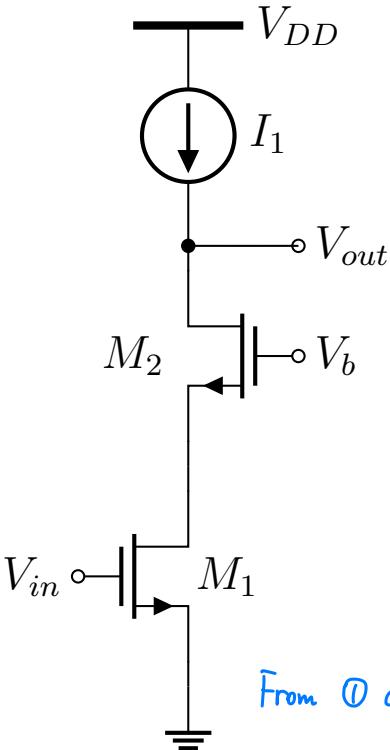
$$\Rightarrow \frac{V_t}{i_t} = R_{out} = r_{o1} + r_{o2} + g_m2 r_{o1} r_{o2} \quad (1)$$



To get  $A_v$ , we need to know  $\frac{\partial V_{out}}{\partial V_{in}}$   
we can use the AC circuit to obtain the relationship between  $V_{out}$  and  $V_{in}$

$$\begin{cases} V_{out} = -V_{gs2} + r_{o2} (I_1 - g_m2 V_{gs2}) \\ 0 = -V_{gs2} - (I_1 - g_m1 V_{gs1}) \cdot r_{o1} \\ V_{gs1} = V_{in} \end{cases}$$

$$\Rightarrow V_{out} = V_{in} - (r_{o1} g_m1 + r_{o2} r_{o1} g_m1 g_m2) I_1 + (r_{o1} + r_{o2} + r_{o1} r_{o2} g_m2) I_1$$

$$\Rightarrow A_v = \frac{\partial V_{out}}{\partial V_{in}} = -r_{o1} g_m1 - r_{o1} r_{o2} g_m1 g_m2 \quad (2)$$

From (1) and (2), we can know that

$$\text{when } I_1 = 0.01mA, \quad r_{o1} = r_{o2} = \frac{1}{\lambda I_1} = 2.5 \times 10^6 \Omega$$

$$g_m1 = g_m2 = \sqrt{2k' \frac{W}{L} I_1} = 2.098 \times 10^{-4} 1/\Omega$$


$$\Rightarrow R_{out} = 1.32 \times 10^9 \Omega, \quad A_v = -2.76 \times 10^5$$

$$\text{when } I_1 = 0.1mA, \quad r_{o1} = r_{o2} = 2.5 \times 10^5 \Omega$$

$$g_m1 = g_m2 = \sqrt{2k' \frac{W}{L} I_1} = 6.633 \times 10^{-4} 1/\Omega$$

$$\Rightarrow R_{out} = 4.196 \times 10^7 \Omega, \quad A_v = -2.77 \times 10^4$$


### Question 1. Common Gate

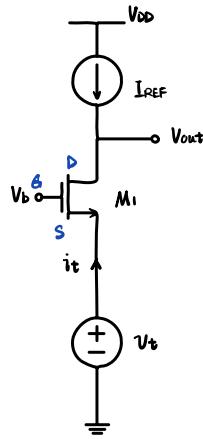



$$\text{Transconductance } g_m = \sqrt{2 k' \frac{W}{L} I_D}$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$

Small Signal Model:

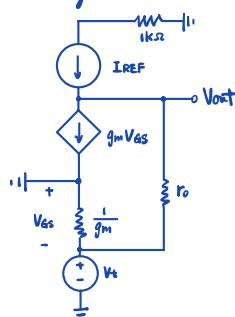

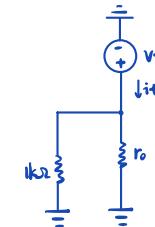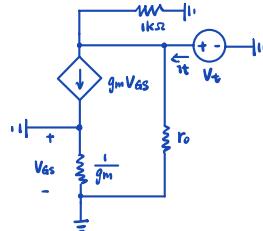To find the resistance looking from output:




$$\Rightarrow R_{out} = R_D // r_o$$

$$\textcircled{1} \quad I_{REF} = 0.1 \text{ mA} = I_D \Rightarrow R_{out} = \frac{1}{\lambda I_D} // 1 \text{ k}\Omega = \frac{1}{0.04 \times 0.1 \times 10^{-3}} // 10^3 = 996.02 \text{ }\Omega$$

$$\textcircled{2} \quad I_{REF} = 0.01 \text{ mA} = I_D \Rightarrow R_{out} = \frac{1}{\lambda I_D} // 1 \text{ k}\Omega = \frac{1}{0.04 \times 0.01 \times 10^{-3}} // 10^3 = 999.99 \text{ }\Omega$$
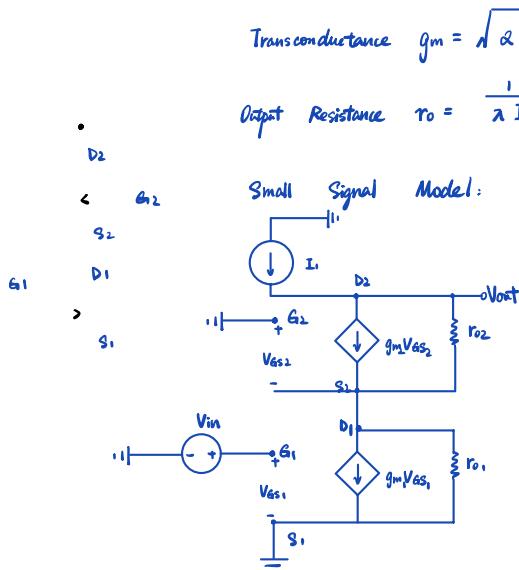
### Question 2. Common Gate Common Source




$$\text{Transconductance } g_m = \sqrt{2 k' \frac{W}{L} I_D}$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$

Small Signal Model:

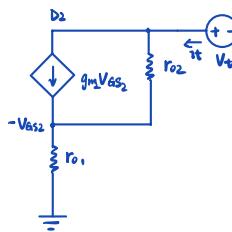To find the resistance looking from output:



$$\begin{cases} -V_{gs2} = i_t r_{o1} \\ i_t = \frac{V_t + V_{gs1}}{r_{o2}} + g_{m2} V_{gs2} \end{cases} \Rightarrow i_t = \frac{V_t - i_t r_{o1}}{r_{o2}} - g_{m2} i_t r_{o1}$$

$$\Rightarrow V_t = i_t r_{o2} + i_t r_{o1} + g_{m2} i_t r_{o1} r_{o2}$$

$$\Rightarrow R_{out} = \frac{V_t}{i_t} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}$$

For Av:

$$\begin{cases} V_{out} = -V_{gs2} + r_{o2} (I_1 - g_{m2} V_{gs2}) \\ -V_{gs2} = r_{o1} (I_1 - g_{m1} V_{gs1}) = r_{o1} (I_1 - g_{m1} V_{in}) \end{cases}$$

$$\Rightarrow V_{out} = r_{o1} I_1 - r_{o1} g_{m1} V_{in} + r_{o2} I_1 + r_{o1} r_{o2} g_{m2} (I_1 - g_{m1} V_{in})$$

$$\Rightarrow Av = \frac{\partial V_{out}}{\partial V_{in}} = -r_{o1} g_{m1} - r_{o1} r_{o2} g_{m1} g_{m2}$$

$$\textcircled{1} \quad I_1 = 0.01 \text{ mA}$$

$$\textcircled{1} \quad I_1 = 0.1 \text{ mA}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda I_1} = 2.5 \times 10^6 \text{ }\Omega$$

$$g_{m1} = g_{m2} = \sqrt{2 k' \frac{W}{L} I_D}$$

$$= \sqrt{2 \times 110 \times 10^{-6} \times 20 \times 0.01 \times 10^{-3}} = 2.098 \times 10^{-4} \text{ A/V}$$

$$R_{out} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2} = 2.5 \times 10^6 \times 2 + (2.5 \times 10^6)^2 \times 2.098 \times 10^{-4} = 1.32 \times 10^9 \text{ }\Omega$$

$$Av = -r_{o1} g_{m1} - r_{o1} r_{o2} g_{m1} g_{m2}$$

$$= -2.5 \times 10^6 \times 2.098 \times 10^{-4} - (2.5 \times 10^6 \times 2.098 \times 10^{-4})^2 = -2.76 \times 10^5$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda I_1} = 2.5 \times 10^5 \text{ }\Omega$$

$$g_{m1} = g_{m2} = \sqrt{2 k' \frac{W}{L} I_D}$$

$$= \sqrt{2 \times 110 \times 10^{-6} \times 20 \times 0.1 \times 10^{-3}} = 6.633 \times 10^{-4}$$

$$R_{out} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2} = 2.5 \times 10^5 \times 2 + (2.5 \times 10^5)^2 \times 6.633 \times 10^{-4} = 4.196 \times 10^7 \text{ }\Omega$$

$$Av = -r_{o1} g_{m1} - r_{o1} r_{o2} g_{m1} g_{m2}$$

$$= -2.5 \times 10^5 \times 6.633 \times 10^{-4} - (2.5 \times 10^5 \times 6.633 \times 10^{-4})^2 = -2.77 \times 10^4$$

### Question 3. Common Gate Common Source (Medium)

Find the intrinsic gain  $A_v$  and output impedance  $R_{out}$  for the amplifier when  $I_1 = 0.01$  and  $0.1mA$  respectively. (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,  $K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,  $K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$

All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$




To find the output resistance:

$$\text{Tranductance } g_{mn} = \sqrt{2k' \frac{W}{L}} I_D$$

$$g_{mp} = \sqrt{2k' \frac{W}{L}} I_D$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$

Small signal analysis:

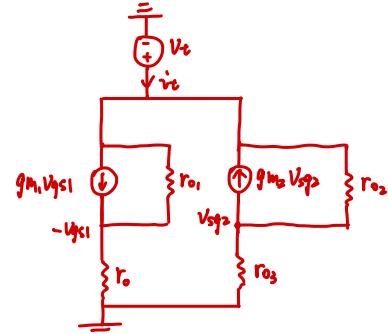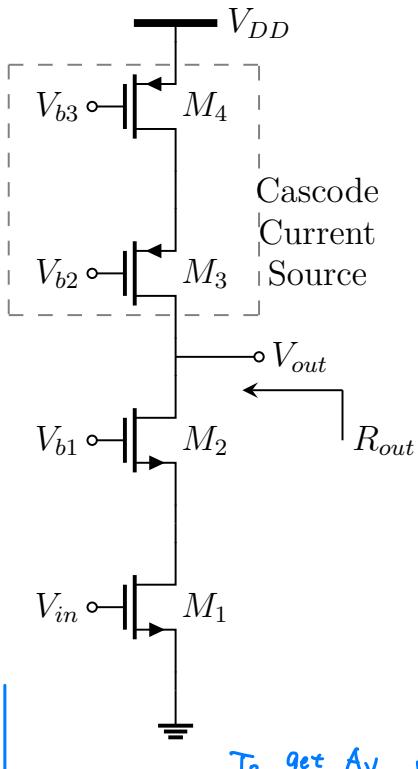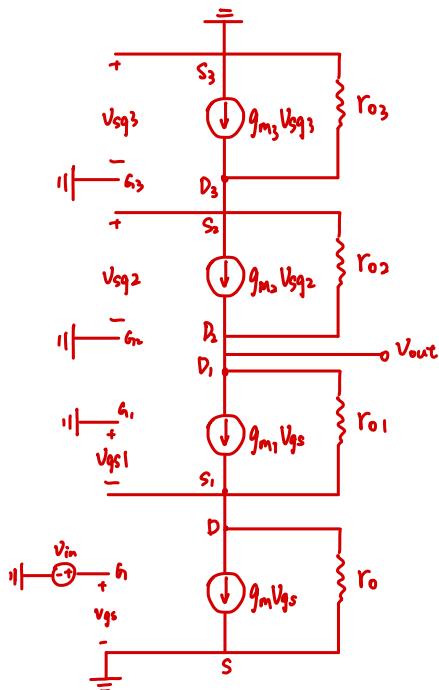

$$\begin{aligned} \frac{v_t + v_{gs1}}{r_{o1}} + g_{m1} v_{gs1} &= -\frac{v_{gs1}}{r_o} \\ \frac{v_t - v_{gs2}}{r_{o2}} - g_{m2} v_{gs2} &= \frac{v_{gs2}}{r_{o3}} \\ i_t &= -\frac{v_{gs1}}{r_o} + \frac{v_{gs2}}{r_{o3}} \\ \Rightarrow R_{out} &= \frac{v_t}{i_t} = \frac{1}{\frac{1}{r_o + r_{o1} + g_{m1} r_{o1}} + \frac{1}{r_{o2} + r_{o3} + g_{m2} r_{o2} r_{o3}}} \end{aligned} \quad (1)$$

To get  $A_v$ , we need to know  $\frac{\partial v_{out}}{\partial v_{in}}$ . We can use the AC circuit to obtain the relationship between  $v_{out}$  and  $v_{in}$

$$g_m v_{in} + \frac{-v_{gs1}}{r_o} = g_{m1} v_{gs1} + \frac{v_{out} + v_{gs1}}{r_{o1}} = g_{m2} v_{gs2} + \frac{v_{gs2} - v_{out}}{r_{o2}} = \frac{v_{out} - v_{gs2}}{r_{o3}}$$

$$\Rightarrow A_v = \frac{\partial v_{out}}{\partial v_{in}} = \frac{g_m}{\left(\frac{1}{r_o} + \frac{1}{r_{o1}} + g_{m1}\right) \left( \frac{g_{m2} + \frac{1}{r_{o2}}}{(g_{m1} + \frac{1}{r_{o1}})(g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o3}}) r_{o2}} - \frac{\frac{1}{r_{o1}} + \frac{1}{r_{o2}}}{g_{m1} + \frac{1}{r_{o1}}} + \frac{1}{r_{o1}} \right)} \quad (2)$$

From ① and ②, we can know that when  $I_1 = 0.01mA$ ,

$$r_{o2} = r_{o3} = 2 \times 10^8 \Omega, r_o = r_{o1} = 2.5 \times 10^6 \Omega, g_{m2} = g_{m3} = \sqrt{2} \times 10^{-4} 1/\Omega, g_{m1} = g_m = \sqrt{4.4} \times 10^{-4} 1/\Omega$$


$$\Rightarrow R_{out} = 3.976 \times 10^8 \Omega, A_v = -8.3 \times 10^4$$

From ① and ②, we can know that when  $I_1 = 0.1mA$ ,

$$r_{o2} = r_{o3} = 2 \times 10^5 \Omega, r_o = r_{o1} = 2.5 \times 10^5 \Omega, g_{m2} = g_{m3} = \sqrt{20} \times 10^{-4} 1/\Omega, g_{m1} = g_m = \sqrt{4.4} \times 10^{-4} 1/\Omega$$

$$\Rightarrow R_{out} = 1.273 \times 10^7 \Omega, A_v = -8.4 \times 10^3$$


Question 3. Common Gate Common Source

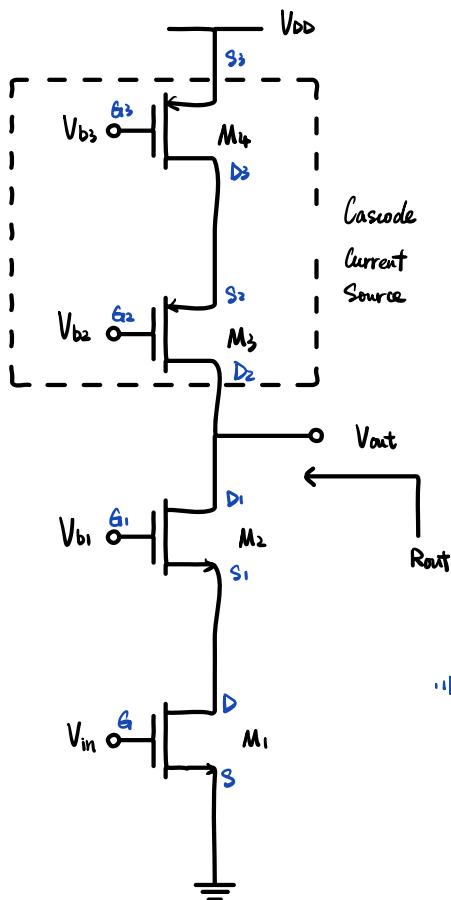


$$\text{Transconductance } g_m = \sqrt{2k'n \frac{W}{L} I_D} \quad \text{or} \quad \sqrt{2k'p \frac{W}{L} I_D}$$

$$\text{Output Resistance } r_o = \frac{1}{2 I_D}$$

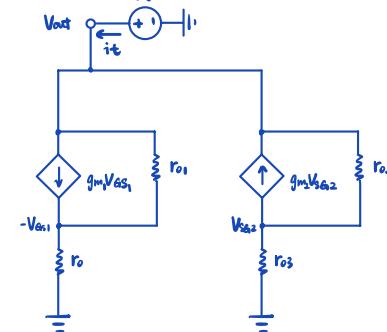To find the resistance looking from output:



Draw the small signal model:

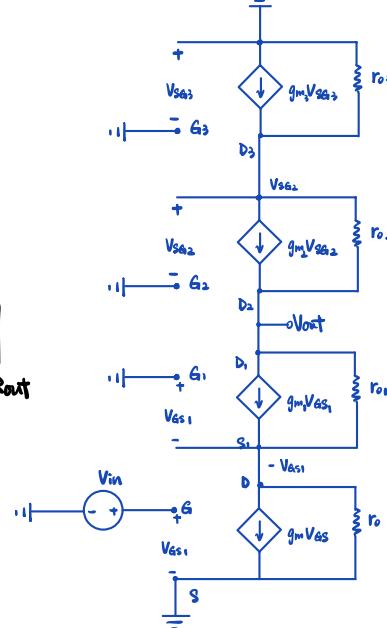

$$\begin{cases} \frac{Vt + V_{AS1}}{r_{o1}} + g_{m1}V_{AS1} = -\frac{V_{AS1}}{r_{o1}} \Rightarrow -\frac{Vt}{r_{o1}} = (\frac{1}{r_{o1}} + \frac{1}{r_{o1}} + g_{m1})V_{AS1} \\ \frac{Vt - V_{AS2}}{r_{o2}} - g_{m2}V_{AS2} = \frac{V_{AS2}}{r_{o3}} \Rightarrow \frac{Vt}{r_{o2}} = (\frac{1}{r_{o2}} + \frac{1}{r_{o2}} + g_{m2})V_{AS2} \\ -\frac{V_{AS1}}{r_{o1}} + \frac{V_{AS2}}{r_{o3}} = i_t \\ \Rightarrow i_t = \frac{Vt}{r_{o1}r_{o2}} - \frac{1}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m1}} + \frac{Vt}{r_{o1}r_{o3}} \frac{1}{\frac{1}{r_{o2}} + \frac{1}{r_{o3}} + g_{m2}} \\ \Rightarrow R_{out} = \frac{Vt}{i_t} = \frac{1}{r_{o1} + r_{o2} + g_{m1}r_{o1}r_{o2}} + \frac{1}{r_{o3} + r_{o2} + g_{m2}r_{o2}r_{o3}} \end{cases}$$

$$\text{For } Av: \quad g_m V_{in} + \frac{-V_{AS1}}{r_0} = g_{m1} V_{AS1} + \frac{V_{out} + V_{AS1}}{r_{o1}} = g_{m2} V_{AS2} + \frac{V_{AS2} - V_{out}}{r_{o2}} = \frac{0 - V_{AS2}}{r_{o3}}$$

$$\Rightarrow V_{out} = (\frac{1}{r_{o2}} + \frac{1}{r_{o3}}) r_{o2} V_{AS2}$$

$$\Rightarrow (g_{m2} + \frac{1}{r_{o1}}) V_{AS1} = (g_{m2} + \frac{1}{r_{o2}}) V_{AS2} - (\frac{1}{r_{o1}} + \frac{1}{r_{o2}}) V_{out}$$

$$\Rightarrow g_m V_{in} = (\frac{1}{r_0} + \frac{1}{r_{o1}} + g_{m1}) V_{AS1} + \frac{1}{r_{o1}} V_{out} = (\frac{1}{r_0} + \frac{1}{r_{o1}} + g_{m1}) (\frac{g_{m2} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}} V_{AS2} - \frac{\frac{1}{r_{o1}} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}} V_{out}) + \frac{1}{r_{o1}} V_{out} = (\frac{1}{r_0} + \frac{1}{r_{o1}} + g_{m1}) (\frac{g_{m2} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}}) \frac{1}{(\frac{1}{g_{m2} + \frac{1}{r_{o2}}} + \frac{1}{r_{o2}}) r_{o2}} - \frac{\frac{1}{r_{o1}} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}} V_{out} + \frac{1}{r_{o1}} V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{g_m}{(\frac{1}{r_0} + \frac{1}{r_{o1}} + g_{m1}) (\frac{g_{m2} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}}) \frac{1}{(\frac{1}{g_{m2} + \frac{1}{r_{o2}}} + \frac{1}{r_{o2}}) r_{o2}} - \frac{\frac{1}{r_{o1}} + \frac{1}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}}} + \frac{1}{r_{o1}}$$

①  $I = 0.01 \text{ mA}$

$$r_{o2} = r_{o3} = \frac{1}{2pI} = \frac{1}{0.05 \times 10^{-5}} = 2 \times 10^6 \Omega$$

$$r_0 = r_{o1} = \frac{1}{2nI} = \frac{1}{0.04 \times 10^{-5}} = 2.5 \times 10^6 \Omega$$

$$g_{m2} = g_{m3} = \sqrt{2k'p \frac{W}{L} I_D} = \sqrt{2 \times 50 \times 10^{-6} \times 80 \times 10^{-5}} = 1.12 \times 10^{-4} \text{ A/V}$$

$$g_m = g_{m1} = \sqrt{2kn \frac{W}{L} I_D} = \sqrt{2 \times 110 \times 10^{-6} \times 80 \times 10^{-5}} = 1.44 \times 10^{-4} \text{ A/V}$$

$$\Rightarrow R_{out} = \frac{1}{\frac{1}{r_0 + g_{m2}r_{o2}} + \frac{1}{r_{o3} + g_{m3}r_{o3}}} = 3.716 \times 10^8 \Omega$$

$$Av = -8.3 \times 10^4$$

②  $I = 0.1 \text{ mA}$

$$r_{o2} = r_{o3} = \frac{1}{2pI} = \frac{1}{0.05 \times 10^{-4}} = 2 \times 10^5 \Omega$$

$$r_0 = r_{o1} = \frac{1}{2nI} = \frac{1}{0.04 \times 10^{-4}} = 2.5 \times 10^5 \Omega$$

$$g_{m2} = g_{m3} = \sqrt{2k'p \frac{W}{L} I_D} = \sqrt{2 \times 50 \times 10^{-6} \times 80 \times 10^{-4}} = 1.12 \times 10^{-4} \text{ A/V}$$

$$g_m = g_{m1} = \sqrt{2kn \frac{W}{L} I_D} = \sqrt{2 \times 110 \times 10^{-6} \times 80 \times 10^{-4}} = 1.44 \times 10^{-4} \text{ A/V}$$

$$\Rightarrow R_{out} = 1.274 \times 10^7 \Omega$$

$$Av = -8.4 \times 10^3$$

#### Question 4. Differential Pair (Hard)

Find the intrinsic gain  $A_v$  for the amplifier when  $I_{SS} = 0.02$  and  $0.2mA$  respectively. (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,  $K_n = 110\mu A/V^2$ ,  $\lambda = 0.04V^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,  $K_p = 50\mu A/V^2$ ,  $\lambda = 0.05V^{-1}$


All the size of transistor is  $W = 20\mu m$ ,  $L = 1\mu m$

$$\text{Transconductance } g_{mn} = \sqrt{2k'_n \frac{W}{L}} I_D$$



$$g_{mp} = \sqrt{2k'_p \frac{W}{L}} I_D$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$

Small signal analysis:

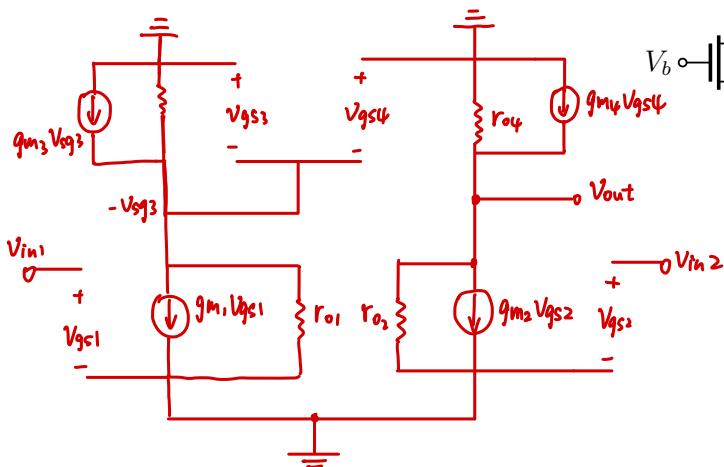

To find the output resistance:

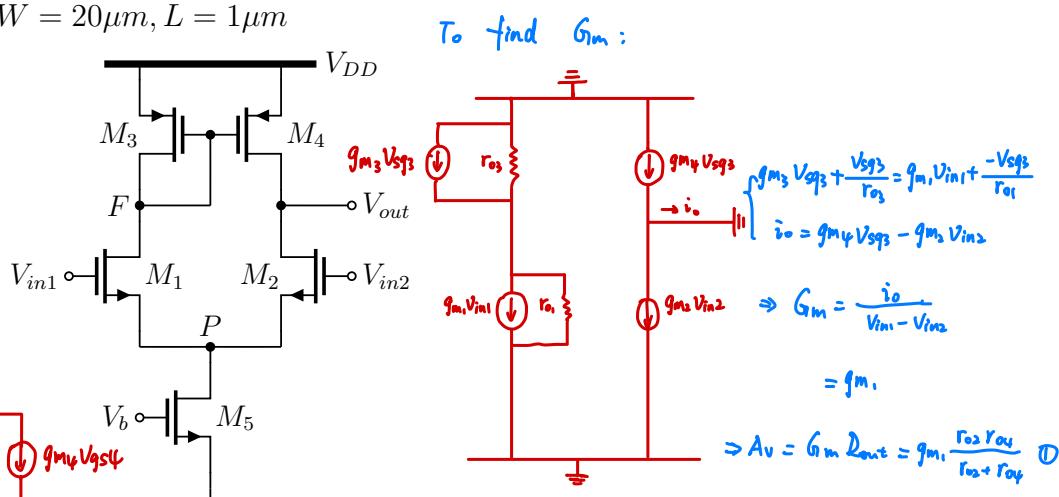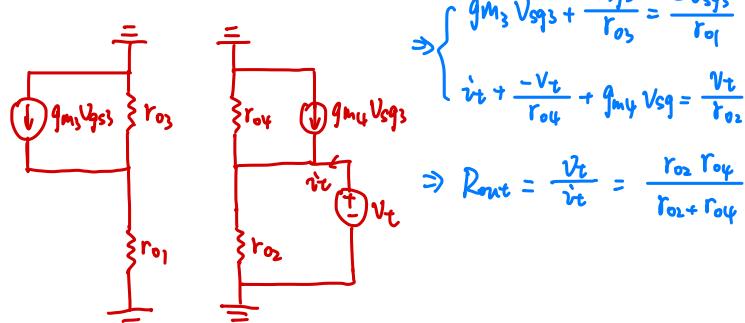

From ①, we can know that when  $I_{SS} = 0.02 mA$

$$\Rightarrow r_{o3} = 2.5 \times 10^6 \Omega, r_{o4} = 2 \times 10^6 \Omega, g_{m1} = \sqrt{44} \times 10^{-4} 1/\Omega$$


$$\Rightarrow A_v = 233.07$$

And when  $I_{SS} = 0.2 mA$

$$\Rightarrow r_{o3} = 2.5 \times 10^5 \Omega, r_{o4} = 2 \times 10^5 \Omega, g_{m1} = \sqrt{44} \times 10^{-4} 1/\Omega$$

$$\Rightarrow A_v = 73.70$$

### Question 4 Differential Pair

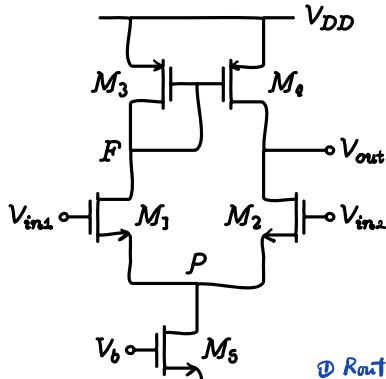


$$\text{Transconductance } g_m = \sqrt{\alpha k' \frac{W}{L} I_D}$$

$$\text{or } \sqrt{\alpha k' \frac{W}{L} I_D}$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$

①  $R_{out}$

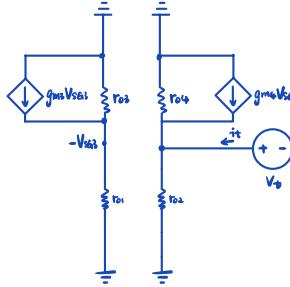

$$\begin{cases} g_m1V_{S1} + \frac{V_{S1}}{r_o1} = -V_{S2} \\ i_t + \frac{-V_t}{r_o4} + g_m4V_{S4} = \frac{V_t}{r_o2} \end{cases}$$

$$\Rightarrow V_{S1} = 0$$

$$\Rightarrow R_{out} = \frac{V_t}{i_t} = \frac{r_o2 r_o4}{r_o4 + r_o2}$$

$$\Rightarrow Av = g_m R_{out} = g_{m1,2} \frac{r_{o1,2} r_{o3,4}}{r_{o1,2} + r_{o3,4}}$$

①  $I_{SS} = 0.02 \text{ mA}$


$$r_{o1,2} = \frac{1}{\lambda n I} = \frac{1}{0.04 \times 10^{-5}} = 2.5 \times 10^6 \Omega$$

$$r_{o3,4} = \frac{1}{\lambda p I} = \frac{1}{0.05 \times 10^{-5}} = 2 \times 10^6 \Omega$$


$$g_{m1,2} = \sqrt{\alpha k' \frac{W}{L} I_D} = \sqrt{\alpha \times 10 \times 10^6 \times 20 \times 10^{-5}} = 144 \times 10^{-4} \text{ A/V}$$

$$\Rightarrow Av = 233.07$$

Draw small signal model:

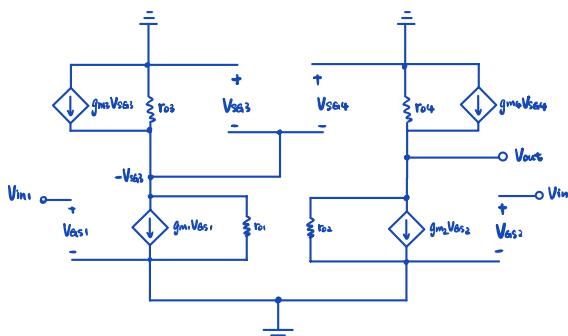

②  $G_m$

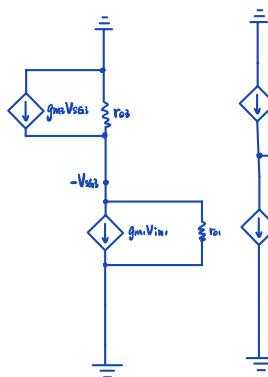

$$\begin{cases} g_m1V_{S1} + \frac{V_{S1}}{r_o1} = g_m1V_{in1} + \frac{-V_{S2}}{r_o2} \\ io = g_m1V_{S1} - g_m2V_{S2} \end{cases}$$

$$\Rightarrow V_{S1} = \frac{g_m1 V_{in1}}{g_{m1} + \frac{1}{r_o1} + \frac{1}{r_o2}} \approx \frac{g_{m1}}{g_{m1} + r_o1} V_{in1}$$

$$\Rightarrow io = g_{m1,2} (V_{in1} - V_{in2})$$

$$\Rightarrow G_m = \frac{io}{V_{in1} - V_{in2}} = g_{m1,2}$$

②  $I_{SS} = 0.2 \text{ mA}$

$$r_{o1,2} = \frac{1}{\lambda n I} = \frac{1}{0.04 \times 10^{-4}} = 2.5 \times 10^5 \Omega$$

$$r_{o3,4} = \frac{1}{\lambda p I} = \frac{1}{0.05 \times 10^{-4}} = 2 \times 10^5 \Omega$$

$$g_{m1,2} = \sqrt{\alpha k' \frac{W}{L} I_D} = \sqrt{\alpha \times 10 \times 10^6 \times 20 \times 10^{-4}} = 144 \times 10^{-4} \text{ A/V}$$

$$\Rightarrow Av = 73.70$$

### Question 5. Differential Pair (Hard)

Find the intrinsic gain  $A_v$  for the amplifier when  $I_{SS} = 0.02$  and  $0.2\text{mA}$  respectively. (Neglect body effect)

Parameter for NMOS:  $V_{THN} = 0.7V$ ,  $K_n = 110\mu\text{A}/\text{V}^2$ ,  $\lambda = 0.04\text{V}^{-1}$

Parameter for PMOS:  $V_{THP} = -0.7V$ ,  $K_p = 50\mu\text{A}/\text{V}^2$ ,  $\lambda = 0.05\text{V}^{-1}$



All the size of transistor is  $W = 20\mu\text{m}$ ,  $L = 1\mu\text{m}$

$$\text{Tranductance } g_{mn} = \sqrt{2k_n \frac{W}{L}} I_D$$


$$g_{mp} = \sqrt{2k_p \frac{W}{L}} I_D$$

$$\text{Output Resistance } r_o = \frac{1}{\lambda I_D}$$

Small signal analysis:

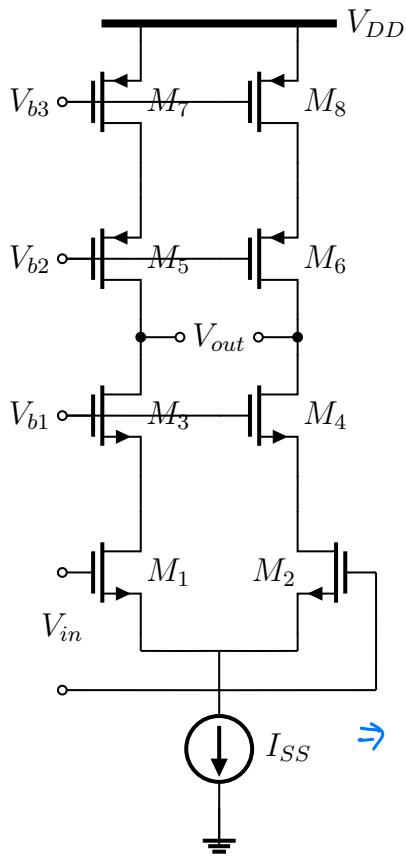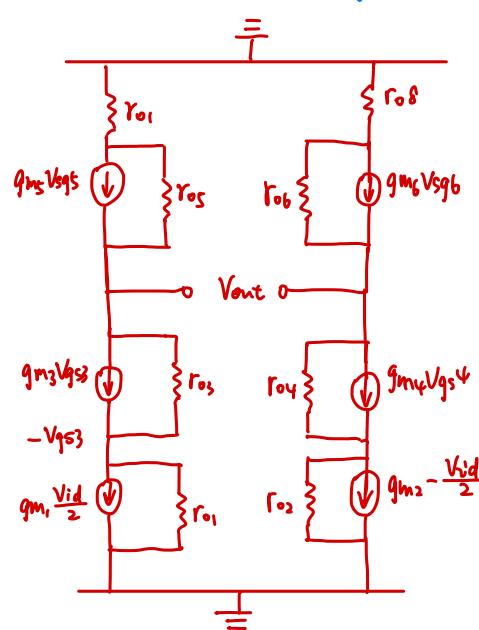

To find  $G_m$ :

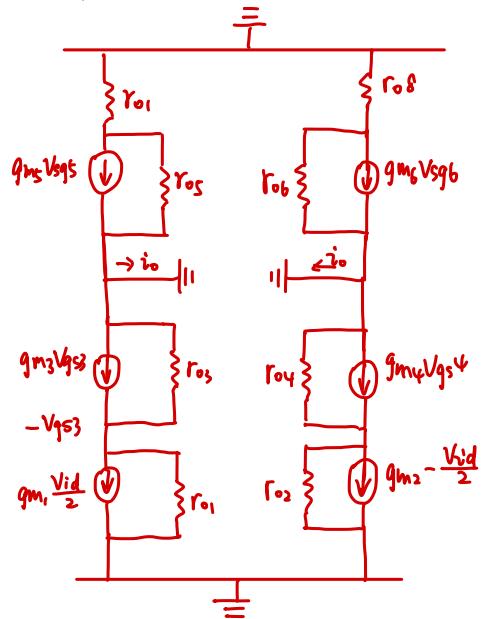

$$\Rightarrow \begin{cases} \frac{-V_{gs5}}{r_o} = \frac{V_{gs5}}{r_o} + g_{mp} V_{gs5} \\ \frac{V_{gs3}}{r_o} + g_{mn} V_{gs3} = g_{mn} \frac{V_{id}}{2} + \frac{-V_{gs3}}{r_o} \end{cases}$$

$$\Rightarrow G_m = \frac{r_o g_m^2}{r_o g_{mn} - 1} = -g_{mn} \text{ (round to } -g_{mn})$$

$$\Rightarrow A_v = R_{out} \cdot G_m = -g_{mn} \cdot \frac{(2+g_{mp}r_o)(2+g_{mn}r_o)r_o}{4+g_{mp}r_o+g_{mn}r_o} \quad \text{①}$$

From ①, we can know that when  $I_{SS} = 0.02\text{ mA}$

$$r_{o2} = 2.5 \times 10^6 \Omega, r_{o4} = 2 \times 10^6 \Omega, g_{mn} = \sqrt{44} \times 10^{-4} \text{ 1/n}, g_{mp} = \sqrt{5} \times 10^{-4} \text{ 1/n}$$

$$\Rightarrow A_v = -8.34 \times 10^4$$

And when  $I_{SS} = 0.2\text{ mA}$

$$r_{o2} = 2.5 \times 10^5 \Omega, r_{o4} = 2 \times 10^5 \Omega, g_{mn} = \sqrt{44} \times 10^{-4} \text{ 1/n}, g_{mp} = \sqrt{50} \times 10^{-4} \text{ 1/n}$$


$$\Rightarrow A_v = -8.449 \times 10^3$$

$$\text{To find } R_{out}: \left\{ \begin{array}{l} \frac{V_{gs5}}{r_o} = \frac{V_t - V_{gs5}}{r_o} - g_{mp} V_{gs5} \\ \frac{V_{gs3} + V_t}{r_o} + g_{mn} V_{gs3} = \frac{-V_{gs3}}{r_o} \\ i_t = \frac{V_{gs5}}{r_o} + \frac{-V_{gs3}}{r_o} \end{array} \right.$$

$$\Rightarrow R_{out} = \frac{(2+g_{mp}r_o)(2+g_{mn}r_o)r_o}{(2+g_{mp}r_o+2+g_{mn}r_o) \cdot r_o}$$

$$= \frac{(2+g_{mp}r_o)(2+g_{mn}r_o)r_o}{4+g_{mp}r_o+g_{mn}r_o}$$

Question 5



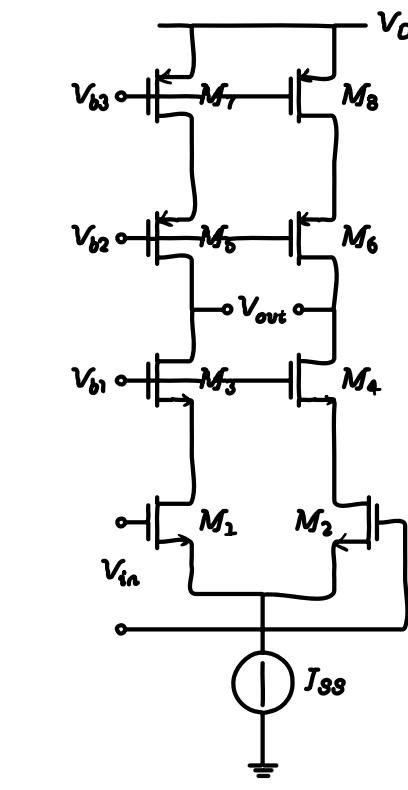


$$\text{Transconductance } g_m = \sqrt{2 k' \frac{W}{L} I_D}$$

$$\text{or } \sqrt{2 k' \frac{W}{L} I_D}$$

$$\text{Output Resistance } r_o = \frac{1}{2 k' \frac{W}{L} I_D}$$

Small Signal Model:

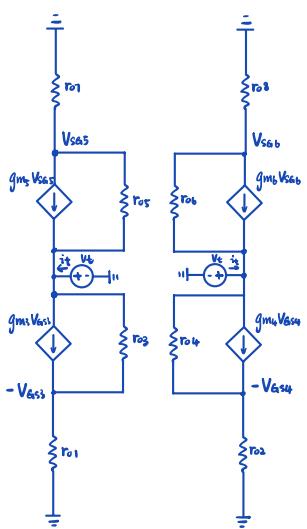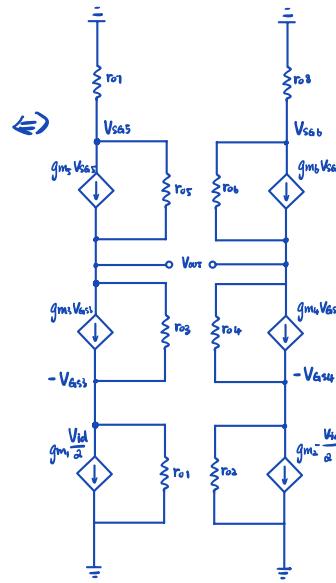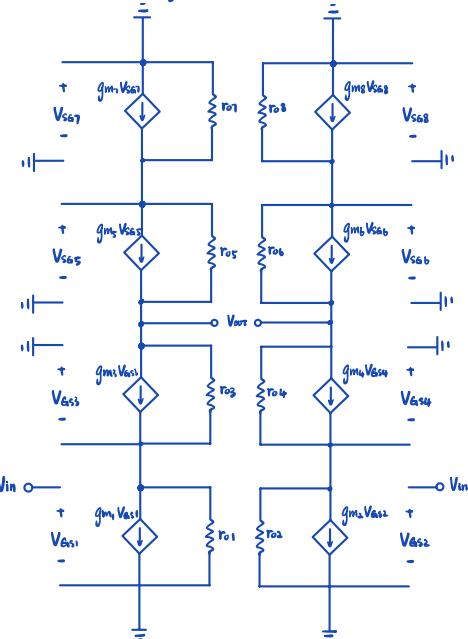

① Rout

$$\begin{cases} r_{o5,6,7,8} = r_{op} \\ r_{o1,2,3,4} = r_{on} \end{cases} \quad \begin{cases} g_{m1,2,3,4} = g_{mn} \\ g_{m5,6,7,8} = g_{mp} \end{cases}$$

Each Half:

$$\begin{cases} \frac{V_{SGS}}{r_{op}} = \frac{V_t - V_{SGS}}{r_{op}} - g_{mp} V_{SGS} \Rightarrow \frac{V_{SGS}}{r_{op}} = \frac{V_t}{(2 + g_{mp}) r_{op}} \\ \frac{V_{SGS} + V_t}{r_{on}} + g_{mn} V_{SGS} = \frac{-V_{SGS}}{r_{on}} \Rightarrow \frac{-V_{SGS}}{r_{on}} = \frac{V_t}{(2 + g_{mn}) r_{on}} \\ i_t = \frac{V_{SGS} + -V_{SGS}}{r_{op}} = \frac{V_t}{(2 + g_{mp}) r_{op}} + \frac{V_t}{(2 + g_{mn}) r_{on}} \end{cases}$$

$$\Rightarrow R_{out} = \frac{(2 + g_{mp}) r_{op} \cdot (2 + g_{mn}) r_{on}}{(2 + g_{mp}) r_{op} + (2 + g_{mn}) r_{on}}$$

$$② I_{SS} = 0.02 \text{ mA}$$

$$r_{on} = \frac{1}{2 k' I} = \frac{1}{0.04 \times 10^{-5}} = 2.5 \times 10^6 \Omega$$

$$r_{op} = \frac{1}{2 p I} = \frac{1}{0.05 \times 10^{-5}} = 2 \times 10^6 \Omega$$

$$g_{mn} = \sqrt{2 k' \frac{W}{L} I_D}$$

$$= \sqrt{2 \times 10 \times 10^6 \times 20 \times 10^{-5}} = 14.4 \times 10^{-4} \text{ A/V}$$

$$g_{mp} = \sqrt{2 k' \frac{W}{L} I_D} = \sqrt{2 \times 50 \times 10^6 \times 20 \times 10^{-5}} = 12 \times 10^{-4} \text{ A/V}$$

$$\Rightarrow A_v = -8.340 \times 10^4$$

$$③ I_{SS} = 0.2 \text{ mA}$$

$$r_{on} = \frac{1}{2 k' I} = \frac{1}{0.04 \times 10^{-4}} = 2.5 \times 10^5 \Omega$$


$$r_{op} = \frac{1}{2 p I} = \frac{1}{0.05 \times 10^{-4}} = 2 \times 10^5 \Omega$$

$$g_{mn} = \sqrt{2 k' \frac{W}{L} I_D}$$

$$= \sqrt{2 \times 10 \times 10^6 \times 20 \times 10^{-4}} = 14.4 \times 10^{-4} \text{ A/V}$$

$$g_{mp} = \sqrt{2 k' \frac{W}{L} I_D} = \sqrt{2 \times 50 \times 10^6 \times 20 \times 10^{-4}} = 120 \times 10^{-4} \text{ A/V}$$

$$\Rightarrow A_v = -8.449 \times 10^3$$

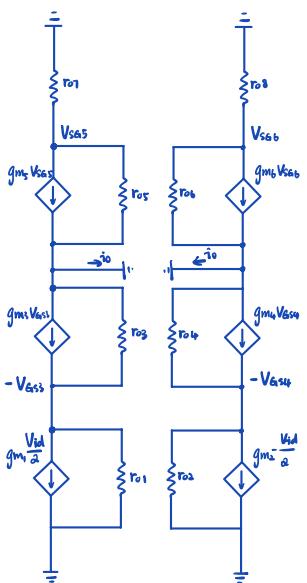

② Gm , for each half:

$$\begin{cases} \frac{-V_{SGS}}{r_{op}} = \frac{V_{SGS}}{r_{op}} + g_{mp} V_{SGS} \Rightarrow V_{SGS} = 0 \\ \frac{V_{SGS}}{r_{on}} + g_{mn} V_{SGS} = g_{mn} \frac{V_{id}}{a} + \frac{-V_{SGS}}{r_{on}} \end{cases}$$

$$\Rightarrow -V_{SGS} = \frac{i_o}{r_{on} + g_{mn}} \approx \frac{i_o}{g_{mn}}$$

$$g_{mn} \frac{V_{id}}{a} + \frac{i_o}{r_{on} g_{mn}} = -i_o$$

$$\Rightarrow G_m = \frac{i_o}{a V_{in}} = \frac{r_{on} g_{mn}}{-r_{on} g_{mn} - 1} \approx -g_{mn}$$

$$\Rightarrow A_v = G_m \cdot R_{out}$$

### Question 6. Common Source with Diode-connected Load (Lunatic)

Consider the circuit of Fig. 2 with  $(W/L)_1 = 50/0.5$  and  $(W/L)_2 = 10/0.5$ . Assume that  $\lambda = \gamma = 0$ . Then 3 V for  $V_{DD}$ , 0.7 V for  $V_{TH1}$ ,  $0.45 V^{\frac{1}{2}}$  for  $\gamma$ , and 0.9 V for  $2\Phi_F$

- 1) At what input voltage is  $M_1$  at the edge of the triode region? What is the small-signal gain under this condition? 线性区到饱和区的转换点
- 2) What input voltage drives  $M_1$  into the triode region by 50mV? What is the small-signal gain under this condition? 由转换点还大 50mV. 即在饱和区 +

1) Since  $M_1$  is at the edge of the triode region:

$$V_{DS1} = V_{GS1} - V_{TH1}$$

$$V_{out} = V_{in} - 0.7$$

Then we analyze  $M_2$ :

$$\text{Since } V_{GS2} = V_{DS2} \Rightarrow V_{GS2} - V_{TH2} < V_{DS2}$$

$\Rightarrow M_2$  at saturation region


$$\Rightarrow I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TH2})^2$$

$$= I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_{in} + V_{TH2} - V_{TH1})^2$$

$$\Rightarrow 5(V_{in} - 0.7)^2 = (3 - V_{in})^2 \Rightarrow V_{in} = 1.41V$$

$$\text{Meanwhile } 5(V_{in} - 0.7)^2 = (2.3 - V_{out})^2 \Rightarrow V_{out} = -\sqrt{5}V_{in} + C$$
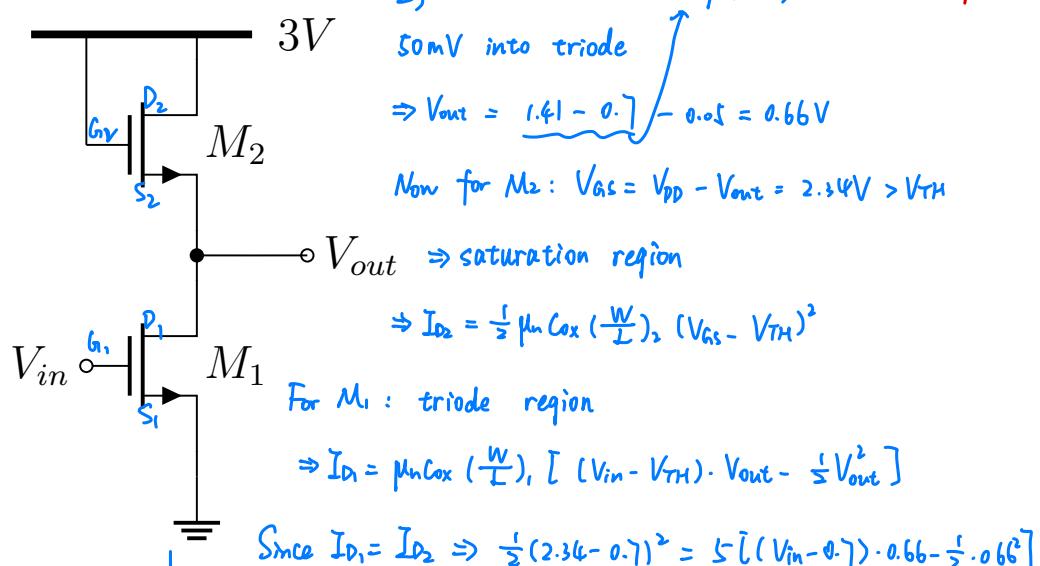
$$\Rightarrow A_V = \frac{\partial V_{out}}{\partial V_{in}} = -\sqrt{5} \quad (C \text{ is constant})$$



$$\text{Then we can get that } V_{in} = 1.4375V$$

$$\text{Meanwhile. } \frac{1}{2}(3 - V_{out} - 0.7)^2 = 5[(V_{in} - 0.7) \cdot V_{out} - \frac{1}{2}V_{out}^2]$$

$$\Rightarrow V_{in} = \frac{(2.3 - V_{out})^2}{10 V_{out}} + \frac{1}{2} V_{out}$$

$$\Rightarrow A_V = \frac{\partial V_{out}}{\partial V_{in}} = -1.93$$

## Question b

1) Edge of triode  $\Rightarrow V_{in} - V_{Th} = V_{out} \wedge V_{in} > V_{Th} = 0.7V$

M2:  $V_{as} = V_{ds} \Rightarrow V_{as} - V_{Th} < V_{ds} \Leftrightarrow$  Saturation Region as long as  $V_{as} > V_{Th}$

$$\Rightarrow I_{D1} = \frac{1}{2} \mu_n Cox \left( \frac{W}{L} \right)_1 (V_{in} - V_{Th})^2 = I_{D2} = \frac{1}{2} \mu_n Cox \left( \frac{W}{L} \right)_2 (V_{dd} - V_{in} + V_{Th} - V_{Th})^2 = \frac{1}{2} \mu_n Cox \left( \frac{W}{L} \right)_2 (V_{dd} - V_{in})^2$$

$$\Rightarrow 5(V_{in} - 0.7)^2 = (3 - V_{in})^2 \Rightarrow V_{in} = 1.41V$$

$$\text{Meanwhile } 5(V_{in} - 0.7)^2 = (2.3 - V_{out})^2 \Rightarrow V_{out} = 2.3 - \sqrt{5}V_{in} + \sqrt{5} \times 0.7$$

$$\Rightarrow Av = \frac{\partial V_{out}}{\partial V_{in}} = -\sqrt{5}$$

a) At triode edge  $V_{out,edge} = 1.41 - 0.7 = 0.71V$

$$\Rightarrow 50mV \text{ into triode } V_{out,into} = 0.71 - 0.05 = 0.66V$$

Now for M2:  $V_{as} = V_{dd} - V_{out,into} = 2.34V > V_{Th} \Rightarrow$  Saturation

$$\Rightarrow I_{D2} = \frac{1}{2} \mu_n Cox \left( \frac{W}{L} \right)_2 (V_{as} - V_{Th})^2$$

For M1: Triode Region

$$\Rightarrow I_{D1} = \mu_n Cox \left( \frac{W}{L} \right)_1 [(V_{in} - V_{Th}) \cdot V_{out,into} - \frac{1}{2} V_{out,into}^2]$$

$$\text{Since } I_{D1} = I_{D2} \Rightarrow \frac{1}{2} (2.34 - 0.7)^2 = 5 [(V_{in} - 0.7) \times 0.66 - \frac{1}{2} \times 0.66^2] \Rightarrow V_{in} = 1.435V$$

$$\text{Meanwhile, } \frac{1}{2} (3 - V_{out} - 0.7)^2 = 5 [(V_{in} - 0.7) \times V_{out} - \frac{1}{2} V_{out}^2]$$

$$V_{in} = \frac{(2.3 - V_{out})^2}{10V_{out}} + \frac{1}{2} V_{out}$$

$$10V_{out}V_{in} = 2.3^2 - 4.6V_{out} + 1.5V_{out}^2$$

$$10 \frac{\partial V_{out}}{\partial V_{in}} + 10V_{in} = 4.6 \frac{\partial V_{out}}{\partial V_{in}} + 3V_{out} \frac{\partial V_{out}}{\partial V_{in}}$$

$$\Rightarrow Av = \frac{\partial V_{out}}{\partial V_{in}} = -1.93$$

### Question 7. Common Source with Resistive Load (Hell)

Assume  $V_{TH} = 0.7 \text{ V}$ ,  $k'_n = 110 \mu\text{A}/\text{V}^2$

Suppose the common-source stage of Fig. 1 is to provide an output swing from 1 V to 2.5 V. Assume that  $(W/L)_1 = 50/0.5$ ,  $R_D = 2\text{k}\Omega$ , and  $\lambda = 0$ .

- 1) Calculate the input voltages that yield  $V_{out} = 1 \text{ V}$  and  $V_{out} = 2.5 \text{ V}$ .
- 2) Calculate the drain current and the transconductance of  $M_1$  for both cases.
- 3) How much does the small-signal gain,  $gm$ ,  $R_D$ , vary as the output goes from 1 V to 2.5 V? (Variation of small-signal gain can be viewed as nonlinearity.)

1)

$$\textcircled{1} \quad V_{out} = 1 \text{ V} \Rightarrow I_D = \frac{V_{DD} - V_{out}}{R_D} = 1 \text{ mA}$$

Assume MOSFET at saturation:

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} k'_n \frac{W}{L} (V_{in} - 0.7)^2 = 10^{-3}$$

$$\Rightarrow V_{in} = 1.126 \text{ V} \Rightarrow V_{GS} - V_{TH} = 0.426 \text{ V} < V_{DS} = 1 \text{ V}$$

$\Rightarrow$  indeed at saturation  $\Rightarrow$  assumption stands


$$\textcircled{2} \quad V_{out} = 2.5 \text{ V} \Rightarrow I_D = \frac{V_{DD} - V_{out}}{R_D} = 0.25 \text{ mA}$$

Assume MOSFET at saturation:

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_{TH})^2 = \frac{1}{2} k'_n \frac{W}{L} (V_{in} - 0.7)^2 = 0.25 \times 10^{-3}$$

$$\Rightarrow V_{in} = 0.9132 \text{ V} \Rightarrow V_{GS} - V_{TH} = 0.2132 \text{ V} < V_{DS} = 2.5 \text{ V}$$

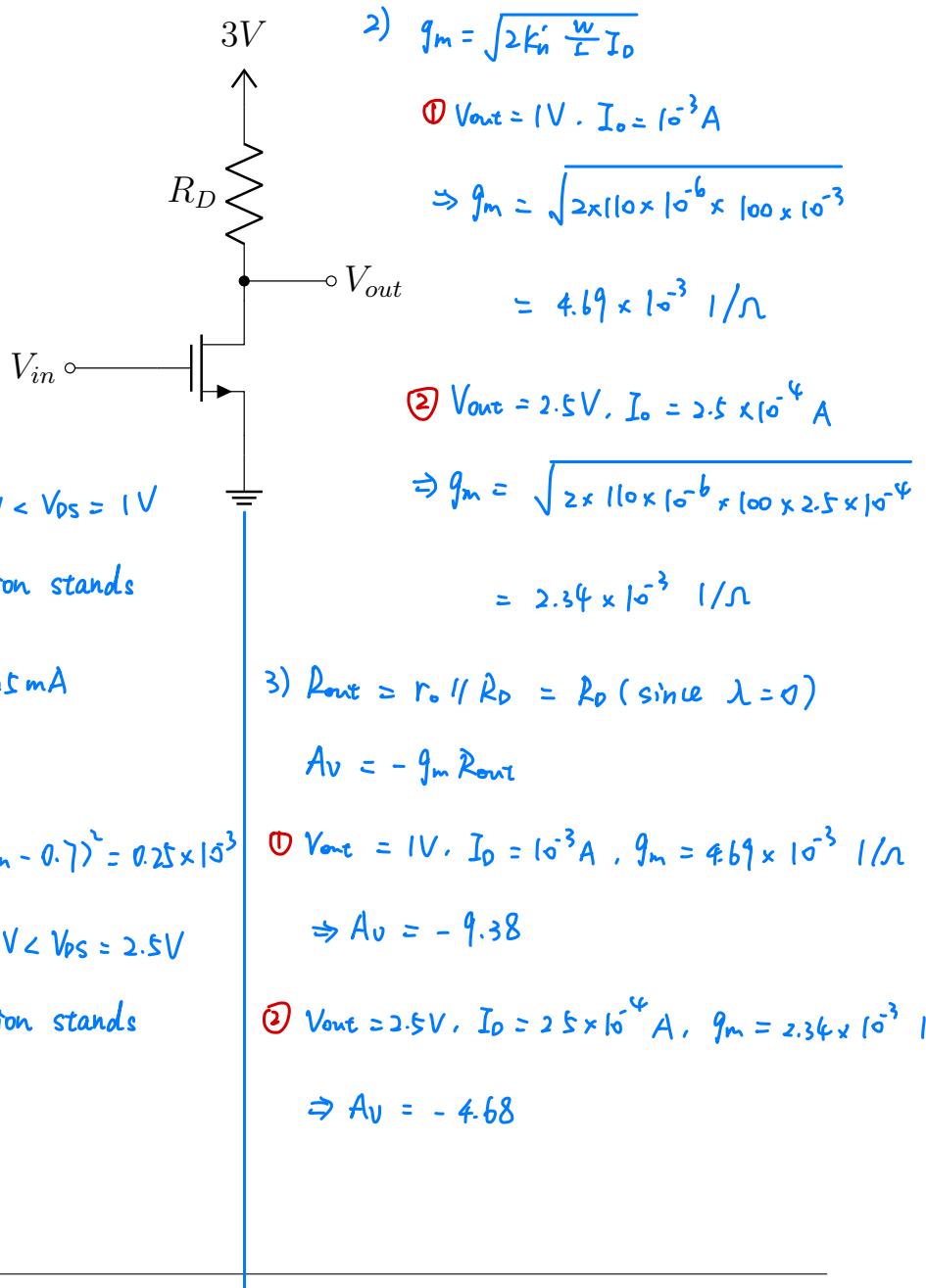$\Rightarrow$  indeed at saturation  $\Rightarrow$  assumption stands



Question 7 If  $V_{Th} = 0.7V$ ,  $K_n' = 110 \mu A/V^2$

$$1) \quad \textcircled{1} \quad V_{out} = 1V \Rightarrow I_D = \frac{V_{DD} - V_{out}}{R_D} = \frac{3-1}{2k} = 1mA$$

$$\text{Assume saturation} \Rightarrow I_D = \frac{1}{2} K_n' \frac{W}{L} (V_{DS} - V_{Th})^2 = \frac{1}{2} \times 110 \times 10^{-6} \times \frac{50}{0.5} (V_{in} - 0.7)^2 = 10^{-3}$$

$$\Rightarrow V_{in} = 1.126V \Rightarrow V_{DS} - V_{Th} = 0.426V < V_{DS} = V_{out} = 1V \text{ indeed in saturation}$$

$$\textcircled{2} \quad V_{out} = 2.5V \Rightarrow I_D = \frac{V_{DD} - V_{out}}{R_D} = \frac{3-2.5}{2k} = 0.5mA$$

$$\text{Assume saturation} \Rightarrow I_D = \frac{1}{2} K_n' \frac{W}{L} (V_{DS} - V_{Th})^2 = \frac{1}{2} \times 110 \times 10^{-6} \times \frac{50}{0.5} (V_{in} - 0.7)^2 = 0.25 \times 10^{-3}$$

$$\Rightarrow V_{in} = 0.9132V \Rightarrow V_{DS} - V_{Th} = 0.2132V < V_{DS} = V_{out} = 2.5V \text{ indeed in saturation}$$

$$\textcircled{3} \quad g_m = \sqrt{2k K_n' \frac{W}{L} I_D}$$

$$\textcircled{1} \quad V_{out} = 1V, I_D = 10^{-3}A \Rightarrow g_m = \sqrt{2 \times 110 \times 10^{-6} \times \frac{50}{0.5} \times 10^{-3}} = 4.69 \times 10^{-3} A/V$$

$$\textcircled{2} \quad V_{out} = 2.5V, I_D = 2.5 \times 10^{-4}A \Rightarrow g_m = \sqrt{2 \times 110 \times 10^{-6} \times \frac{50}{0.5} \times 2.5 \times 10^{-4}} = 2.34 \times 10^{-3} A/V$$

$$\textcircled{3} \quad R_{out} = r_{01} \parallel R_D = \frac{1}{2I_D} \parallel R_D \xrightarrow{\lambda=0} R_D$$

$$Av = -g_m R_{out}$$

$$\textcircled{1} \quad V_{out} = 1V, I_D = 10^{-3}A, g_m = 4.69 \times 10^{-3} A/V$$

$$\Rightarrow Av = -g_m R_D = -9.38$$

$$\textcircled{2} \quad V_{out} = 2.5V, I_D = 2.5 \times 10^{-4}A, g_m = 2.34 \times 10^{-3} A/V$$

$$\Rightarrow Av = -g_m R_{out} = -4.68$$