
VE311 Electronic Circuit Homework 2



Due: June 4th

Note:

- 1) Please use A4 size paper or page.
- 2) Please clearly state out your final result for each question.
- 3) Please attach the screenshot of Pspice simulation result if necessary.


Question 1. Diode Circuit Exercise 1

Find the values of I and V in the circuits shown below.

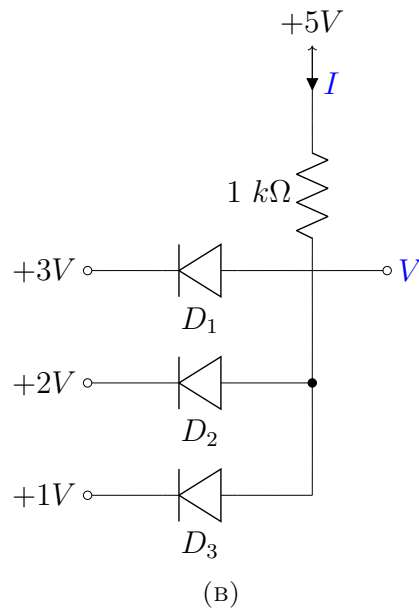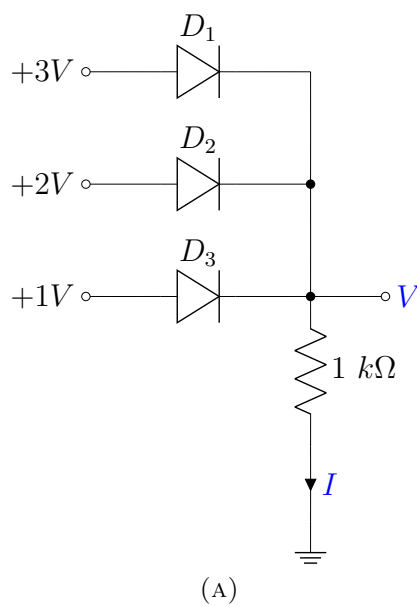

Question 2. Diode Circuit Exercise 2

In the following problem, D_1 has 10 times the junction area of D_2 . What value of V results?
To obtain a value for V of 60mV, what current I_2 is needed.

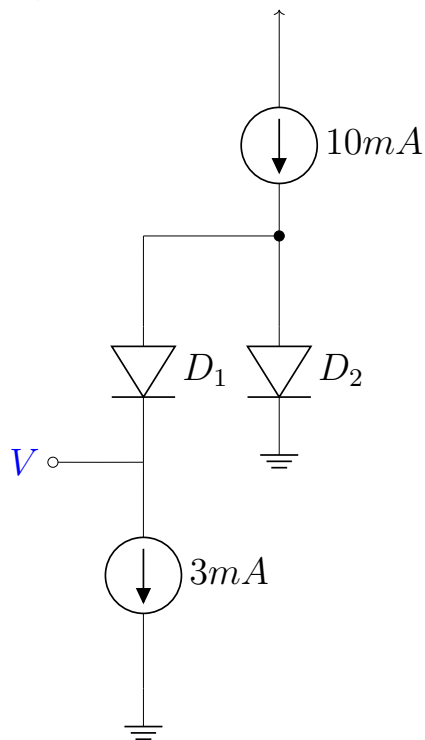


Question 3. Voltage Regulator

A voltage regulator consisting of two diodes in series fed with a constant-current source is used as a replacement for a single carbon-zinc cell (battery) of nominal voltage 1.5 V. The regulator load current varies from 2 mA to 7 mA. Constant-current supplies of 5 mA, 10 mA, and 15 mA are available. Which would you choose, and why? What change in output voltage would result when the load current varies over its full range?

Question 4. Half-Wave Rectifier

Design a half-wave rectifier circuit, such as below, which can convert a sinusoidal voltage input, $V_s = 5 \sin(2\pi 100 \cdot \text{time})$, to an almost constant voltage output.

- 1) Assuming $V_{\text{on}} = 0.9 \text{ V}$ and $R = 100\Omega$, calculate C which makes the ripple voltage (V_r) is smaller than 0.1 V . Estimate V_{dc} , I_{dc} , θ_c , ΔT , I_{peak} , I_{surge} and PIV of the designed half-wave rectifier.
- 2) Plot V_s and V_{out} versus time on the sample graph.

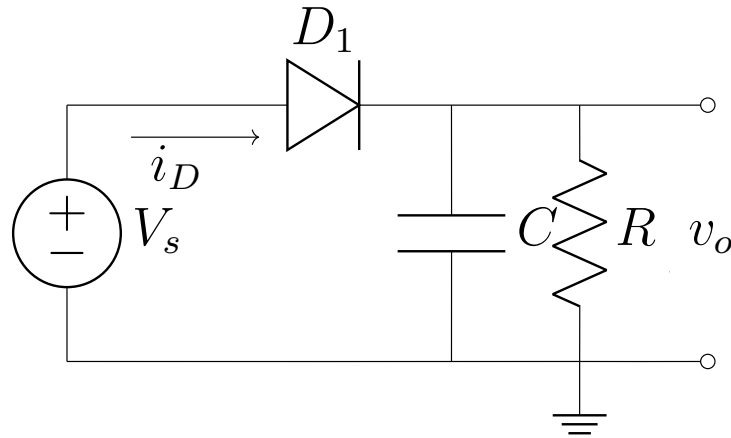

Question 5. Full-Wave Bridge Rectifier

Design a full-wave bridge rectifier circuit, such as below, which can convert a sinusoidal voltage input, $V_s = 5 \sin(2\pi 100 \cdot \text{time})$, to an almost constant voltage output.

- 1) Assuming $V_{on} = 0.9 \text{ V}$ and $R = 100\Omega$, calculate C which makes the ripple voltage (V_r) smaller than 0.1 V . Estimate V_{dc} , I_{dc} , θ_c , ΔT , I_{peak} , I_{surge} and PIV of the designed full-wave bridge rectifier.
- 2) Plot V_s (using "voltage differential marker" function) and V_{out} versus time on the sample graph.

