



Lecture 23: General Time Constant Approach

VE311 Electronic Circuits

Xuyang Lu
2023 Summer



上海交通大學
SHANGHAI JIAO TONG UNIVERSITY



Recap of Last Lecture

- Bandwidth estimation:
 - Solving for KCL and KVL
 - Miller effect + Pole associated with nodes



Topic to be Covered

- General Time constant approach

$$\omega_{p,A} = \frac{1}{R_S \left[C_{GS1} + \left(1 + \frac{gm_1}{gm_2 + gmb_2} \right) C_{GD1} \right]} \quad (1)$$

$$\omega_{p,X} = \frac{1}{\frac{1}{gm_2+gmb_2} \left[C_{DB1} + C_{SB2} + C_{GS2} + \left(1 + \frac{gm_2+gmb_2}{gm_1} \right) C_{GD1} \right]} \quad (2)$$

$$\omega_{p,Y} = \frac{1}{R_D [C_{GD2} + C_{DB2} + C_L]} \quad (3)$$

$$\frac{v_{\text{out}}}{v_{\text{in}}} = -gm_1 R_D \frac{1}{\left(1 + \frac{S}{\omega_{p,A}}\right) \left(1 + \frac{S}{\omega_{p,X}}\right) \left(1 + \frac{S}{\omega_{p,Y}}\right)} \quad (4)$$

Cascode


Recall for CS stages:

$$\omega_{in} = \frac{1}{R_S [C_{GS} + (1 + g_{m1} R_D) C_{GD}]} \quad (5)$$



SHANGHAI JIAO TONG UNIVERSITY

Cascode

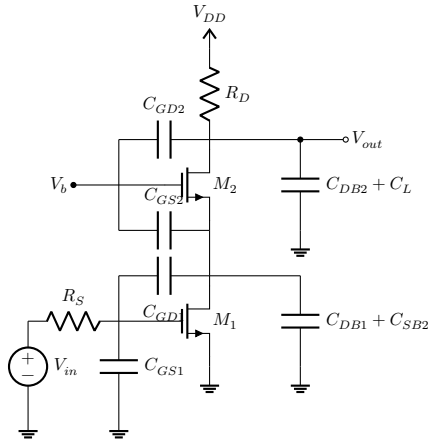

First Order Systems

Read 10.1 and 10.4 for BJTs of Sedra Smith (OCTC & SCTC for UM VE311).
Hajimiri for General Method

- No energy is store in the circle. In general, a one pole one zero system
- $H(S) = \frac{a_0+a_1S}{1+bS}$

First Order Systems

- The low frequency is represented by a_0
- $a_0 = H(s) |_{c_1=0} = H^\circ$
- The time constant determines b_1 (This is the pole of the system)
- $b_1 = \tau = RC_1$
- The ratio of a_0 and a_1 determines the location of the zero

First Order Systems

$$H(s) = \frac{a_0 + a_1s + a_2s^2 + \cdots + a_ms^m}{1 + b_1s + b_2s^2 + \cdots + b_ns^n} = a_0 \cdot \frac{\left(1 - \frac{s}{z_1}\right) \left(1 - \frac{s}{z_2}\right) \cdots \left(1 - \frac{s}{z_m}\right)}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \cdots \left(1 - \frac{s}{p_n}\right)} \quad (6)$$

$$b_1 = -\sum_i \frac{1}{p_i} \quad (7)$$

$$b_1 = -\sum_i \frac{1}{p_i} \quad (10)$$

$$b_2 = \sum_i \sum_{j \atop i < j} \frac{1}{p_i p_j} \quad (8)$$

$$b_2 = \sum_i \sum_{j \atop i < j} \frac{1}{p_i p_j} \quad (11)$$

$$b_n = \frac{(-1)^n}{p_1 p_2 \cdots p_n} \quad (9)$$

$$b_n = \frac{(-1)^n}{p_1 p_2 \cdots p_n} \quad (12)$$


First Order Systems

- $H(S) = \frac{a_0 + a_1 S}{1 + bS}$
- $H_i(s) = \frac{a_0 + \alpha_1^i C_i s}{1 + \beta_1^i C_i s}$
- (It is easy to convince ourselves that a_1 is also related to the capacitor. For a capacitor, $1/j\omega C$ means C and S always come together.)
- The transfer function shall be valid for all capacitor values including zero and infinity.
- the first denominator coefficient b_1 , is simply given by the sum of these zero-value time constants (ZVT)
- $b_1 = \sum_{i=1}^N \tau_i^0$

First Order Systems

- $H_i(s) = \frac{a_0 + \alpha_1^i C_i s}{1 + \beta_1^i C_i s}$ If C_i goes to ∞ , $H(s) = \frac{\alpha_1}{\beta_1}$
- $H(s) = \frac{H^0 + H^1 \tau S}{1 + \tau S}$
- If it is an inductor, $\tau = \frac{L_1}{R_0}$
- To find the time constant, remove the cap/ind nulling all the sources, find the resistance.
- To find transfer constant H^0 , it is just the low frequency gain.
- To find the transfer constant H^1 , we look into high frequency response, so the cap shall be shorted. For inductor it is the opposite.

First Order Systems

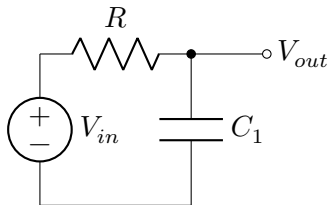


$$H^0 = 1 \quad (13)$$

$$\tau = RC_1 \quad (14)$$

$$H^1 = 0 \quad (15)$$


$$H(s) = \frac{1}{1 + RCS} \quad (16)$$

First Order Systems

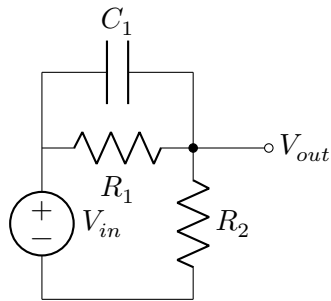

- We do zero frequency response to find out H^0
- $H^0 = \frac{R_2}{R_1 + R_2}$
- We null sources to find τ_1
- $\tau_1 = (R_1 \parallel R_2) C_1$
- We short circuit to find H^1
- $H^1 = 1$
- $H(S) = \frac{R_2}{R_1 + R_2} \frac{1 + R_2 C_1 S}{1 + (R_1 \parallel R_2) C_1 S}$


First Order Systems

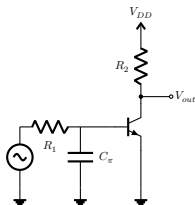

$$H^0 = -\frac{r_\pi}{R_1 + r_\pi} g_m R_2 \quad (17)$$

$$\tau = (R_1 \parallel r_\pi) C_\pi \quad (18)$$


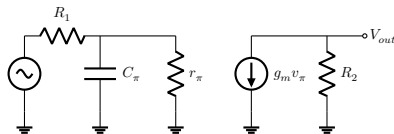
If there is a zero in the system, then we can test it with a shorted cap / open ind and see if the output still have some value.





$$H^\pi = 0 \quad (19)$$

$$H(S) = \frac{H^0}{1 + \tau S} \quad (20)$$

MOSFET T Model

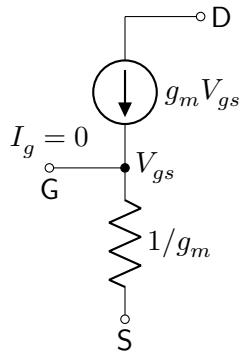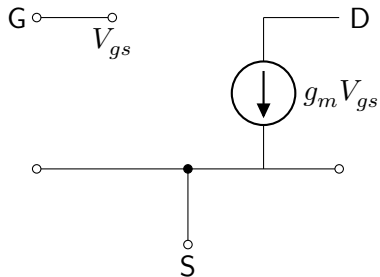


First Order Source Follower

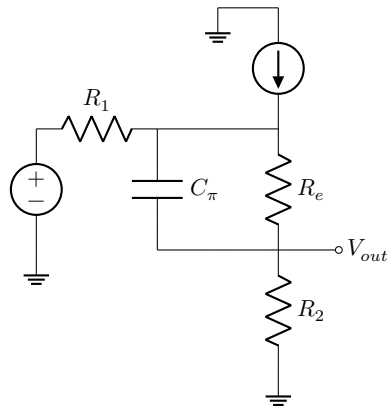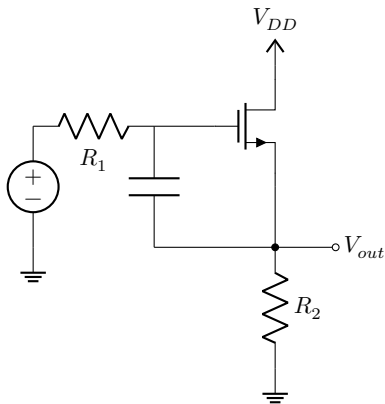

First Order Source Follower

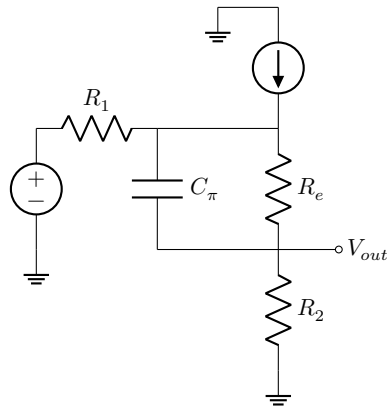- Low frequency, $V_x = V_{in}$
- V_{out} is voltage divider,
- $H^0 = \frac{R_2}{R_2 + r_e}$ (assume it's a BJT)
- $H^1 = \frac{R_2}{R_2 + r_1}$
- $R_2(g_m v_x - i_x) + v_x = R_1 i_x$
- $R = \frac{R_1 + R_2}{1 + g_m R_2}$
- You can imagine the existence of a zero and a pole.





First Order Source Follower

$$H(s) = \frac{R_2}{R_2 + R_e} \cdot \frac{1 + \frac{R_e + R_2}{R_1 + R_2} \cdot \frac{R_1 + R_2}{1 + g_e R_2} C_\pi S}{1 + R_\pi^0 C_\pi S} \quad (21)$$

$$= \frac{R_2}{R_2 + r_e} \cdot \frac{1 + r_e C_\pi S}{1 + R_\pi^0 C_\pi S} \quad (22)$$


- $Z = -\frac{g_m}{C_\pi}$ @ high frequency
- $P = -\frac{1}{R_\pi^0 C_\pi}$ @ high frequency
- Therefore, source follower is quite wide band

First Order Common Source

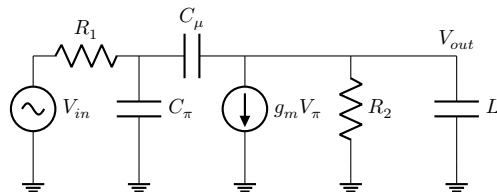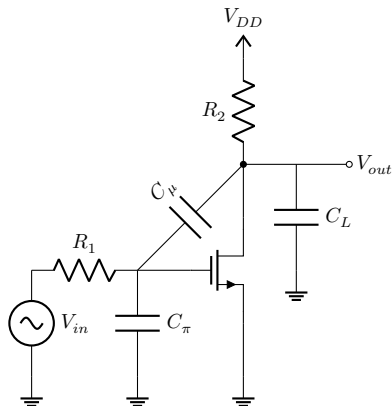

First Order Common Source

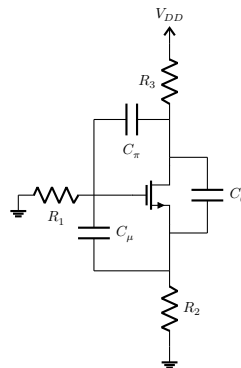- $R_{\pi}^0 = r_{\pi} \parallel \frac{R_1 + R_2}{1 + g_m R_2}$
- $R_{\mu}^0 = R_{\text{left}} + R_{\text{right}} + G_m R_{\text{left}} R_{\text{right}}$
- For BJT we have
 $R_{\text{left}} = R_B \parallel [r_{\pi} + (1 + \beta)R_E]$
- $R_{\text{right}} = R_3$
- $G_m = \frac{g_m}{1 + g_m R_2}$
- $R_{\theta}^0 \approx \frac{R_2 + R_3}{1 + g_m R_2}$
- $b_1 = \sum_{i=1}^N \tau_i^0$



First Order Common Source

$$R_{\theta}^0 \approx \frac{R_2 + R_3}{1 + g_m R_2} \quad (23)$$

First Order Common Source



$$R_{\text{left}} = R_B \parallel [r_{\pi} + (1 + \beta)R_E] \quad (24)$$

First Order Common Source

```
.model Q2N696 NPN (Is=14.34f Xti=3 Eg=1.11 Vaf=74.03 Bf=65.62 Ne=1.208  
Ise=19.48f Ikf=.2385 Xtb=1.5 Br=9.715 Nc=2 Isc=0 Ikr=0 Rc=1 Cjc=9.393p  
Mjc=.3416 Vjc=.75 Fc=.5 Cje=22.01p Mje=.377 Vje=.75 Tr=58.98n Tf=408.8p  
Itf=.6 Vtf=1.7 Xtf=3 Rb=10)  
.model NPN NPN  
.model PNP PNP  
cje Zero bias B-E depletion capacitance
```

First Order Common Source

We can use those parameters to determine small signal parameters. a collector current of 1mA which give you a $Gm = 40mS$ $\beta_0 = 100$

$$C_{\pi} = C_{je} + C_b = 100fF \quad (25)$$

$$r_{\pi} = \frac{\beta + 1}{gm} = \frac{101}{40} \approx 2500\Omega \quad (30)$$

$$C_L = C_{out} + C_{js} = 200fF \quad (26)$$

$$R_{left} = R_B \parallel [r_{\pi} + (1 + \beta)R_E] = \quad (31)$$

$$C_u = g_m \tau_F = 16fF \quad (27)$$

$$1K \parallel (2.5K + (101) \cdot 0) = 0.7K \quad (32)$$

$$R_1 = 1K\Omega \quad (28)$$

$$R_{\mu}^0 = R_{left} + R_{right} + G_m R_{left} R_{right} \quad (33)$$

$$R_2 = 1K\Omega \quad (29)$$

$$= 0.7K + 2K + 40e-3 \cdot 0.7K \cdot 2K \quad (34)$$

First Order Common Source

$$b_1 = \sum_i \tau_i^0 = \tau_\pi^0 + \tau_\mu^0 + \tau_L^0 \quad (35)$$


$$H^0 = -57 \quad (36)$$

$$\tau_\pi^0 \approx 70\text{ps} \quad \tau_\mu^0 \approx 1000\text{ps} \quad \tau_L^0 = 400\text{ps} \quad (37)$$

$$\omega_h \approx 1/b_1 \approx 2\pi \cdot 95\text{MHz} \quad (38)$$

- This allows you to determine the lowest operating frequency, and also the contribution of each nodes in the circuit.

Practice on BJT Case

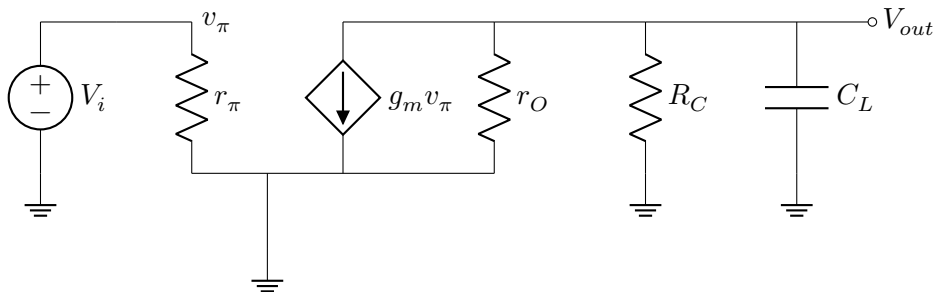

Practice on BJT Case

$$g_m v_i + \frac{v_0}{r_0 \parallel R_c} + v_0 SC_L = 0 \quad (39)$$

$$g_m v_i + v_0 \frac{1 + r_0 \parallel R_c SC_L}{r_0 \parallel R_c} = 0 \quad (40)$$

$$v_0 = -g_m \frac{r_0 \parallel R_c}{1 + r_0 \parallel R_c SC_L} v_i \quad (41)$$

- Single pole at :
- Often $r_O \gg RC$