

VE311 Electronic Circuit Homework 2


Due: June 4th

Note:


- 1) Please use A4 size paper or page.
- 2) Please clearly state out your final result for each question.
- 3) Please attach the screenshot of Pspice simulation result if necessary.

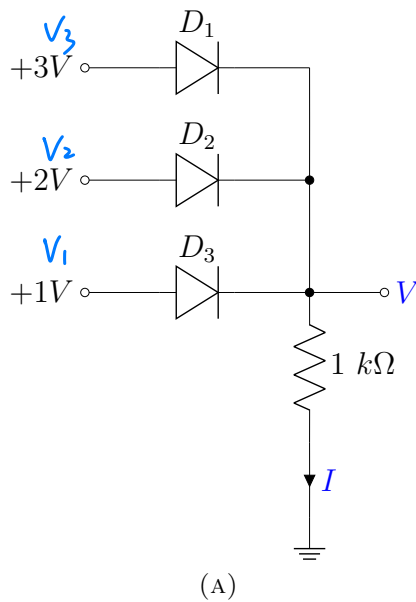Question 1. Diode Circuit Exercise 1 (ideal model)

Find the values of I and V in the circuits shown below.



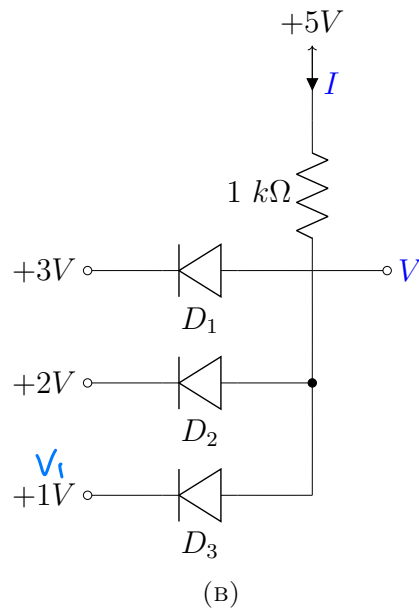① If $V < 3V$,
then $V = V_3 = 3V$
which is impossible
② If $V > 3V$
then no current
which is also impossible
 $\Rightarrow V = 3V$
 $I = 3mA$



① If $V > 1V$,
then $V = V_1 = 1V$.
which is impossible
② If $V < 1V$,
then there is no current
which is also impossible
 $\Rightarrow V = 1V$
 $I = 4mA$

Question 2. Diode Circuit Exercise 2 (exponential model)

In the following problem, D_1 has 10 times the junction area of D_2 . What value of V results?
To obtain a value for V of 60mV, what current I_2 is needed.

$$I_{D1} = I_{S1} \cdot (e^{\frac{qV_1}{kT}} - 1)$$

$$I_{D2} = I_{S2} \cdot (e^{\frac{qV_2}{kT}} - 1)$$


$$\Rightarrow \frac{I_{D1}}{I_{D2}} = 10 \frac{e^{\frac{qV_1}{kT}} - 1}{e^{\frac{qV_2}{kT}} - 1}$$

$$\approx 10 e^{\frac{q}{kT}(V_1 - V_2)}$$

① here $I_{D1} = 3mA$
and $I_{D2} = 7mA$

$$\Rightarrow \frac{3}{7} = 10 e^{(V_1 - V_2)/0.026}$$
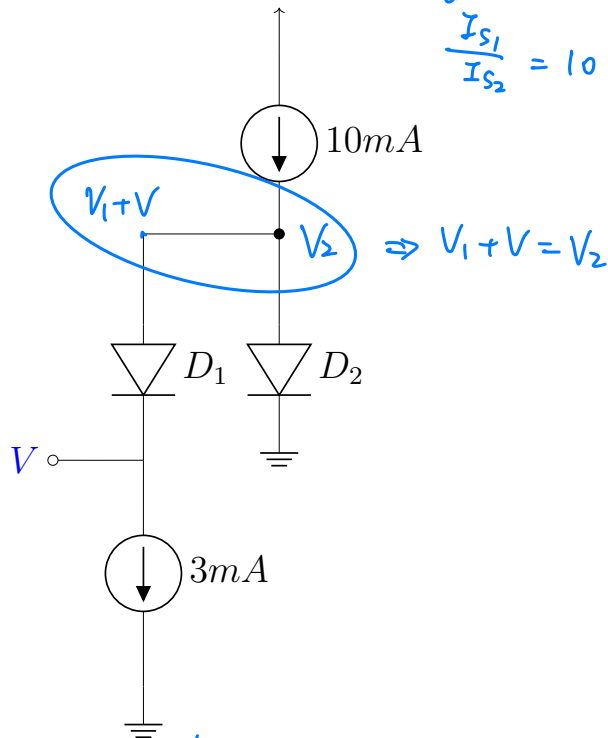
$$\Rightarrow \frac{3}{70} = e^{-V/0.026} \Rightarrow V = 81.8 \text{ mV}$$



② If we want $V = 60mV$


$$\text{then } \frac{I_{D2}}{10 - I_{D2}} = \frac{1}{10} e^{60 \times 10^{-3} / 0.026} \quad (= \frac{I_{D2}}{I_{D1}})$$

$$\Rightarrow I_{D2} = 5.013 \text{ mA}$$

$$\Rightarrow I_{D1} = 10 - I_{D2} = 4.987 \text{ mA}$$

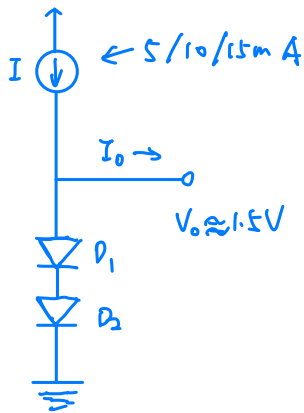Question 3. Voltage Regulator

A voltage regulator consisting of two diodes in series fed with a constant-current source is used as a replacement for a single carbon-zinc cell (battery) of nominal voltage 1.5 V. The regulator load current varies from 2 mA to 7 mA. Constant-current supplies of 5 mA, 10 mA, and 15 mA are available. Which would you choose, and why? What change in output voltage would result when the load current varies over its full range?



since I_0 varies from 2mA to 7mA $\Rightarrow I > 7mA \Rightarrow I = 10mA / 15mA$

$$\textcircled{1} I_0 = 2mA : I_S \cdot e^{\frac{qV_1}{2kT}} = I - 2 \times 10^{-3}$$

$$\textcircled{2} I_0 = 7mA : I_S \cdot e^{\frac{qV_2}{2kT}} = I - 7 \times 10^{-3}$$

$$\Rightarrow e^{\frac{q}{2kT}(V_1 - V_2)} = \frac{I - 2 \times 10^{-3}}{I - 7 \times 10^{-3}}$$

$$\Rightarrow V_1 - V_2 = \frac{2kT}{q} \ln \left(\frac{I - 2 \times 10^{-3}}{I - 7 \times 10^{-3}} \right)$$

$$\text{when } I = 10mA, V_1 - V_2 = 0.05V$$

$$\text{when } I = 15mA, V_1 - V_2 = 0.055V$$

\Rightarrow choose $I = 10mA$ to minimize $\frac{\partial V}{\partial I}$ since

we want to obtain a battery of nominal voltage 1.5V

Question 4. Half-Wave Rectifier

Design a half-wave rectifier circuit, such as below, which can convert a sinusoidal voltage input, $V_s = 5 \sin(2\pi 100 \cdot \text{time})$, to an almost constant voltage output.

- 1) Assuming $V_{on} = 0.9 \text{ V}$ and $R = 100\Omega$, calculate C which makes the ripple voltage (V_r) is smaller than 0.1 V . Estimate V_{dc} , I_{dc} , θ_c , ΔT , I_{peak} , I_{surge} and PIV of the designed half-wave rectifier.
- 2) Plot V_s and V_{out} versus time on the sample graph.

$$1) T = \frac{2\pi}{2\pi \cdot 100} = 0.01 \text{ s}$$

$$V_s - V_{on} = 5 - 0.9 \text{ V} \\ = 4.1 \text{ V}$$

$$\Rightarrow V_r = 4.1 \cdot \frac{0.01}{100 \cdot C}$$

$$\text{when } V_r \leq 0.1 \Rightarrow C \geq \frac{0.41}{100} = 4.1 \times 10^{-3} \text{ F}$$

$$V_{dc} = V_s - V_{on} = 4.1 \text{ V}$$

$$I_{dc} = \frac{4.1 \text{ V}}{100 \Omega} = 0.041 \text{ A}$$


$$\theta_c = \sqrt{\frac{2V_r}{V_s}} = \sqrt{\frac{0.2}{5}} = 0.2$$

$$\Delta T = \frac{0.2}{2\pi \cdot 100} = \frac{10^{-3}}{\pi}$$

$$I_{peak} = 2 \frac{I_{dc} T}{\Delta T} = 2 \cdot \frac{0.041 \cdot 0.01}{\frac{10^{-3}}{\pi}} = 0.82\pi$$



$$I_{surge} = 2\pi \cdot 100 \cdot 4.1 \times 10^{-3} \cdot 5 = 4.1\pi$$

$$PIV = 2V_s - V_{on} = 9.1 \text{ V}$$

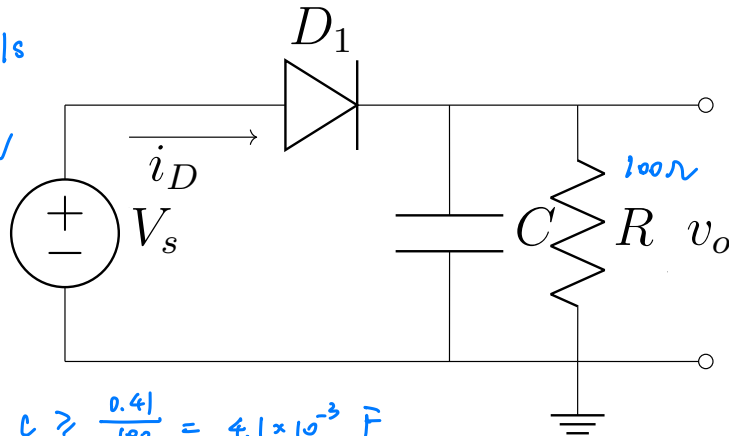

2)


V_s :

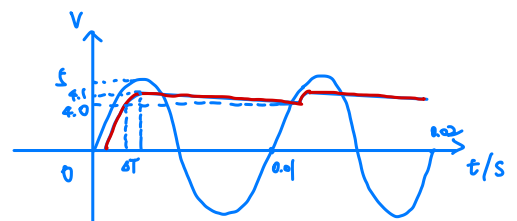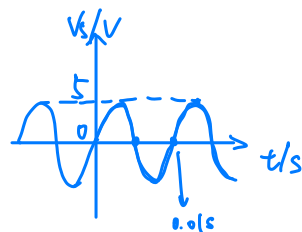

Question 5. Full-Wave Bridge Rectifier

Design a full-wave bridge rectifier circuit, such as below, which can convert a sinusoidal voltage input, $V_s = 5 \sin(2\pi 100 \cdot \text{time})$, to an almost constant voltage output.

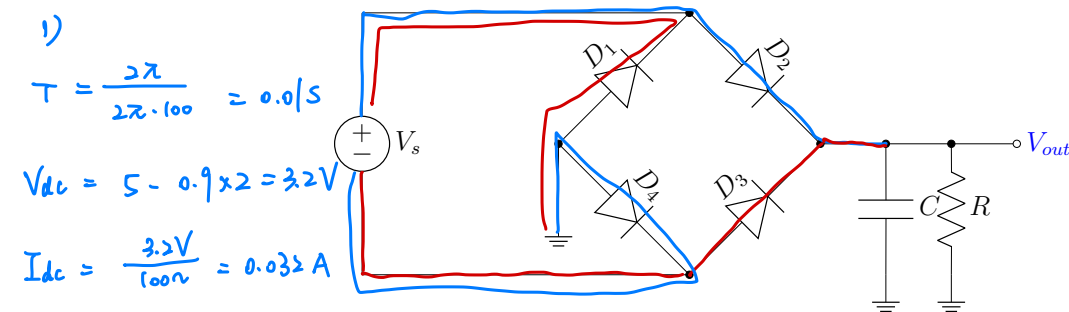- 1) Assuming $V_{on} = 0.9 \text{ V}$ and $R = 100\Omega$, calculate C which makes the ripple voltage (V_r) smaller than 0.1 V . Estimate V_{dc} , I_{dc} , θ_c , ΔT , I_{peak} , I_{surge} and PIV of the designed full-wave bridge rectifier.
- 2) Plot V_s (using "voltage differential marker" function) and V_{out} versus time on the sample graph.



$$V_r = V_{dc} \cdot \frac{T}{2RC} = 3.2 \cdot \frac{0.01}{200 \cdot C}$$

if $V_r \leq 0.1$, then $C \geq 1.6 \times 10^{-3} \text{ F}$

$$\theta_c = \sqrt{\frac{2V_r}{V_s}} = \sqrt{\frac{0.2}{5}} = 0.2$$

$$\Delta T = \frac{\theta_c}{\omega} = \frac{1}{200\pi} \cdot 0.2 = \frac{10^{-3}}{\pi}$$

$$I_{peak} = \frac{I_{dc} T}{\Delta T} = \frac{0.032 \cdot 0.01 \cdot \pi}{10^{-3}} = 1.005 \text{ A}$$

$$I_{surge} = \omega C \cdot V_s = 2\pi \cdot 100 \cdot 1.6 \times 10^{-3} \cdot 5 = 5.03 \pi$$

$$PIV = V_s - V_{on} = 5 - 0.9 = 4.1 \text{ V}$$

2)
 V_s :

V_s :

