

VE311 Mid Review - Op Amp

Zeyu Zhang

University of Michigan-Shanghai Jiao Tong University Joint Institute


June 28, 2023




JOINT INSTITUTE
交大密西根学院

1 Op Amp

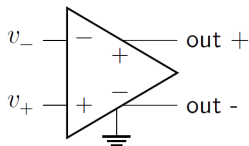- ▶ Op Amp is a nonlinear circuit element
 - ▶ Low input signal \rightarrow Linear
 - ▶ High input signal \rightarrow Saturation
 - ▶ Op Amp \Leftrightarrow Differential & Single-ended amplifier
- Single-ended: the output appears between terminal 3 and ground (not differential)



Differential Amplifier

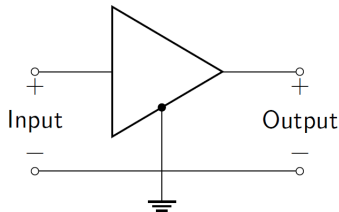

single-ended Amplifier

An amplifier receives a signal from a source and delivers it to a load. Gains are dimensionless, and are usually expressed in terms of decibels (dB):

$$A_v = \frac{v_o}{v_i} \quad (1)$$

$$A_v(dB) = 20 \log A_v \quad (4)$$

$$A_i = \frac{i_o}{i_i} \quad (2)$$


$$A_i(dB) = 20 \log A_i \quad (5)$$

$$A_p = A_v A_i \quad (3)$$

$$A_p(dB) = 10 \log A_p \quad (6)$$


Ideal op amp

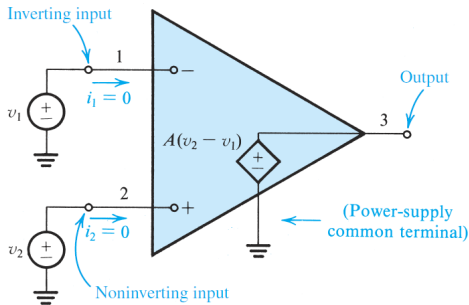- ▶ Infinite input impedance
- ▶ Zero output impedance
- ▶ Zero common-mode gain or, equivalently, infinite common-mode rejection
- ▶ Infinite open-loop gain A
- ▶ Infinite bandwidth



$$v_{Id} = v_2 - v_1 \quad v_{Icm} = \frac{1}{2}(v_1 + v_2) \quad (7)$$

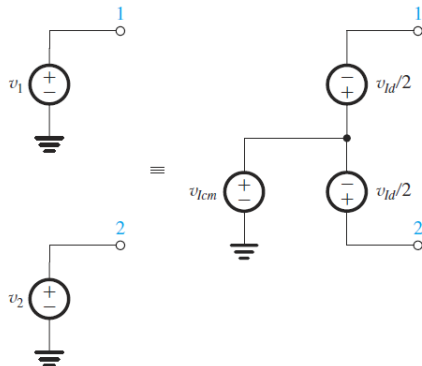
$$v_1 = v_{Icm} - \frac{v_{Id}}{2} \quad v_2 = v_{Icm} + \frac{v_{Id}}{2} \quad (8)$$



The inverting configuration

Determine the closed-loop gain using virtual ground ($v_- = v_+ = 0$)


$$v_O = -\frac{R_2}{R_1} v_I \quad (9)$$

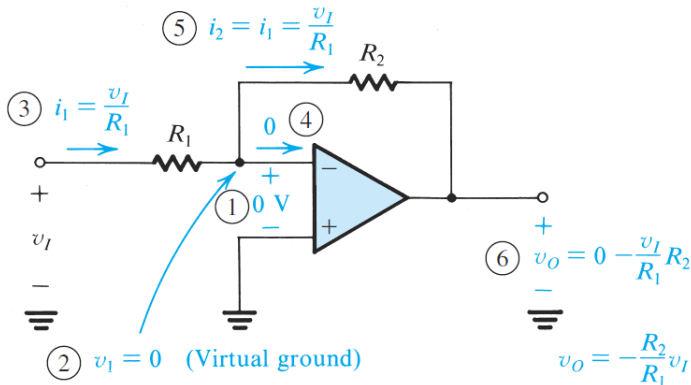

Hw3 Question 2


The Weighted Summer
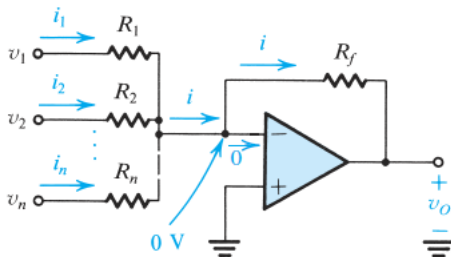
$$v_O = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \cdots + \frac{R_f}{R_n} v_n \right) \quad (10)$$



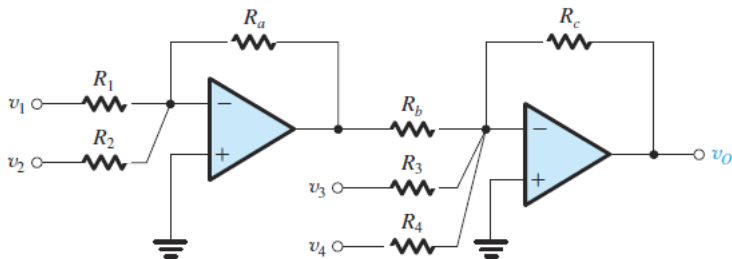
Exercise

$R_1 = 5\text{k}\Omega$, $R_2 = 10\text{k}\Omega$, $R_a = 10\text{k}\Omega$, $R_b = 10\text{k}\Omega$, $R_3 = 2.5\text{k}\Omega$, $R_c = 10\text{k}\Omega$, $R_4 = 10\text{k}\Omega$, determine v_O



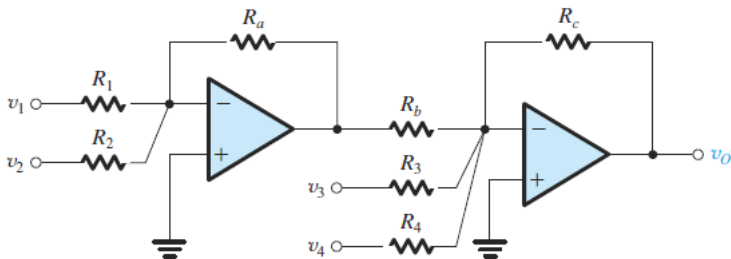Exercise


$R_1 = 5\text{k}\Omega$, $R_2 = 10\text{k}\Omega$, $R_a = 10\text{k}\Omega$, $R_b = 10\text{k}\Omega$, $R_3 = 2.5\text{k}\Omega$, $R_c = 10\text{k}\Omega$, $R_4 = 10\text{k}\Omega$, determine v_O



Solution: $v_O = 2v_1 + v_2 - 4v_3 - v_4$

The noninverting configuration


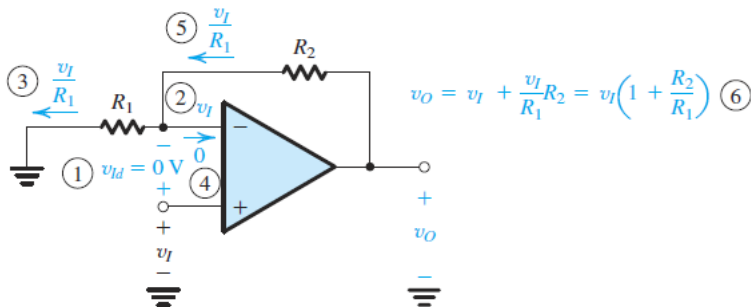
$$v_O = v_I \left(1 + \frac{R_2}{R_1} \right) \quad (11)$$



The voltage follower


A special noninverting case such that $R_1 = \infty$ and $R_2 = 0$

$$v_O = v_I \quad (12)$$

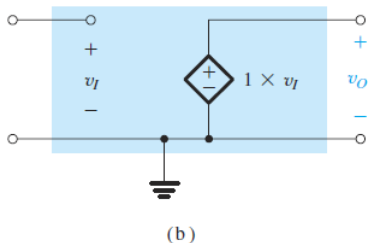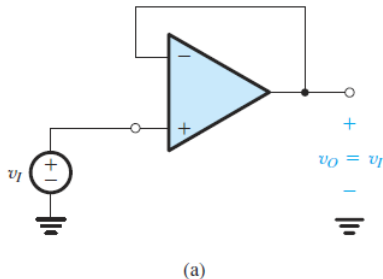

$$v_O = A_d v_{Id} + A_{cm} v_{Icm} \quad (13)$$

$$\text{CMRR} = 20 \log \frac{|A_d|}{|A_{cm}|} \quad (14)$$

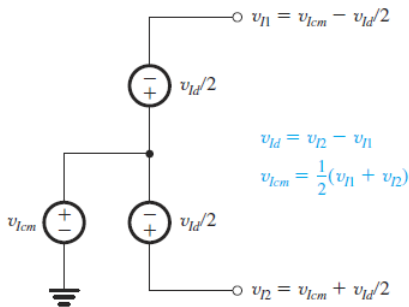


Difference Amplifier

Inverting part + noninverting part + voltage divider (superposition)

$$\frac{R_4}{R_4 + R_3} \left(1 + \frac{R_2}{R_1} \right) = \frac{R_2}{R_1} \quad (15)$$
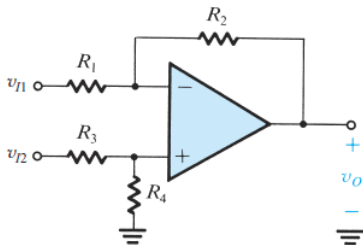
$$\frac{R_4}{R_3} = \frac{R_2}{R_1} \quad (16)$$



The differential gain

$$A_d = \frac{v_O}{v_{Id}} = \frac{R_2}{R_1} \quad (17)$$


What about the common-mode gain A_{cm} ?

$$A_{cm} \equiv \frac{v_O}{v_{Icm}} = \left(\frac{R_4}{R_4 + R_3} \right) \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right) \quad (18)$$

The Instrumentation Amplifier

Two noninverting (A_1, A_2) + difference amplifier (A_3)
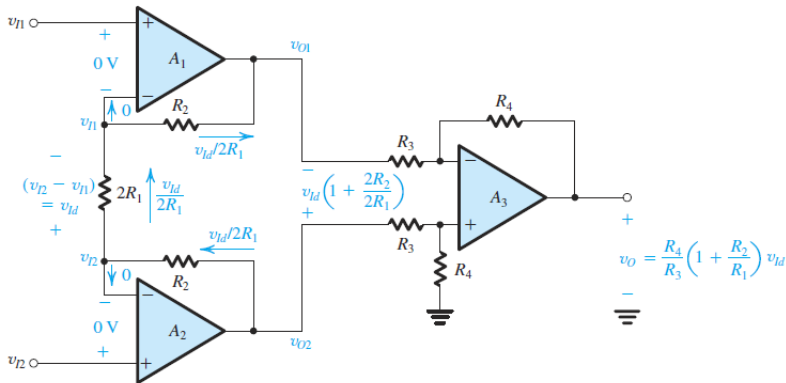
$$v_O = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1} \right) v_{Id} \quad (19)$$



Hw3 Question 3

Inverting & Noninverting (Finite gain)

Inverting:

$$G \equiv \frac{v_O}{v_I} = \frac{-R_2/R_1}{1 + (1 + R_2/R_1)/A} \quad (20)$$

Noninverting:

$$G \equiv \frac{v_O}{v_I} = \frac{1 + (R_2/R_1)}{1 + \frac{1 + (R_2/R_1)}{A}} = \frac{A}{1 + A\beta} \quad (21)$$

where $\beta = \frac{R_1}{R_1 + R_2}$ is called the feedback factor.

Output resistance (both inverting and noninverting):

$$R_{out} = \frac{R_o}{1 + A\beta} \parallel (R_1 + R_2) \quad (22)$$

Input resistance (noninverting):

$$R_{in} = R_{id}(1 + A\beta) \quad (23)$$

Input resistance (inverting):

$$R_{in} = R_1 + R_{id} \parallel \left(\frac{R_2}{1 + A} \right) \quad (24)$$

Hw3 Question 4

Voltage follower (Finite gain)

$$v_{Id} = v_I - v_O \quad v_{Icm} = \frac{v_I + v_O}{2} \quad (25)$$


$$v_O = A_d v_{Id} + A_{cm} v_{Icm} \quad (26)$$

$$v_O = A_d \left[(v_I - v_O) + \frac{v_I + v_O}{2CMRR} \right] \quad (27)$$

$$A_v = \frac{v_O}{v_I} = \frac{A_d \left[1 + \frac{1}{2CMRR} \right]}{1 + A_d \left[1 - \frac{1}{2CMRR} \right]} \quad (28)$$

Input offset voltage V_{OS} , usually $1\text{mV} \leq V_{OS} \leq 5\text{mV}$

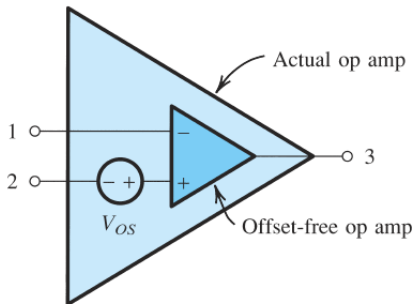Exercise: Use the model below to sketch the transfer characteristic v_O versus v_{Id} ($v_O = v_3$ and $v_{Id} = v_2 - v_1$) of an op amp having an open-loop dc gain $A_0 = 10^4 \text{ V/V}$, output saturation levels of $\pm 10\text{V}$, and V_{OS} of $+5\text{mV}$.



Transfer characteristic

Solution:


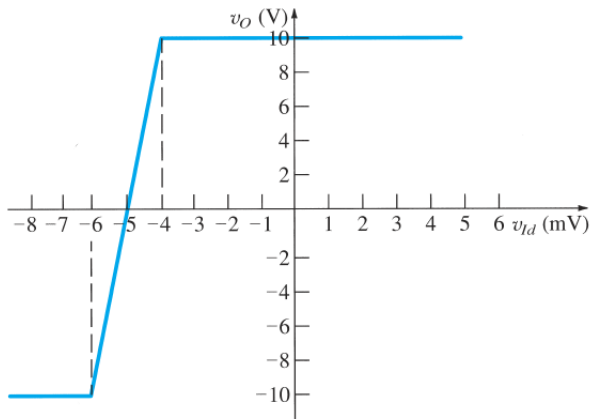


Figure E2.21 Transfer characteristic of an op amp with $V_{OS} = 5$ mV.

Output saturation

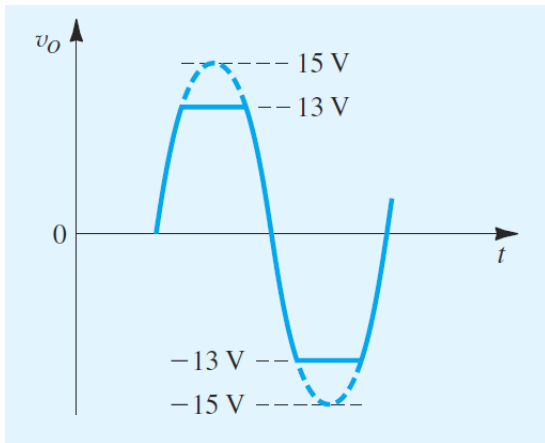Clipping: Theoretical output voltage $>$ Rated output voltage




Consider an op amp connected in the inverting configuration to realize a closed-loop gain of $-100V/V$ utilizing resistors of $1k\Omega$ and $100k\Omega$. A load resistance R_L is connected from the output to ground, and a low-frequency sine-wave signal of peak amplitude V_p is applied to the input. Let the op amp be ideal except that its output voltage saturates at $\pm 10V$ and its output current is limited to the range $\pm 20mA$.

- ▶ For $R_L = 1k\Omega$, what is the maximum possible value of V_p while an undistorted output sinusoid is obtained?
- ▶ Repeat (a) for $R_L = 200k\Omega$.
- ▶ If it is desired to obtain an output sinusoid of $10 - V$ peak amplitude, what minimum value of R_L is allowed?


A large signal effect, "saturation in rate of change of output voltage"

$$SR = \left. \frac{dv_O}{dt} \right|_{\max} \quad (29)$$

For a unity-gain voltage-follower,

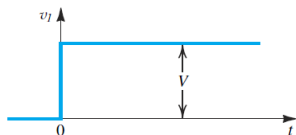

Input

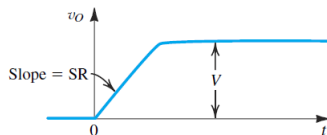

Output

- ▶ Read questions carefully (inverting&noninverting, ideal&nonideal, AC&DC...)
- ▶ Practice more to get familiar with simple models mentioned in class
- ▶ Write some important conclusions and definitions in your ctp (e.g. voltage gain, CMRR)
- ▶ Try to decompose complex circuits to multiple simple circuits when you get stucked in exam (superposition principle)
- ▶ ...

Thank You&Good Luck