

VE311 RC1

Jiaying Li

University of Michigan-Shanghai Jiao Tong University Joint Institute

June 29, 2023




JOINT INSTITUTE

交大密西根学院

- 1 Diode and Diode Circuit
- 2 BJT
- 3 BJT Common-Emitter Amplifier

PN Junction Diode

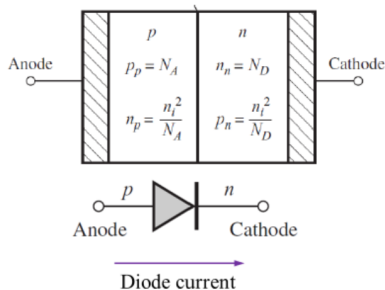

N_A, N_D : doping densities
 n_i : intrinsic carrier
concentration

hole in p:

$$p_p = N_A \quad (1)$$

electron in p:

$$n_p = \frac{n_i^2}{N_A} \quad (2)$$


electron in n:

$$n_n = N_D \quad (3)$$

hole in n:

$$p_n = \frac{n_i^2}{N_D} \quad (4)$$

PN Junction Diode

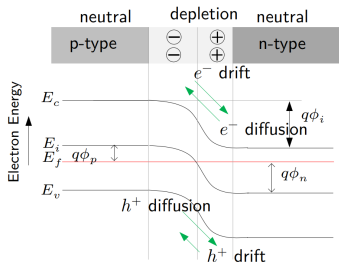

built-in potential:

$$V_{bi} = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right) \quad (5)$$


- ▶ Some electrons/holes in the **neutral regions** with sufficient energy continuously diffuse to the opposite sides. → Formation of diffusion
- ▶ Some electrons/holes wandering into the in the **depletion region** get swept by the built-in electric field. → Formation of drift current
- ▶ Diffusion current cancels drift current. **No net current flowing.**

- ▶ **Forward Bias:** Diode is on. Current flows from p to n.
- ▶ **Reverse Bias:** Diode is off. Current doesn't flow, but saturation current exists.


$$I_D = I_S \left(e^{\frac{qV_D}{kT}} - 1 \right) = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right) \quad (6)$$

Note:

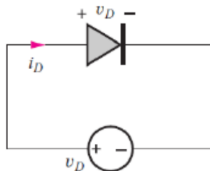- ▶ k = Boltzmann's constant, 8.62×10^{-5} eV/K
- ▶ $\frac{kT}{q} = 0.026(0.025875)$ V at 300K when calculation.



IV Characteristics of Diode

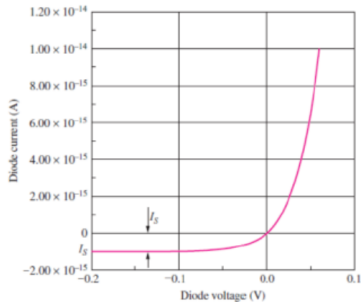

Non-linear, or rectifying, behavior


- ▶ **Non-linear** behavior
- ▶ turn-on voltage $> V_{bi}$

Exercise 1

(23FA Mid/1) Choose one description that is not right.

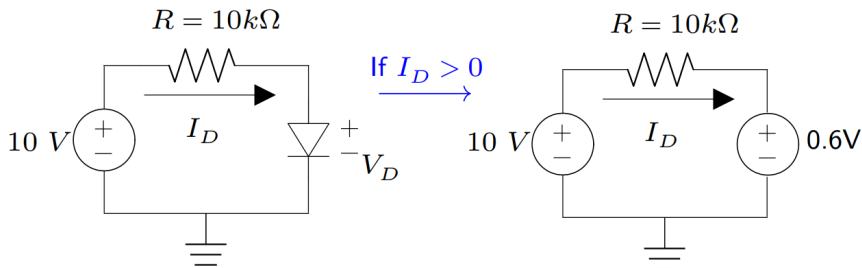- (1) At equilibrium, a PN diode current is zero.
- (2) Under a forward bias, a PN diode current increases exponentially.
- (3) Under a forward bias, a PN diode current is from P to N.
- (4) Under a moderate reverse bias (before the breakdown), a PN diode current is almost zero.
- (5) A PN diode shows a rectifying behavior, i.e. nonlinear I-V curve, because a drift current is dominant over a diffusion current under a forward bias.


- ▶ **Ideal Diode Model:** **Short circuit** for Forward Bias and **Open Circuit** for Reverse Bias
- ▶ **Constant Voltage Drop Model:** **Replace Diode with a voltage source** for Forward Bias and **Open Circuit** for Reverse Bias.



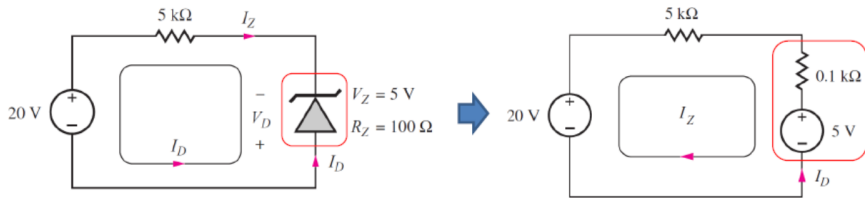1. **Identify** the model for simplification.
2. **Assume** the voltage applied on the diode
3. **Transform** the diode to source and resistor according to the assumption.
4. **Validate** that the assumption is correct or not.


Diodes (Zener) in Breakdown Region

Method: Replace the Diode with a "Reverse" voltage source and a resistance.





IV Characteristics

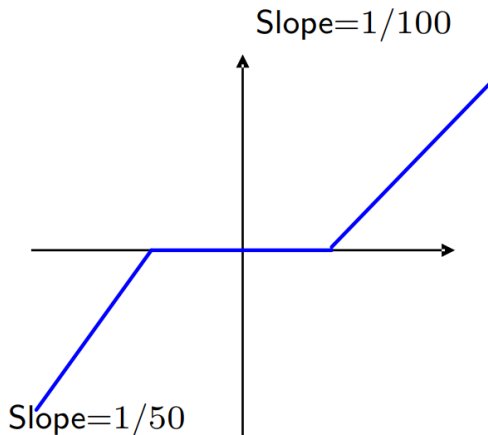When $V_D < V_{break}$, voltage source is V_{break} , slope is $\frac{1}{R_Z}$.



Voltage Regulator

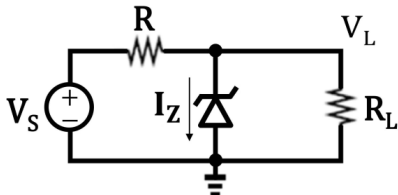
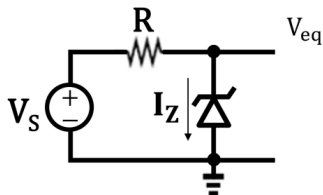
Assume the zener diode operates in reverse breakdown region.



$$V_{eq} = V_{break} + \frac{V_S - V_{break}}{R + R_Z} R_Z \quad (7)$$

$$V_L = V_{eq} \frac{R_L}{(R \parallel R_Z) + R_L} \quad (8)$$

Voltage Regulator

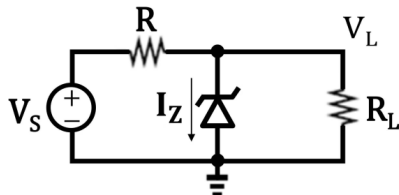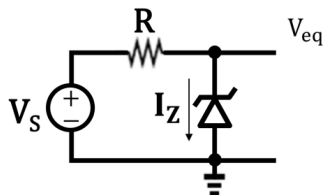

$$\text{Line Regulation} = \frac{dV_L}{dV_S} = \frac{R_Z}{R + R_Z} (R_L = \infty) \quad (9)$$


$$\text{Load Regulation} = \frac{dV_L}{dI_L} = R \parallel R_Z \quad (10)$$

Exercise 2

(23FA Mid/6) For the diode circuit below:



(1) Calculate the value I_L . [10 points]

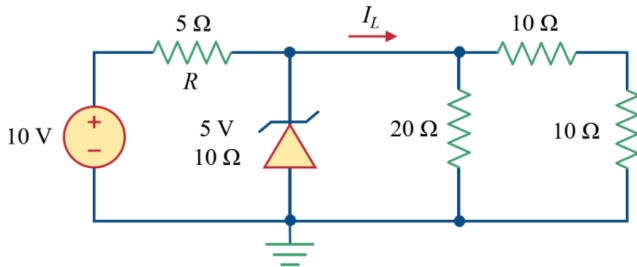(2) Find the maximum value of R required for reverse breakdown to happen. [5 points]



Half-Wave Rectifier

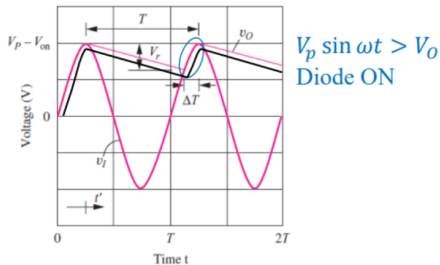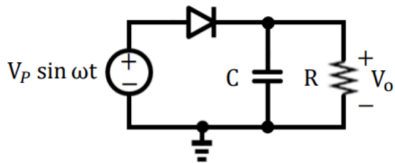The basic rectifier circuit converts an AC voltage to a pulsating DC voltage.





CTPP Time!

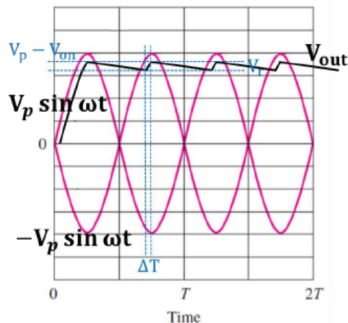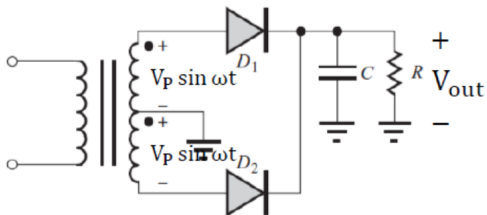1. $V_{dc} = V_s - V_{on}$
2. $I_{dc} = \frac{V_{dc}}{R}$
3. Ripple Voltage: $V_r = V_{dc}(1 - e^{-\frac{T-\Delta T}{RC}}) \approx V_{dc} \frac{T}{RC}$
4. Conduction Angle: $\theta_c = \sqrt{\frac{2V_r}{V_s}}$
5. Conduction Interval: $\Delta T = \frac{\theta_c}{\omega}$
6. Diode Current: $I_{peak} = \frac{2I_{dc}T}{\Delta T}$
7. Surge Current: $I_{surge} = C \frac{dV}{dt} = \omega CV_s(t=0)$
8. Peak Inverse Voltage (PIV): $PIV = 2V_s - V_{on}$

Full-Wave Rectifier

Full-wave rectifier circuits cut the capacitor discharge time in half and offer the advantage of requiring only one-half the filter capacitance to achieve a given ripple voltage



CTPP Time!

Just replace T with $\frac{T}{2}$ in the Half-Wave rectifier.

1. $V_{dc} = V_s - V_{on}$

2. $I_{dc} = \frac{V_{dc}}{R}$

3. Ripple Voltage: $V_r = V_{dc}(1 - e^{-\frac{T/2 - \Delta T}{RC}}) \approx V_{dc} \frac{T}{2RC}$

4. Conduction Angle: $\theta_c = \sqrt{\frac{2V_r}{V_s}}$

5. Conduction Interval: $\Delta T = \frac{\theta_c}{\omega}$



6. Diode Current: $I_{peak} = \frac{I_{dc} T}{\Delta T}$

7. Surge Current: $I_{surge} = C \frac{dV}{dt} = \omega C V_s (t = 0)$

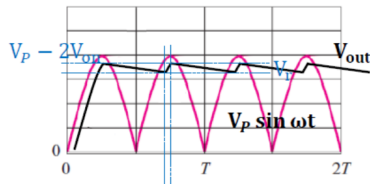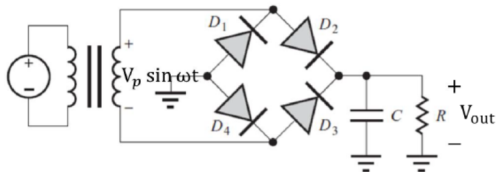8. Peak Inverse Voltage (PIV): $PIV = 2V_s - V_{on}$

Full-Wave Bridge Rectifier

- ▶ For $v_I > 0$, D_2 and D_4 will be on and D_1 and D_3 will be off.
- ▶ For $v_I < 0$, D_2 and D_4 will be off and D_1 and D_3 will be on.



CTPP Time!

Just replace V_{on} with $2V_{on}$ in the Full-Wave rectifier and change PIV.

1. $V_{dc} = V_s - 2V_{on}$

2. $I_{dc} = \frac{V_{dc}}{R}$

3. Ripple Voltage: $V_r = V_{dc}(1 - e^{-\frac{T/2 - \Delta T}{RC}}) \approx V_{dc} \frac{T}{2RC}$

4. Conduction Angle: $\theta_c = \sqrt{\frac{2V_r}{V_s}}$

5. Conduction Interval: $\Delta T = \frac{\theta_c}{\omega}$





6. Diode Current: $I_{peak} = \frac{I_{dc} T}{\Delta T}$

7. Surge Current: $I_{surge} = C \frac{dV}{dt} = \omega C V_s (t = 0)$


8. Peak Inverse Voltage (PIV): $PIV = V_s - V_{on}$

- 1 Diode and Diode Circuit
- 2 BJT
- 3 BJT Common-Emitter Amplifier


npn and pnp

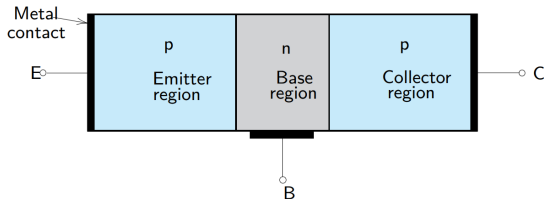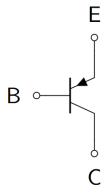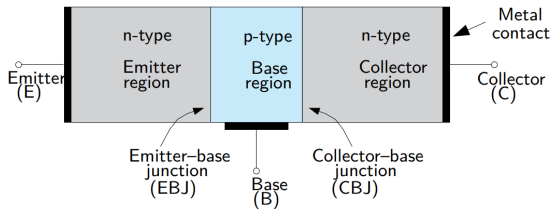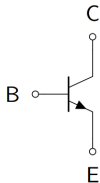

Forward Active Mode

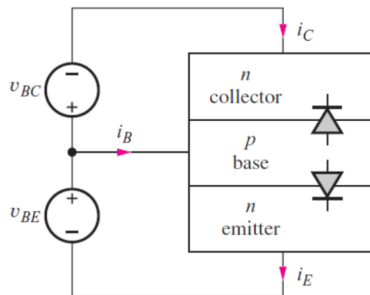


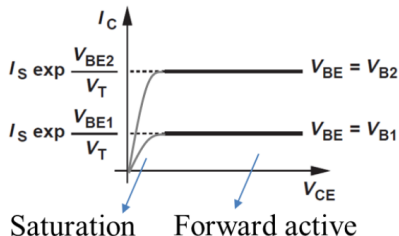- ▶ EB diode is forward biased ($V_{BE} > 0$ or $V_{EB} < 0$)
- ▶ BC diode is reversed biased ($V_{BC} < 0$ or $V_{CB} > 0$)



- ▶ $V_{CE} < V_{BE}$, then $V_{CB} < 0$ or $V_{BC} > 0$, meaning that BC diode is forward biased. Both diodes are on, which is called as saturation.
- ▶ $V_{CE} > V_{BE}$, then $V_{CB} > 0$ or $V_{BC} < 0$, meaning that BC diode is reverse biased. → Forward Active

Summary:

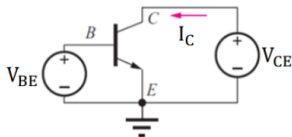

$V_{CE} \geq V_{BE}$
 \Rightarrow Forward – Active

Ideal case

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right)$$

$$\alpha = \frac{I_C}{I_E} \cong 1$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$



$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right)$$

$$\alpha = \frac{I_C}{I_E} = 1$$

$$\beta = \frac{I_C}{I_B} = \infty$$

Don't forget this: $I_E = I_C + I_B$

Early effect: V_A is called the Early voltage

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right) \quad (11)$$

or

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} \right) \left(1 + \frac{V_{CE}}{V_A} \right) \quad (12)$$

$$V_{out} = V_{OUT} + v_{out}$$


V_{out} : DC+AC, V_{OUT} : DC, v_{out} : AC

It is important to bear in mind that small-signal analysis deals with only (small) changes in voltages and currents in a circuit around their quiescent values. Thus, all constant sources, i.e., **voltage and current sources that do not vary with time (independent sources)**, must be set to zero for small-signal analysis.

How to get a small signal circuit:


- ▶ DC voltage source: short circuit
- ▶ DC current source: open circuit
- ▶ Capacitor: short circuit (short in AC, open in DC)

Small-Signal
Model

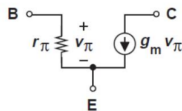

Without Early Effect

Modified Small-Signal
Model

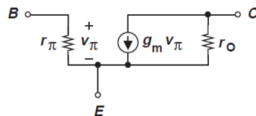


With Early Effect

$$r_\pi = \frac{dV_{BE}}{dI_B} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} = \frac{1}{\frac{g_m}{\beta}} = \frac{\beta}{g_m} \quad (13)$$

$$g_m = \frac{dI_C}{dV_{BE}} \cong \frac{I_C}{kT/q} \quad (14)$$
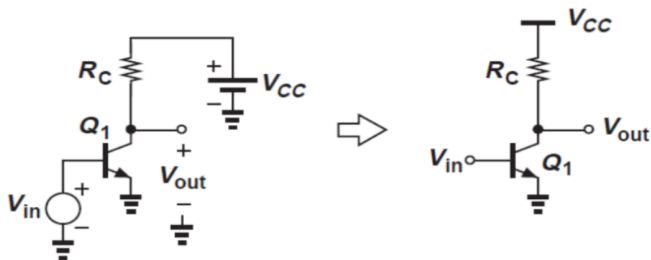
$$r_o = \frac{1}{\frac{dI_C}{dV_{CE}}} \cong \frac{V_A}{I_C} \quad (15)$$



Attention:

- ▶ V_{out} is not connected in the circuit! There is no current to it.
- ▶ V_{in} is connected. There is current from it.

Tips: See V_{out} as a voltmeter, V_{in} as a voltage source.

How to calculate R_{out} ?


1. Draw small signal model.
2. Connect port with V_{in} to ground. Connect a test voltage v_t on port with V_{out} .
3. Derive i_t .
4. Calculate $R_{out} = \frac{v_t}{i_t}$

How to calculate R_{in} ?

1. Draw small signal model.
2. Connect a test voltage v_t on port with V_{in} . Do nothing on output port.
3. Derive i_t .
4. Calculate $R_{in} = \frac{v_t}{i_t}$


Exercise 3

Assuming that the BJT operates in the forward active region, determine the impedance seen into the collector of Q1. Please **consider the Early effect**.

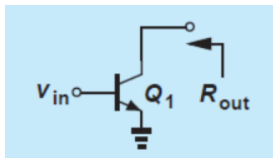

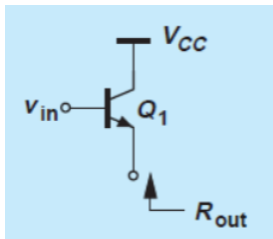
Exercise 4

Assuming that the BJT operates in the forward active region, determine the impedance seen at the emitter. Please **neglect the Early effect** for simplicity.



- 1 Diode and Diode Circuit
- 2 BJT
- 3 BJT Common-Emitter Amplifier**

CE Amplifier (Without Early Effect)

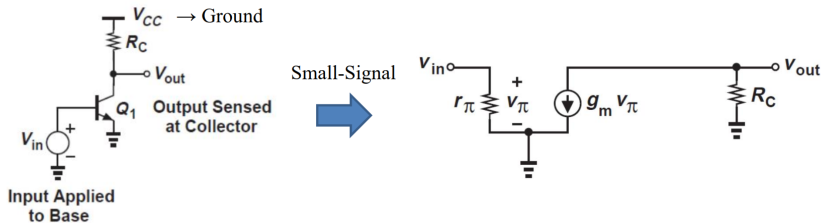

$$A_v = \frac{V_{out}}{V_{in}} = -g_m R_C \quad (16)$$

$$R_{in} = r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} \quad (17)$$

$$R_{out} = R_C \quad (18)$$

Important properties of the CE stage:


1. The small-signal gain is negative, i.e. $V_{BE} \uparrow$ and $I_C \uparrow$ lower V_{out} .
2. The voltage gain of the stage is limited by the supply voltage.

$$|A_v| = g_m R_C = \frac{I_C R_C}{V_T} \quad (19)$$

$I_C R_C$ indicates the voltage drops at the collector resistor R_C . Because $I_C R_C < V_{CC}$, $|A_v| < \frac{V_{CC}}{V_T}$. Finally, as the BJT is in the active region, we can say that, $|A_v| < \frac{V_{CC} - V_{BE}}{V_T}$.

However, when $R_C \rightarrow \infty$, $|A_v| \rightarrow \infty$. Contradiction!

CE Amplifier (With Early Effect)

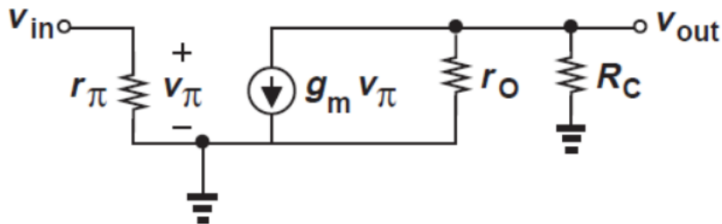

$$A_v = \frac{V_{out}}{V_{in}} = -g_m(R_C \parallel r_o) \quad (20)$$

$$R_{in} = r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} \quad (21)$$

$$R_{out} = R_C \parallel r_o \quad (22)$$

CE Amplifier (With Early Effect)

If $R_C \rightarrow \infty$, $A_v = -g_m r_O \rightarrow$ intrinsic gain

Because

$$g_m = \frac{I_C}{V_T} \quad (23)$$

and



$$r_O = \frac{V_A}{I_C}, \quad (24)$$

we can get

$$A_v = -\frac{V_A}{V_T} \quad (25)$$

The Early effect limits the voltage gain even if R_C approaches infinity.

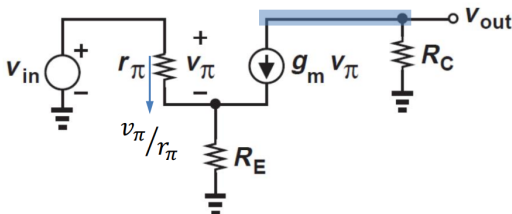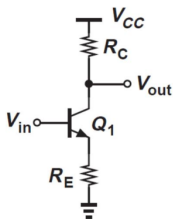CE Stage With Emitter Degeneration (Without Early Effect)





$$A_v = \frac{V_{out}}{V_{in}} = \frac{-g_m R_C}{1 + \left(\frac{1}{r_\pi} + g_m\right) R_E} \quad (26)$$

$$R_{in} = r_\pi + (\beta + 1) R_E \quad (27)$$


$$R_{out} = R_C \quad (28)$$

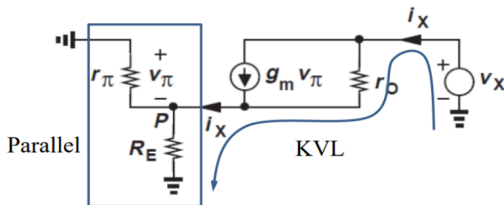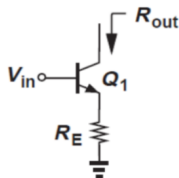CE Stage With Emitter Degeneration (With Early Effect)



$$R_{out} = r_o + (g_m r_o + 1)(R_E \parallel r_\pi) \approx r_o[1 + g_m(R_E \parallel r_\pi)] \quad (29)$$

Summary

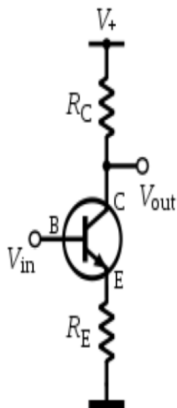


	Definition	Expression	
		With emitter degeneration	Without emitter degeneration; i.e., $R_E = 0$
Current gain	$A_i \triangleq \frac{i_{out}}{i_{in}}$	β	β
Voltage gain	$A_v \triangleq \frac{v_{out}}{v_{in}}$	$-\frac{\beta R_C}{r_\pi + (\beta + 1)R_E}$	$-g_m R_C$
Input impedance	$r_{in} \triangleq \frac{v_{in}}{i_{in}}$	$r_\pi + (\beta + 1)R_E$	r_π
Output impedance	$r_{out} \triangleq \frac{v_{out}}{i_{out}}$	R_C	R_C

Suggestion:

- ▶ Remember the general case
- ▶ First identify B, C, E port
- ▶ Know how to analyze small signal model
- ▶ Understand all the exercise in lecture slides
- ▶ Don't ignore some small values too easily! Be careful!


Exercise 5

(23FA Mid/5) Using a small-signal model, determine output impedance of the circuit shown below with and without Early effect. [10 points]

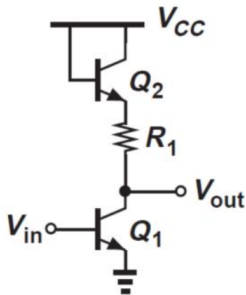

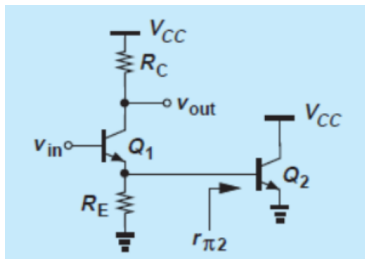
Exercise 6

Determine the voltage gain of the stage shown below. No Early effect.




Extra Exercise 1

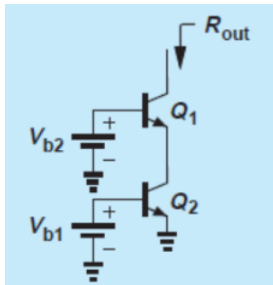Determine the output resistance of the circuit below. With Early Effect.



Extra Exercise 2

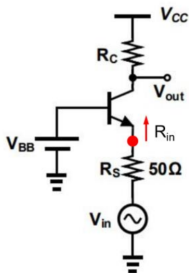(23FA Mid/9) The figure below shows a BJT amplifier. Assume $V_{BE} = 0.7\text{ V}$, $V_T = 25\text{ mV}$, β is very large (to be infinity). No Early effect. [15 points]



(a) Draw the small signal model and derive the gain for the amplifier. [5 points]

Extra Exercise 2

(b) Find values of V_{BB} and R_C to have a gain of 20 and a matched resistance of $100\ \Omega$ at the input, i.e. $R_{in} = 100\ \Omega$ from the point above R_S . [5 points]

(c) By cascading another BJT circuit to the circuit in part b as shown below, find the total parametric gain of the amplifier. [5 points]

