VE311 Mid Review - Diode

Jiaying Li

University of Michigan-Shanghai Jiao Tong University Joint Institute

June 26, 2023




Overview



Diode and Diode Circuit

PN Junction Diode



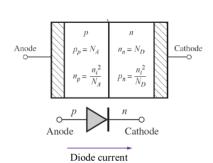

 N_A , N_D : doping densities n_i : intrinsic carrier concentration

hole in p:

$$p_p = N_A \tag{1}$$

electron in p:

$$n_p = \frac{n_i^2}{N_A} \tag{2}$$

electron in n:


$$n_n = N_D \tag{3}$$

hole in n:

$$p_n = \frac{n_i^2}{N_D} \tag{4}$$

PN Junction Diode



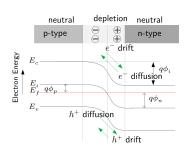

built-in potential:

$$V_{bi} = V_T \ln(\frac{N_A N_D}{n_i^2}) \quad (5)$$

- ➤ Some electrons/holes in the neutral regions with sufficient energy continuously diffuse to the opposite sides. → Formation of diffusion
- Some electrons/holes wandering into the in the depletion region get swept by the built-in electric field. → Formation of drift current
- Diffusion current cancels drift current. No net current flowing.

Diode Equation




- Forward Bias: Diode is on. Current flows from p to n.
- ► Reverse Bias: Diode is off. Current doesn't flow, but saturation current exists.

$$I_D = I_S \left(e^{\frac{qV_D}{KT}} - 1 \right) = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$
 (6)


Note:

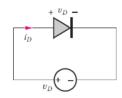- ightharpoonup k = Boltzmann's constant, 8.62 imes 105 eV/K
- $ightharpoonup \frac{kT}{q} = 0.026(0.025875) V$ at 300K when calculation.



IV Characteristics of Diode



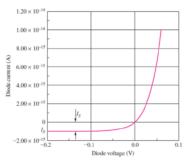


Non-linear, or rectifying, behavior

- ► Non-linear behavior
- ightharpoonup turn-on voltage> V_{bi}

Diode Simplification



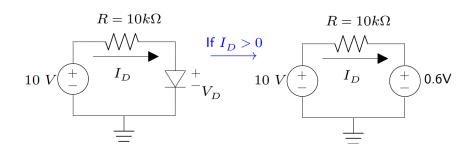- ► Ideal Diode Model: Short circuit for Forward Bias and Open Circuit for Reverse Bias
- ► Constant Voltage Drop Model: Replace Diode with a voltage source for Forward Bias and Open Circuit for Reverse Bias.



Diode Simplification




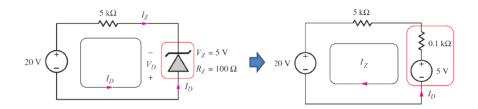- 1. Identify the model for simplification.
- 2. Assume the voltage applied on the diode
- 3. Transform the diode to source and resistor according to the assumption.
- 4. Validate that the assumption is correct or not.

Diodes (Zener) in Breakdown Region




Method: Replace the Diode with a "Reverse" voltage source and a resistance.



IV Characteristics



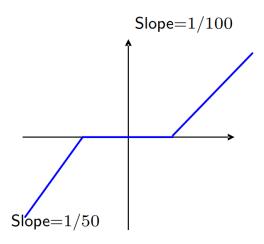
When $V_D < V_{break}$, voltage source is V_{break} , slope is $\frac{1}{R_Z}$.




Voltage Regulator



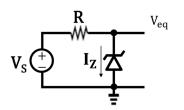Assume the zener diode operates in reverse breakdown region.



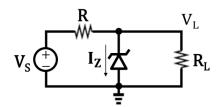



$$V_{eq} = V_{break} + \frac{V_s - V_{break}}{R + R_Z} R_Z \tag{7}$$

$$V_L = V_{eq} \frac{R_L}{(R||R_Z) + R_L} \tag{8}$$

Voltage Regulator



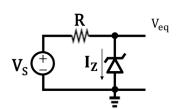

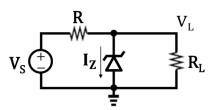


Line Regulation =
$$\frac{dV_L}{dV_S} = \frac{R_Z}{R + R_Z} (R_L = \infty)$$
 (9)


Load Regulation =
$$\frac{dV_L}{dI_L} = R \parallel R_Z$$
 (10)

Half-Wave Rectifier



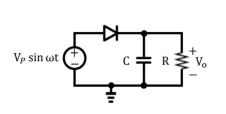The basic rectifier circuit converts an AC voltage to a pulsating DC voltage.



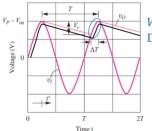

 $V_p \sin \omega t > V_0$ Diode ON

Half-Wave Rectifier




CTPP Time!

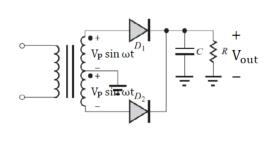
- 1. $V_{dc} = V_s V_{on}$
- 2. $I_{dc} = \frac{V_{dc}}{R}$
- 3. Ripple Voltage: $V_r = V_{dc}(1 e^{\frac{T \Delta T}{RC}}) \approx V_{dc} \frac{T}{RC}$
- 4. Conduction Angle: $\theta_c = \sqrt{\frac{2V_r}{V_S}}$
- 5. Conduction Interval: $\Delta T = \frac{\theta_c}{\omega}$
- 6. Diode Current: $I_{peak} = \frac{2I_{dc}T}{\Delta T}$
- 7. Surge Current: $I_{surge} = C \frac{dV}{dt} = \omega CV_S(t=0)$
- 8. Peak Inverse Voltage (PIV): $PIV = 2V_s V_{on}$

Full-Wave Rectifier



Full-wave rectifier circuits cut the capacitor discharge time in half and offer the advantage of requiring only one-half the filter capacitance to achieve a given ripple voltage



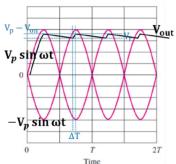

Full-Wave Rectifier



CTPP Time!


Just replace T with $\frac{T}{2}$ in the Half-Wave rectifier.

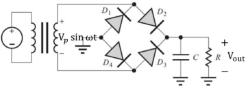
- 1. $V_{dc} = V_s V_{on}$
- $2. I_{dc} = \frac{V_{dc}}{R}$
- 3. Ripple Voltage: $V_r = V_{dc}(1 e^{\frac{T/2 \Delta T}{RC}}) \approx V_{dc} \frac{T}{2RC}$
- 4. Conduction Angle: $\theta_c = \sqrt{\frac{2V_r}{V_S}}$
- 5. Conduction Interval: $\Delta T = \frac{\theta c}{\omega}$
- 6. Diode Current: $I_{peak} = \frac{I_{dc}T}{\Delta T}$
- 7. Surge Current: $I_{surge} = C \frac{dV}{dt} = \omega CV_S(t=0)$
- 8. Peak Inverse Voltage (PIV): $PIV = 2V_s V_{on}$

Full-Wave Bridge Rectifier



- ▶ For $v_1 > 0$, D_2 and D_4 will be on and D_1 and D_3 will be off.
- ▶ For v_1 < 0, D_2 and D_4 will be off and D_1 and D_3 will be on.



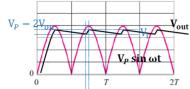

Full-Wave Bridge Rectifier



CTPP Time!

Just replace V_{on} with $2V_{on}$ in the Full-Wave rectifier and change PIV.

- 1. $V_{dc} = V_s 2V_{on}$
- 2. $I_{dc} = \frac{V_{dc}}{R}$
- 3. Ripple Voltage: $V_r = V_{dc}(1 e^{\frac{T/2 \Delta T}{RC}}) \approx V_{dc} \frac{T}{2RC}$
- 4. Conduction Angle: $\theta_c = \sqrt{\frac{2V_r}{V_S}}$
- 5. Conduction Interval: $\Delta T = \frac{\theta_c}{\omega}$
- 6. Diode Current: $I_{peak} = \frac{I_{dc}T}{\Delta T}$
- 7. Surge Current: $I_{surge} = C \frac{dV}{dt} = \omega CV_S(t=0)$
- 8. Peak Inverse Voltage (PIV): $PIV = V_s V_{on}$

End



Good Luck!