

Final RC - part3

Jiaying Li


University of Michigan-Shanghai Jiao Tong University Joint Institute

July 28, 2023



JOINT INSTITUTE
交大密西根学院

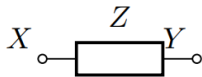
- 1 Miller Effect
- 2 First Order Systems
- 3 Nth Order Systems





$$A_v = \frac{Y}{X} \quad (1)$$

$$Z_1 = \frac{Z}{1 - A_v} \quad (2)$$


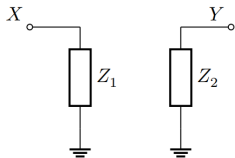
$$Z_2 = \frac{Z}{1 - \frac{1}{A_v}} \quad (3)$$



If the impedance Z forms the **ONLY** signal path between X and Y , then Miller conversion is often invalid.

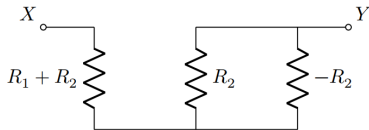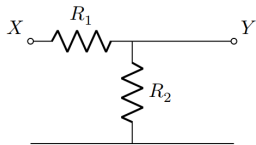

Example 1

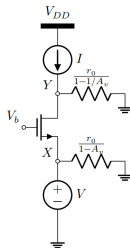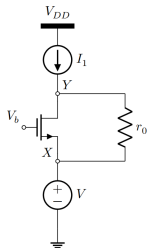

$$A_v = \frac{Y}{X} = 1 + (g_{m1} + g_{mb1}) r_{o1} \quad (4)$$

$$Z_1 = \frac{r_{o1}}{1 - [1 + (g_{m1} + g_{mb1}) r_{o1}]} = \frac{-1}{g_{m1} + g_{mb1}} \quad (5)$$

$$R_{in} = \frac{-1}{g_{m1} + g_{mb1}} \parallel \frac{1}{g_{m1} + g_{mb1}} = \infty \quad (6)$$

Example 1

R_{in} from source in NMOS:


$\lambda = 0$:

$$R_{in} = \frac{1}{g_{m1} + g_{mb1}} \quad (7)$$

$\lambda \neq 0$:

Apply Miller Effect


Association of Poles with Nodes

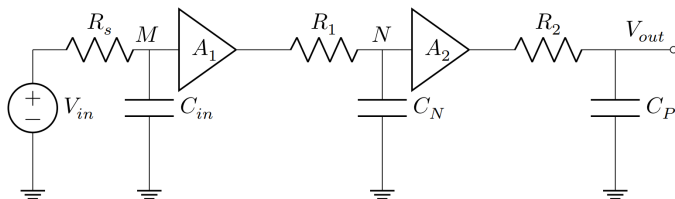

$$\frac{V_{out}}{V_{in}}(\omega) = A_1 A_2 \frac{1}{\left(1 + \frac{s}{\omega_M}\right) \left(1 + \frac{s}{\omega_N}\right) \left(1 + \frac{s}{\omega_P}\right)} \quad (8)$$

$$\omega_M = \frac{1}{R_S C_{in}} \quad (9) \quad \omega_N = \frac{1}{R_1 C_N} \quad (10) \quad \omega_P = \frac{1}{R_2 C_P} \quad (rad/s) \quad (11)$$

Example 2

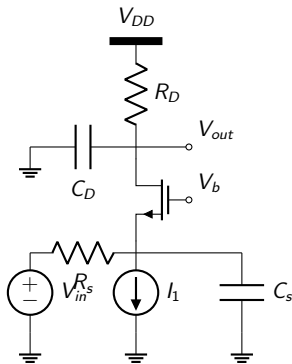

$$\frac{V_{out}}{V_{in}} = \frac{(g_{m1} + g_{mb1}) R_D}{1 + (g_{m1} + g_{mb1}) R_s} \frac{1}{\left(1 + \frac{s}{\omega_X}\right) \left(1 + \frac{s}{\omega_Y}\right)} \quad (12)$$

$$\omega_X = \frac{1}{\left(\frac{1}{g_{m1} + g_{mb1}} \parallel R_s\right) C_s} \text{ (rad/s)} \quad (13)$$

$$\omega_Y = \frac{1}{R_D C_D} \text{ (rad/s)} \quad (14)$$

Exercise 1

Assume the op amp to be ideal except for having a finite differential gain A and $V_{sig} = 1V$. Use Miller's theorem to find R_{in} , V_i , V_o for each of the following values of A : 10, 100, 1000 (without using knowledge of op-amp circuit analysis)

$$Z_1 = \frac{Z}{1+A}$$


$$Z_2 = \frac{Z}{1+\frac{1}{A}}$$

$$Z = 10k\Omega$$

$$A_v = -A$$

$$-V_o = \frac{Z_1}{1k + Z_1} \cdot V_{sig}$$

$$V_o = A V_i$$

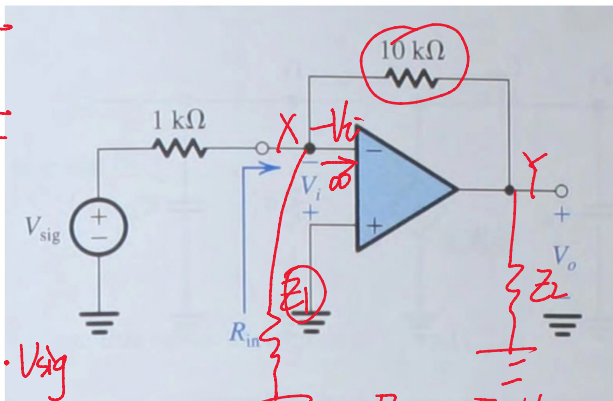

$$Z_1$$

$$R_{in} = Z_1 || \infty = Z_1$$


- 1 Miller Effect
- 2 First Order Systems
- 3 Nth Order Systems



$$H(s) = \frac{H^0 + H^1 \tau s}{1 + \tau s} \quad (15)$$

- ▶ Time constant: τ (1) For capacitor: $\tau = RC$; (2) For inductor: $\tau = \frac{L}{R}$
- ▶ To find the time constant, remove the cap/ind nulling all the sources and find the resistance.
- ▶ To find H^0 , use low frequency gain (cap cut off and ind shorted).
- ▶ To find H^1 , use high frequency gain (cap shorted and ind cut off).

Example 1

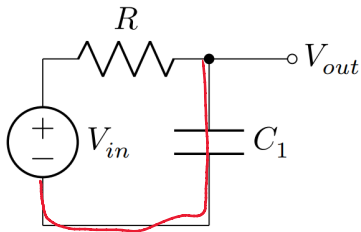

$$H^0 = 1 \quad \text{cut off } C_1 \quad (16)$$

$$\tau = \underline{RC_1} \quad (17)$$

$$H^1 = 0 \quad \text{short } C_1 \quad (18)$$

$$H(s) = \frac{1}{1 + RCS} \quad (19)$$

$$\begin{aligned} H(s) &= \frac{H^0 + H^1 s}{1 + \tau s} \\ &= \frac{1 + 0}{1 + RCs} \end{aligned}$$

Example 2

$$V_{gs} = V_t$$



$$R_2 g_m V_t - i_t$$

$$+ V_t$$

$$= R_1 \cdot i_t$$

$$\frac{V_t}{i_t} = R$$

$$T = RC\pi$$

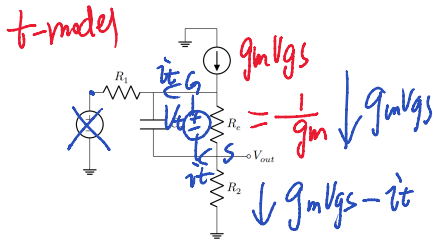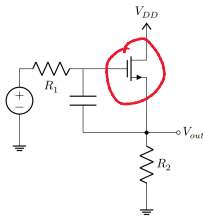

$$H^0 = \frac{R_2}{R_2 + R_e} \quad \text{cut off } C_{\pi} \quad (20)$$

$$H^1 = \frac{R_2}{R_2 + R_1} \quad \text{short } C_{\pi} \quad (21)$$

$$R = \frac{R_1 + R_2}{1 + g_m R_2} \quad (22)$$

Example 2

$$H(s) = \frac{R_2}{R_2 + R_e} \cdot \frac{1 + \frac{R_e + R_2}{R_1 + R_2} \cdot \frac{R_1 + R_2}{1 + g_m R_2} C_\pi S}{1 + R_\pi^0 C_\pi S} \quad (23)$$

$$= \frac{R_2}{R_2 + R_e} \cdot \frac{1 + R_e C_\pi S}{1 + R_\pi^0 C_\pi S} \quad (24)$$

Exercise 2


For the circuit shown below

- Calculate H^0, H^1, τ
- Write down the transfer function

③ T: $\begin{cases} g_m V_1 R_S = -V_1 + V_t \\ -i_t R_G + V_t = (i_t - g_m V_1) R_D \end{cases}$

$i_t \Rightarrow R = \frac{V_t}{i_t}$
 $= R_D + \left(\frac{g_m R_D}{1 + g_m R_S} + 1 \right) R_G$

$T = R C_{GD}$

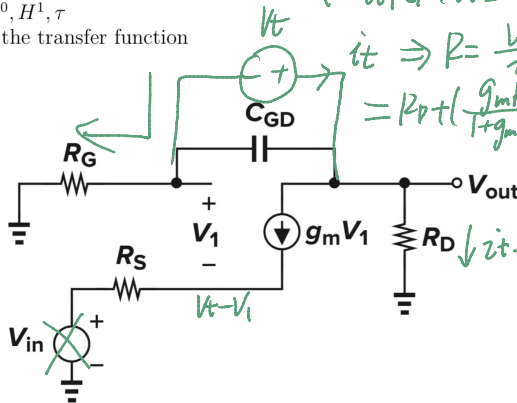

① H^0 : cut off C_{GD}

$V_{in} + R_S \cdot g_m V_1 = -V_{out}$
 $V_{out} = -R_D g_m V_1$

$\Rightarrow H^0 = \frac{V_{out}}{V_{in}}$
 $= \frac{g_m R_D}{R_S g_m + 1}$

② H^1 : short C_{GD}

$\begin{cases} V_{in} + R_S g_m V_1 = V_{out} - V_1 \\ \frac{V_{out}}{R_G} + \frac{V_{out}}{R_D} + g_m V_1 = 0 \end{cases}$

$\Rightarrow H^1 = \frac{1}{1 + \left(R_S + \frac{1}{g_m} \right) \left(\frac{1}{R_D} + \frac{1}{R_G} \right)}$

- 1 Miller Effect
- 2 First Order Systems
- 3 Nth Order Systems

$$H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2} \quad (25)$$

$$b_1 = \sum_{i=1}^N \tau_i^0 \quad (26)$$


$$b_2 = \sum_i^{i < j < N} \sum_j^0 \tau_j^i \quad (28)$$

$$a_1 = \sum_{i=1}^N \tau_i^0 H^i \quad (27)$$

$$a_2 = \sum_{i < j < N} \sum_j \tau_i^0 \tau_j^i H^{ij} \quad (29)$$

- ▶ τ_j^i : the time constant of capacitor j when capacitor i is shorted
- ▶ τ_i^0 : cut off all other caps

Example

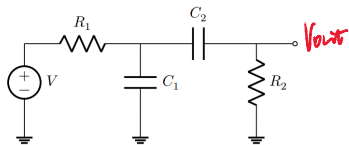

- C_2 's time constant when C_1 is shorted*
- ▶ $\tau_2^1 = R_2 C_2$
 - ▶ $\tau_1^2 = (R_1 \parallel R_2) C_1$
 - ▶ $\tau_1^0 \tau_2^1 = R_1 C_1 R_2 C_2 = \tau_2^0 \tau_1^2$
 - ▶ $\tau_2^0 \tau_1^2 = (R_1 + R_2) C_2 \frac{R_1 R_2}{R_1 + R_2} C_1$
 - ▶ $\tau_2^0 = (R_1 + R_2) C_2$
 - ▶ $\underline{H^1} = 0$ *C_1 shorted*
 - ▶ $H^2 = \frac{R_2}{R_2 + R_1}$
 - ▶ $\underline{H^{12}} = 0$ *C_1, C_2 shorted*

Example

- ▶ $H(s) = \frac{a_0 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2}$
- ▶ $b_2 = \tau_1^0 \tau_2^1 = \tau_2^0 \tau_1^2$
- ▶ $a_2 = \tau_1^0 \tau_2^1 H^{12} = \tau_2^0 \tau_1^2 H^{12}$
- ▶ $b_1 = \tau_1^0 + \tau_2^0$
- ▶ $a_1 = \tau_1^0 H^1 + \tau_2^0 H^2$

$$H(s) = \frac{R_2 C_2 S}{1 + (R_1 C_1 + R_1 C_2 + R_2 C_2) S + R_1 C_1 R_2 C_2 S^2} \quad (30)$$

If you couldn't understand first order systems and n-th order systems clearly, just treat capacitor as $\frac{1}{sC}$ and inductor as sL , then use KCL and KVL!

Good luck in final exam!