



## Lecture 8

VE 311 Analog Circuits

Xuyang Lu  
2023 Summer



上海交通大學  
SHANGHAI JIAO TONG UNIVERSITY

# Recap of Last Lecture




- Reviewed Op-amps
- BJT

# Topics to Be Covered



- BJT

# DC Condition Calculation

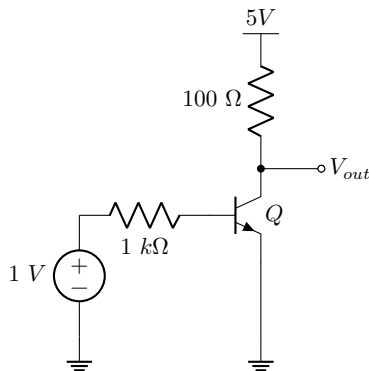

Given:

$$\beta = 100, v_{BE,on} = 0.6V \quad (1)$$


What is  $v_O$ ? Assume FAR

$$i_B = \frac{1 - 0.6V}{R_B} = 0.4mA \quad (2)$$

$$i_C = \beta i_B = 100 \cdot 0.4mA = 40mA \quad (3)$$


$$v_O = 5V - 100\Omega \cdot 40mA = 1V \quad (4)$$

# pn<sub>p</sub> Transistor

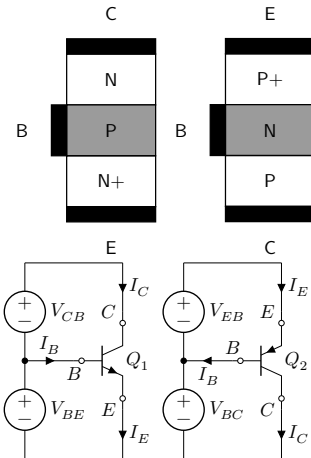


- For pnp, the basics of the operation are the same, except now instead of  $e^-$  crossing the base,  $h^+$  cross the base.
- Because holes move a lot slower than  $e^-$ , there would be more recombination and fewer of them make it to the collector. Thus, the current gain is much lower for pnp than for npn.
- Note that all polarities are now different, for example for FAR operation, the BE junction has to be forward biased which means that the base-emitter voltage should be  $-0.7V$ , so the BE junction is forward biased.

# npn Transistor

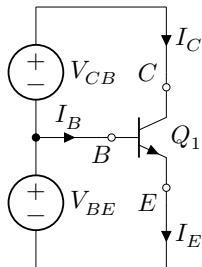

Applied Voltages	B-E junction Bias (PNP)	B-C junction Bias (PNP)	Mode(NPN)
$E < B < C$	Reverse	Forward	Reverse-active
$E < B > C$	Reverse	Reverse	Cut-off
$E > B < C$	Forward	Forward	Saturation
$E > B > C$	Forward	Reverse	Forward-active

# pnP Transistor

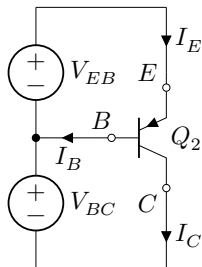


Applied Voltages	B-E junction Bias (NPN)	B-C junction Bias (NPN)	Mode(NPN)
$E < B < C$	Forward	Reverse	Forward-active
$E < B > C$	Forward	Forward	Saturation
$E > B < C$	Reverse	Reverse	Cut-off
$E > B > C$	Reverse	Forward	Reverse-active
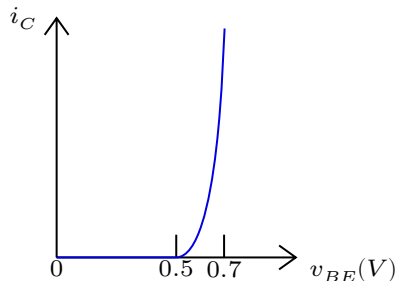
## Large Signal Model: T-Model



- We can now easily establish large signal models for the transistor that describe the current-voltage relation ship

$$i_C \approx I_S e^{v_{BE}/V_T} \quad (5)$$






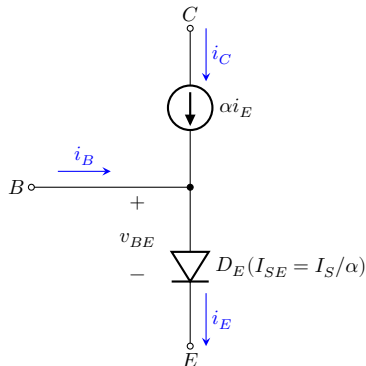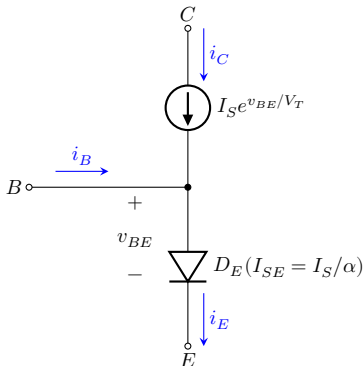
# Large Signal Model: T-Model



- The base is shared between the input port (B-E) and the output port (B-C)





# Hybrid- $\pi$ Model




- In hybrid- $\pi$  model, where the collector current is shown as a voltage controlled current source (VCCS).
- The hybrid- $\pi$  model is more useful for analyzing the common-emitter amplifier. Notice that the emitter in this model is shared between the input port (B-E), and the output port (C-E).

# Hybrid- $\pi$ Model

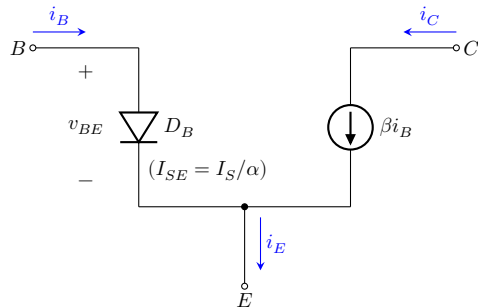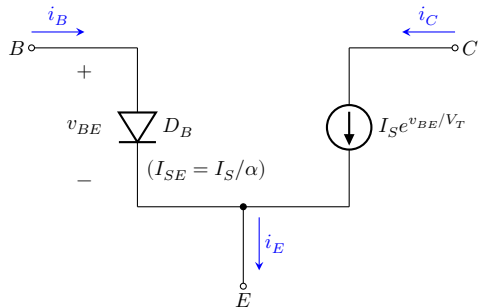

# Small Signal

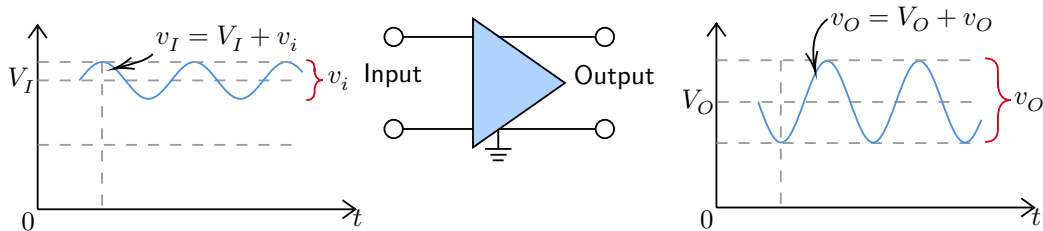


- Amplifiers refer to circuits that amplify AC (time varying) signals; there is generally no interest in the DC component of a signal.
- Circuits that change the DC value of the input to produce an output with a different DC value are generally referred to as level shifters, or DC-DC converters.

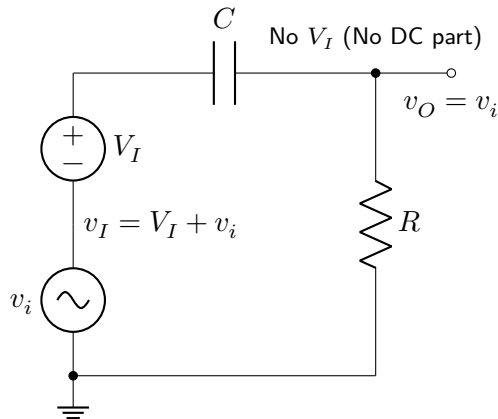
## AC-Coupled or DC-Coupled



- AC-coupled, means only AC signals will pass through to the input of the next stage.
- DC coupled means there is no capacitor separating one part of a circuit from another part when the two are connected.




## Small-Signal/Large-Signal


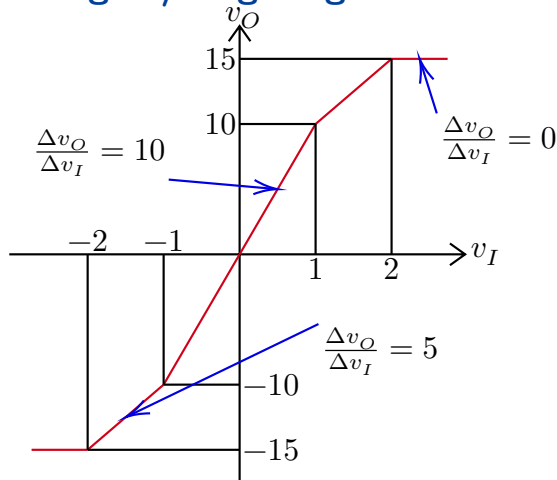


- A circuit with linear behavior over a specific range of signals, could be used as a linear circuit, when/if the range of signals applied to it is limited to where response is linear

# Small-Signal/Large-Signal

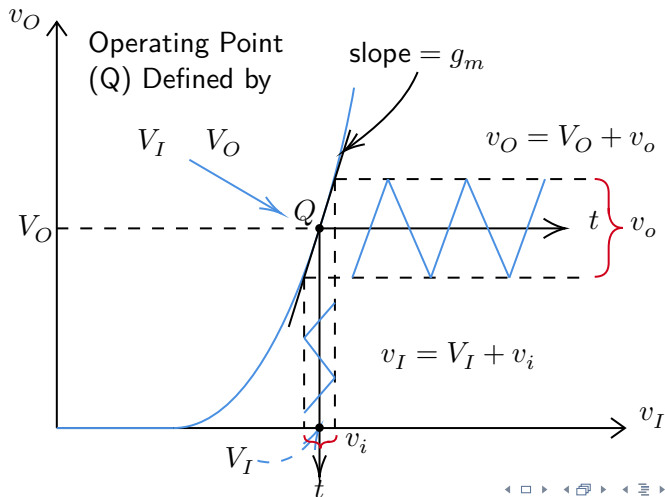


# BJT CE Gain

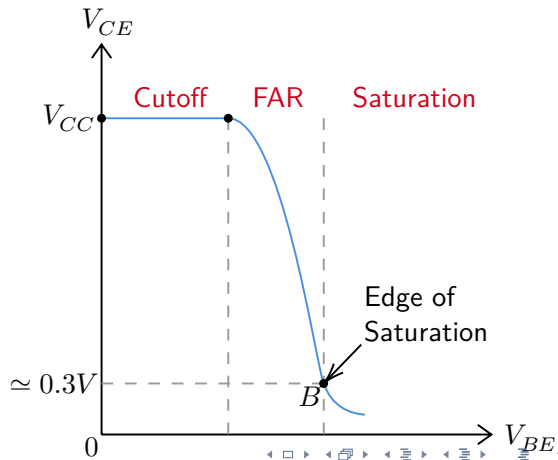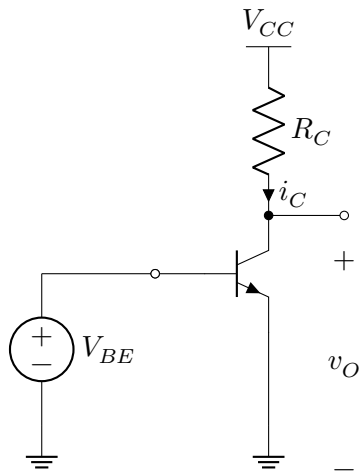





# Small Signal Gain

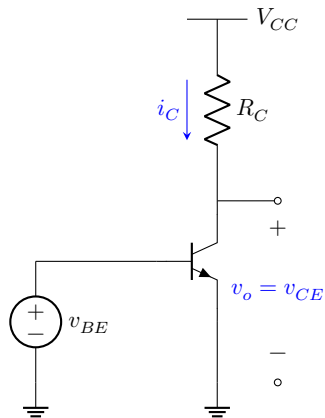


$$A_v = \frac{dv_o}{dv_{BE}} \quad (6)$$

$$A_v = -\frac{I_C}{V_T} R_C \quad (7)$$

# Small Signal Gain

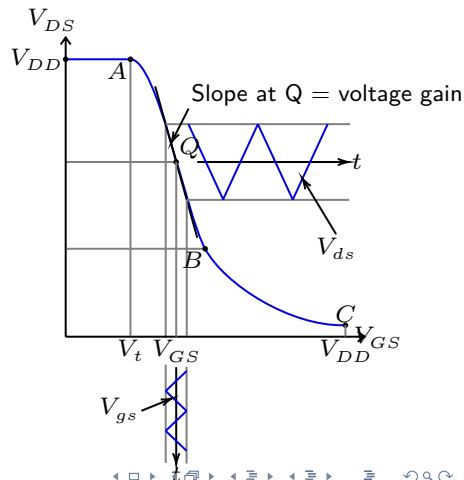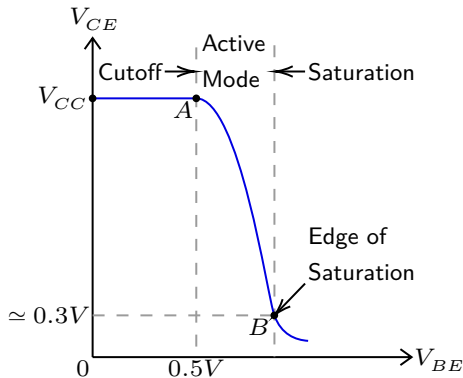


# Small Signal Gain

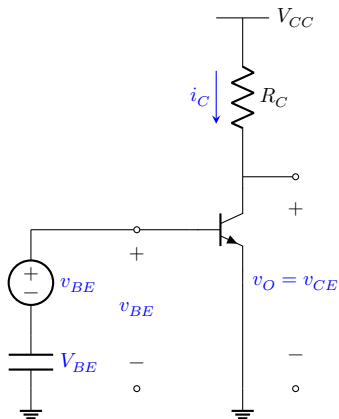

$$v_{CE}(t) = V_{CE} + v_{ce}(t) \quad (8)$$

$$v_{BE}(t) = V_{BE} + v_{be}(t) \quad (9)$$

## Quiescent Point (Q)

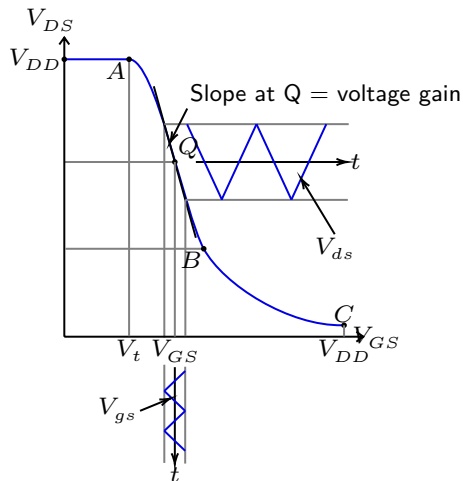


- Operating point for circuit
- Often called “bias” point

$$A_v = \frac{V_o}{v_{be}} \quad (10)$$

$$V_o = V_{CC} - R_C I_S e^{v_{BE}/V_T} \quad (11)$$


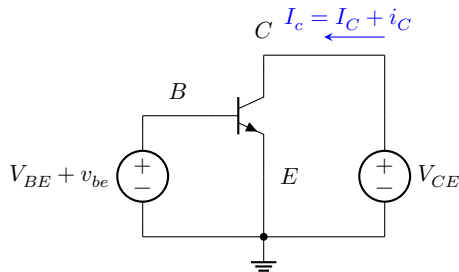
# Hybrid- $\pi$ Model ( $g_m$ and $r_\pi$ )



$V_{CE} \geq V_{BE} \Rightarrow \text{Forward-Active}$


$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right) \quad (12)$$



# Hybrid- $\pi$ Model (Derivation of $g_m$ and $r_\pi$ )



Small-signal circuit:

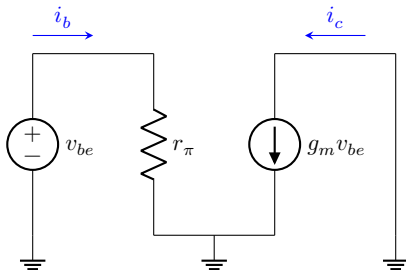

$$r_\pi = \frac{dV_{BE}}{dI_B} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} \quad (13)$$

$$= \frac{1}{\frac{g_m}{\beta}} = \frac{\beta}{g_m} \quad (14)$$

$$g_m = \frac{dI_C}{dV_{BE}} \cong \frac{I_C}{kT/q} \quad (15)$$

## Models with the Early Effect Included




- As we see from this relationship, the collector current should change when the collector-emitter voltage changes:

$$i_C \approx I_S e^{v_{EB}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right) \quad (16)$$

- So, this effect is included in the model shown below where:

$$r_o = \frac{V_A}{I_C} = \frac{\Delta v_{CE}}{\Delta i_C} \quad (17)$$


# Models with the Early Effect Included

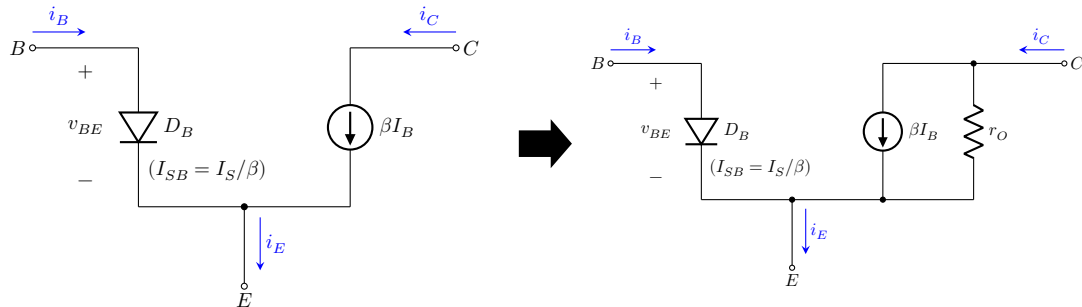




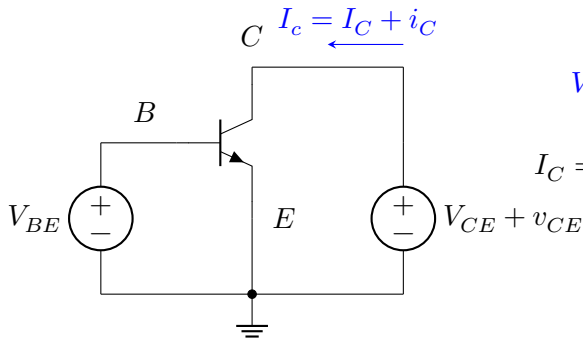
# Hybrid- $\pi$ Model (how to get $r_o$ )




$V_{CE} \geq V_{BE} \Rightarrow$  Forward—Active

$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right) \quad (18)$$



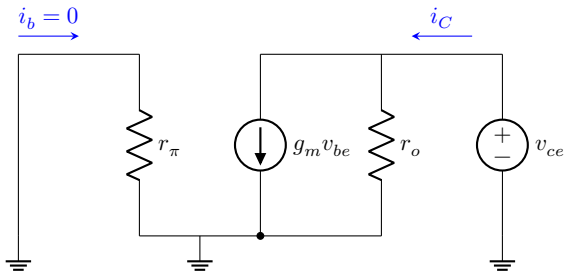
## Hybrid- $\pi$ Model (Derivation of $r_o$ )



$$r_o = \frac{1}{\frac{dI_C}{dV_{CE}}} \approx \frac{V_A}{I_C} \quad (19)$$

# Temperature Variation

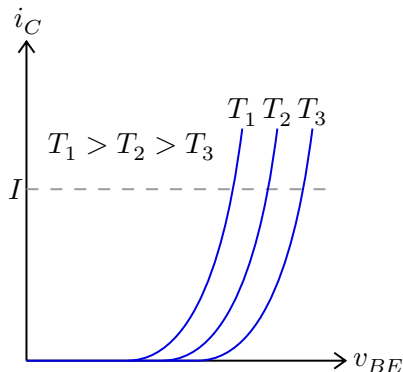


$$i_C = I_S e^{v_{BE}/V_T} \quad (20)$$

- Both  $I_S$  and  $V_T$  are temperature dependent

# Common-Emitter Amplifier



- Sedra 7.1, 7.2.2, 7.2.3

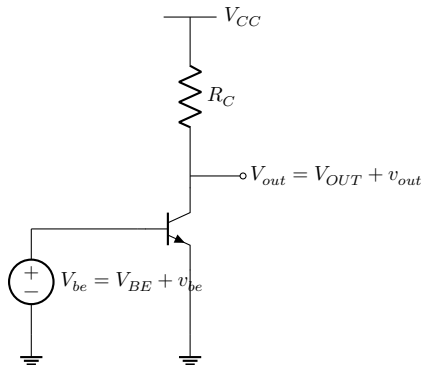

# Common-Emitter Amplifier




$$V_{OUT} = V_{CC} - I_C R_C \quad (21)$$

$$= V_{CC} - \frac{AqD_n n_i^2}{N_a W_B} \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) R_C \quad (22)$$

$$A_V = \frac{dV_{OUT}}{dV_{BE}} \quad (23)$$
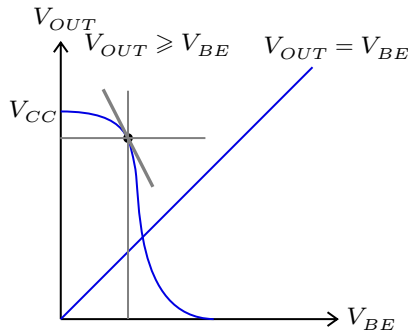
$$\cong -\frac{I_C}{kT/q} R_C = -g_m R_C \quad (24)$$



# Common-Emitter Amplifier




Gain varies a lot in the FAR region.


$$A_v = \frac{dv_o}{dv_{BE}} \quad (25)$$

$$A_V = \frac{dV_{OUT}}{dV_{BE}} \quad (26)$$

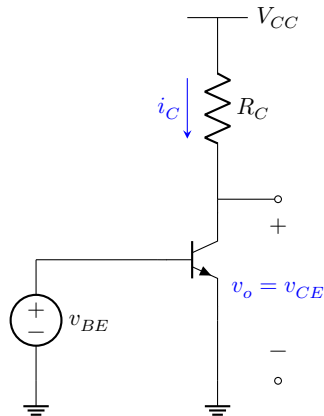
$$\cong -\frac{I_C}{kT/q} R_C = -g_m R_C \quad (27)$$


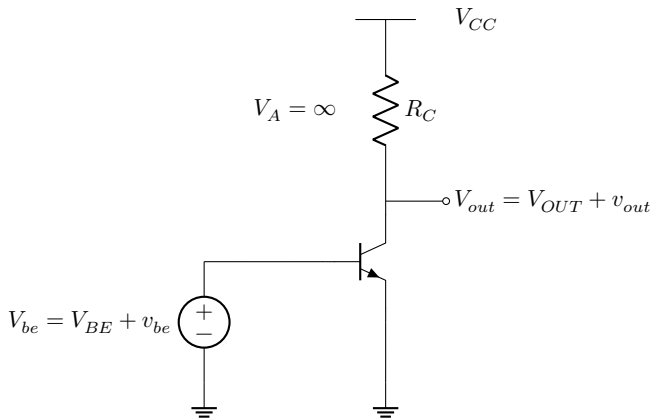
# Common-Emitter Amplifier ( $V_A = \infty$ )


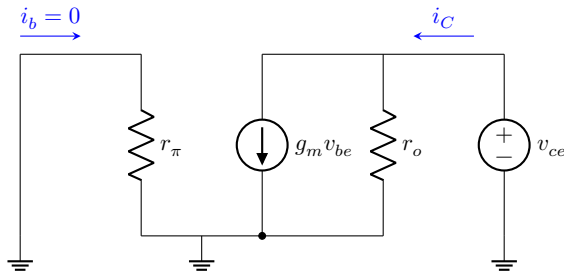
# Common-Emitter Amplifier ( $V_A = \infty$ )




$$A_v = \frac{v_{out}}{v_{be}} = -g_m (R_C \parallel r_o) \quad (28)$$

$$= -g_m R_C \quad (\text{since } r_o = \infty) \quad (29)$$




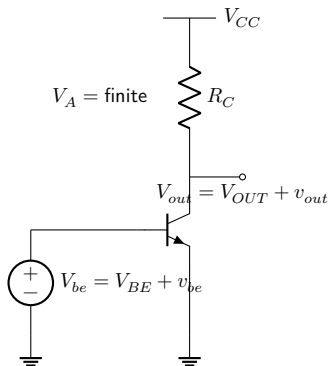
# Common-Emitter Amplifier ( $V_A = \text{finite}$ )




$$V_{OUT} = V_{CC} - I_C R_C \quad (30)$$

$$= V_{CC} - I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{OUT}}{V_A} \right) R_C \quad (31)$$

$$\frac{dV_{OUT}}{dV_{BE}} = -\frac{q}{kT} I_S e^{\frac{qV_{BE}}{kT}} \left( 1 + \frac{V_{OUT}}{V_A} \right) R_C \quad (32)$$


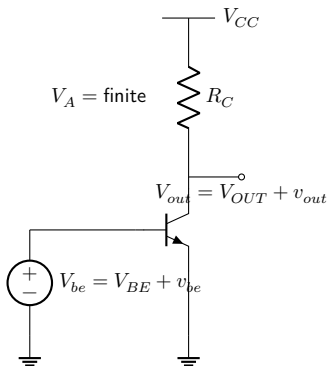
# Common-Emitter Amplifier ( $V_A = \text{finite}$ )



$$-I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \frac{1}{V_A} \frac{dV_{OUT}}{dV_{BE}} R_C \quad (33)$$


$$\cong -g_m R_C - \frac{1}{r_o} \frac{dV_{OUT}}{dV_{BE}} R_C \quad (34)$$
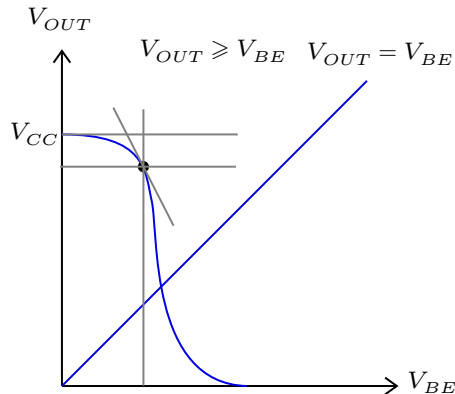
# Common-Emitter Amplifier ( $V_A = \text{finite}$ )



$$A_V = \frac{dV_{OUT}}{dV_{BE}} \quad (35)$$


$$\cong g_m(R_C \parallel r_O) \quad (36)$$



# Common-Emitter Amplifier ( $V_A = \text{finite}$ )




- Small-Signal Analysis

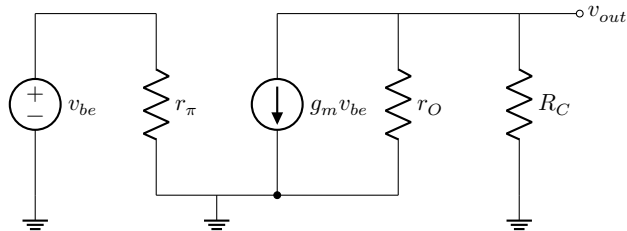

$$A_v = \frac{v_{out}}{v_{be}} = -g_m(R_C \parallel r_O) \quad (37)$$
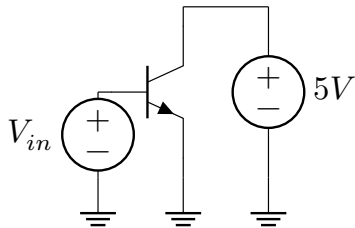
## Example 1: $I_S = 1e-15$ $\beta = 100$ $V_{AF} = 50$

- What is current?
- What is small signal gain?
- What is the output if input =  $2 + 0.001 \sin(2 \cdot \pi \cdot 100t)$



$$I_C = I_S \left( e^{\frac{qV_{BE}}{kT}} - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right) \quad (38)$$


# Example 1



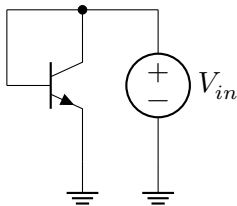**Example 2:**  $I_S = 10^{-15}$ ,  $\beta = 100$ ,  $V_{AF} = 50$



Find the output if input =  $2 + 0.001 \sin(2\pi 100t)$



## Example 2

